

# Parametric, Floating Point Arithmetic Logic Unit

---

by Nathan Sketch, Saher Al-Khrayyef, Raymon Benjamin

# Objectives


- Design Parametric Floating Point Arithmetic Logic Unit
  - ❖ Addition
  - ❖ Subtraction
  - ❖ Multiplication
- Interface the FPU to a ARM processor via an AXI4 lite bus.

# IEEE single and double precision floating point representation

This figure shows the IEEE single and double precision

floating point format.

 
- Where  $s$  is the sign bit.
- $Exp$  is the exponent, it depends on the binary number size.
- Mantissa, also it depends on the binary number size.
- Bias single is 127 and double is 1023



# IEEE-754 Standard Representation

- The representation is as follows:

$$X = \pm 1. f \times 2^e$$

 

Significand:  $f$  is the mantissa. We should add 1 to the beginning of the mantissa before start addition/subtraction.

Significand range should be  $[1, 2 - 2^{-p}] = [1, 2)$

Biased Exponent:

- $E$  is the number of the bits.
- Bias = 127 or 1023
- $e = \text{exp} - \text{bias}$

# Floating Point Addition/Subtraction Equations

$$b1 = \pm s1 * 2^{e1}, \quad s1 = 1.f1$$

$$b2 = \pm s2 * 2^{e2}, \quad s2 = 1.f2$$

- $b1 + b2 = \pm s1 * 2^{e1} \pm s2 * 2^{e2}$

# Floating Point Adder/Subtractor Sign

- An add-subtract operation has three sign inputs,  $a\_sign$ ,  $b\_sign$ , and  $op$ .
- We can transform the normal equation into one that better serves the output floating-point format.

$$-a+(-b)$$

$$-a-b$$

$$-(a+b)$$


$$a-(+b)$$

$$a-b$$

$$a-b$$

## DESIGN OF FLOATING POINT ADDITION/SUBTRACTION

- Flow Chart Diagram

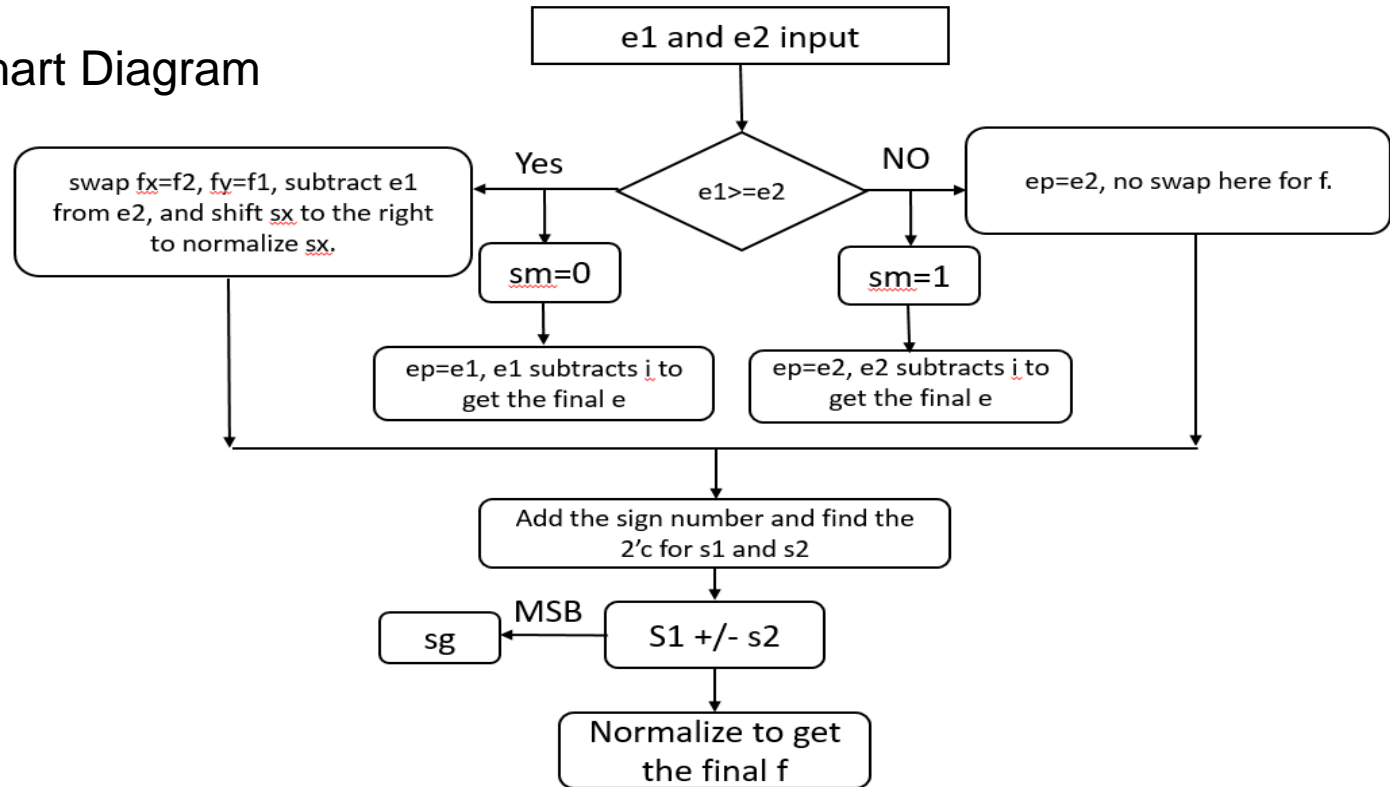


## Normalized left shift


- The normalized left shift in the post-normalization step removes leading zeros.



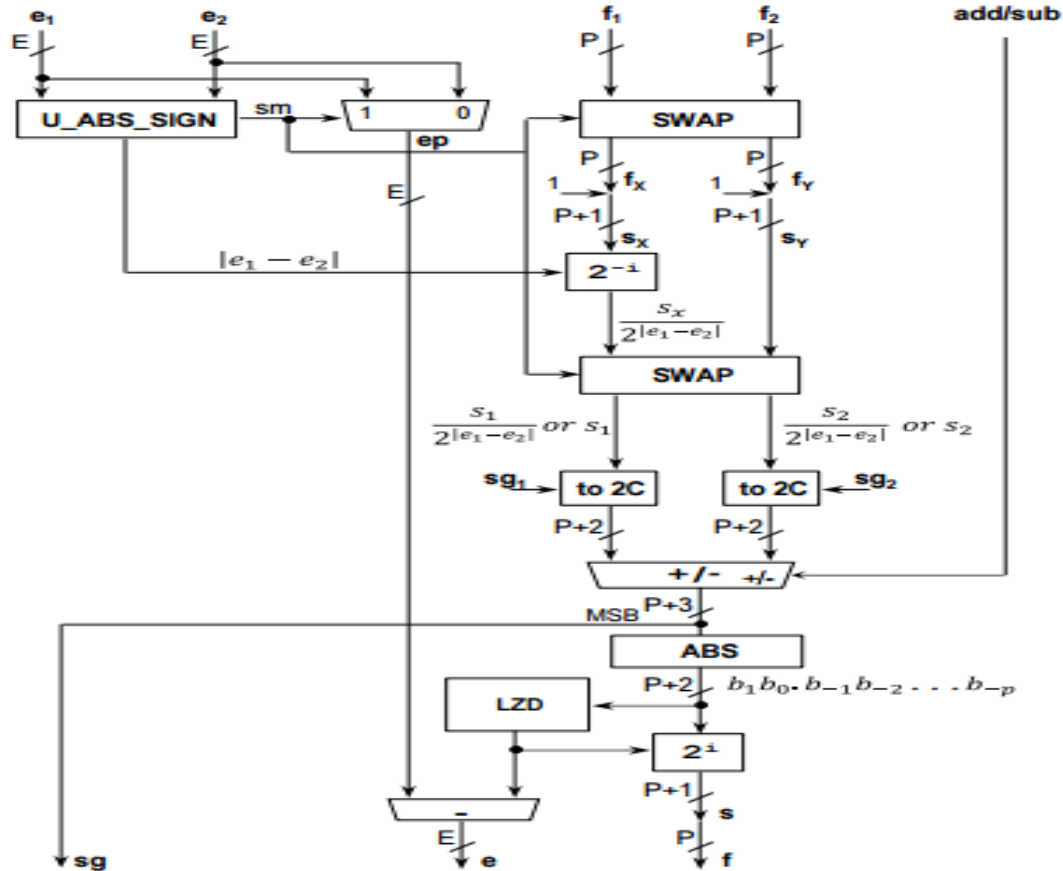
# DESIGN OF FLOATING POINT ADDITION/SUBTRACTION .... Cont.




# Addition Simulation Part 1

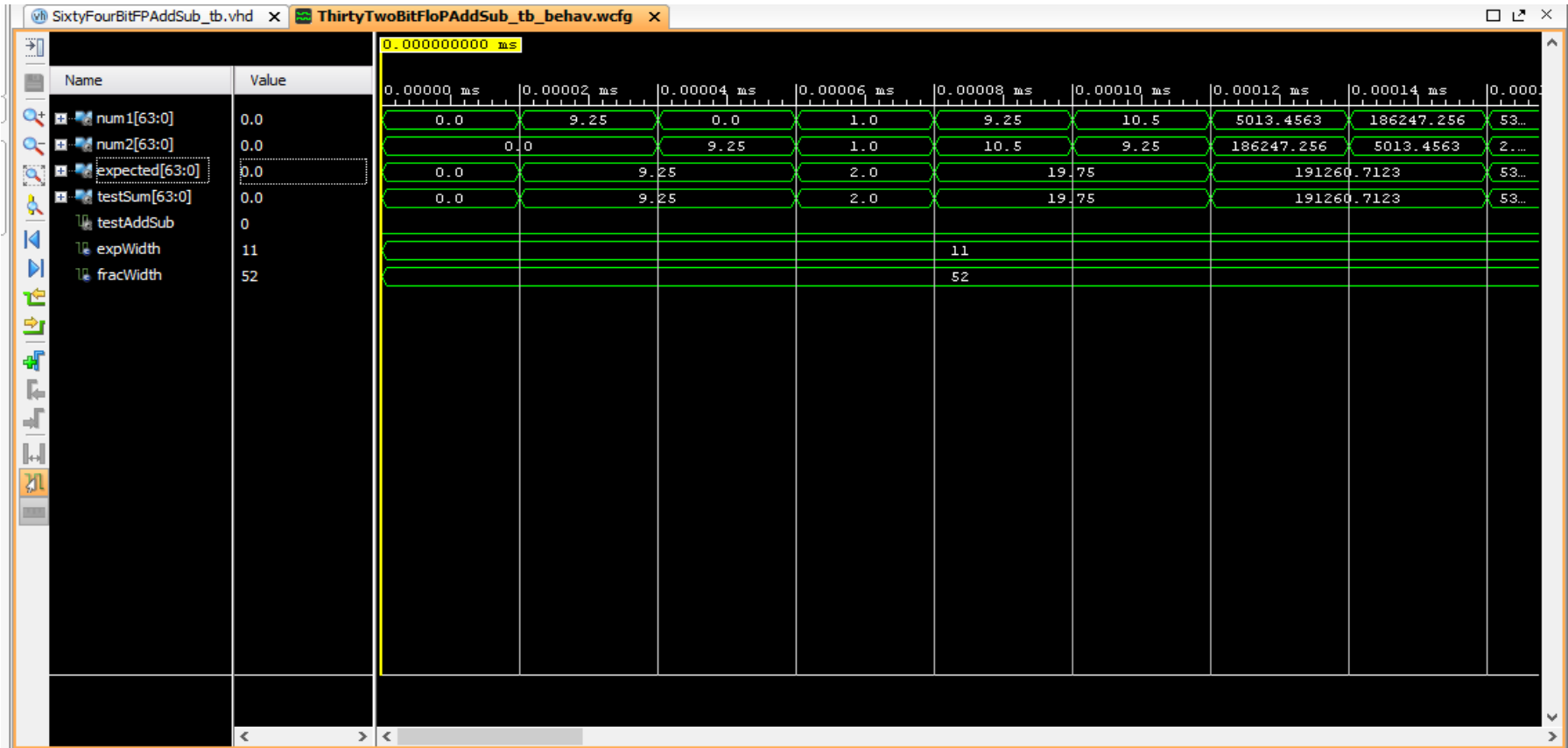


# Addition Simulation Part 2

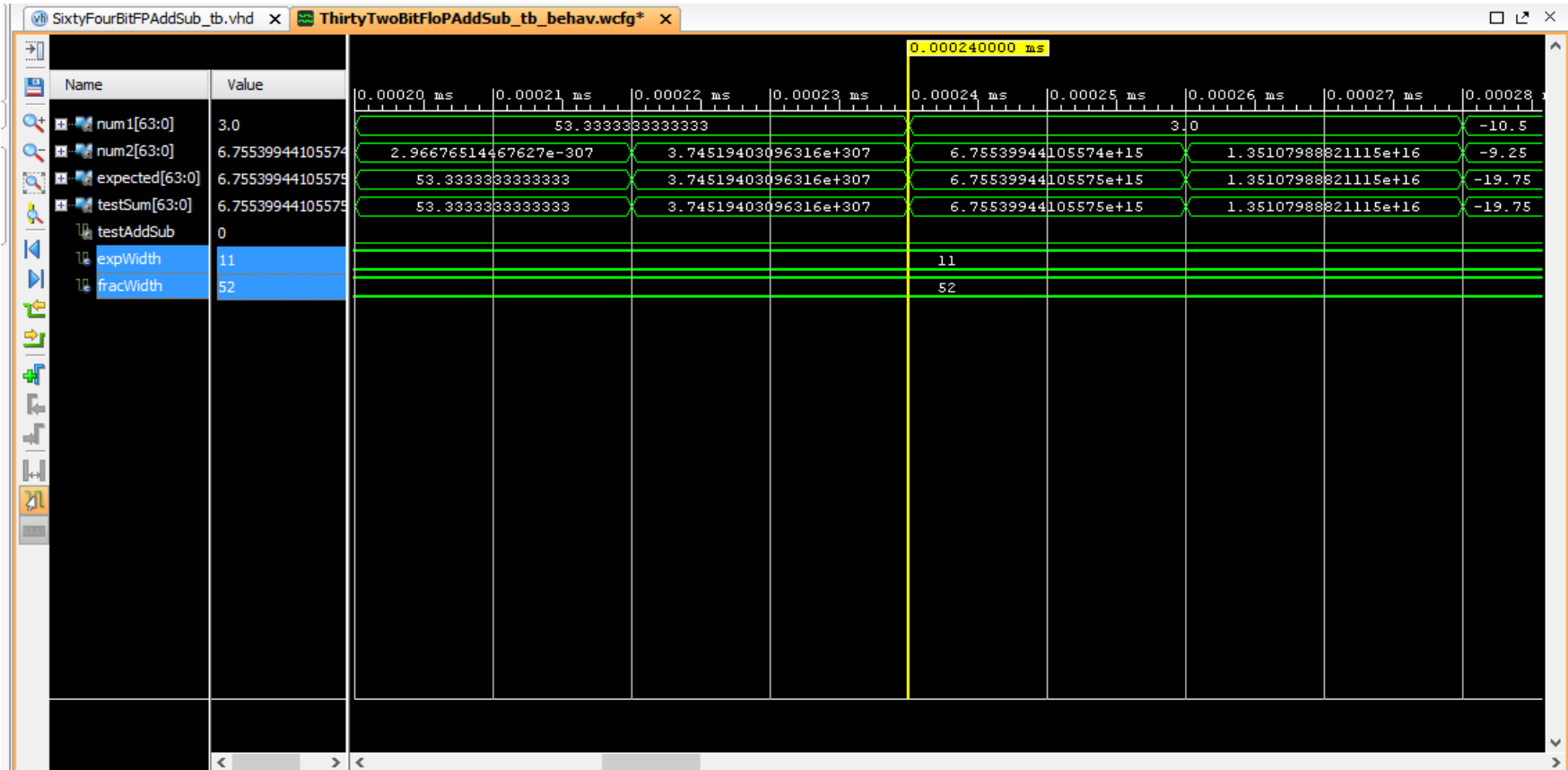

# Subtraction Simulation Part 1

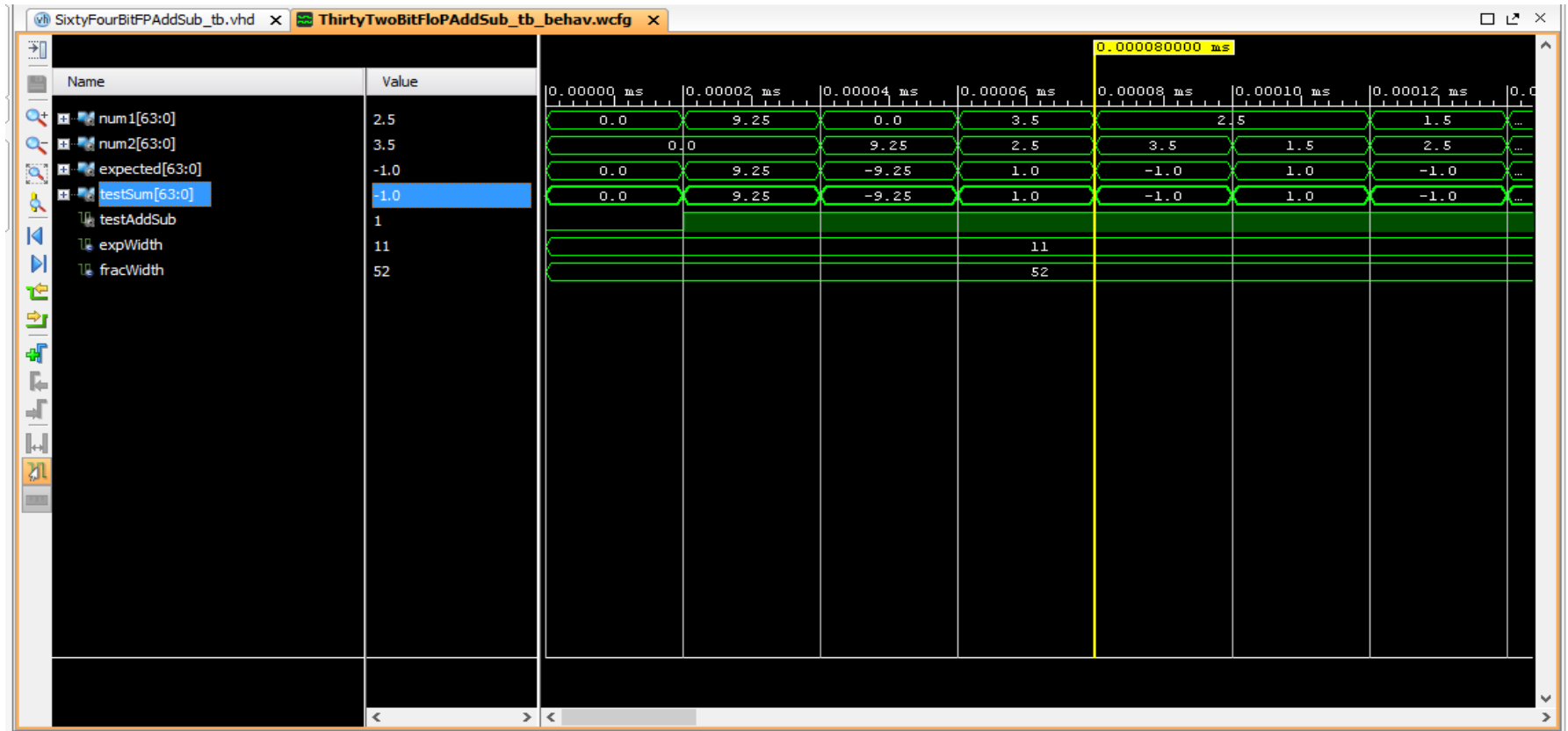

# Subtraction Simulation Part 2

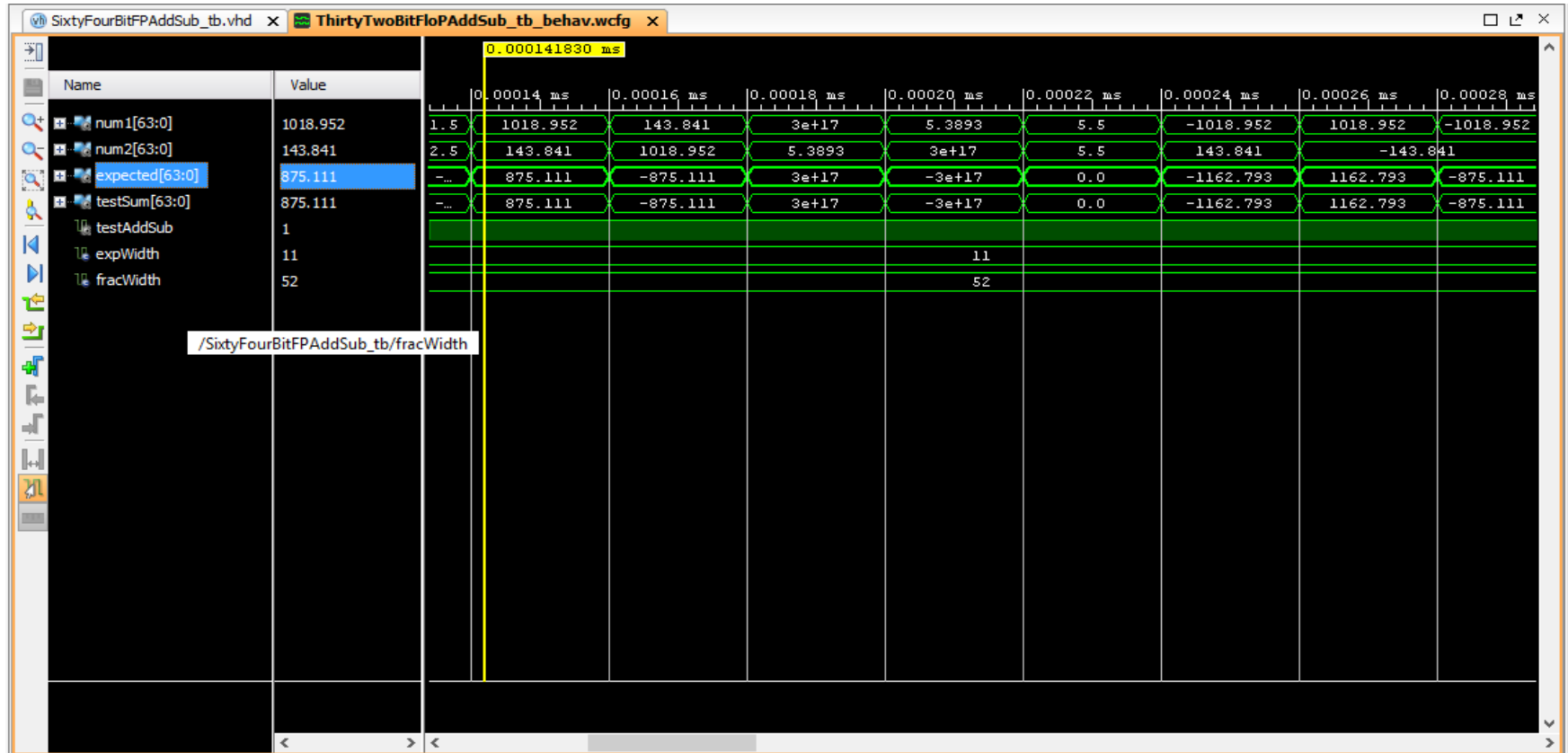


## DESIGN OF FLOATING POINT MULTIPLICATION EQUATIONS

- $b_1 = \pm s_1 \cdot 2^{e_1}$   
 $b_2 = \pm s_2 \cdot 2^{e_2}$
- $b_1 \times b_2 = (\pm s_1 \cdot 2^{e_1}) \times (\pm s_2 \cdot 2^{e_2}) = \pm (s_1 \times s_2) \cdot 2^{(e_1+e_2)}$
- $s = (s_1 \times s_2) \in [1, 4)$ .
 
## DESIGN OF FLOATING POINT MULTIPLICATION


- Sign Bit Calculation
- Multiplying two number's result is a negative sign if one of the multiplied numbers is of a negative value. By the aid of a truth table we find that this can be obtained by XORing the sign of two inputs.



A	B	Y=A⊕B
0	0	0
0	1	1
1	0	1
1	1	0


# DESIGN OF FLOATING POINT MULTIPLICATION .... Cont.

Flow chart Diagram

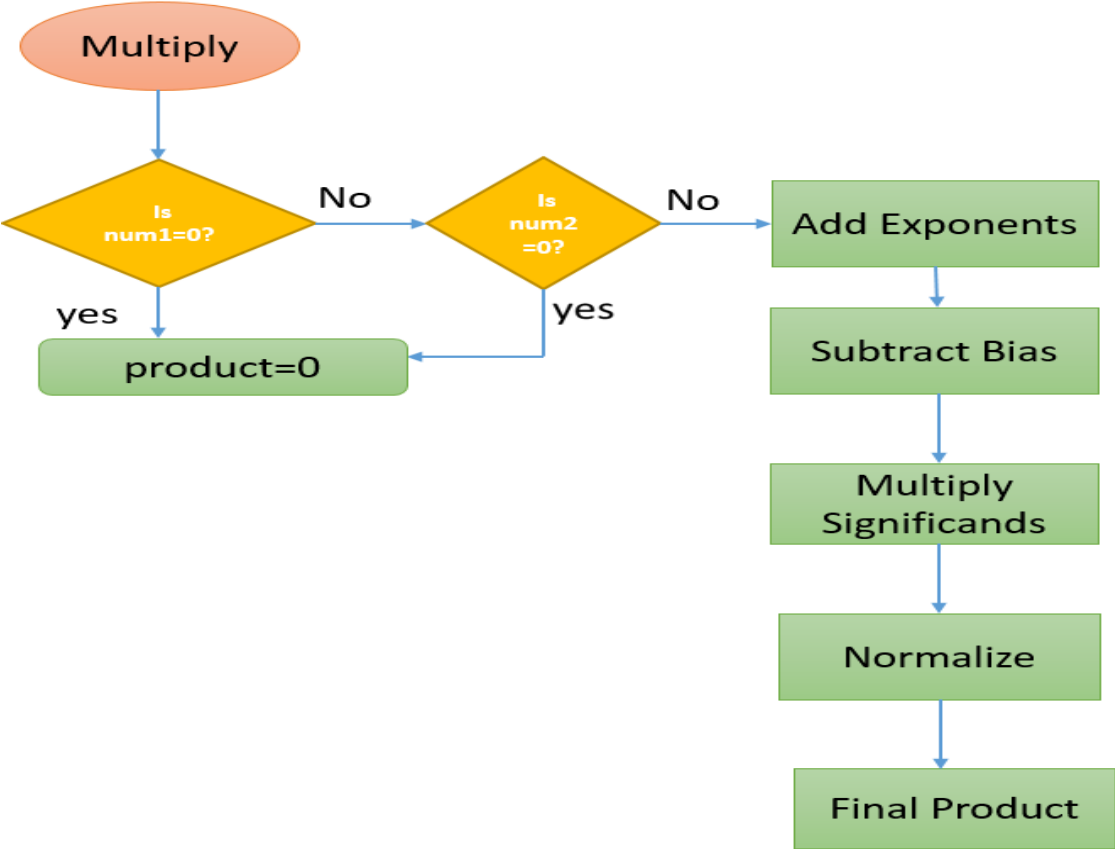





# Multiplication Simulation

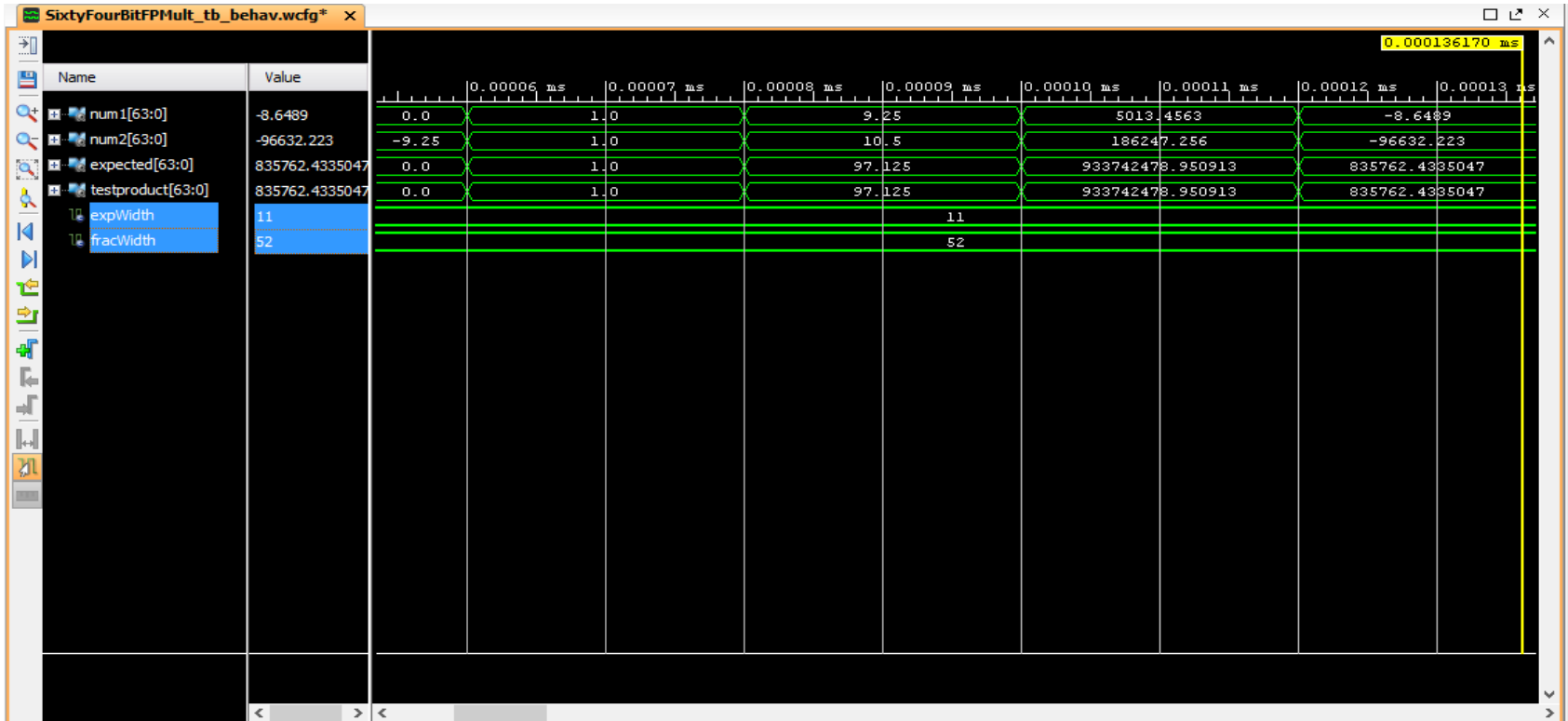


# Floating Point Top Circuit

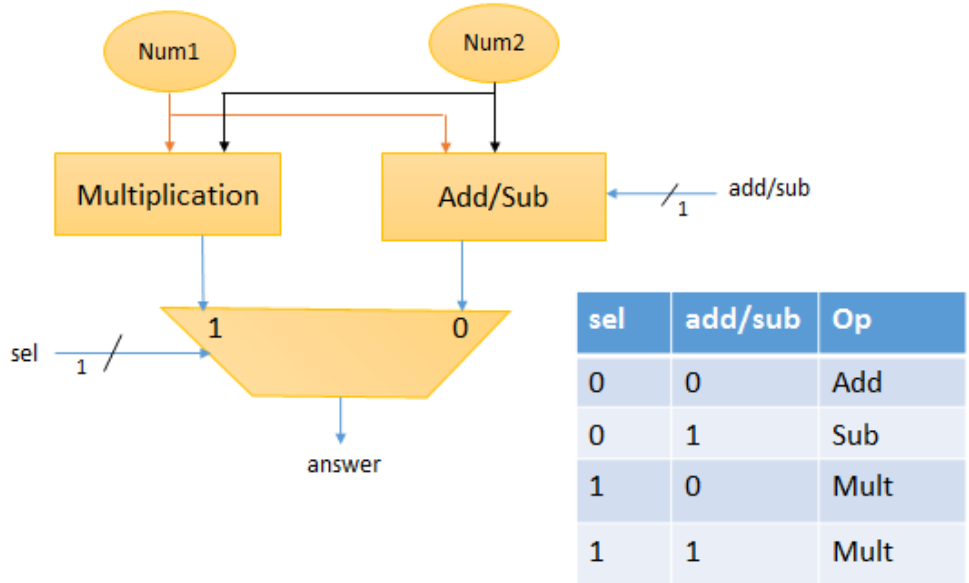

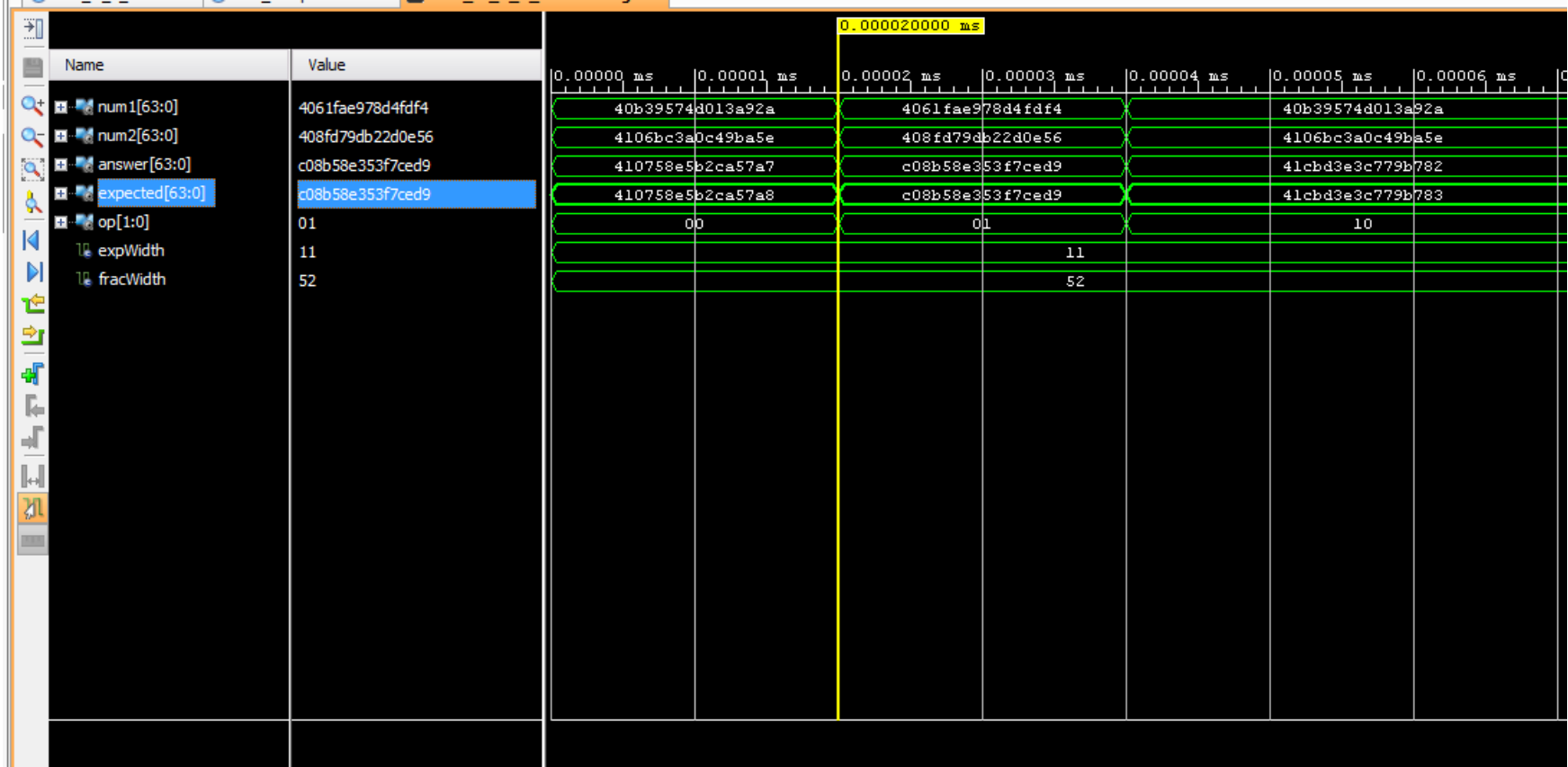
# Top Floating Point Arithmetic Circuit Simulation


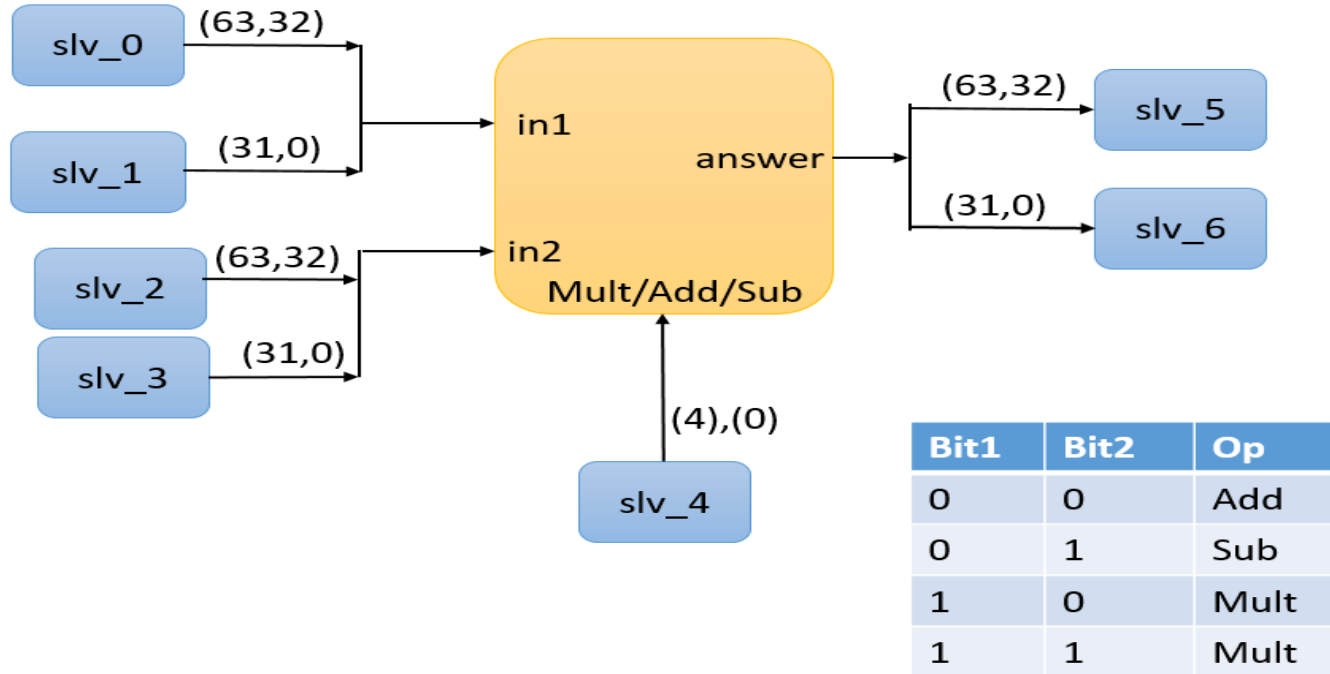
# Addition/Subtraction/Multiplication AXI4 lite Interface



# IP Block Diagram

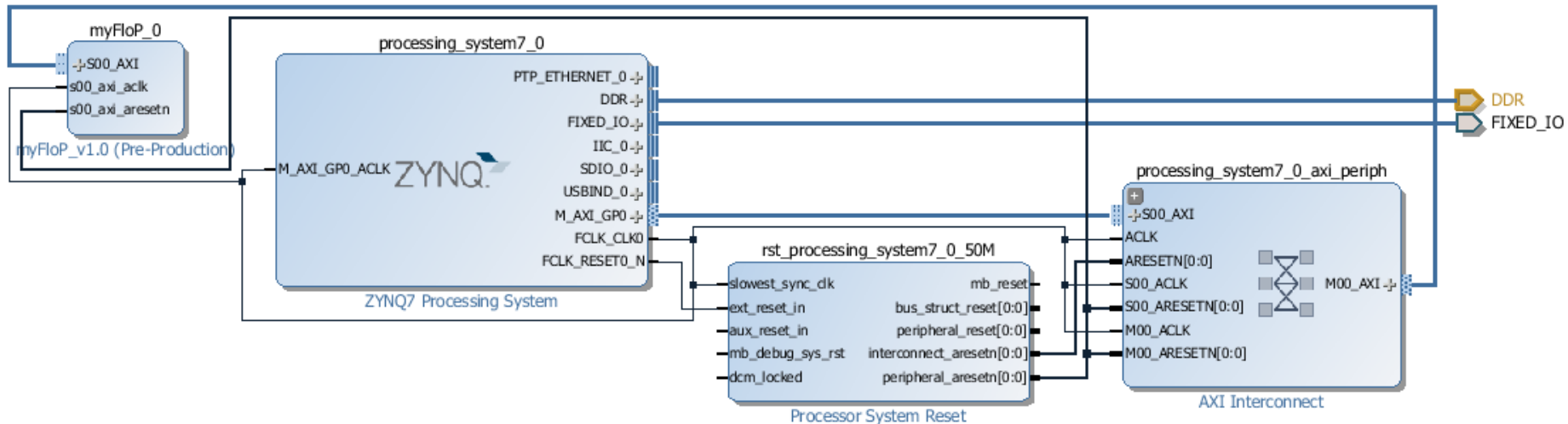

# Challenges/Improvements

- Challenges VHDL
- Improvements Testbench and Divider

Any Questions?

Thank You