

# DIGITAL LOGIC DESIGN

## VHDL Coding for FPGAs


### Unit 2

- ✓ *CONCURRENT DESCRIPTION*
  - *‘with-select’, ‘when-else’ statements*
  - *Arithmetic expressions*
  - *Examples: multiplexor, LUT, decoder, tri-state buffer*
 
## ✓ CONCURRENT DESCRIPTION

- In this description, the order of the statements is irrelevant: all the statements represent circuits that are working at the same time. This type of description is well-suited for combinatorial circuits.
- The use of sentences with ‘and’, ‘or’, ‘xor’, ‘nand’, ‘nor’, ‘xnor’, and ‘not’ is a basic instance of the concurrent description. It is sometimes called ‘horizontal description’.
- In Unit 4, the so-called ‘structural description’ is just a generalization of the concurrent description.
- Since we already know how to build circuits based on logic gates, we now present two concurrent assignment statements (*with - select*, *when - else*), which are far more powerful than the statements with logic gates when it comes to describe complex circuits.

- **CONCURRENT ASSIGNMENT STATEMENTS:**
  - **Selected Signal Assignment: WITH-SELECT:** This statement allows assigning values to a signal based on certain criterion.
  - **MUX 2-to-1:**



$$y = \bar{s}(a \bar{b} + a b) + s(\bar{a} b + a b)$$

$$y = \bar{s}a + sb$$

with s select: 's' specifies the selection criterion  
 when specifies the value assigned to 'y' for each value of 's'  
 when others: we need to include all the possible values of 's', that are 9 according to *std\_logic* type.

```


library ieee;
use ieee.std_logic_1164.all;

entity my_mux21 is
  port ( a, b, s: in std_logic;
        y: out std_logic);
end my_mux21;

architecture st of my_mux21 is
begin
  with s select
    y <= a when '0',
        b when others;
end st;
  
```

# Selected Signal Assignment (WITH – SELECT):

## MUX 8-to-1

 

```

library ieee;
use ieee.std_logic_1164.all;


entity my_mux81 is
  port ( a,b,c,d,e,f,g,h: in std_logic;
         s: in std_logic_vector (2 downto 0);
         y: out std_logic);
end my_mux81;

architecture struct of my_mux81 is
begin
  with s select
    y <= a when "000", -- note ',' instead of ';'
         b when "001",
         c when "010",
         d when "011",
         e when "100",
         f when "101",
         g when "110",
         h when others;
end struct;

```



 - **Selected Signal Assignment (WITH – SELECT):**
- **MUX 6-to-1**



```


library ieee;
use ieee.std_logic_1164.all;

entity my_mux61 is
  port ( a,b,c,d,e,f: in std_logic;
        s: in std_logic_vector (2 downto 0);
        y: out std_logic);
end my_mux61;

architecture struct of my_mux61 is
begin
  with s select
    y <= a when "000",
        b when "001",
        c when "010",
        d when "011",
        e when "100",
        f when "101",
        '- ' when others;
end struct;


```

 Value '-': Don't care output  
 It helps the synthesizer to optimize the circuit



# Selected Signal Statement

## Example: 4-to-1 LUT

 

```

library ieee;
use ieee.std_logic_1164.all;

entity my4to1LUT is
  generic (data: std_logic_vector (15 downto 0) :=x"FEAB");
  port ( ILUT: in std_logic_vector (3 downto 0);
        OLUt: out std_logic);
end my4to1LUT;

architecture struct of my4to1LUT is
begin
  with ILUT select
    OLUt <= data(0) when "0000",
           data(1) when "0001",
           data(2) when "0010",
           data(3) when "0011",
           data(4) when "0100",
           data(5) when "0101",
           data(6) when "0110",
           data(7) when "0111",
           data(8) when "1000",
           data(9) when "1001",
           data(10) when "1010",
           data(11) when "1011",
           data(12) when "1100",
           data(13) when "1101",
           data(14) when "1110",
           data(15) when "1111",
           '0' when others;
end struct;

```

generic clause: Note how 'data' is not an input, but a constant parameter

- **my4to1LUT.zip:**
  - my4to1LUT.vhd,
  - tb\_my4to1LUT.vhd

## 7-segment DECODER (outputs $\geq$ inputs)

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity sevensseg is
    port ( bcd: in std_logic_vector (3 downto 0);
          sevensseg: out std_logic_vector (6 downto 0);
          EN: in std_logic_vector (3 downto 0));
end sevensseg;
```

```
architecture struct of sevensseg is
    signal leds: std_logic_vector (6 downto 0);
begin
```

```
-- | a | b | c | d | e | f | g |
-- |leds6|leds5|leds4|leds3|leds2|leds1|leds0|
```

```
with bcd select
```

```
    leds <= "1111110" when "0000",
           "0110000" when "0001",
           "1101101" when "0010",
           "1111001" when "0011",
           "0110011" when "0100",
           "1011011" when "0101",
           "1011111" when "0110",
           "1110000" when "0111",
           "1111111" when "1000",
           "1111011" when "1001",
           "-----" when others;
```


```
-- Nexys4: LEDs are active low.
```

```
-- Each 7-seg display has an active-low enable
```

```
EN <= "1110";
```


```
sevensseg <= not(leds);
```

```
end struct;
```

 

➤ **sevensseg.zip:** sevensseg.vhd,  
tb\_sevensseg.vhd, sevensseg.ucf

## Decoder 2-to-4 with enable:

 

```

library ieee;
use ieee.std_logic_1164.all;

entity dec2to4 is
  port (w: in std_logic_vector (1 downto 0);
        E: in std_logic;
        y: out std_logic_vector (3 downto 0));
end dec2to4;

architecture struct of dec2to4 is
  signal Ew: std_logic_vector (2 downto 0);
begin
  Ew <= E & w; -- concatenation
  with Ew select
    y <= "0001" when "100",
         "0010" when "101",
         "0100" when "110",
         "1000" when "111",
         "0000" when others;
end struct;

```




▪ **CONCURRENT ASSIGNMENT STATEMENTS :**

▪ **Conditional signal assignment: WHEN - ELSE:**

Similarly to the selected signal assignment, this statement allows a signal to take one out of many values based on a certain condition. The syntax however is different and it allows to describe circuits in a more compact fashion.

▪ **Example: MUX 2-to-1**

 

```

library ieee;
use ieee.std_logic_1164.all;

entity mux21_cond is
  port ( a, b, s: in std_logic;
         y: out std_logic);
end mux21_cond;

```


```

architecture est of mux21_cond is
begin
  y <= a when s = '0' else b;
end est;

```

- If the condition on **when** is FALSE, we assign a value to 'y' after **else**. This assignment can also be conditioned by another **when-else** clause (see next example)

 - **Conditional signal assignment (WHEN - ELSE):**
- **Example:** MUX 4-to-1



- Note that the assignment on 'b' is conditioned by another **when-else** clause. Same for 'c'. Only the assignment of 'd' is not conditioned. There is no limit to the number of nested conditions.

```

library ieee;
use ieee.std_logic_1164.all;


entity mux41_cond is
  port (a, b, c, d: in std_logic;
        s: in std_logic_vector (1 downto 0);
        y: out std_logic);
end mux41_cond;

architecture est of mux41_cond is
begin
  y <= a when s = "00" else
      b when s = "01" else
      c when s = "10" else
      d;
end est;

```

# Conditional signal assignment (WHEN - ELSE):

## Example: Priority Encoder 4-to-2

 

w <sub>3</sub>	w <sub>2</sub>	w <sub>1</sub>	w <sub>0</sub>	y <sub>1</sub>	y <sub>0</sub>	z
0	0	0	0	0	0	0
1	x	x	x	1	1	1
0	1	x	x	1	0	1
0	0	1	x	0	1	1
0	0	0	1	0	0	1

**when-else** has a priority level,  $\Rightarrow$  it is easy to describe a priority encoder. With **with-select**, this circuit description would be very tedious.  $\triangleright$

```

library ieee;
use ieee.std_logic_1164.all;

entity my_prienc is
  port ( w: in std_logic_vector (3 downto 0);
        y: out std_logic_vector (1 downto 0);
        z: out std_logic);
end my_prienc;


architecture struct of my_prienc is
begin
  y <= "11" when w(3) = '1' else
      "10" when w(2) = '1' else
      "01" when w(1) = '1' else
      "00";
  z <= '0' when w = "0000" else '1';
  -- If no input is '1', z is '0'
end struct;

```
 
### Example: Priority encoder 8 to 3:

$\triangleright$  **my\_prienc8to3.zip**: my\_prienc8to3.vhd, tb\_my\_prienc8to3.vhd, my\_prienc8to3.ucf

- **Conditional signal assignment (WHEN - ELSE):**
- **Example:** 4-bit comparator



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- unsigned #s

```

```

entity my_comp is
  port ( A,B: in std_logic_vector (3 downto 0);
         AeqB, AgB, AlB: out std_logic);
end my_comp;

```

```

architecture struct of my_comp is
begin

```

```

    AeqB <= '1' when A = B else '0';
    AgB  <= '1' when A > B else '0';
    AlB  <= '1' when A < B else '0';

```


```

end struct;

```

- Note the use of the operators '=', '>', '<' to compare integer numbers
- Always indicate what type of numbers we are working with. In the example we are using unsigned numbers. For 2's complement, use 'signed'.

 - **Conditional Signal Assignment (WHEN - ELSE):**
- **Example:** Demultiplexor



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity my_demux is
  port ( s: in std_logic_vector (1 downto 0);
        x: in std_logic;
        a,b,c,d: out std_logic);
end my_demux;

```

```

architecture struct of my_demux is
begin

```

```

  a <= x when s = "00" else '0';
  b <= x when s = "01" else '0';
  c <= x when s = "10" else '0';
  d <= x when s = "11" else '0';

```


```

end struct;

```

- Concurrent  
Description: Note that the order of the statements is not relevant.

 - **Example:** 4-to-1 Bus Mux using with-select and when-else.



```

library ieee;
use ieee.std_logic_1164.all;

entity my_busmux4to1 is
    generic (N: INTEGER:= 8);
    port (a,b,c,d: in std_logic_vector (N-1 downto 0);
          s: in std_logic_vector (1 downto 0);
          y_r, y_t: out std_logic_vector (N-1 downto 0));
end my_busmux4to1;

architecture structure of my_busmux4to1 is
begin
    with s select
        y_r <= a when "00",
              b when "01",
              c when "10",
              d when others;

        y_t <= a when s = "00" else
              b when s = "01" else
              c when s = "10" else
              d;
end structure;


```

'generic' clause: It allows the definition of signals with customizable widths.

➤ **my\_busmux4to1.zip:** my\_busmux4to1.vhd, tb\_my\_busmux4to1.vhd

- **Conditional Signal Assignment (WHEN - ELSE):**

- **Example:** Tri-State Buffer

 

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity my_tristate is
  port ( A, OE: in std_logic;
        F: out std_logic);
end my_tristate;
```

```
architecture struct of my_tristate is
begin
```

```
  F <= A when OE = '1' else 'Z';
```

```
end struct;
```

➤ **my\_tristate.zip:** my\_tristate.vhd, tb\_my\_stristate.vhd,  
my\_tristate.ucf

- **Conditional Signal Assignment (WHEN - ELSE):**

- **Example:** Bidirectional Port

```
library ieee;
use ieee.std_logic_1164.all;
```


```
entity my_bidport is
  port ( WDAT: in std_logic_vector (3 downto 0);
        RDAT: out std_logic_vector (3 downto 0);
        OE: in std_logic;
        DATA: inout std_logic_vector (3 downto 0));
end my_bidport;
```

```
architecture struct of my_bidport is
```

```
begin
```

```
  DATA <= WDAT when OE = '0' else (others => 'Z');
  RDAT <= DATA when OE = '1' else (others => 'Z');
```

```
end struct;
```

 



## Example: Bidirectional Port (test bench)

```
library ieee;
use ieee.std_logic_1164.all;
```


```
entity my_bidport is
end my_bidport;
```

```
architecture struct of my_bidport is
```

```
...
begin
  uut: my_bidport port map (WDAT, RDAT, OE, DATA);
```

```
  process
  begin
    DATA <= "ZZZZ"; wait for 100 ns;
    OE <= '0'; WDAT <= x"A"; DATA <= "ZZZZ"; wait for 20 ns;
    OE <= '1'; DATA <= x"E"; wait for 20 ns;
    OE <= '0'; WDAT <= x"9"; DATA <= "ZZZZ"; wait for 20 ns;
    OE <= '1'; DATA <= x"3"; wait for 20 ns;
    DATA <= x"C"; wait;
```

```
  end process
end;
```

 

To avoid data contention, make sure that **DATA = Z** when **DATA** is to be an output.

➤ **my\_bidport.zip:** my\_bidport.vhd, tb\_my\_bidport.vhd

## ■ ARITHMETIC STATEMENTS:

- We can use the operators  $+$ ,  $-$ , and  $*$  for rapid specification of arithmetic operations for integer numbers.
- For  $+/ -$ , the result and the operands must have the same bit width.
- **Example:** Adder/subtractor implemented by multiplexing the adder and subtractor outputs:

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```

Be aware of:

- Integer numerical representation (signed/unsigned)
- Bit Width: If overflow occurs, the result will not be correct. Here, you might need to sign-extend the input operands.

```
entity ex_addsub is  
    port (a,b: in std_logic_vector (3 downto 0);  
          s: in std_logic;  
          f: out std_logic_vector (3 downto 0));  
end ex_addsub;  
  
architecture structure of ex_addsub is  
begin  
    with s select  
        f <= a+b when '0',  
          a-b when others;  
end structure;
```

- **ex\_addsub.zip:** ex\_addsub.vhd,  
tb\_ex\_addsub.vhd, ex\_addsub.xdc