


Final Exam

(December 8th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

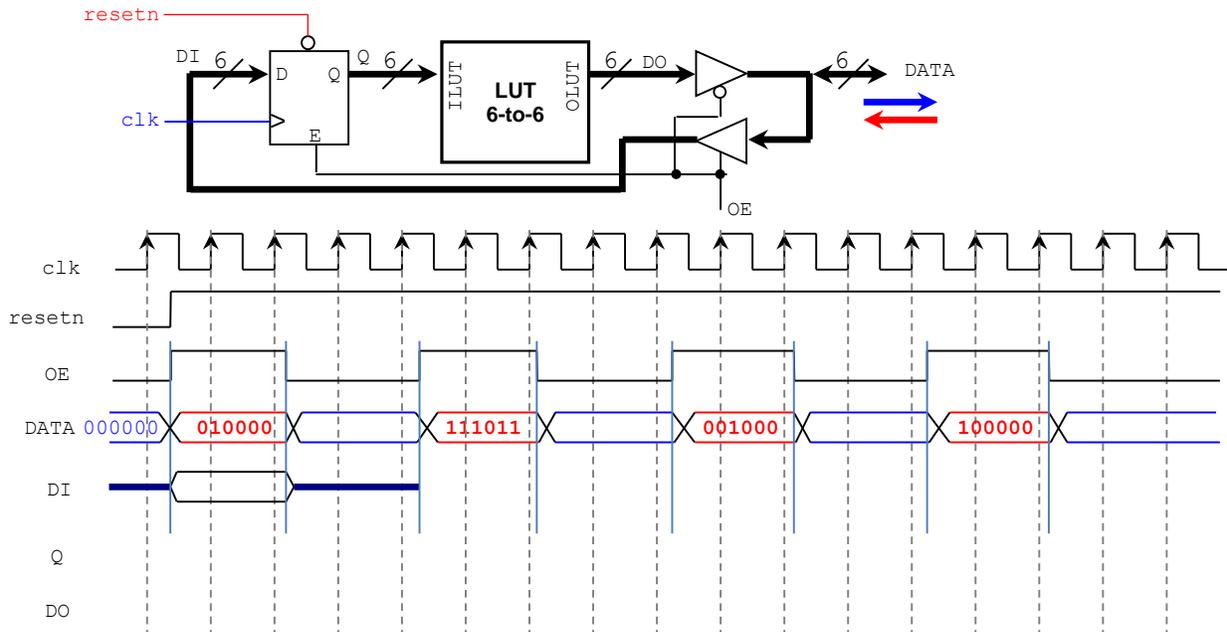
PROBLEM 1 (12 PTS)

- Given the following circuit, complete the timing diagram.
 The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where $ILUT$ is a 6-bit unsigned number.
 For example $ILUT = 35 (100011_2) \rightarrow OLUT = \lceil \sqrt{35} \rceil = 6 (000110_2)$



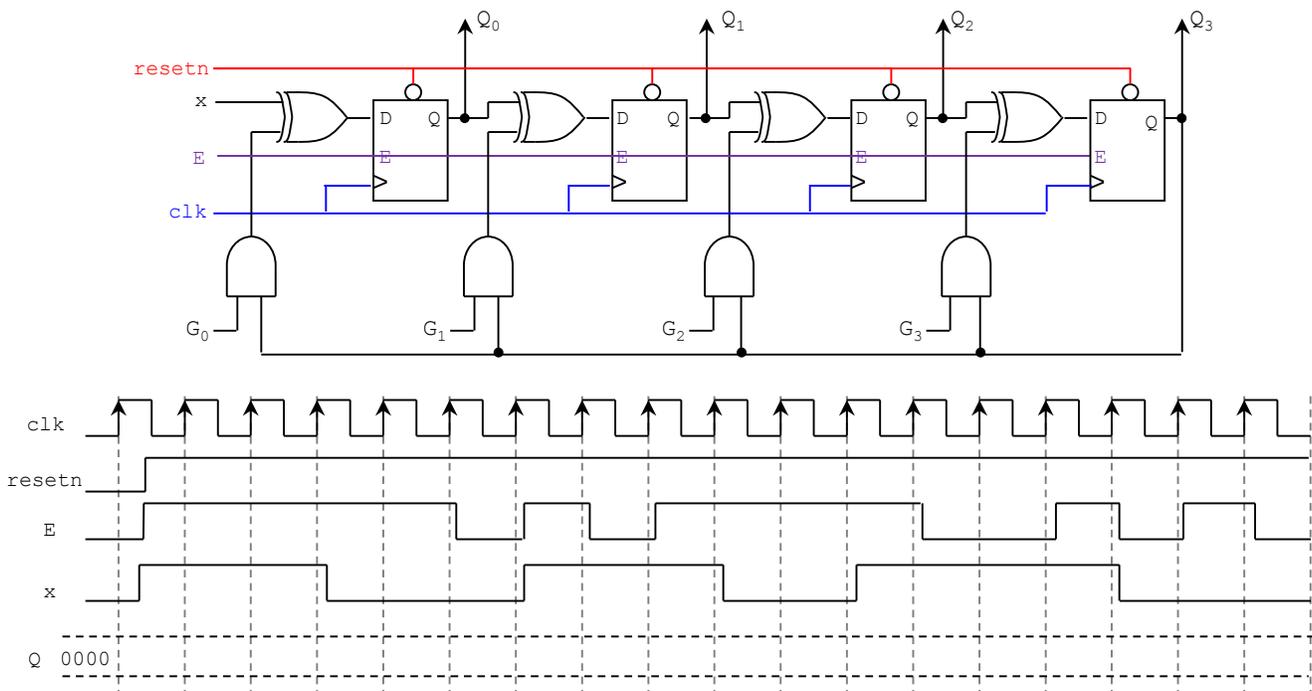
PROBLEM 2 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



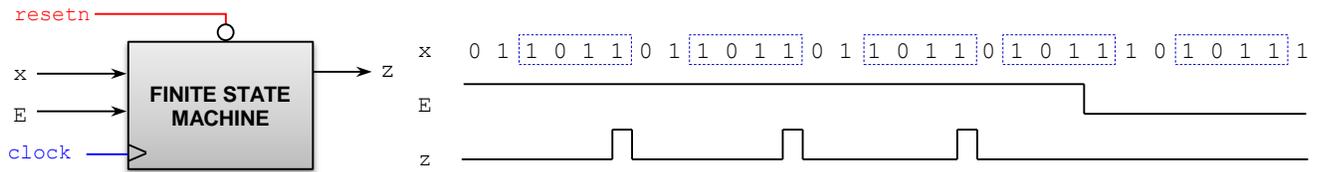PROBLEM 3 (22 PTS)


- Sequence detector: The machine has to generate $z = 1$ when it detects the sequence 1011. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid.




- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with inputs E and x and output z . Is this a Mealy or a Moore machine? Why? (15 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (4 pts)
- Sketch the circuit. (3 pts)

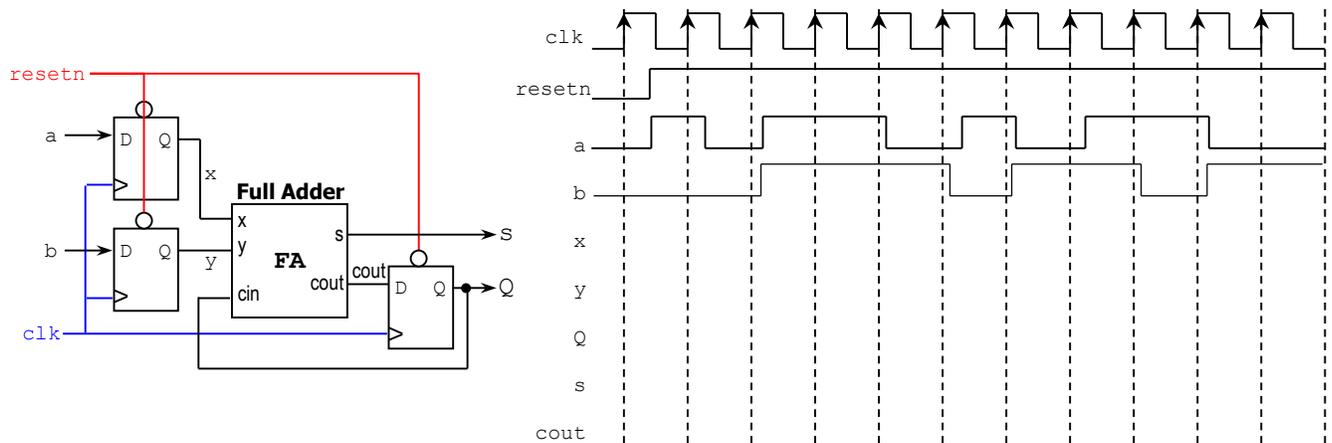PROBLEM 4 (20 PTS)

- Complete the timing diagram of the circuit shown below: (8 pts)



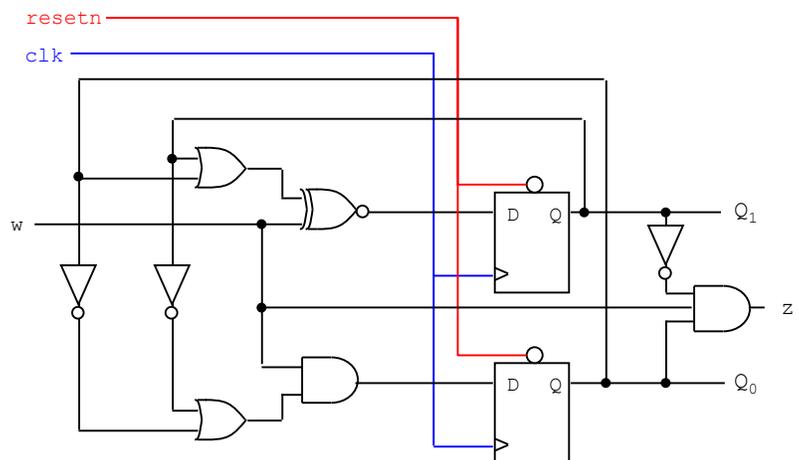- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (12 pts)



PROBLEM 5 (16 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;

                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;

                when S3 =>
                    if q = '1' then y <= S3; else y <= S2; end if;

            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                if p = '0' then
                    w <= '1'; x <= '1';
                end if;
            end if;

            when S2 => if q = '0' then x <= '1'; end if;
                if p = '0' then z <= '1'; end if;

            when S3 => if q = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

