

ECE 278 Final Project

2 x 2 Matrix Multiplier

Chris Folden
Dane Zetouna
Jimmy Galat
Alec Spurlock

12-1-2016


How Matrix Multiplication Works


$$\begin{bmatrix} e & f \\ g & h \end{bmatrix} \begin{bmatrix} a & b \\ c & d \end{bmatrix} = \begin{bmatrix} ae + cf & be + df \\ ag + ch & bg + dh \end{bmatrix}$$

- A matrix organizes a group of numbers using specified arithmetic rules.
- Matrix multiplication is a binary operation that generates a single matrix from two matrices.
- This is applicable to many different mathematical disciplines as well as several branches of science.

Applications of Matrix Multiplication

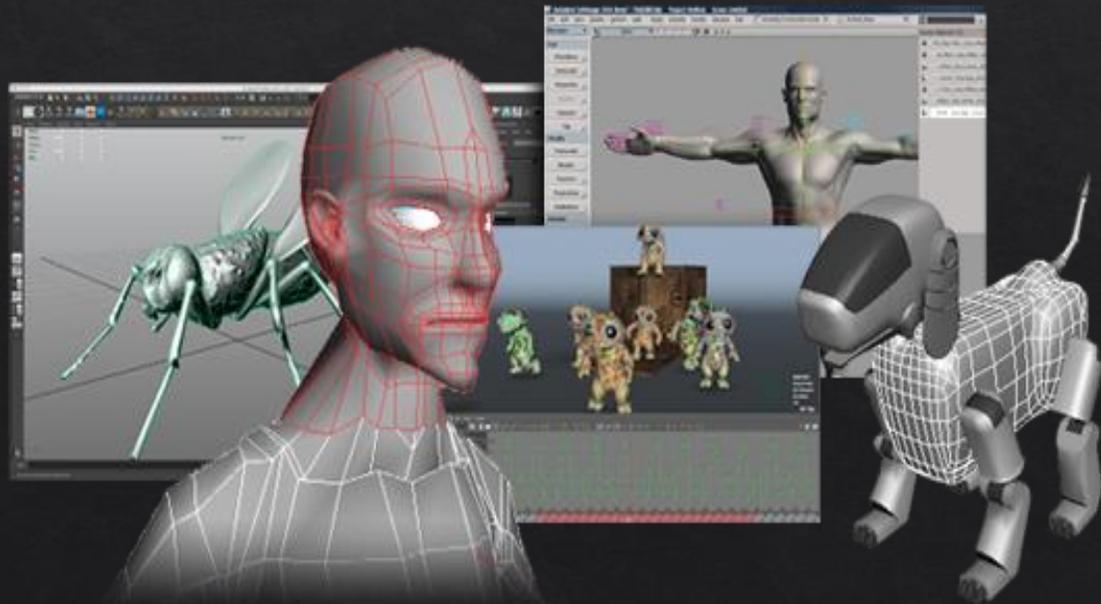- Matrix multiplication is applicable to many different mathematical disciplines as well as several branches of science.
- One application you can relate to easily is perspective projections, which is the foundation for 3D animation.
- Another example is in the field of medicine, CAT scans and MRI's use matrices.



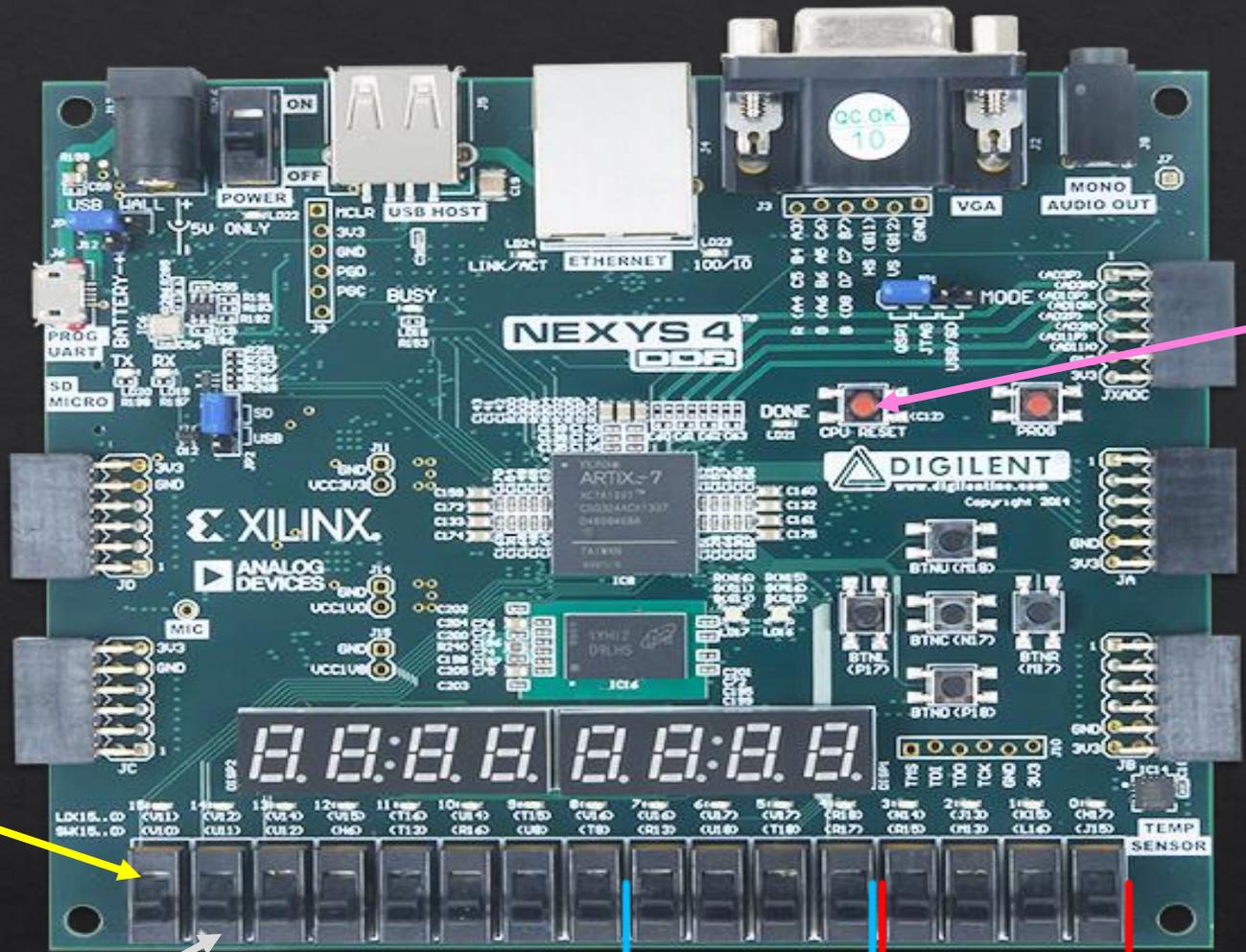

Reset

Enabler/Writer

Operator/Reader


Address

Data in

Layout of the Project

- After many ideas were discussed, the plan was to have a 4-bit address input into the decoder.
- This will select which of the 8 registers to write into and which registers to read the data from.
- From there, the data will be taken from the first 8 registers and then multiplied and added together in the format shown in the first slide.

Matrix Multiplication Top-File

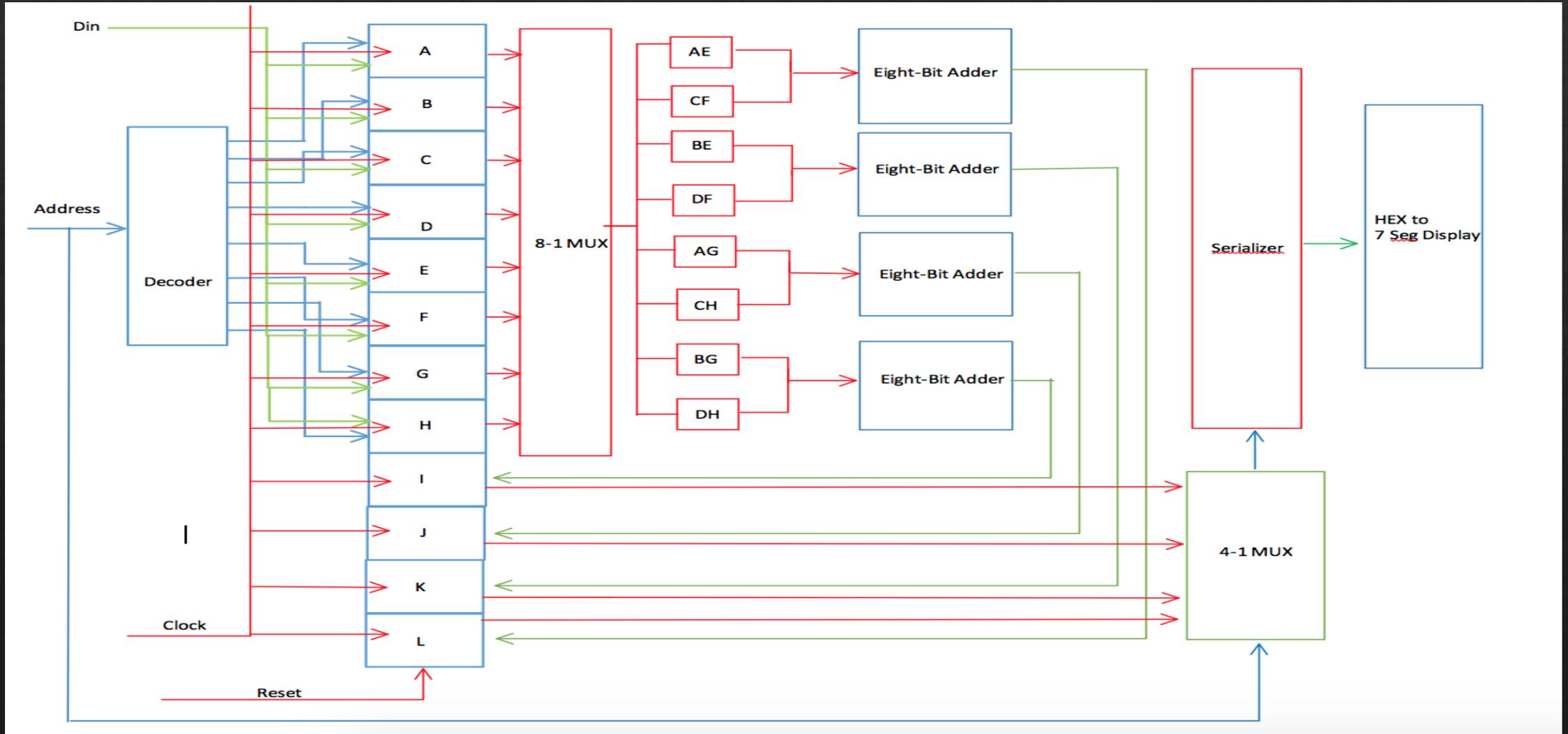

Code Sample


```
a20: Multiplexer port map (mux0 => qmux0, mux1 => qmux1, mux2 => qmux2, mux3 => qmux3, mux4 => qmux4, mux5 => qmux5, mux6 => qmux6, mux7 => qmux
mux_out => h, address => "0111", inv_E => Operator);

a21: Multiplexer2 port map (mux8 => qmux8, mux9 => qmux9, mux10 => qmux10, mux11 => qmux11, mux_out => MatrixOut, address => address, inv_E => 0

f0: Array_Multiplier port map (a => a, b => e, p => ae);-- multiplies a and e
f1: Array_Multiplier port map (a => b, b => g, p => bg);-- multiplies b and g
f2: Array_Multiplier port map (a => a, b => f, p => af);-- multiplies a and f
f3: Array_Multiplier port map (a => b, b => h, p => bh);-- multiplies b and h
f4: Array_Multiplier port map (a => c, b => e, p => ce);-- multiplies c and e
f5: Array_Multiplier port map (a => d, b => g, p => dg);-- multiplies d and g
f6: Array_Multiplier port map (a => c, b => f, p => cf);-- multiplies c and f
f7: Array_Multiplier port map (a => d, b => h, p => dh);-- multiplies d and h

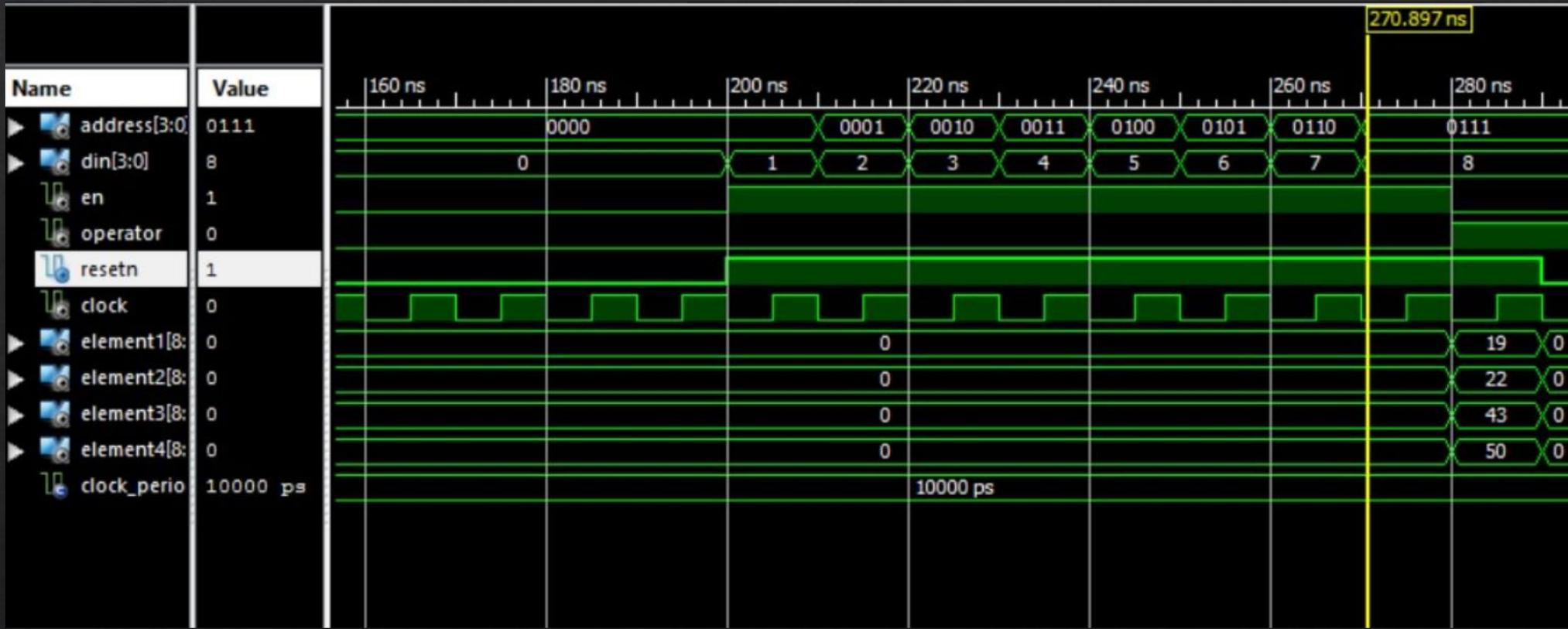f8: Five_Bit_Adder port map (Cin => '0', x => ae, y => bg, s => ae_bg, Cout => C_ae_bg); -- Adding ae + bg
ele1 <= C_ae_bg & ae_bg;
```





Demonstration Time!!



Problems and Possible Improvements

- Signed Numbers
- Displaying in Decimal
- Bigger Matrices