

Digital Alarm Clock

(Ben Jackson, Devin Liu)

Electrical and Computer Engineering Department

School of Engineering and Computer Science

Oakland University, Rochester, MI

E-mails: bwjacks2@oakland.edu, daliu@oakland.edu

Abstract: Our project contains an attempt to develop a digital clock containing the functionality of a clock and an alarm. Switches and buttons are utilized to set the alarm times, and the activation the RGB LEDs will represent the alarm. The display used will be four of the eight, 7-segment display.

I. INTRODUCTION

The project's scope is designing and writing code that would reflect the use of a 24 hour digital alarm clock. This will be a running clock that also has an alarm. The alarm is represented by the use of RGB LEDs, which turn on when the alarm time is equal to that of the clock time. The alarm itself can be set quickly on the fly. The intent was to program a fully fledged operating alarm clock, which would have the ability to set a clock and an alarm.

II. METHODOLOGY

A. Design

The plan is to use four, seven segment displays to in the orientation of HH:MM to represent the clock. To represent this, we used the 10 millisecond counter that was demonstrated in class that originally counts in 10 millisecond increments that counted up to one minute. We modified this counter with two additional modulo counters, and adjusted the increment counter to count every 1 second. Thus we utilized six total counters that represent the HH:MM:SS, but we'll only display the HH:MM on the seven segment displays.

We used the switches to set our alarm, using switches J15 to R15 to resent the ones' minutes, R17 to R13 as the tens' minutes, T8 to T13 as the ones' hours, and H6 to V10 as the tens' hours. We used the right half of the segment displays, an0 to an3, to display our time. The values from counters are stored in a multiplexor which is then checked every one millisecond to update the segment displays.

Four 4-bit registers are used to store the alarm time. Upon the press of a push button (N17), the values on the switches are then stored in these four registers (See Figure 1, for the ASM model of our second state machine).

From state two, it constantly checks for when the values stored on the registers are equal to that of the

clock, it would then move to state three. In state three, it activates our RGB LED's, one which produces white and one which produces a purple color. From state three it would wait for another push button to be pushed (P18), to move back to state one, which has the RGB LED's off and waiting for the alarm to be enabled again.

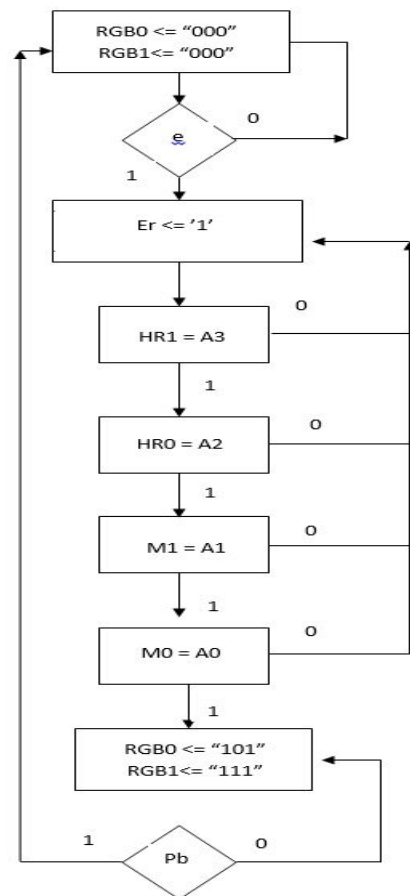


Figure 1: Alarm Control Finite State Machine

