



# Traffic Buildup Detection System

By: Tammy Luu, Yinkai Liu, Shengzhuo Liu, Patrick Pantis

278 Digital Logic – Final Project – Fall 2016

School of Engineering and Computer Science, Oakland University

Instructor: Prof. Daniel Llamocca Obregon


# Introduction

- The Purpose of this project is to create a traffic buildup detection system that will better help the flow of traffic at a traffic intersection.
- By using state codes that loop repeatedly, the traffic light system could be created. Having a push button ground sensor, the code could determine if there was a build up of cars at the traffic intersection. This is done to prevent build up of traffic.
- During midnight traffic slows down significantly, so the main road is implemented to change to a flashing yellow light, as well as the side roads are changed to a flashing red. This is done to prevent cars waiting at a light when no other vehicles are driving at night.
- With all this a clock is displayed on a 7-segment display to show the timing of the lights at the traffic intersect. This makes it easier to follow the timing of the state codes as well as implementing a cross walk timer for pedestrians.


 
# Methodology

The software used in this project is Xilinx ISE Webpack Design Software 14.7 coding with VHDL. All the code was then programmed to our Nexys™-4DDR Artix-7 FPGA board to displaying the traffic intersection lights. These are the Methodology of the coding in our project:


- Traffic Light
- Blinking Yellow
- Main Road Traffic Build Up Sensor
- 7-seg Timing display




# ASM - Main and Side Traffic Light

  

# Traffic Detected

 

# Yellow Flickering Light

 

# Constraints

```
## Clock signal
NET "clk" LOC = "E3" | IOSTANDARD = "LVCMOS33"; #Bank = 35, Pin name = #IO_L12P_T1_MRCC_35, Sch name = clk100mhz
NET "clk" TNM_NET = sys_clk_pin;
TIMESPEC TS_sys_clk_pin = PERIOD sys_clk_pin 100 MHz HIGH 50%;

## BUTTONS
NET "day" LOC=N17 | IOSTANDARD=LVCMOS33; #IO_L9P_T1_DQS_14
NET "night" LOC=P18 | IOSTANDARD=LVCMOS33; #IO_L9N_T1_DQS_D13_14
NET "traf" LOC=P17 | IOSTANDARD=LVCMOS33; #IO_L12P_T1_MRCC_14
#NET "btnr" LOC=M17 | IOSTANDARD=LVCMOS33; #IO_L10N_T1_D15_14
#NET "btneu" LOC=M18 | IOSTANDARD=LVCMOS33; #IO_L4N_T0_D05_14

## LEDs
NET "ld<0>" LOC=H17 | IOSTANDARD=LVCMOS33; #IO_L18P_T2_A24_15
NET "ld<1>" LOC=K15 | IOSTANDARD=LVCMOS33; #IO_L24P_T3_RS1_15
NET "ld<2>" LOC=J13 | IOSTANDARD=LVCMOS33; #IO_L17N_T2_A25_15
NET "ld<3>" LOC=N14 | IOSTANDARD=LVCMOS33; #IO_L8P_T1_D11_14
NET "ld<4>" LOC=R18 | IOSTANDARD=LVCMOS33; #IO_L7P_T1_D09_14
NET "ld<5>" LOC=V17 | IOSTANDARD=LVCMOS33; #IO_L18N_T2_A11_D27_14

## 7 segment display
NET "seg<6>" LOC=T10 | IOSTANDARD=LVCMOS33; #IO_L24N_T3_A00_D16_14
NET "seg<5>" LOC=R10 | IOSTANDARD=LVCMOS33; #IO_25_14
NET "seg<4>" LOC=K16 | IOSTANDARD=LVCMOS33; #IO_25_15
NET "seg<3>" LOC=K13 | IOSTANDARD=LVCMOS33; #IO_L17P_T2_A26_15
NET "seg<2>" LOC=P15 | IOSTANDARD=LVCMOS33; #IO_L13P_T2_MRCC_14
NET "seg<1>" LOC=T11 | IOSTANDARD=LVCMOS33; #IO_L19P_T3_A10_D26_14
NET "seg<0>" LOC=L18 | IOSTANDARD=LVCMOS33; #IO_L4P_T0_D04_14

NET "an<0>" LOC=J17 | IOSTANDARD=LVCMOS33; #IO_L23P_T3_F0E_B_15
NET "an<1>" LOC=J18 | IOSTANDARD=LVCMOS33; #IO_L23N_T3_FWE_B_15
NET "an<2>" LOC=T9 | IOSTANDARD=LVCMOS33; #IO_L24P_T3_A01_D17_14
NET "an<3>" LOC=J14 | IOSTANDARD=LVCMOS33; #IO_L19P_T3_A22_15
NET "an<4>" LOC=P14 | IOSTANDARD=LVCMOS33; #IO_L8N_T1_D12_14
NET "an<5>" LOC=T14 | IOSTANDARD=LVCMOS33; #IO_L14P_T2_SRCC_14
NET "an<6>" LOC=K2 | IOSTANDARD=LVCMOS33; #IO_L23P_T3_35
NET "an<7>" LOC=U13 | IOSTANDARD=LVCMOS33; #IO_L23N_T3_A02_D18_14
```

# Code Traffic

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
entity traffic is
    port (clk: in STD_LOGIC;
          clr: in STD_LOGIC;
          sensor: in STD_LOGIC;
          clrr: in STD_LOGIC;
          lights: out STD_LOGIC_VECTOR(5 downto 0));
end traffic;

architecture traffic of traffic is
    type state_type is (s0, s1, s2, s3, s4, s5, s6, s7, s8, s9, s10);
    signal state: state_type;
    signal count: STD_LOGIC_VECTOR(5 downto 0);
    constant SEC10: STD_LOGIC_VECTOR(5 downto 0) := "011110";
    constant SEC15: STD_LOGIC_VECTOR(5 downto 0) := "101101";
    constant SEC3: STD_LOGIC_VECTOR(5 downto 0) := "001001";
    constant SEC1: STD_LOGIC_VECTOR(5 downto 0) := "000011";
    constant SEC: STD_LOGIC_VECTOR(5 downto 0) := "000001";
begin

process(clk, clrr, clr, sensor)
begin
    if clr = '1' then
        state <= s1;
        count <= "000000";
    elsif clrr = '1' then
        state <= s6;
        count <= "000000";
    elsif sensor = '1' then
        state <= s9;
        count <= "000000";

    else if clk'event and clk = '1' then
        case state is

            when s1 =>
                if count < SEC3 then
                    state <= s1;
                    count <= count + 1;
                else
                    state <= s2;
                    count <= "000000";
                end if;
            when s2 =>
                if count < SEC1 then
                    state <= s2;
                    count <= count + 1;
                else
                    state <= s3;
                    count <= "000000";
                end if;
            when s3 =>
                if count < SEC10 then
                    state <= s3;


```

```

else
    state <= s3;
    count <= "000000";
end if;
when s3 =>
    if count < SEC10 then
        state <= s3;
        count <= count + 1;
    else
        state <= s4;
        count <= "000000";
    end if;
when s4 =>
    if count < SEC3 then
        state <= s4;
        count <= count + 1;
    else
        state <= s5;
        count <= "000000";
    end if;
when s5 =>
    if count < SEC1 then
        state <= s5;
        count <= count + 1;
    else
        state <= s0;
        count <= "000000";
    end if;
when s0 =>
    if count < SEC15 then
        state <= s0;
        count <= count + 1;
    else
        state <= s1;
        count <= "000000";
    end if;
when s1 =>
    if count < SEC9 then
        state <= s1;
        count <= count + 1;
    else
        state <= s2;
        count <= "000000";
    end if;
when s2 =>
    if count < SEC30 then
        state <= s2;
        count <= count + 1;
    else
        state <= s3;
        count <= "000000";
    end if;
when s3 =>
    if count < SEC9 then
        state <= s3;
        count <= count + 1;
    else
        state <= s4;
        count <= "000000";
    end if;
when s4 =>
    if count < SEC9 then
        state <= s4;
        count <= count + 1;
    else
        state <= s8;
        count <= "000000";
    end if;
when s8 =>
    if count < SEC45 then
        state <= s8;
        count <= count + 1;
    else
        state <= s9;
        count <= "000000";
    end if;
when s9 =>
    if count < SEC3 then
        state <= s9;
        count <= count + 1;
    else
        state <= s10;
        count <= "000000";
    end if;
when s10 =>
    if count < SEC1 then
        state <= s10;
        count <= count + 1;
    else
        state <= s0;
        count <= "000000";
    end if;
when s0 =>
    if count < SEC45 then
        state <= s0;
        count <= count + 1;
    else
        state <= s5;
        count <= "000000";
    end if;
when s5 =>
    if count < SEC3 then
        state <= s5;
        count <= count + 1;
    else
        state <= s6;
        count <= "000000";
    end if;
when s6 =>
    if count < SEC3 then
        state <= s6;
        count <= count + 1;
    else
        state <= s0;
        count <= "000000";
    end if;
end process;

--Flashing Yellow Light
when s6 =>
    if count < SEC1 then
        state <= s6;
        count <= count + 1;
    else
        state <= s7;
        count <= "000000";
    end if;
when s7 =>
    if count < SEC then
        state <= s7;
        count <= count + 1;
    else
        state <= s6;
        count <= "000000";
    end if;
when s9 =>
    if count < SEC3 then

```

 

--when the ground sensor is detected, the light is changed to red, yellow and then green, red.

# Code Traffic

```

else
    state <= s6;
    count <= "0000000";
end if;
--when the ground sensor is detected, the light is changed to red, yellow and then green, red.
when s9 =>
    when s9 =>
        if count < SEC3 then
            state <= s9;
            count <= count +1;
        else
            state <= s10;
            count <= "0000000";
        end if;
    when s10 =>
        if count < SEC1 then
            state <= s10;
            count <= count +1;
        else
            state <= s8;
            count <= "0000000";
        end if;
    when s8 =>
        if count < SEC15 then
            state <= s8;
            count <= count +1;
        else
            state <= s4;
            count <= "0000000";
        end if;
    when others =>
        state <= s1;
    end case;
end if;
end process;

C2: process(state)
begin
    case state is
        when s0 => lights <= "100001";
        when s1 => lights <= "100010";
        when s2 => lights <= "100100";
        when s3 => lights <= "001100";
        when s4 => lights <= "010100";
        when s5 => lights <= "100100";
        when s6 => lights <= "100010";
        when s7 => lights <= "0000000";
        when s8 => lights <= "001100";
        when s9 => lights <= "100010";
        when s10 => lights <= "100100";
        when others => lights <= "100010";
    end case;
end process;
end traffic;

```

		Branch Street			Main street]		
Time	RED	YELLOW	GREEN	RED	YELLOW	GREEN	
3	1	0	0	0	1	0	
1	1	0	0	1	0	0	
10	0	0	1	1	0	0	
3	0	1	0	1	0	0	
1	1	0	0	1	0	0	
15	1	0	0	0	0	1	

		Branch Street			Main street]		
Time	RED	YELLOW	GREEN	RED	YELLOW	GREEN	
3	1	0	0	0	1	0	
1	1	0	0	1	0	0	
15	0	0	1	1	0	0	

# Code Digi Clk

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity digi_clk is
port (clr: in std_logic;
      clrr: in std_logic;
      sensor: in std_logic;
      clk1 : in std_logic;
      seconds : out std_logic_vector(5 downto 0)
      );
end digi_clk;

architecture Behavioral of digi_clk is
signal sec : integer range 0 to 60 :=0;
signal count : integer :=1;
signal clk : std_logic :='0';
begin
seconds <= conv_std_logic_vector(sec,6);
--clk generation.For 100 MHz clock this generates 1 Hz clock.
process (clk1,clr,clrr,sensor)
begin
if clr = '1' then
count <= 0;
elsif sensor= '1' then
count <= 0;
elsif clrr = '1' then
count <= 0;
else if (clk1'event and clk1='1') then
count <=count+1;
if(count = 50000000) then
clk <= not clk;
count <= 1;
end if;
end if;
end if;
end process;
process (clk,clr,sensor,clrr) --period of clk is 1 second.
begin
if clr = '1' then
sec <= 0;
elsif sensor = '1' then
sec <= 15;
elsif clrr = '1' then
sec <= 19;
else if (clk'event and clk='1') then
sec <= sec+ 1;
if(sec = 34) then
sec<=0;

end if;
end if;
end if;
end process;
end Behavioral;
```

# Code Hex

```
entity HEX is
  Port (
    R : in  STD_LOGIC_VECTOR (5 downto 0);
    AN : out STD_LOGIC_VECTOR (6 downto 0));
end HEX;

architecture Behavioral of HEX is
  signal temp:STD_LOGIC_VECTOR (6 downto 0);
begin

  with R select
  temp <= |
    "0110000" when "000000",--1
    "1101101" when "000001",--2
    "1111001" when "000010",--3
    "0110000" when "000011",--1
    "1111110" when "000100",--0
    "0110000" when "000101",--1
    "1101101" when "000110",--2
    "1111001" when "000111",--3
    "0110011" when "001000",--4
    "1011011" when "001001",--5
    "1011111" when "001010",--6
    "1110000" when "001011",--7
    "1111111" when "001100",--8
    "1111011" when "001101",--9
    "1110111" when "001110",--A
    "1111110" when "001111",--0
    "0110000" when "010000",--1
    "1101101" when "010001",--2
    "1111001" when "010010",--3
    "1111110" when "010011",--0
    "0110000" when "010100",--1
    "1101101" when "010101",--2
    "1111001" when "010110",--3
    "0110011" when "010111",--4
    "1011011" when "011000",--5
    "1011111" when "011001",--6
    "1110000" when "011010",--7
    "1111111" when "011011",--8
    "1111011" when "011100",--9
    "1110111" when "011101",--A
    "0011111" when "011110",--B
    "1001110" when "011111",--C
    "0111101" when "100000",--D
    "1001111" when "100001",--E
    "1000111" when "100010",--F
    "0000000" when others;

  AN <= not temp;
end Behavioral;
```

# Code Top Level

```
entity traffic_lights_top is
  port (
    clk : in STD_LOGIC;
    day : in STD_LOGIC;
    night: in STD_LOGIC;
    traf: in STD_LOGIC;
    an : out STD_LOGIC_VECTOR(7 downto 0);
    seg : out STD_LOGIC_VECTOR (6 downto 0);
    ld : out STD_LOGIC_VECTOR(5 downto 0)
  );
end traffic_lights_top;

architecture traffic_lights_top of traffic_lights_top is
  component clkdiv is
    port (
      mclk : in STD_LOGIC;
      clr : in STD_LOGIC;
      clk3 : out STD_LOGIC
    );
  end component;

  component traffic is
    port (clk: in STD_LOGIC;
          clr: in STD_LOGIC;
          clrr: in STD_LOGIC;
          sensor: in STD_LOGIC;
          lights: out STD_LOGIC_VECTOR(5 downto 0));
  end component;
  component HEX is
    Port ( R : in STD_LOGIC_VECTOR (5 downto 0);
          AN : out STD_LOGIC_VECTOR (6 downto 0));
  end component;
  component digi_clk is
  port (clr :in std_logic;
        clrr: in std_logic;
        clk1 : in std_logic;
        sensor: in std_logic;
        seconds : out std_logic_vector(5 downto 0)
  );
  end component;
  signal clr, clk3, clrr, sensor: STD_LOGIC;
  signal lol : std_logic_vector(5 downto 0);
begin
```

```
  an <="11111110";
  clr <= day;
  clrr <= night;
  sensor <= traf;
  U1: clkdiv
  port map (
    mclk=>clk,
    clr=>clr,
    clk3=>clk3);

  U2: traffic
  port map (
    clk=>clk3,
    clr=>clr,
    clrr=>clrr,
    sensor=>sensor,
    lights=>ld);

  U3: digi_clk
  port map (
    clrr=>clrr,
    clr => clr,
    sensor=> sensor,
    clk1=>clk,
    seconds=> lol);

  U4:HEX
  port map (
    R=> lol,
    AN=> seg);


end traffic_lights_top;
```

# Possible Improvements

- Count down timer could be implemented instead of a count up timer.
- Using all 2 7-seg displays to show the timing of the lights could be changed.
- More lights at the intersection, more state codes
- Improved coding the implement changing light at main intersection when build up of traffic if the button is held for 5 or more seconds. Current iteration changes the light instantly when the button is pressed.
 
# Conclusion

- From this project we learned how to use state codes and timing functions to create a traffic signal. This is extremely beneficial when programming things that go from one state into another depending on whether the program passes that case. If it passes it will continue onto the next case or loop its current case until the code is passed.



Any Questions about our project?

Thank you for your attention!