

# THREE COLOR CHANGING DEVICE USING ACCELEROMETER

---

TIA SHERRARD

RYAN TOOHEY

ALEX DIETRICH

NATE ABRAHAM


FINAL PROJECT: ECE 278



INSTRUCTOR: DANIEL LLAMOCCA (PH.D.)

THE CAPTURE TO THE RIGHT REPRESENTS THE DESIGN OF THE DEVICE. ALSO, TO THE RIGHT OF THE CAPTURE IS THE BLOCK DIAGRAM WHICH CHARACTERIZES THE MAIN STATE MACHINE (FSM).

The components used include:

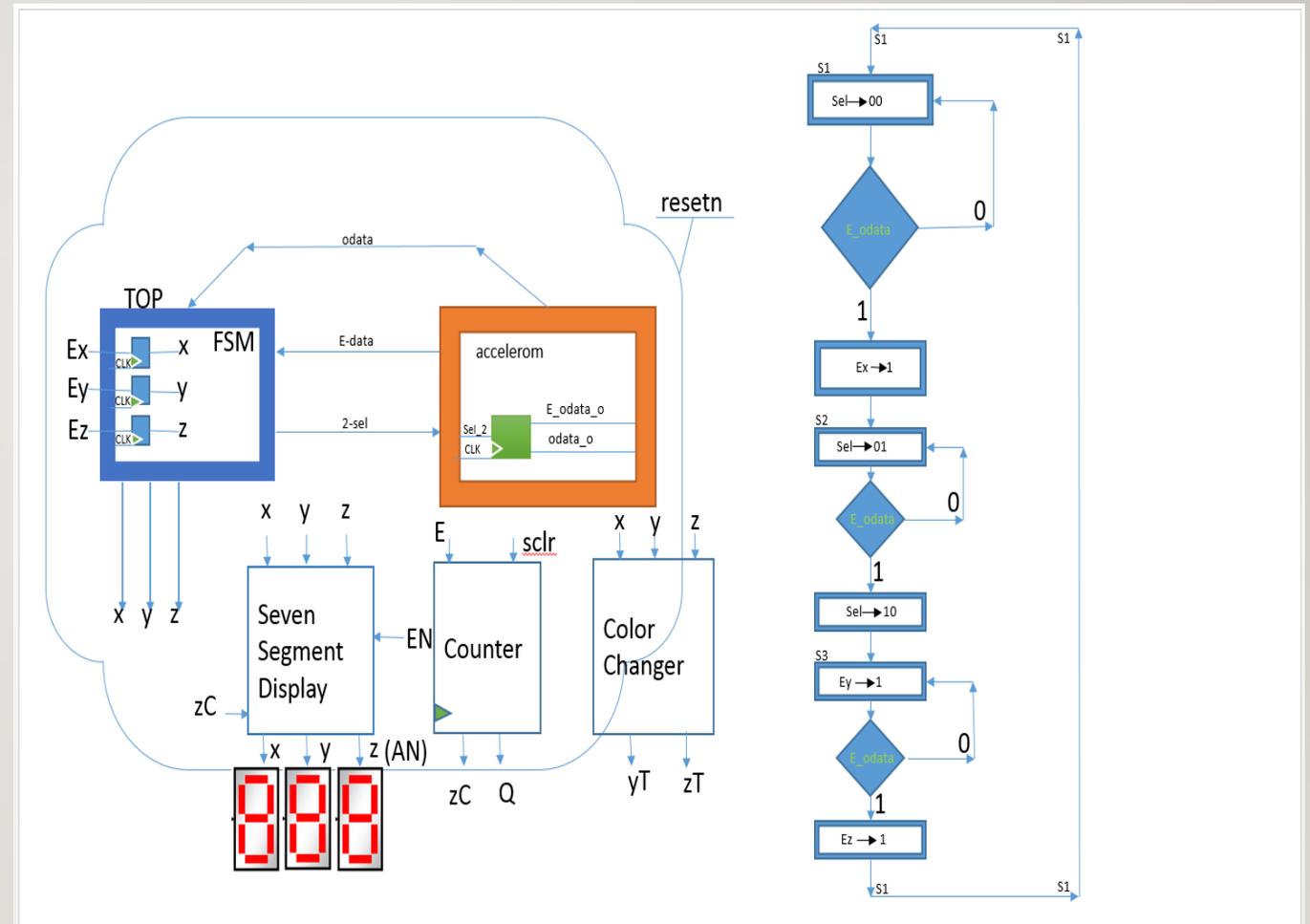- The accelerometer
- 3 registers for 8 bit data x, y, and z.
- Seven Segment Display (with a state machine inside of module).
- Counter
- Color Changing Module.



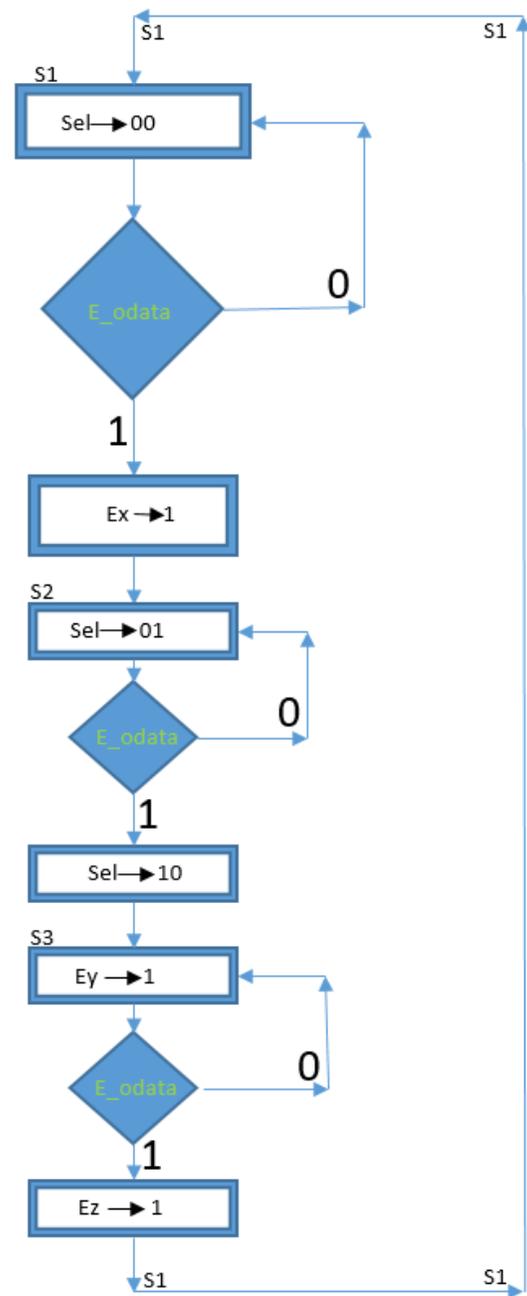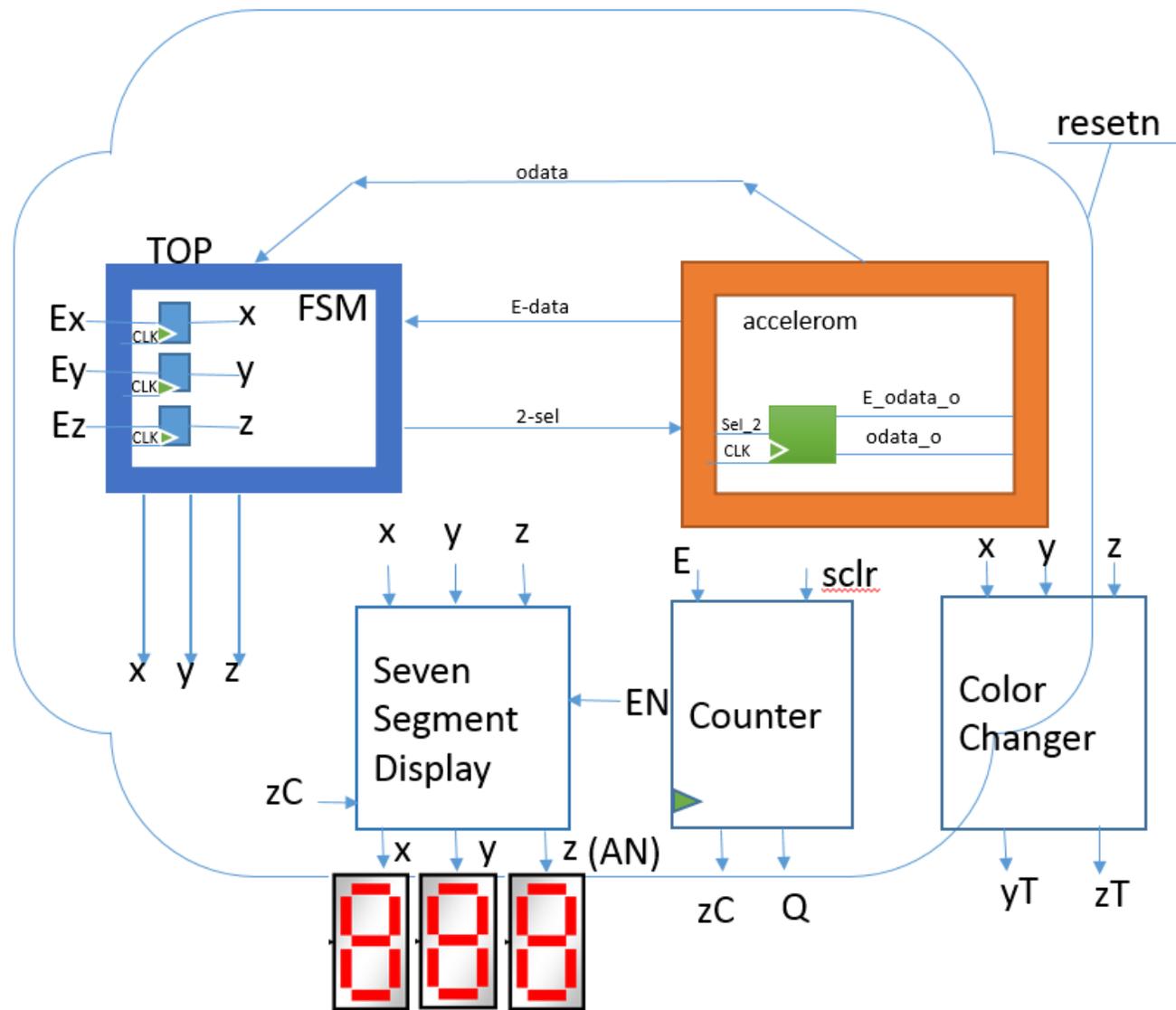

THE NEXYS 4 DDR HAS AN ANALOG DEVICE ADXL362 ACCELEROMETER BUILT IN. THIS DEVICE USES  $(2 \times 10^{-6})A$  AT 100HZ. THIS DEVICE BEHAVES AS A SLAVE DEVICE THAT USES THE SPI INTERFACE TO COMMUNICATE BETWEEN THE USER (OR MASTER) AND THE ACCELEROMETER (OR SLAVE).

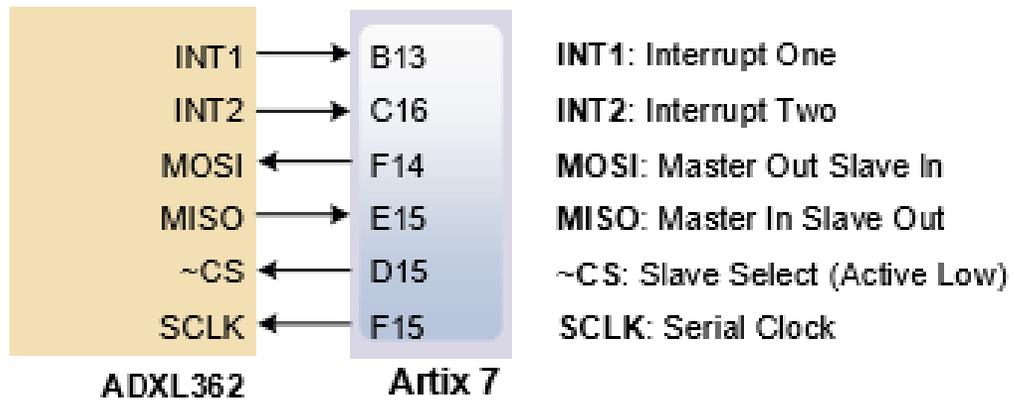


Figure 23. Accelerometer interface.


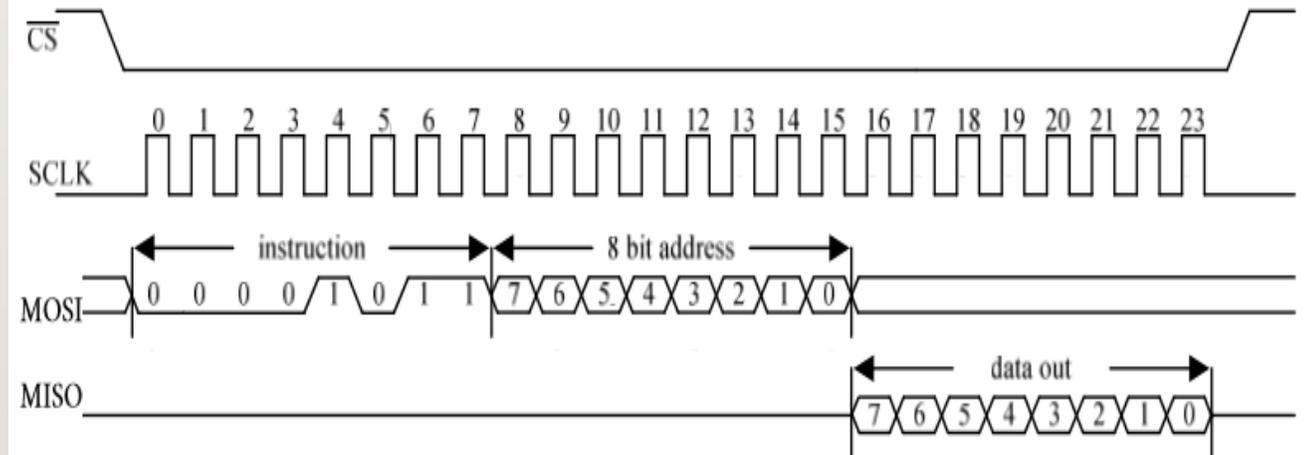


Figure 7. Register Read
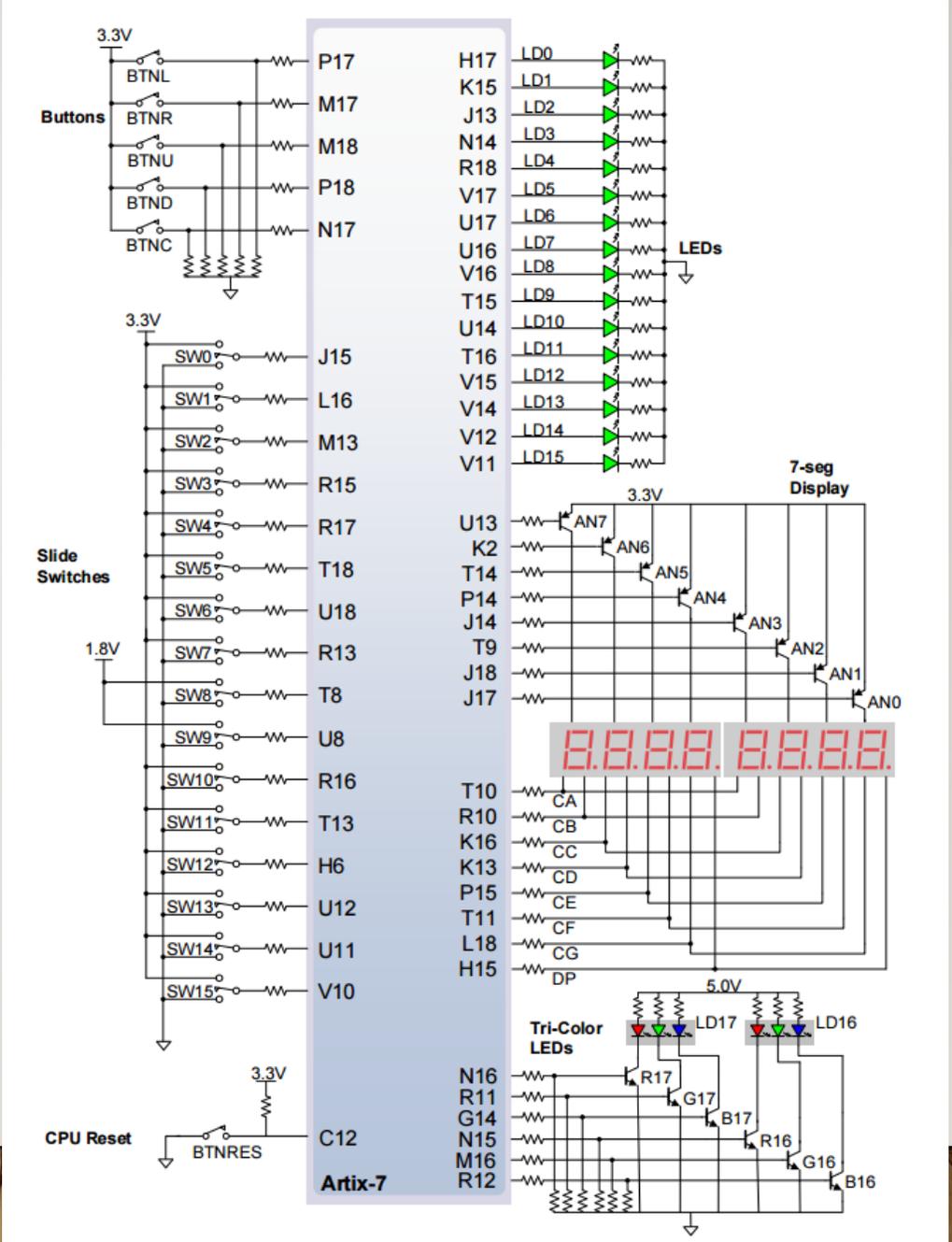
# NEXYS4 FPGA INPUTS AND OUTPUTS

The Nexys4 DDR board includes two tri-color LEDs, and an eight-digit seven-segment display which are controlled by the SevenSeg and ColorChanger modules.



# SEVEN SEGMENT DISPLAY.

This if statement is used to change the led lights on the 7 segment display according to what range the data from mux signal is in. The numbers are represented in binary(8 bits), but the integer range is 0 to 255.

```
entity SevenSeg is
  Port ( clock, resetn : in STD_LOGIC;
        x, y, z : in STD_LOGIC_VECTOR (7 downto 0);
        zC: in std_logic;
        seg : out STD_LOGIC_VECTOR (6 downto 0);
        AN : out STD_LOGIC_VECTOR (7 downto 0);
        EN: in std_logic);
end SevenSeg;

architecture Behavioral of SevenSeg is
  signal leds: std_logic_vector (6 downto 0 );
  signal mux: std_logic_vector (7 downto 0);

  type state is (S1, S2, S3);
  signal currentState: state;

begin
  process (mux)
  begin
    -- | a | b | c | d | e | f | g |
    -- |leds6|leds5|leds4|leds3|leds2|leds1|leds0|

    if (mux >= "00000000" and mux < "00010000") then
      leds <= "1000111" ;

    elsif (mux >= "00010000" and mux < "00100000") then
      leds <= "1001111";

    elsif (mux >= "00100000" and mux < "00110000") then
      leds <= "0111101";

    elsif (mux >= "00110000" and mux < "01000000") then
      leds <= "1001110";

    elsif (mux >= "01000000" and mux < "01010000") then
      leds <= "0011111";

    elsif (mux >= "01010000" and mux < "01100000") then
      leds <= "1110111";

    elsif (mux >= "01100000" and mux < "01110000") then
```

# SEVEN SEGMENT DISPLAY STATE MACHINE.

This FSM within the seven segment display, sets the mux signal to the input values x, y, and z. It also sets the location of the display (AN).

```
Transitions: process (resetn, clock)
begin
  if resetn = '0' then
    currentState <= S1;

    elsif (clock'event and clock = '1') then
      if zC = '1' then
        case currentState is
          when S1 =>
            currentState <= S2;
          when S2 =>
            currentState <= S3;
          when S3 =>
            currentState <= S1;
        end case;
      end if;
    end if;
end process;


Outputs: process (currentState,x,y,z)
begin
  mux <= "00000000";
  case currentState is

    when S1 =>
      mux <= x;
      AN <= "11111011";
    when S2 =>
      mux <= y;
      AN <= "11111101";
    when S3 =>
      mux <= z;
      AN <= "11111110";
  end case;

end process;

with EN select
seg <= not leds when '1',
"11111111" when others;

--SevenSegDisp <= not(leds);
```

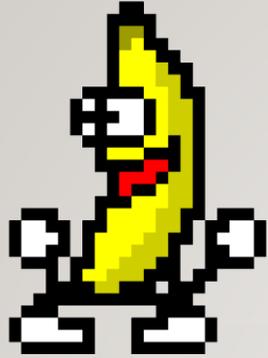

## COLOR CHANGING MODULE.

---

8 bit numbers in Hex, and the Colors  
that mark the different positions:

X = C, Color = Green

Y = 4, Color = Red

Z = 3, Color = Blue

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;



entity ColorChanger is
    Port ( x : in  STD_LOGIC_VECTOR (7 downto 0);
          y : in  STD_LOGIC_VECTOR (7 downto 0);
          z : in  STD_LOGIC_VECTOR (7 downto 0);
          yT : out STD_LOGIC_VECTOR (2 downto 0);
          zT : out STD_LOGIC_VECTOR (2 downto 0));
end ColorChanger;

architecture Behavioral of ColorChanger is
begin
    process (x, y, z)
    begin
        if (z < x and z < y) then
            yT <= "100";
            zT <= "100";
        elsif (x < y and x < z) then
            yT <= "010";
            zT <= "010";
        elsif (y < x and y < z) then
            yT <= "001";
            zT <= "001";
        else
            yT <= "000";
            zT <= "000";
        end if;
    end process;
end Behavioral;
```
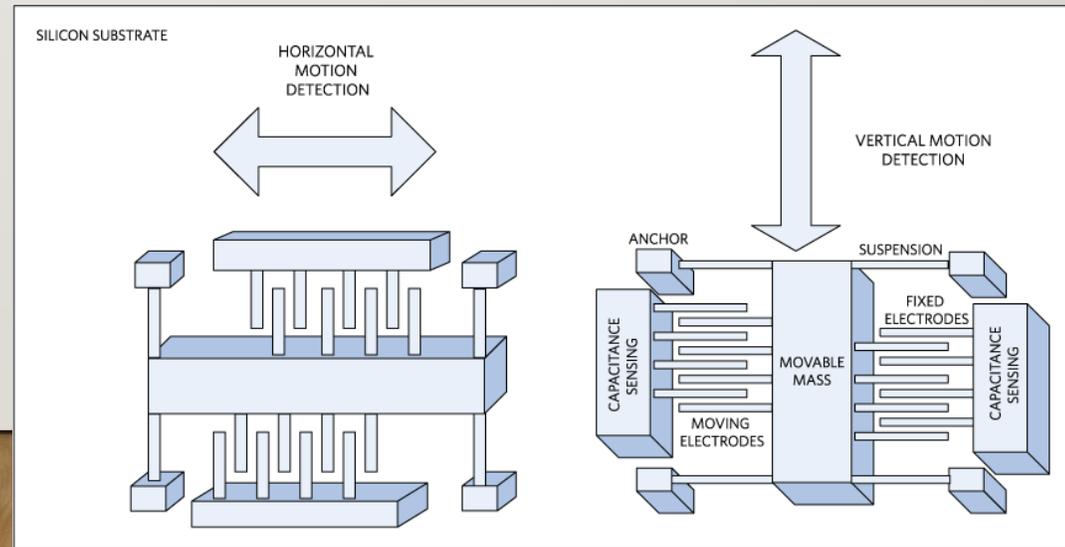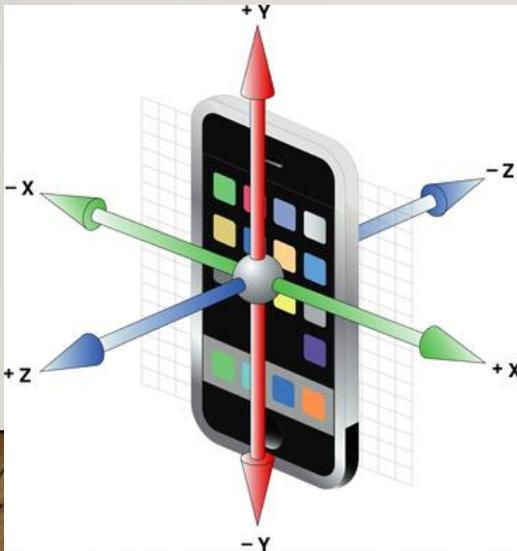
# COMMON AND UNCOMMON USES OF ACCELEROMETERS:

---

- Roller Coasters: Accelerometers are used for testing.
- Weapons (Missiles, and Aircraft): Accelerometers can be used for
- Fall Detection Devices “Help! I’ve fallen and I can’t get up!”: Devices to detect a fall.
- Smart phone and Devices: Screen rotation, compasses, and fall detection, etc.



# THREE COLOR CHANGING DEVICE USING ACCELEROMETER

YAY!

