

# Laboratory 1

(Due date: **002/003**: September 19<sup>th</sup>, **004**: September 20<sup>th</sup>)

## OBJECTIVES

- ✓ Introduce VHDL Coding for FPGAs.
- ✓ Learn to write testbenches in VHDL.
- ✓ Learn the Xilinx FPGA Design Flow with the ISE 14.7 Webpack: Synthesis, Simulation, and Bitstream Generation.
- ✓ Learn how to assign FPGA I/O pins and download the bitstream on the Nexys™-4 DDR Artix-7 FPGA Board.

## VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

## NEXYS™-4 DDR ARTIX-7 FPGA BOARD SETUP

- The Nexys-4 DDR Board can receive power from the Digilent USB-JTAG Port (J6). Connect your Board to a computer via the USB cable. If it does not turn on, connect the power supply of the Board.
- Nexys-4 DDR documentation: Available in [class website](#).

## FIRST ACTIVITY (100/100)

- **PROBLEM:** A lock is opened ( $f=1$ ) only for three combinations of switches: 0110, 1000, 1110, where '1' represents the ON position of a switch and '0' the OFF position.

- ✓ Complete the truth table for this circuit:

- ✓ Simplify the Boolean expression:

$$f =$$

A	B	C	D	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

- **XILINX FPGA DESIGN FLOW:**

- ✓ Create a new ISE Project. Select the **XC7A100T-1CSG324 Artix-7 FPGA** device.
- ✓ Write the VHDL code that implements the simplified Boolean expression. Synthesize your circuit (Synthesize – XST)
- ✓ Write the VHDL testbench to test the circuit for every possible combination of the inputs.
- ✓ Perform [Functional Simulation](#) (Simulate Behavioral Model). **Demonstrate this to your TA.**
- ✓ I/O Assignment: Create the UCF file. Use SW0-SW3 on the Nexys-4 DDR Board for the inputs, and LED(0) for the output
- ✓ Implement your design (Implement Design).
- ✓ Perform [Timing Simulation](#) (Simulate Post-Place & Route Model). **Demonstrate this to your TA.**
- ✓ Generate the bitstream file (Generate Programming File).
- ✓ Download the bitstream on the FPGA (Configure Target Device) and test. **Demonstrate this to your TA.**

- Submit ([as a .zip file](#)) the generated files: VHDL code, VHDL testbench, and UCF file to Moodle (an assignment will be created). DO NOT submit the whole ISE Project.

TA signature: \_\_\_\_\_

Date: \_\_\_\_\_