

# Laboratory 6

(Due date: **002/003**: November 21<sup>st</sup>, **004**: November 22<sup>nd</sup>)

## OBJECTIVES


- ✓ Describe Finite State Machines (FSMs) in VHDL.
- ✓ Implement a Digital System: Control Unit and Datapath Unit.

## VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.
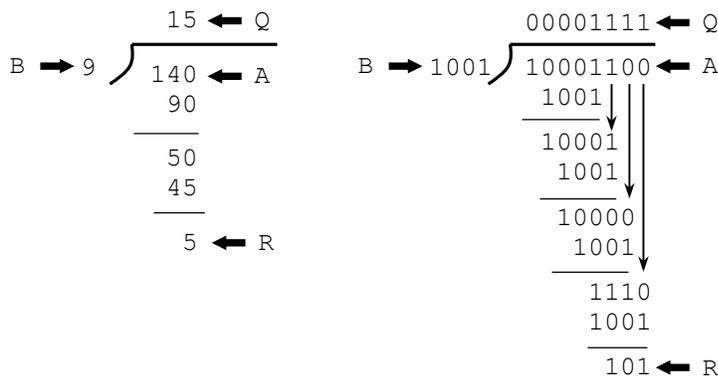
## ITERATIVE DIVIDER IMPLEMENTATION (100/100)

- Given two unsigned numbers  $A$  and  $B$ , we want to design a circuit that produces the quotient  $Q$  and a remainder  $R$ .  $A = B \times Q + R$ . The algorithm that implements the traditional long-hand division is as follows:





### ALGORITHM

```

R = 0
for i = n-1 downto 0
    left shift R (input = ai)
    if R ≥ B
        qi = 1, R ← R-B
    else
        qi = 0
    end
end
end
    
```

- An iterative architecture is depicted in the figure for  $A$  with 6 bits and  $B$  with 4 bits. The register  $R$  stores the remainder. A division operation is started when  $E = 1$  (where  $A$  and  $B$  values are captured). Then, at every clock cycle, we either: i) shift in the next bit of  $A$ , or ii) shift in the next bit of  $A$  and subtract  $B$ . The signal  $done$  is asserted to indicate that the operation has been completed and the result appears in  $Q$  and  $R$ .

  

- Modulo-6 counter: It includes: i) a synchronous input *sclr* that clears the count when  $E = sclr = 1$ , and ii) an output *zC* that is asserted when the count reaches 5.
- Left-shift register: Note that one of the shift registers includes a synchronous input *sclr* that clears the register outputs when  $E = sclr = 1$ .
- Each sequential component has *resetn* and *clock* inputs.
  
- The circuit is an example of a Digital System: It includes a Control Circuit (FSM) and a Datapath Circuit. The Datapath Circuit is made out of combinational and sequential components. The circuit is also called a Special-Purpose Processor. In this case, the special purpose is the unsigned division.
  - ✓ Create a new ISE Project. Select the **XC7A100T-1CSG324 Artix-7 FPGA** device.
  - ✓ Write the VHDL code for the given circuit. Suggestion: create a separate file for modulo-6 counter, shift Register, shift register with *sclr* input, register, adder, hex to 7-segments decoder, FSM, and top file.
  - ✓ Write the VHDL testbench (you must generate a 100 MHz input clock for your simulations) to test the following cases:
    - DataA = 011011 (27), DataB = 1001 (9)
    - DataA = 010100 (20), DataB = 0111 (7)
    - DataA = 101010 (42), DataB = 1111 (15)
    - DataA = 100101 (37), DataB = 0101 (5)
    - DataA = 001101 (13), DataB = 1100 (12)
    - DataA = 101111 (47), DataB = 0010 (2)
  - ✓ Perform Functional Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
  - ✓ I/O Assignment: Create the UCF file. Nexys-4-DDR: Use SW0 to SW10 for the inputs, CLK100MHZ for the input *clock*, CPU\_RESET push-button for *resetn*, a LED for 'done', six LEDs for *Q*, and the 7-segment display for *R*.
  - ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**
  
- Submit (as a .zip file) all the generated files: VHDL code files, VHDL testbench, and UCF file to Moodle (an assignment will be created). DO NOT submit the whole ISE Project.

TA signature: \_\_\_\_\_

Date: \_\_\_\_\_