

Solutions - Homework 1

(Due date: September 15th @ 5:30 pm)
Presentation and clarity are very important!

PROBLEM 1 (25 PTS)

- a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (12 pts)


✓ $F(X, Y, Z) = \prod(M_1, M_2, M_4, M_6)$

✓ $F = (A + \bar{C} + \bar{D})(\bar{B} + \bar{C} + D)(A + \bar{B} + \bar{C})$


✓ $F = (X \oplus \bar{Y})Z + XY\bar{Z}$

✓ $F = B(\bar{C} + \bar{A}) + \bar{A}\bar{B}$

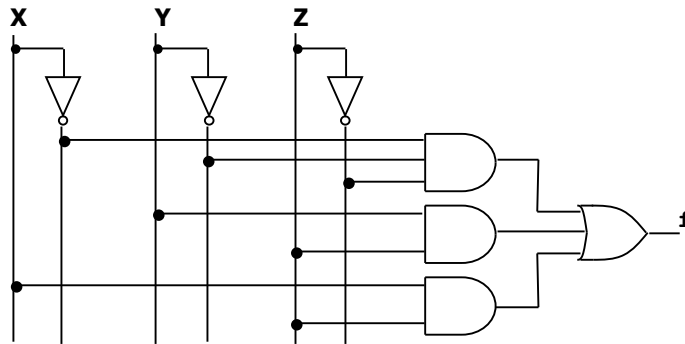
✓ $F(X, Y, Z) = \prod(M_1, M_2, M_4, M_6) = \sum(m_0, m_3, m_5, m_7) = \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XYZ = \bar{X}\bar{Y}\bar{Z} + Z(\bar{X}Y + X\bar{Y} + XY) = \bar{X}\bar{Y}\bar{Z} + Z(\bar{X}Y + X) = \bar{X}\bar{Y}\bar{Z} + Z(\bar{X} + X)(Y + X) = \bar{X}\bar{Y}\bar{Z} + ZY + ZX$



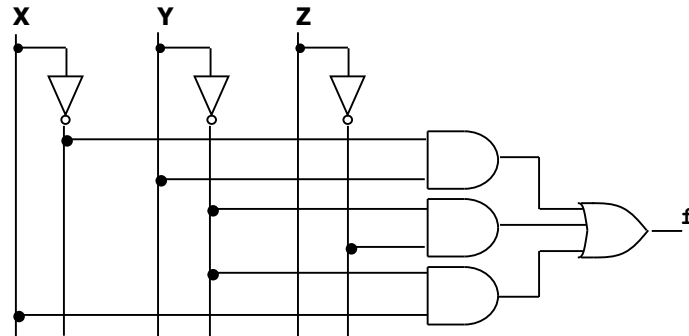
✓ $F = (X \oplus \bar{Y})Z + XY\bar{Z} = (XY + \bar{X}\bar{Y})Z + XY\bar{Z} = XYZ + \bar{X}\bar{Y}Z + XY\bar{Z} = XY + \bar{X}\bar{Y}Z = \bar{X}Y \cdot \bar{X}\bar{Y}Z = (\bar{X} + \bar{Y})(X + Y + \bar{Z}) = \bar{X}Y + \bar{X}\bar{Z} + \bar{Y}X + \bar{Y}\bar{Z} = \bar{X}\bar{Z} + \bar{Y}\bar{Z} + \bar{Y}X = \bar{Z}(\bar{X} + \bar{Y}) + \bar{Y}X = \bar{Z}(\bar{X} + \bar{Y}) + \bar{Y}X$



✓ $F = (A + \bar{C} + \bar{D})(\bar{B} + \bar{C} + D)(A + \bar{B} + \bar{C}) = (D + \bar{B} + \bar{C})(\bar{D} + A + \bar{C})(A + \bar{B} + \bar{C}) = (D + \bar{B} + \bar{C})(\bar{D} + A + \bar{C}) = (D + \bar{B} + \bar{C})(\bar{D} + A + \bar{C}) = D(\bar{A} + \bar{C}) + \bar{D}(\bar{B} + \bar{C}) + (A + \bar{C})(\bar{B} + \bar{C}) = D(\bar{A} + \bar{C}) + \bar{D}(\bar{B} + \bar{C}) = \bar{D}\bar{B} + DA + \bar{C}$

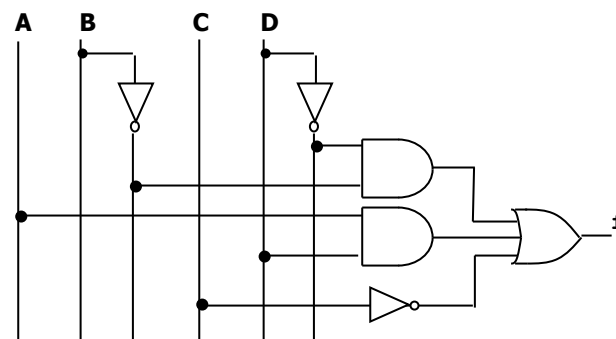

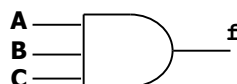✓ $F = \overline{B(\bar{C} + \bar{A})} + \overline{AB} = \bar{B}\bar{C} + \bar{B}\bar{A} + \bar{A} + \bar{B} = \bar{B}\bar{C} + \bar{A} + \bar{B} = \bar{A} + (\bar{B} + B)(\bar{B} + \bar{C}) = \bar{A} + \bar{B} + \bar{C} = ABC$



- b) Using ONLY Boolean Algebra Theorems, determine whether or not the following expression is valid, i.e., whether the left- and right-hand sides represent the same function: (5 pts)

$$x_1 \bar{x}_3 + x_2 x_3 + \bar{x}_2 \bar{x}_3 = (x_1 + \bar{x}_2 + x_3)(x_1 + x_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3)$$

$$\begin{aligned} (x_1 + \bar{x}_2 + x_3)(x_1 + x_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3) &= (x_1 + (\bar{x}_2 + x_3)(x_2 + \bar{x}_3))(\bar{x}_1 + x_2 + \bar{x}_3) \\ &= (x_1 + \bar{x}_2 \bar{x}_3 + x_2 x_3)(\bar{x}_1 + x_2 + \bar{x}_3) \\ &= x_1 \bar{x}_2 + x_1 \bar{x}_3 + \bar{x}_2 \bar{x}_3 \bar{x}_1 + \bar{x}_2 \bar{x}_3 x_2 + x_2 x_3 \bar{x}_1 + x_2 x_3 x_2 = x_1 \bar{x}_2 + x_1 \bar{x}_3 + \bar{x}_2 \bar{x}_3 + x_2 x_3 \\ &= x_3 x_2 + \bar{x}_3 x_1 + \bar{x}_2 \bar{x}_3 = x_1 \bar{x}_3 + x_2 x_3 + \bar{x}_2 \bar{x}_3 \end{aligned}$$

- c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

x	y	z	f ₁	f ₂
0	0	0	0	1
0	0	1	0	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

Sum of Products

$$f_1 = \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z} + XYZ$$



$$f_2 = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + \bar{X}YZ + XY\bar{Z}$$

Product of Sums

$$f_1 = (X + Y + Z)(X + Y + \bar{Z})(X + \bar{Y} + \bar{Z})(\bar{X} + Y + \bar{Z})$$

$$f_2 = (\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})$$

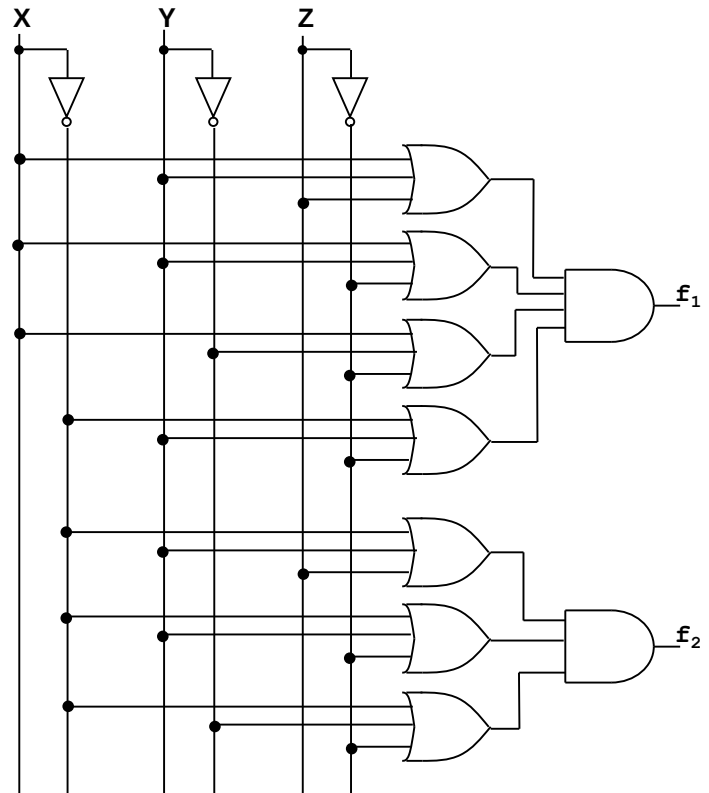
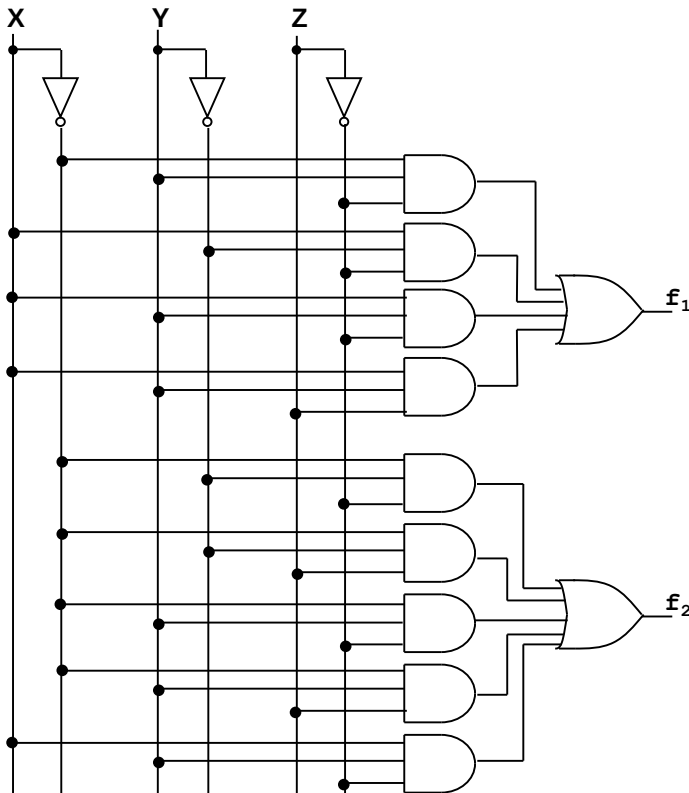
Minterms and maxterms: $f_1 = \sum(m_2, m_4, m_6, m_7) = \prod(M_0, M_1, M_3, M_5).$
 $f_2 = \sum(m_0, m_1, m_2, m_3, m_6) = \prod(M_4, M_5, M_7).$



PROBLEM 2 (15 PTS)

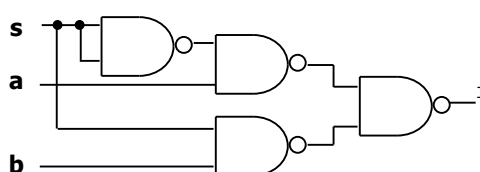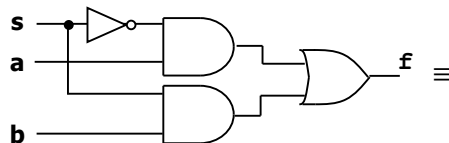- a) The following circuit has the following logic function: $f = \bar{s}a + sb$.

- Complete the truth table of the circuit, and sketch the logic circuit using ONLY 2-input NAND gates. (5 pts)




s	a	b	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

b) The circuit on the right can be used to realize various different functions. (10 pts)

- For example, the following selection of inputs produce the function: $g = x_1x_2 + x_2x_3$. Demonstrate that this is the case.

in1	in2	in3	in4	in5	in6	in7
0	x_3	x_2	0	1	x_2	x_1

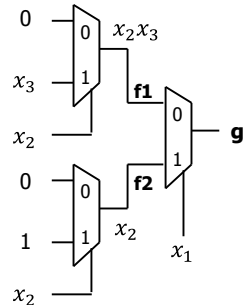


$$f_1 = \overline{x_2}(0) + x_2(x_3) = x_2x_3$$

$$f_2 = \overline{x_2}(0) + x_2(1) = x_2$$


$$g = \overline{x_1}(x_2x_3) + x_1(x_2) = x_2(x_1 + \overline{x_1}x_3) = x_2(x_1 + \overline{x_1})(x_1 + x_3)$$

$$g = x_2(x_1 + x_3) = x_1x_2 + x_2x_3$$

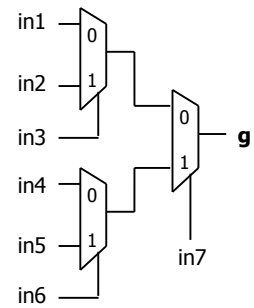

- Given the following inputs, provide the resulting function g (minimize the function).

in1	in2	in3	in4	in5	in6	in7
x_1	0	x_3	1	0	x_1	x_2

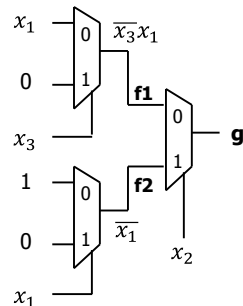


$$f_1 = \overline{x_3}(x_1) + x_3(0) = \overline{x_3}(x_1)$$

$$f_2 = \overline{x_1}(1) + x_1(0) = \overline{x_1}$$


$$g = \overline{x_2}(\overline{x_3}x_1) + x_2(\overline{x_1}) = \overline{x_1}x_2 + \overline{x_2}x_1\overline{x_3}$$

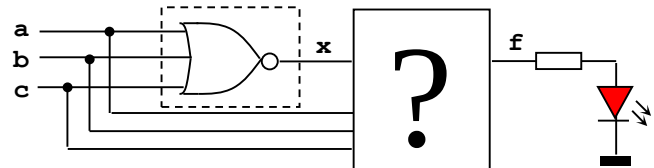PROBLEM 3 (12 PTS)

- Design a circuit (simplify your circuit) that verifies the logical operation of a 3-input NOR gate. $f = '1'$ (LED ON) if the NOR gate does NOT work properly. Assumption: when the NOR gate is not working, it generates 1's instead of 0's and vice versa.



x	a	b	c	f	x_{good}
0	0	0	0	1	1
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	0

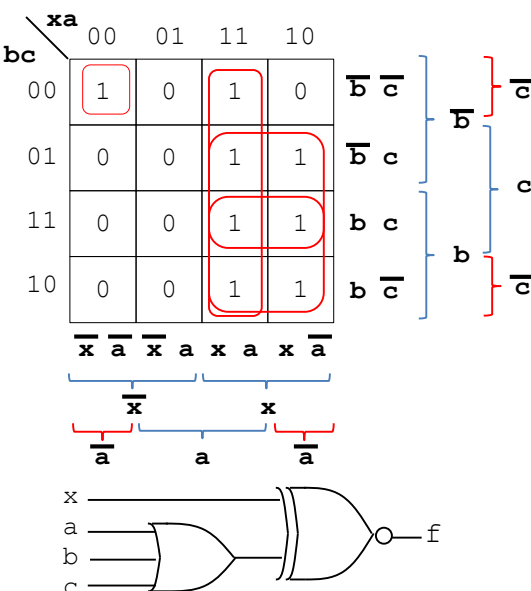


PROBLEM 4 (20 PTS)

a) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

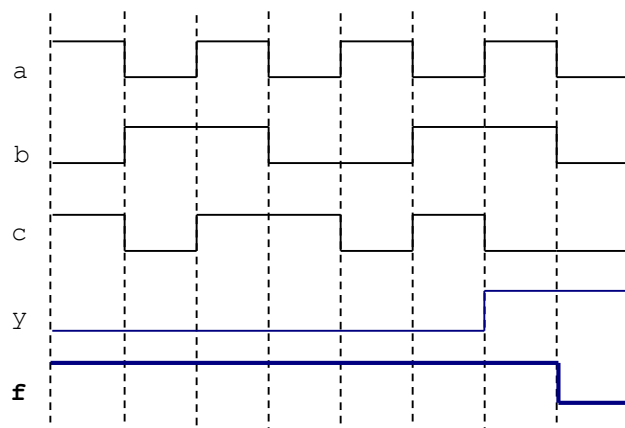architecture st of circ is
  signal x, y: std_logic;
begin
  x <= a xor b;
  y <= x nor c;
  f <= y nand (not b);
end st;
```




b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;

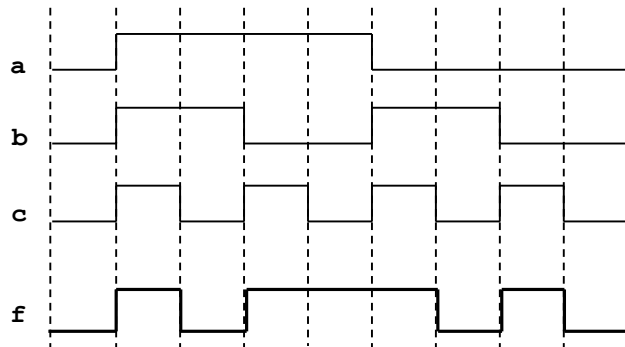
architecture st of wav is
begin
  f <= c or (a and not (b));
end st;
```




a	b	c	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

c \ ab	00 01 11 10			
	0	0	0	1
0	0	0	0	1
1	1	1	1	1


$$f = c + a\bar{b}$$

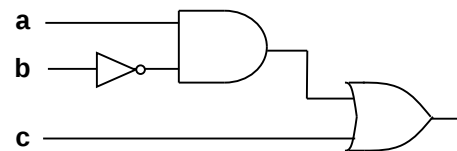

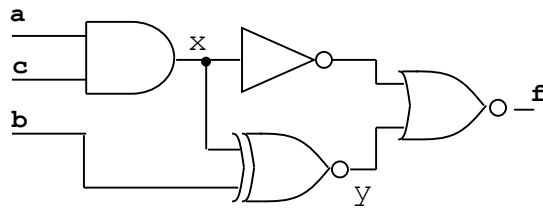c) Complete the timing diagram of the following circuit: (6 pts)




$$f = a\bar{b}c$$

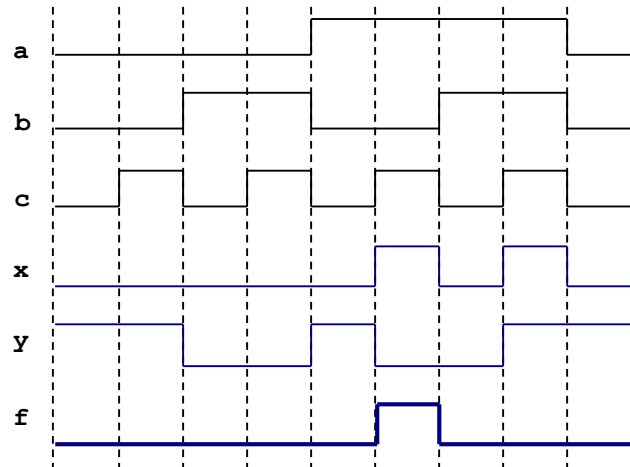


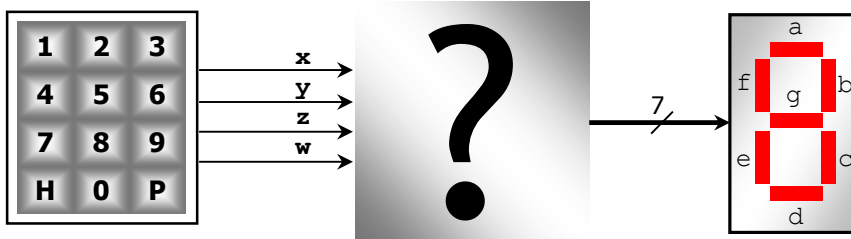PROBLEM 5 (28 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED: A LED is ON if it is given a logic '1'. A LED is OFF if it is given a logic '0'.
- Complete the truth table for each output (a, b, c, d, e, f, g).
- Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for c, d, e, f, g and the Quine-McCluskey algorithm for a, b . Note that it is safe to assume that the codes 1100 to 1111 will not be produced by the keypad.



Value	x	y	z	w	a	b	c	d	e	f	g
0	0	0	0	0							
1	0	0	0	1							
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1							
8	1	0	0	0							
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0							
H	1	0	1	1							
	1	1	0	0							
	1	1	0	1							
	1	1	1	0							
	1	1	1	1							

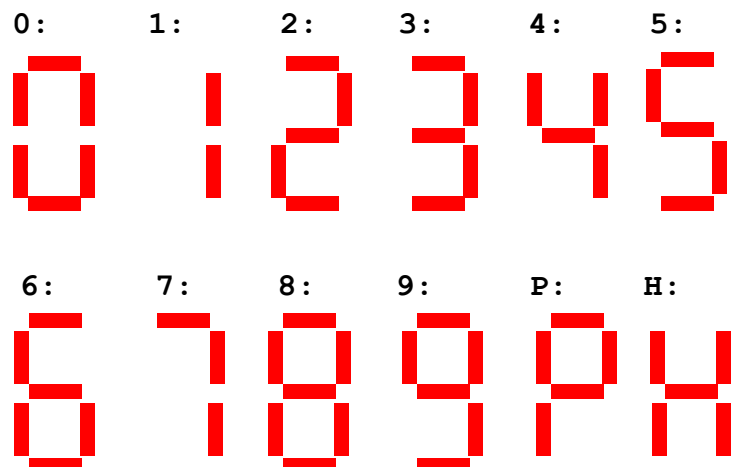

Value	X	Y	Z	W	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	1	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
P	1	0	1	0	1	1	0	0	1	1	1
H	1	0	1	1	0	1	1	0	1	1	1
	1	1	0	0	X	X	X	X	X	X	X
	1	1	0	1	X	X	X	X	X	X	X
	1	1	1	0	X	X	X	X	X	X	X
	1	1	1	1	X	X	X	X	X	X	X

$$c = y + \bar{z} + w$$

$$d = x\bar{z} + \bar{x}\bar{y}\bar{w} + \bar{x}\bar{y}z + \bar{z}wy + z\bar{w}y$$

$$e = \bar{w}\bar{y} + z\bar{w} + xz$$

$$f = x + \bar{z}\bar{w} + y\bar{z} + y\bar{w}$$

$$g = x + z\bar{w} + y\bar{z} + \bar{y}z$$

c

xy \ zw	00	01	11	10
00	1	1	X	1
01	1	1	X	1
11	1	1	X	1
10	0	1	X	0

d

xy \ zw	00	01	11	10
00	1	0	X	1
01	0	1	X	1
11	1	0	X	0
10	1	1	X	0

e

xy \ zw	00	01	11	10
00	1	0	X	1
01	0	0	X	0
11	0	0	X	1
10	1	1	X	1

f

xy \ zw	00	01	11	10
00	1	1	X	1
01	0	1	X	1
11	0	0	X	1
10	0	1	X	1

g

xy \ zw	00	01	11	10
00	0	1	X	1
01	0	1	X	1
11	1	0	X	1
10	1	1	X	1

- $a = \sum m(0,2,3,5,6,7,8,9,10) + \sum d(12,13,14,15)$.
Too many minterms. We better optimize: $\bar{a} = \sum m(1,4,11) + \sum d(12,13,14,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_1 = 0001$ $m_4 = 0100$ ✓	$m_{4,12} = -100$		
2	$m_{12} = 1100$ ✓	$m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$ ✓	
3	$m_{11} = 1011$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓ $m_{11,15} = 1-11$		
4	$m_{15} = 1111$ ✓			

$$\bar{a} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xzw + xy$$

Prime Implicants		Minterms		
		1	4	11
m_1	$\bar{x}\bar{y}\bar{z}w$	X		
$m_{4,12}$	$y\bar{z}\bar{w}$		X	
$m_{11,15}$	xzw			X
$m_{12,13,14,15}$	xy			

$$\bar{a} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xzw \Rightarrow a = (x + y + z + \bar{w})(\bar{y} + z + w)(\bar{x} + \bar{z} + \bar{w})$$

- $b = \sum m(0,1,2,3,4,7,8,9,10,11) + \sum d(12,13,14,15)$.

Too many minterms. We better optimize: $\bar{b} = \sum m(5,6) + \sum d(12,13,14,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
2	$m_5 = 0101 \checkmark$ $m_6 = 0110 \checkmark$ $m_{12} = 1100 \checkmark$	$m_{5,13} = -101$ $m_{6,14} = -110$ $m_{12,13} = 110- \checkmark$ $m_{12,14} = 11-0 \checkmark$	$m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11$	
3	$m_{13} = 1101 \checkmark$ $m_{14} = 1110 \checkmark$	$m_{13,15} = 11-1 \checkmark$ $m_{14,15} = 111- \checkmark$		
4	$m_{15} = 1111 \checkmark$			

$$\bar{b} = \bar{x}\bar{y}\bar{z}w + y\bar{z}\bar{w} + xzw + xy$$

Prime Implicants		Minterms	
		5	6
$m_{5,13}$	$y\bar{z}w$	x	
$m_{6,14}$	$yz\bar{w}$		x
$m_{12,13,14,15}$	xy		

$$\bar{b} = y\bar{z}w + yz\bar{w} \quad \Rightarrow \quad b = (\bar{y} + z + \bar{w})(\bar{y} + \bar{z} + w)$$