


Solutions - Homework 3

(Due date: October 27th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (25 PTS)

 a) Complete the timing diagram of the circuit shown below. (5 pts)



b) Complete the timing diagram of the circuit whose VHDL description is shown below: (5 pts)


```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( prn, x, clk: in std_logic;
        q: out std_logic);
end circ;



architecture a of circ is
  signal qt: std_logic;

begin
  process (prn, clk, x)
  begin
    if prn = '0' then
      qt <= '1';
    
```
 
```
    elsif (clk'event and clk = '0') then
      if x = '1' then
        qt <= not(qt);
      end if;
    end if;
  end process;
  q <= qt;
end a;
```




  c) Complete the timing diagram of the circuits shown below: (15 pts)



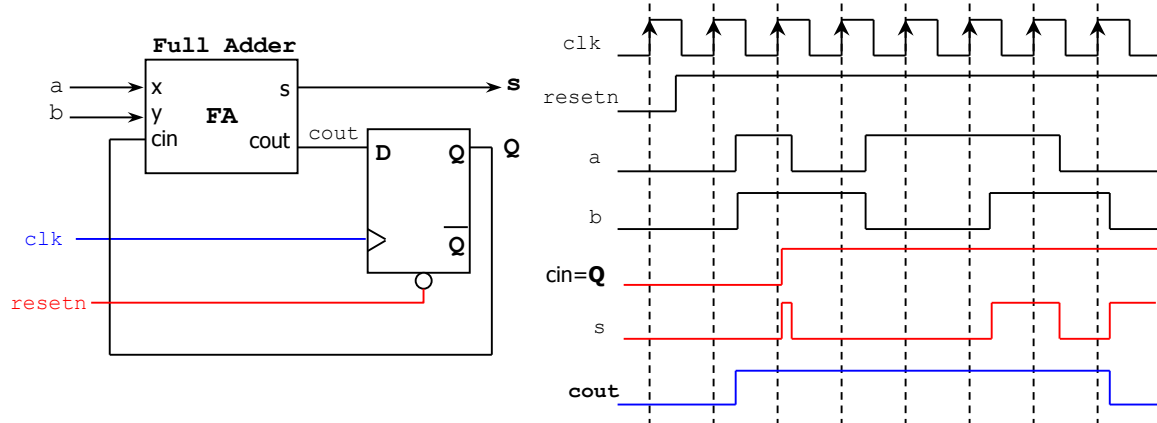PROBLEM 2 (25 PTS)

- Complete the timing diagram of the circuit shown below: (10 pts)



- Complete the VHDL description of the synchronous sequential circuit whose truth table is shown below: (5 pts)


```
library ieee;
use ieee.std_logic_1164.all;

entity my_ff is
    port ( a, b, c: in std_logic;
          clrn, clk: in std_logic;
          q: out std_logic);
end my_ff;

architecture a of my_ff is
    signal qt: std_logic;
begin
    process (clrn, clk, a, b, c)
    begin
        if clrn = '0' then qt <= '0';
        elsif (clk'event and clk='1') then
            if (a = '0' and b = '1') then
                qt <= not (qt);
            elsif (a = '1' and b = '0') then
                qt <= not (c);
            elsif (a = '1' and b = '1') then
                qt <= b;
            end if;
        end if;
    end process;
    q <= qt;
end a;
```

clrn	clk	A	B	Q_{t+1}
1		0	0	Q_t
1		0	1	$\overline{Q_t}$
1		1	0	$\overline{C}$
1		1	1	B
0	X	X	X	0

 
- Complete the timing diagram of the circuit shown below. $Q = Q_3Q_2Q_1Q_0$ (10 pts)



PROBLEM 3 (20 PTS)


- Given the following circuit, complete the timing diagram (signals *DO* and *DATA*).
The LUT 6-to-6 implements the following function: $OLUT = \lceil ILUT^{0.95} \rceil$, where *ILUT* is an unsigned number.
For example $ILUT = 35 (10011_2) \rightarrow OLUT = \lceil 35^{0.95} \rceil = 30 (011110_2)$

$$\begin{array}{l|l} ILUT = 21 (010101_2) \rightarrow OLUT = \lceil 21^{0.95} \rceil = 19 (010011_2) & ILUT = 62 (111110_2) \rightarrow OLUT = \lceil 62^{0.95} \rceil = 51 (110011_2) \\ ILUT = 43 (101011_2) \rightarrow OLUT = \lceil 43^{0.95} \rceil = 36 (100100_2) & ILUT = 19 (010011_2) \rightarrow OLUT = \lceil 19^{0.95} \rceil = 17 (010001_2) \end{array}$$

 

 PROBLEM 4 (30 PTS)

- The following circuit is a 4-bit parallel/serial load shift register with enable input.
Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$
- Write a structural VHDL code. You MUST create a file for: i) flip flop, ii) MUX 2-to-1, and iii) top file (where you will interconnect the flip flops and MUXes). Provide a printout. (10 pts)
- Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Timing Simulation). The clock frequency must be 50 MHz with 50% duty cycle. Provide a printout. (20 pts)



✓ **VHDL Code: Top File**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_st_shiftreg is
    generic (N: INTEGER:= 4;
            DIR: STRING:= "LEFT"); -- RIGHT/LEFT
    port (D: in std_logic_vector (N-1 downto 0);
          resetn, clock, din, E, s_l: in std_logic;
          Q: out std_logic_vector (N-1 downto 0));
end my_st_shiftreg;

architecture structure of my_st_shiftreg is
    component dffe
        port ( d : in  STD_LOGIC;
              clrn, prn, clk, ena: in std_logic;
              q : out  STD_LOGIC);
    end component;

    component mux2to1
        port (a,b, sel : in std_logic;
              y : out std_logic);
    end component;

    signal ds, md, Qt: std_logic_vector (N-1 downto 0);
begin

    a0: assert (DIR = "LEFT" or DIR = "RIGHT")
        report "DIR can only be LEFT or RIGHT"
        severity error;

    rr: if DIR = "RIGHT" generate
        ds(N-1) <= din;
        ds(N-2 downto 0) <= Qt(N-1 downto 1);
    end generate;

    rl: if DIR = "LEFT" generate
        ds(0) <= din;
        ds(N-1 downto 1) <= Qt(N-2 downto 0);
    end generate;

    ti: for i in N-1 downto 0 generate
        fi: dffe port map (d => md(i), clrn => resetn, prn => '1', clk => clock, ena => E, q => Qt(i));
        mi: mux2to1 port map (a => ds(i), b => D(i), sel => s_l, y => md(i));
    end generate;

    Q <= Qt;
end structure;
```

✓ **VHDL Code: D-Type flip flop**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dffe is
    port ( d : in  STD_LOGIC;
          clrn, prn, clk, ena: in std_logic;
          q : out  STD_LOGIC);
end dffe;

architecture behaviour of dffe is
begin
    process (clk, ena, prn, clrn)
    begin
        if clrn = '0' then q <= '0';
        elsif prn = '0' then q <= '1';
        elsif (clk'event and clk='1') then
            if ena = '1' then q <= d; end if;
        end if;
    end process;
end behaviour;
```

✓ **VHDL Code: MUX 2-to-1**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2to1 is
    port (a,b, sel: in std_logic;
          y : out std_logic);
end mux2to1;

architecture structure of mux2to1 is
begin
    with sel select
        y <= a when '0',
            b when others;
end structure;
```

✓ **VHDL Tesbench:**

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_my_st_shiftreg IS
    generic (N: INTEGER:= 4);
END tb_my_st_shiftreg;

ARCHITECTURE behavior OF tb_my_st_shiftreg IS
    COMPONENT my_st_shiftreg
    PORT(
        D : IN  std_logic_vector(N-1 downto 0);
        resetn, clock, din : IN  std_logic;
        E, s_l : IN  std_logic;
        Q : OUT std_logic_vector(N-1 downto 0));
    END COMPONENT;

    --Inputs
    signal D : std_logic_vector(N-1 downto 0) := (others => '0');
    signal resetn : std_logic := '0';
    signal clock : std_logic := '0';
    signal din : std_logic := '0';
    signal E : std_logic := '0';
    signal s_l : std_logic := '0';

    --Outputs
    signal Q : std_logic_vector(N-1 downto 0);

    -- Clock period definitions
    constant T : time := 20 ns;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: my_st_shiftreg PORT MAP (D => D, resetn => resetn, clock => clock, din => din,
        E => E, s_l => s_l, Q => Q);

    -- Clock process definitions
    clock_process: process
    begin
        clock <= '0'; wait for T/2;
        clock <= '1'; wait for T/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        D <= "1011"; resetn <= '0'; wait for 100 ns;
        resetn <= '0'; wait for T*2;
        resetn <= '1';
        D <= "1011"; din <= '0'; E <= '1'; s_l <= '0'; wait for T;
        D <= "1011"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
        D <= "1010"; din <= '1'; E <= '1'; s_l <= '1'; wait for T;
        D <= "1010"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
        D <= "1010"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
        D <= "1010"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
        D <= "1100"; din <= '0'; E <= '0'; s_l <= '0'; wait for T;
        D <= "1100"; din <= '1'; E <= '0'; s_l <= '1'; wait for T;
        D <= "1100"; din <= '1'; E <= '0'; s_l <= '0'; wait for T;
        D <= "0111"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
        D <= "0111"; din <= '1'; E <= '1'; s_l <= '1'; wait for T;
        D <= "0111"; din <= '0'; E <= '1'; s_l <= '0'; wait for T;
        D <= "0101"; din <= '1'; E <= '0'; s_l <= '0'; wait for T;
        D <= "0101"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
        D <= "0101"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
        D <= "0101"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
        D <= "0101"; din <= '0'; E <= '1'; s_l <= '0';
        wait;
    end process;
END;
```