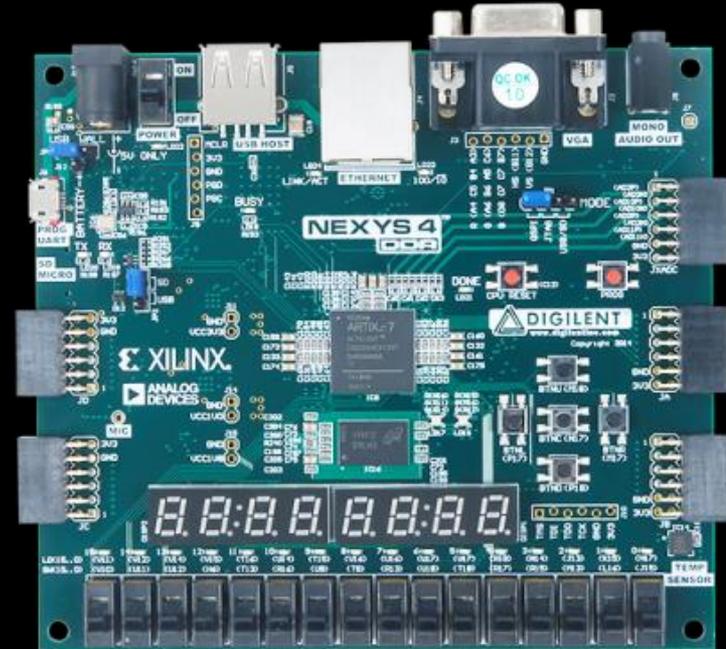



The Calculator

By: Kevin Bobernick, Dino Reed, Stephanie Rider, and Hang Zhang

Introduction

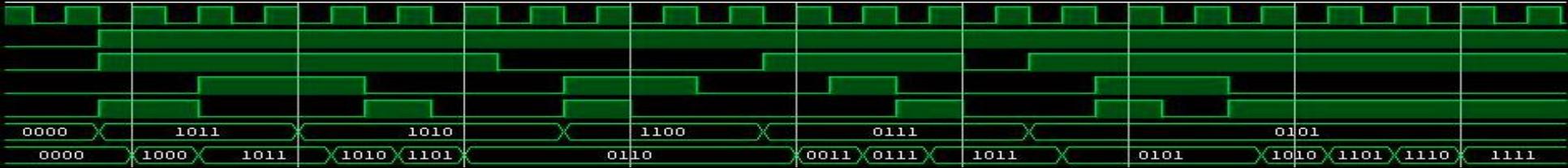
- Design a simple calculator
 - Addition
 - Subtraction
 - Division
 - Multiplication
- Display the Inputs
 - Switches
 - LEDs
- Display the Output
 - 7-Segment Display






Purpose

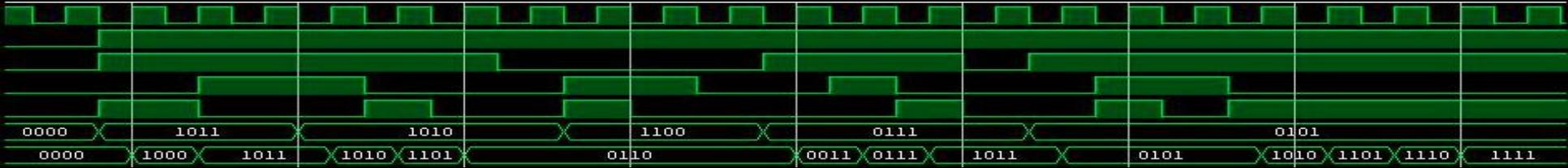
- Create a calculator that operates off binary inputs
- Able to calculate up to 4 bit outputs
- Utilizes switches as inputs
- Utilizes 7-segment display to represent outputs in hex
- Utilizes LEDs to display the inputs in binary



Inputs


- The switches are used as the inputs for the calculator
- All inputs are unsigned binary
 - DataA is the first input and will always start the equation
 - 4-bit: SW(0-3)
 - DataB is the second input and always operates on DataA
 - 4-bit: SW(4-7)
- The operation of the calculator will also be selected by the switches
 - Addition: SW(12)
 - Subtraction: SW(13)
 - Multiplication: SW(14)
 - Division: SW(15)

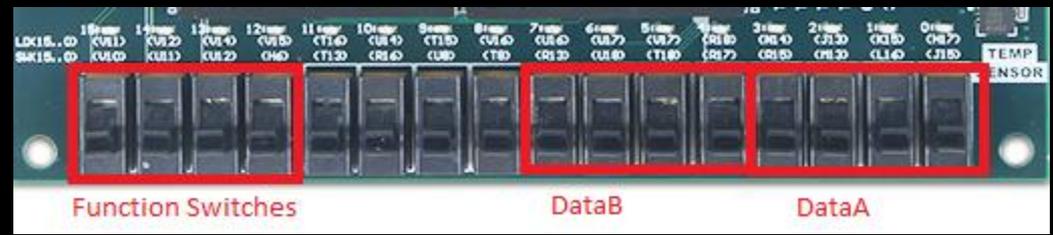

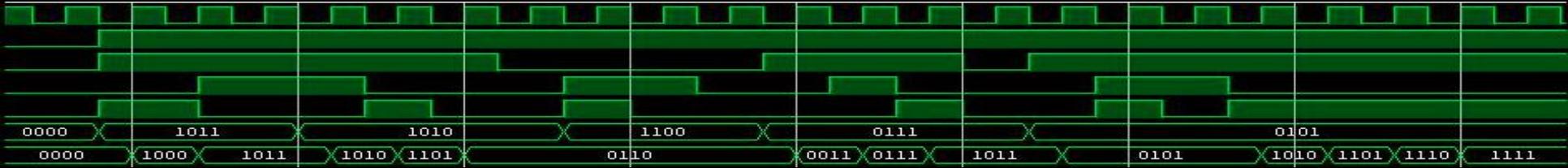


Outputs

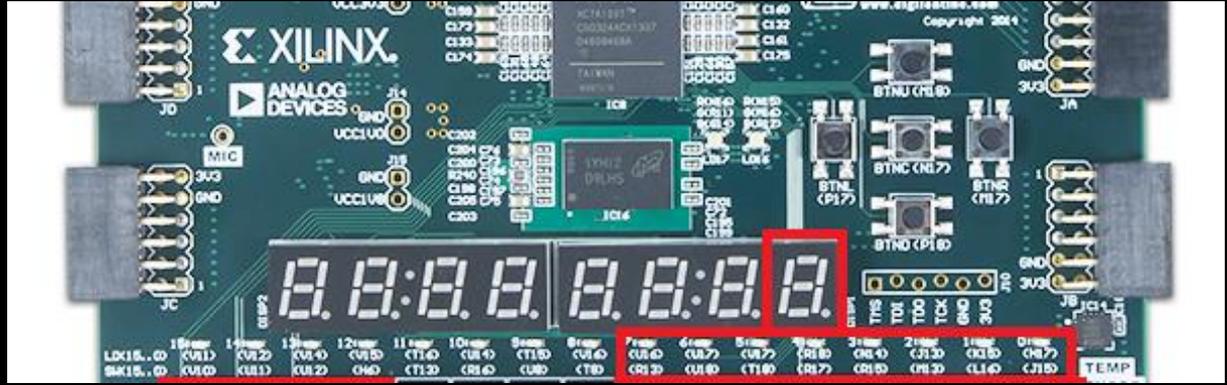
- The 7-segment display is used to display the answer of the selected equation.
 - The display on the right side will display the answer in hexadecimal form.
- The LEDs above the switches will light to show the binary of the input.



0000	1011	1010	1100	0111	0101								
0000	1000	1011	1010	1101	0110	0011	0111	1011	0101	1010	1101	1110	1111


Inputs and Outputs

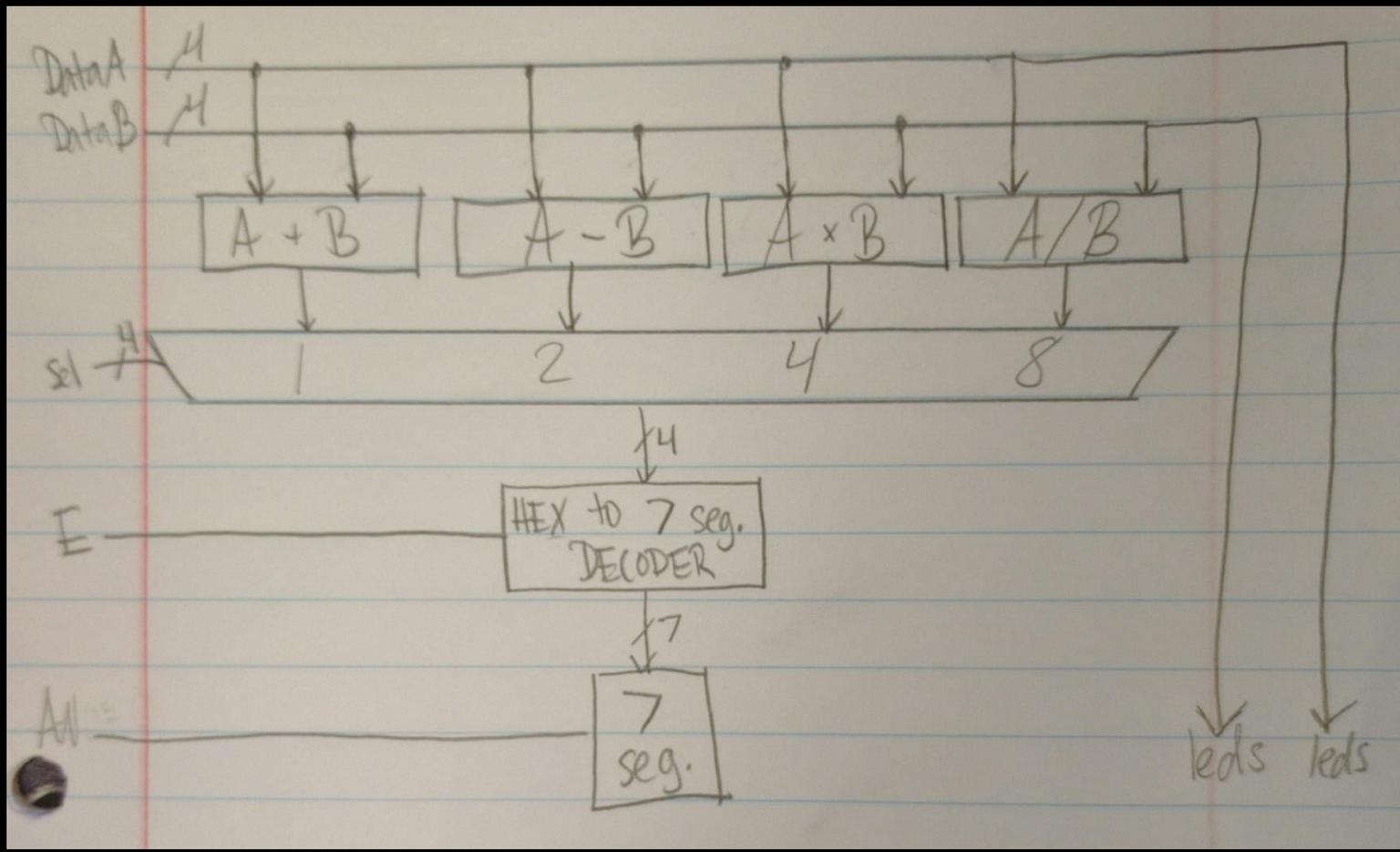

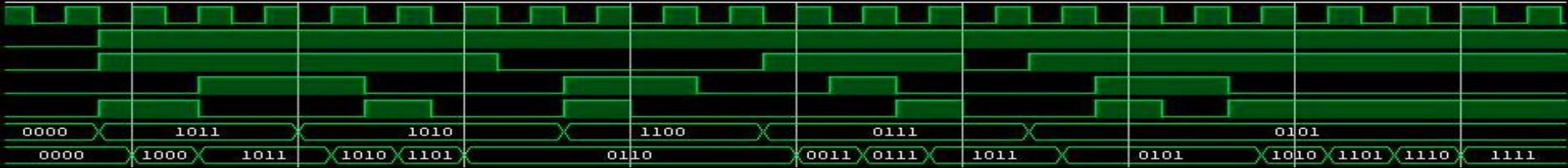


Difficulties

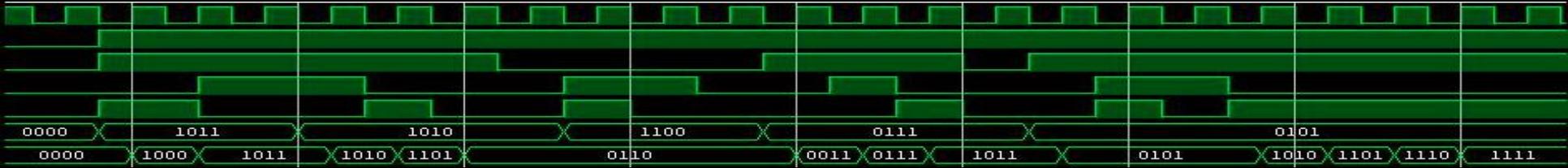- Extending the 7-segment display
- Original Top file idea
- Time



Improvements

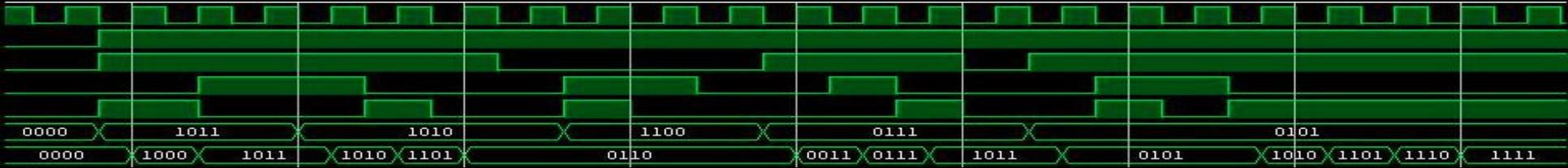- Extend the number of bits in the input and output
- Use a keyboard or number pad as the input
- Use a VGA display to show the output
- Allow it to work with signed binary inputs
- Add more functions to the calculator:
 - Square Root
 - Exponentials



References

- <https://www.alteraforum.com/forum/showthread.php?t=47925>
- <http://www.secs.oakland.edu/~llamocca/VHDLforFPGAs.html>