

# **TRAFFIC LIGHT CONTROLLER**

**By: James Todd, Thierno Barry, Andrew Tamer, Gurashish Grewal**

**Date: 12/07/2017**


**FALL-2017**

# INTRODUCTION


- 4 way intersection light system.
- Night time system- Lights start blinking Red after defined amount of time.
- Emergency Light System- If an emergency switch is on, all lights go to red.
- Counter, Clock divider, LEDs, FSM, Seven Segment Display files were used.
 
# METHODOLOGY




- The states would move on as per inputs, with delays accounted at each state change in the diagram.
- As the states change, the LED displays change simultaneously as per the states showing both NS and EW signals.
- Seven Segment display constantly displays in letters the states of the signals. For ex- Red/Red or Red/Green and so on.




# FSM

 

# FSM

   

# FSM

 

# NEXYS DISPLAY

- Two modes ( Day time mode, and the night mode)
- Used four colors for the LEDs ( RED, YELLOW, GREEN, and BLUE for demonstration purposes)
- Clock and States run simultaneously in Seven Segment file in order to be able to make all the letters visible at the same time.

The LED and Seven Segment Display files receive a three bit input unique to the present state controlled by the top file. Based upon the present state, the LEDs will display the appropriate color and the Seven Segment will display the state the signal is in. Both, the LEDs and Seven Segment will represent the north/south signal, and the east west signal.

# LED file

```
begin
  if ColorChange = '1' then
    case sel is
      when "000" => NorthSouthLED <= "100"; EastWestLED <= "100"; -- red red
      when "001" => NorthSouthLED <= "010"; EastWestLED <= "100"; -- green red
      when "010" => NorthSouthLED <= "110"; EastWestLED <= "100"; -- yellow red
      when "011" => NorthSouthLED <= "100"; EastWestLED <= "100"; -- red red
      when "100" => NorthSouthLED <= "100"; EastWestLED <= "010"; -- red green
      when "101" => NorthSouthLED <= "100"; EastWestLED <= "110"; -- red yellow
      when "110" => NorthSouthLED <= "100"; EastWestLED <= "000"; -- red OFF
      when "111" => NorthSouthLED <= "000"; EastWestLED <= "110"; -- OFF Yellow
      when others => NorthSouthLED <= "100"; EastWestLED <= "100"; -- red red
    end case;

  elsif ColorChange = '0' then
    case sel is
      when "000" => NorthSouthLED <= "100"; EastWestLED <= "100"; -- red red
      when "001" => NorthSouthLED <= "010"; EastWestLED <= "100"; -- green red
      when "010" => NorthSouthLED <= "001"; EastWestLED <= "100"; -- yellow red
      when "011" => NorthSouthLED <= "100"; EastWestLED <= "100"; -- red red
      when "100" => NorthSouthLED <= "100"; EastWestLED <= "010"; -- red green
      when "101" => NorthSouthLED <= "100"; EastWestLED <= "001"; -- red yellow
      when "110" => NorthSouthLED <= "100"; EastWestLED <= "000"; -- red OFF
      when "111" => NorthSouthLED <= "000"; EastWestLED <= "001"; -- OFF Yellow
      when others => NorthSouthLED <= "100"; EastWestLED <= "100"; -- red red
    end case;
  end if;
end;
```

yellow

yellow

yellow

blue

blue

blue

# Seven Segment Display

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity SevSeg is
    Port ( SlowerClock : in STD_LOGIC;
          P : out STD_LOGIC_VECTOR (6 downto 0);
          AN : out STD_LOGIC_VECTOR (7 downto 0);
          sel : in STD_LOGIC_VECTOR (2 downto 0));
end SevSeg;

architecture Behavioral of SevSeg is

    type state is (D0, D1, D2, D3, D4, D5, D6, D7);
    signal y: state;
    signal Letter: STD_LOGIC_VECTOR (6 downto 0);
    signal NotAN: std_logic_vector (7 downto 0);

begin


    P <= not Letter;
    AN <= not NotAN;

    CycleThroughDisplays: process ( SlowerClock )
    begin
        if (SlowerClock'event and SlowerClock = '1') then
            case y is
                when D0 => y <= D1;
                when D1 => y <= D2;
                when D2 => y <= D3;
                when D3 => y <= D4;
                when D4 => y <= D5;
                when D5 => y <= D6;
                when D6 => y <= D7;
                when D7 => y <= D0;
            end case;
        end if;
    end process;

end SevSeg;
```

```
DisplayOutput: process (sel, y)
begin
    case sel is
        when "000" =>
            case y is
                when D0 => NotAN <= "10000000"; Letter<= "1010000"; -- r
                when D1 => NotAN <= "01000000"; Letter<= "1111001"; -- E
                when D2 => NotAN <= "00100000"; Letter<= "1011110"; -- d
                when D3 => NotAN <= "00010000"; Letter<= "00000000";
                when D4 => NotAN <= "00001000"; Letter<= "1010000"; -- r
                when D5 => NotAN <= "00000100"; Letter<= "1111001"; -- E
                when D6 => NotAN <= "00000010"; Letter<= "1011110"; -- d
                when D7 => NotAN <= "00000001"; Letter<= "00000000";
            end case;
        when "001" =>
            case y is
                when D0 => NotAN <= "10000000"; Letter<= "1010000"; -- r
                when D1 => NotAN <= "01000000"; Letter<= "1111001"; -- E
                when D2 => NotAN <= "00100000"; Letter<= "1011110"; -- d
                when D3 => NotAN <= "00010000"; Letter<= "00000000";
                when D4 => NotAN <= "00001000"; Letter<= "1101111"; -- G
                when D5 => NotAN <= "00000100"; Letter<= "1010000"; -- r
                when D6 => NotAN <= "00000010"; Letter<= "1111001"; -- E
                when D7 => NotAN <= "00000001"; Letter<= "1111001"; -- E
            end case;
        when "010" =>
            case y is
                when D0 => NotAN <= "10000000"; Letter<= "1010000"; -- r
                when D1 => NotAN <= "01000000"; Letter<= "1111001"; -- E
                when D2 => NotAN <= "00100000"; Letter<= "1011110"; -- d
                when D3 => NotAN <= "00010000"; Letter<= "00000000";
                when D4 => NotAN <= "00001000"; Letter<= "1101110"; -- Y
                when D5 => NotAN <= "00000100"; Letter<= "1111001"; -- E
                when D6 => NotAN <= "00000010"; Letter<= "0111000"; -- L
                when D7 => NotAN <= "00000001"; Letter<= "0111000"; -- L
            end case;
    end case;
end DisplayOutput;
```

# TRAFFIC LIGHT SYSTEM - DATAPATH

 

35

28

# DIFFICULTIES / ANY IMPROVEMENTS

$$R1 = A + BCD + B'C'D'E'$$

time (s)	North/South					East/West					
	A	B	C	D	E	R	Y	G	R	Y	G
0	0	0	0	0	0	1	0	0	1	0	0
1	0	0	0	0	1	0	0	1	1	0	0
2	0	0	0	1	0	0	0	1	1	0	0
3	0	0	0	1	1	0	0	1	1	0	0
4	0	0	1	0	0	0	0	1	1	0	0
5	0	0	1	0	1	0	0	1	1	0	0
6	0	0	1	1	0	0	0	1	1	0	0
7	0	0	1	1	1	0	0	1	1	0	0
8	0	1	0	0	0	0	0	1	1	0	0
9	0	1	0	0	1	0	0	1	1	0	0
10	0	1	0	1	0	0	0	1	1	0	0
11	0	1	0	1	1	0	1	0	1	0	0
12	0	1	1	0	0	0	1	0	1	0	0
13	0	1	1	0	1	0	1	0	1	0	0
14	0	1	1	1	0	1	0	0	1	0	0
15	0	1	1	1	1	1	0	0	0	0	1
16	1	0	0	0	0	1	0	0	0	0	1
17	1	0	0	0	1	1	0	0	0	0	1
18	1	0	0	1	0	1	0	0	0	0	1
19	1	0	0	1	1	1	0	0	0	0	1
20	1	0	1	0	0	1	0	0	0	0	1
21	1	0	1	0	1	1	0	0	0	0	1
22	1	0	1	1	0	1	0	0	0	0	1
23	1	0	1	1	1	1	0	0	0	0	1
24	1	1	0	0	0	1	0	0	0	0	1
25	1	1	0	0	1	1	0	0	0	1	0
26	1	1	0	1	0	1	0	0	0	1	0
27	1	1	0	1	1	1	0	0	0	1	0

DE	00	01	11	10
000	1	0	0	0
001	0	0	0	0
011	0	0	1	1
010	0	0	0	0
100	1	1	1	1
101	1	1	1	1
111	x	x	x	x
110	1	1	1	1

# DIFFICULTIES/ ANY IMPROVEMENTS

```
--clkDiv: process (Divider)
--begin
--  case Divider is
--    when 0 => Y <= "000";
--    when 1 => Y <= "001";
--    when 2 => Y <= "010";
--    when 3 => Y <= "011";
--    when 4 => Y <= "100";
--    when 5 => Y <= "101";
--    when 6 => Y <= "110";
--    when 7 => Y <= "111";

--  end case;
--end process;
```

```
if qt = 1000 then --101_1111_0101_1110_0001_0000_0000 1 sec 101111101011110000100000000
```

```
--      Q: out std_logic_vector (26 downto 0);
```

```
01DCD6500
```

```
signal count: integer := 0;
signal DividerCount: integer := 0;
```



**QUESTIONS?**