



Keyboard to 7-Segment Display


Chris Mathewson, Jason Mansour, and Kristine Miller

Introduction


- Input a number (0-9) from a keyboard
- Display the number on the 7-segment display
- Shift the previously entered numbers to the left when a new number is entered

Top-Level Design


PS/2 Keyboard to Seven-Segment Display

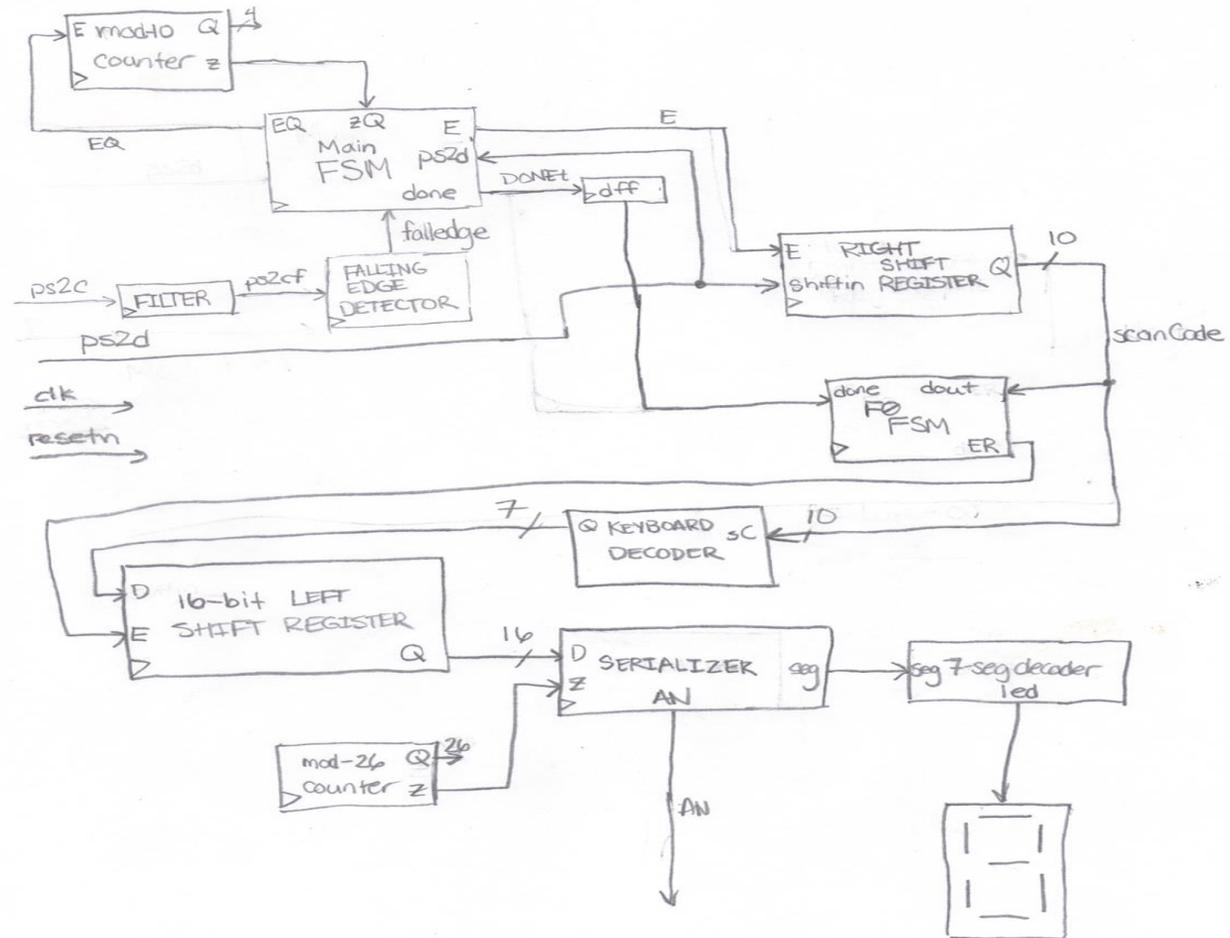


Falling Edge Finite State Machine

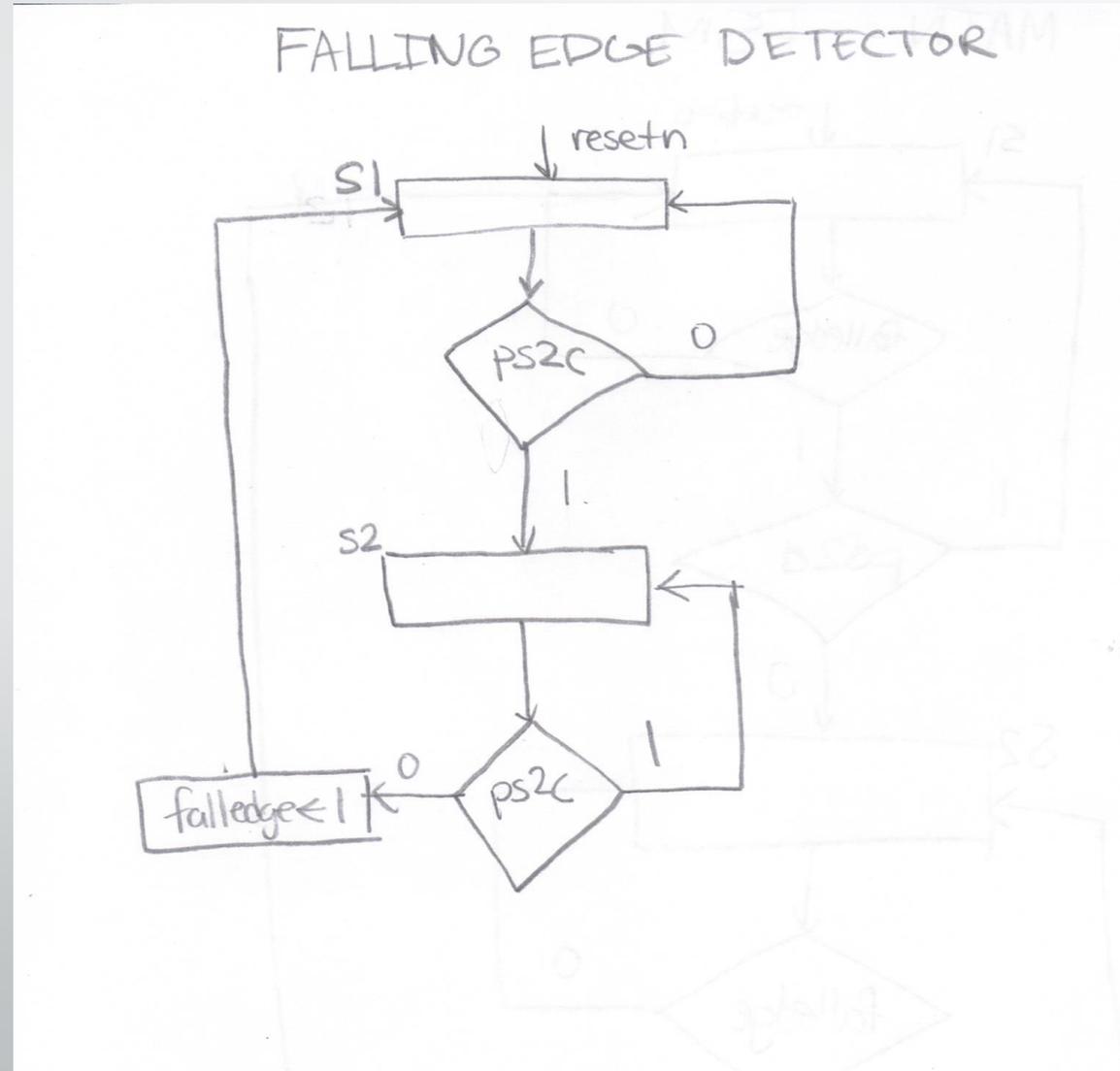

Main Finite State Machine

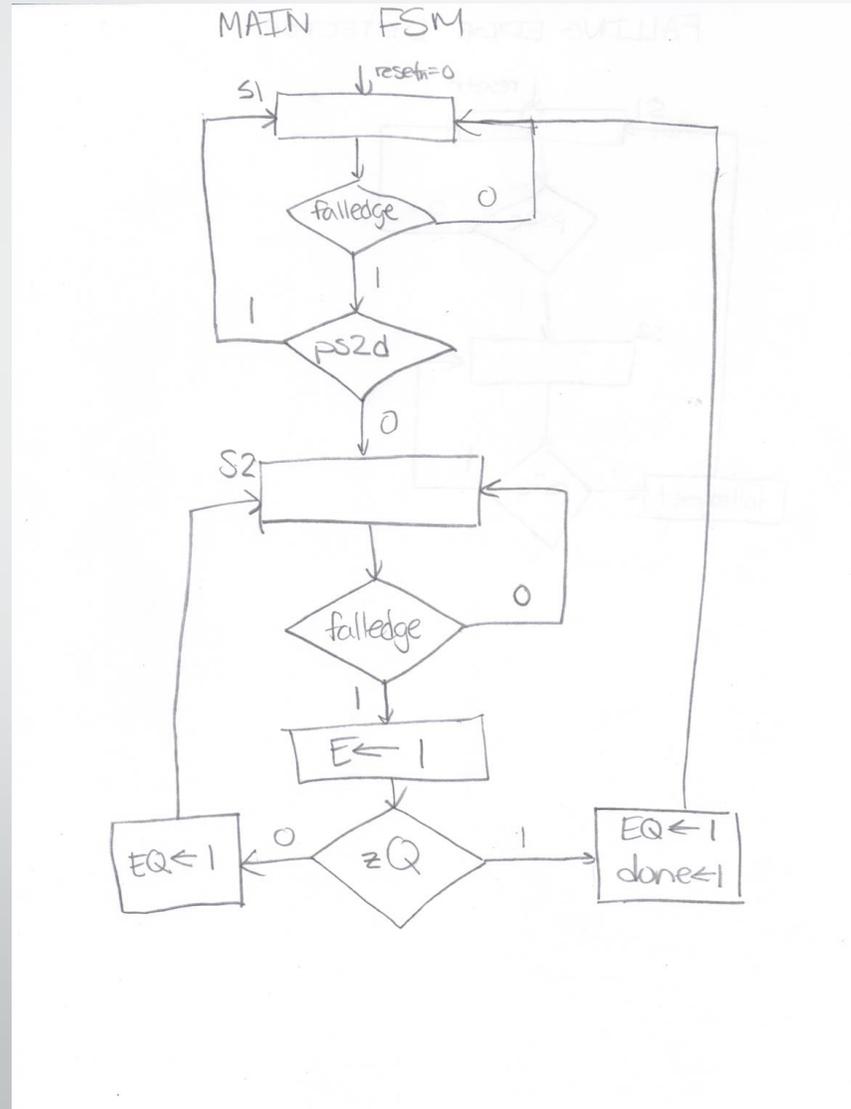

Fo Detector Finite State Machine

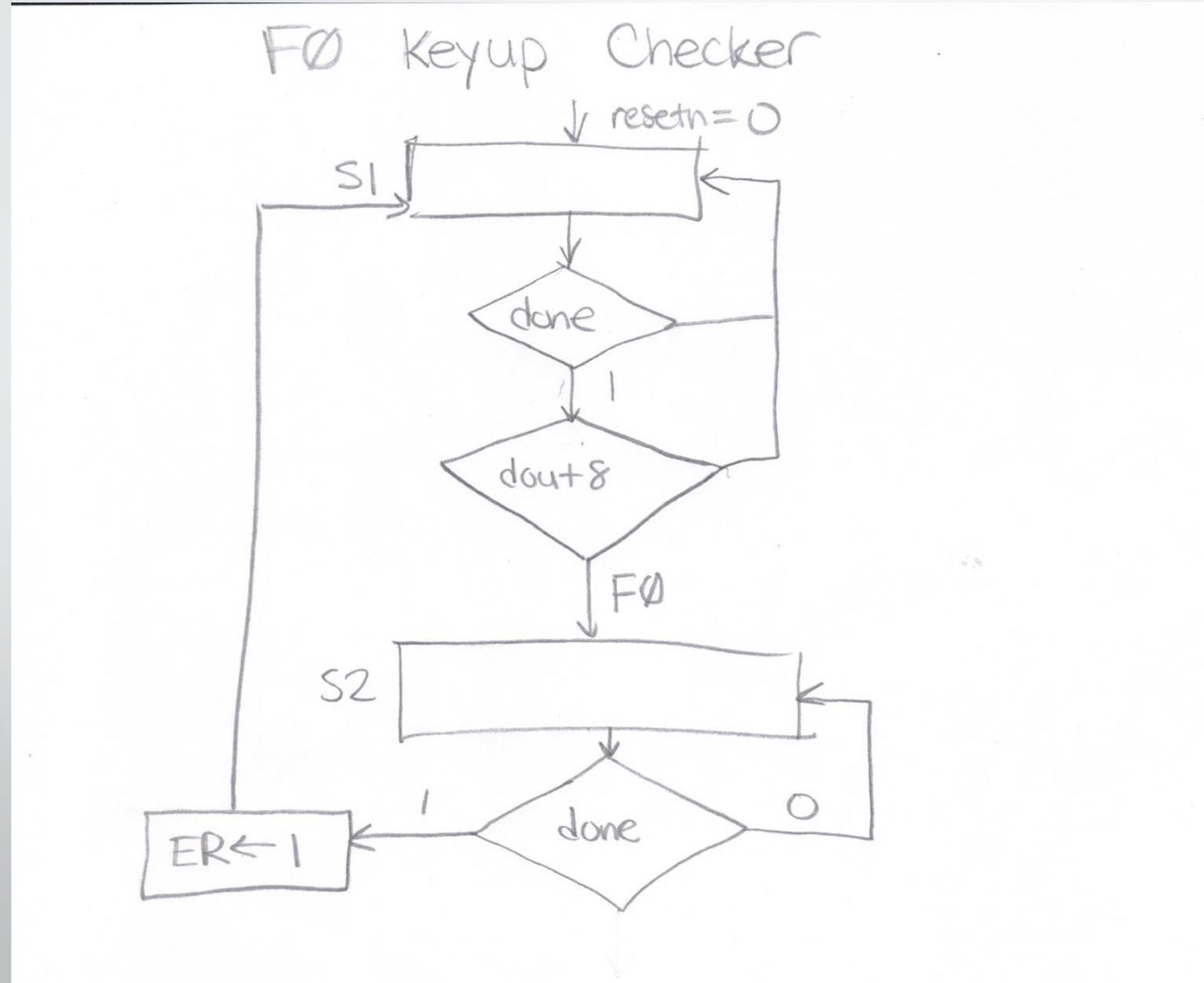

Challenges

- Getting the Correct Scan Code
- Designing the FSM's
- Dealing with the Keyup Signal
- Creating the filter\5

Conclusion

- The Program mostly works
- Three FSM's were used
- A number (0-9) is input from a Keyboard and output onto a 7-segment display



Any Questions?



Thanks!