

Homework 1

(Due date: September 21st @ 5:30 pm)
Presentation and clarity are very important!

PROBLEM 1 (25 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (12 pts)

✓ $F(X, Y, Z) = \prod(M_0, M_1, M_4, M_6)$

✓ $F = (A + \bar{C} + D)(\bar{A}C + \bar{D})$

✓ $F = \overline{X(\bar{Y} \oplus \bar{Z})} + \bar{Y}$

✓ $F = \overline{(A + \bar{B})C} + AB\bar{D}$

b) Determine whether or not the following expression is valid, i.e., whether the left- and right-hand sides represent the same function. Suggestion: complete the truth tables for both sides: (5 pts)

$$\bar{x}_1 \bar{x}_3 + x_2 x_3 + x_1 \bar{x}_2 = \bar{x}_1 x_2 + x_1 x_3 + \bar{x}_2 \bar{x}_3$$

x	y	z	f ₁	f ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.


PROBLEM 2 (15 PTS)

Design a logic circuit (simplify your circuit) that opens a lock ($f = 1$) whenever the user presses the correct number on each numpad (numpad 1: **8**, numpad 2: **3**). The numpad encodes each decimal number using BCD encoding (see figure). We expect that the 4-bit groups generated by each numpad be in the range from 0000 to 1001. Note that the values from 1010 to 1111 are assumed not to occur.

Suggestion: Create two circuits: one that verifies the first number (**8**), and another that verifies the second number (**3**). Then perform the AND operation on the two outputs. This avoids creating a truth table with 8 inputs.


Sketch the resulting logic circuit using ONLY 2-input NAND gates. (5 pts)

BCD code				Number pressed
x	y	z	w	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

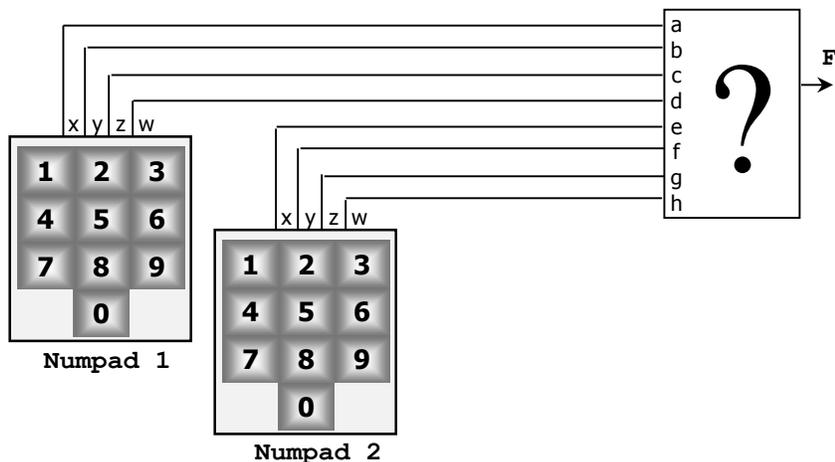

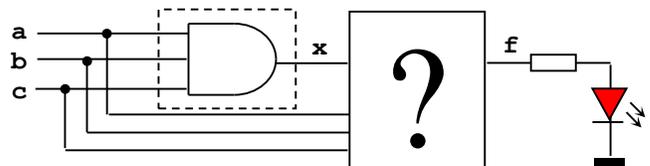
PROBLEM 3 (11 PTS)

Design a circuit (simplify your circuit) that verifies the logical operation of a 3-input AND gate. $f = '1'$ (LED ON) if the AND gate works properly. Assumption: when the AND gate is not working, it generates 1's instead of 0's and vice versa.



PROBLEM 4 (23 PTS)

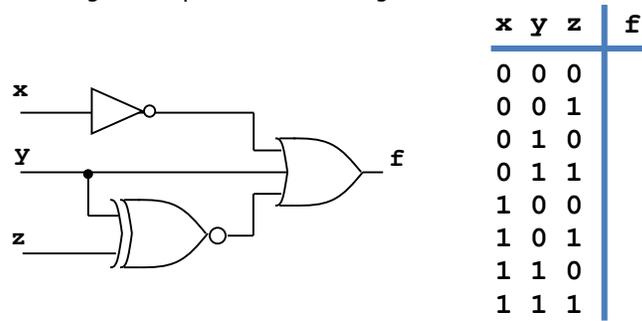a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (5 pts).




f =

b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

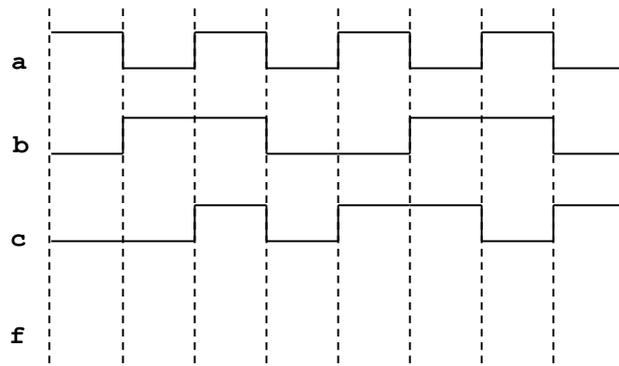architecture struct of circ is
  signal x, y: std_logic;
begin
  x <= a xnor c;
  y <= x nand b;
  f <= y and (not b);
end struct;
```




c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)



```
library ieee;
use ieee.std_logic_1164.all;

entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;

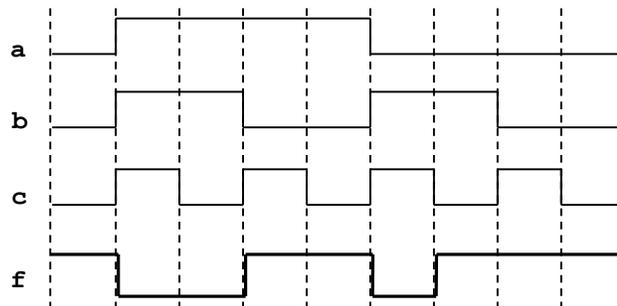architecture struct of wav is
  -- ???
begin
  -- ???
end struct;
```



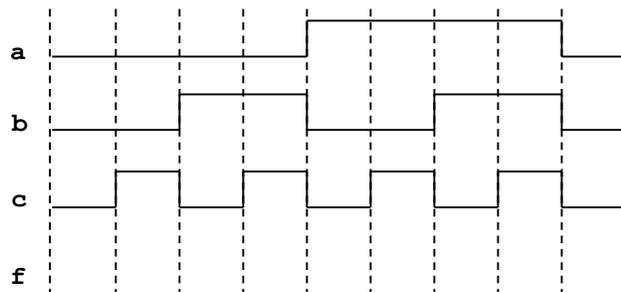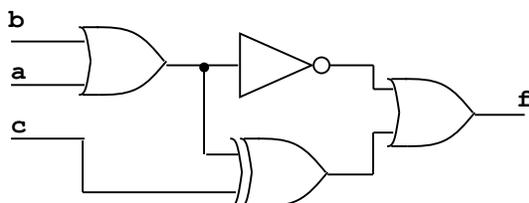d) Complete the timing diagram of the following circuit: (5 pts)



PROBLEM 5 (26 PTS)

- A 14-letter keypad produces a 4-bit code as shown in the table. We want to design a logic circuit that converts those 4-bit codes to Braille code, where the 6 dots are represented by LEDs. A raised (or embossed) dot is represented by an LED ON (logic value of '1'). A missing dot is represented by a LED off (logic value of '0').
- ✓ Complete the truth table for each output (Q_0 - Q_5).
- ✓ Provide the simplified expression for each output (Q_0 - Q_5). Use Karnaugh maps for Q_5, Q_4, Q_1, Q_0 and the Quine-McCluskey algorithm for Q_3 - Q_2 . Note it is safe to assume that the codes 1110 and 1111 will not be produced by the keypad.

a	b	c	d
e	f	g	h
i	j	k	l
m		n	

x
 y
 z
 w

Q
 6

Q_0		Q_1
Q_2		Q_3
Q_4		Q_5

x	y	z	w	Letter
0	0	0	0	a
0	0	0	1	b
0	0	1	0	c
0	0	1	1	d
0	1	0	0	e
0	1	0	1	f
0	1	1	0	g
0	1	1	1	h
1	0	0	0	i
1	0	0	1	j
1	0	1	0	k
1	0	1	1	l
1	1	0	0	m
1	1	0	1	n
1	1	1	0	
1	1	1	1	

a	b	c	d	e	f	g	h	i	j	k	l	m	n
● ○	● ○	● ●	● ●	● ○	● ●	● ●	● ○	○ ●	○ ●	● ○	● ○	● ●	● ●
○ ○	● ○	○ ○	○ ●	○ ●	● ○	● ●	● ●	● ○	● ●	○ ○	● ○	○ ○	○ ●
○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	○ ○	● ○	● ○	● ○	● ○