

Quiz 3

(November 7th @ 5:30 pm)


PROBLEM 1 (30 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;



entity circ is
port ( rstn, a,b, x, clk: in std_logic;
      q: out std_logic);
end circ;
```
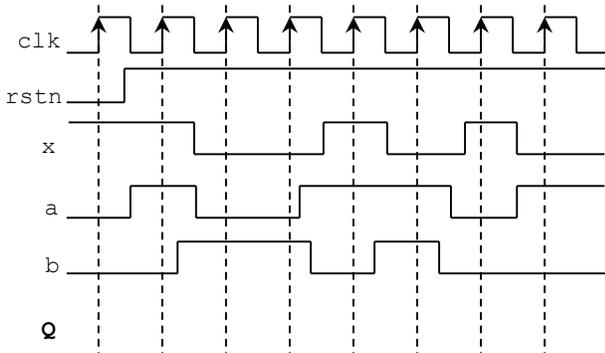
```
architecture xst of circ is
signal qt: std_logic;
begin
process (rstn, clk, a, b, x)
begin
if rstn = '0' then
qt <= '0';
elsif (clk'event and clk = '1') then
if x = '1' then
qt <= a or b;
end if;
end if;
end process;
q <= qt;
end xst;
```



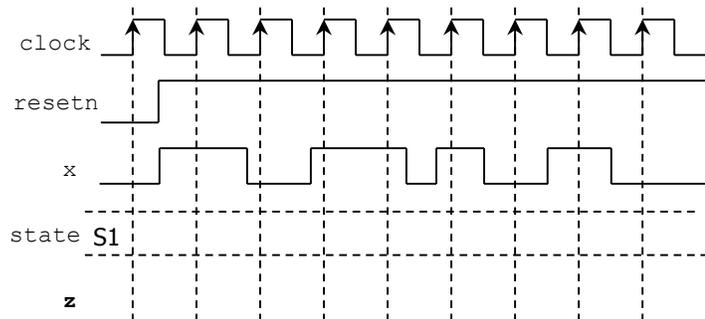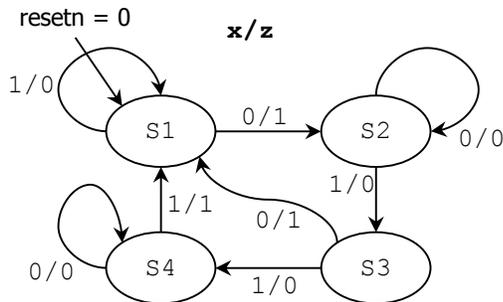PROBLEM 2 (35 PTS)

- Complete the timing diagram of the following state machine:



PROBLEM 3 (35 PTS)

- Complete the timing diagram of the following circuit: $Q = Q_3Q_2Q_1Q_0$

