


Solutions - Final Exam

(December 14th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

 
PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 0110$, $Q = Q_3Q_2Q_1Q_0$



 PROBLEM 2 (19 PTS)

- Complete the timing diagram of the circuit shown below: (8 pts)



- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (11 pts)


$$Q_1(t+1) = Q_0(t)$$

$$Q_0(t+1) = Q_1(t) \oplus w$$

$$z = (Q_1(t) \oplus w) \oplus Q_0(t)$$

State Assignment:


S1: Q=00 S2: Q=01
S3: Q=10 S4: Q=11

 

PRESENT STATE			NEXTSTATE		
w	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)	z	
0	0 0		0 1	0	
0	0 1		1 1	1	
0	1 0		0 0	1	
0	1 1		1 0	0	
1	0 0		0 0	1	
1	0 1		1 0	0	
1	1 0		0 1	0	
1	1 1		1 1	1	




PRESENT STATE			NEXT STATE		
w	PRESENT STATE		NEXT STATE	z	
0	S1		S2	0	
0	S2		S4	1	
0	S3		S1	1	
0	S4		S3	0	
1	S1		S1	1	
1	S2		S3	0	
1	S3		S2	0	
1	S4		S4	1	

 

 
PROBLEM 3 (10 PTS)

- Given the following circuit, complete the timing diagram.
The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where $ILUT$ is a 6-bit unsigned number.
For example $ILUT = 35 (10011_2) \rightarrow OLUT = \lceil \sqrt{35} \rceil = 6 (000110_2)$



 PROBLEM 4 (23 PTS)

- Sequence detector: The machine has to generate $z = 1$ when it detects the sequence 1010011. Once the sequence is detected, the circuit looks for a new sequence.




- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with input x and output z . Is this a Mealy or a Moore machine? Why? (15 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)

- State Diagram, State Table, and Excitation Table:

State Assignment:

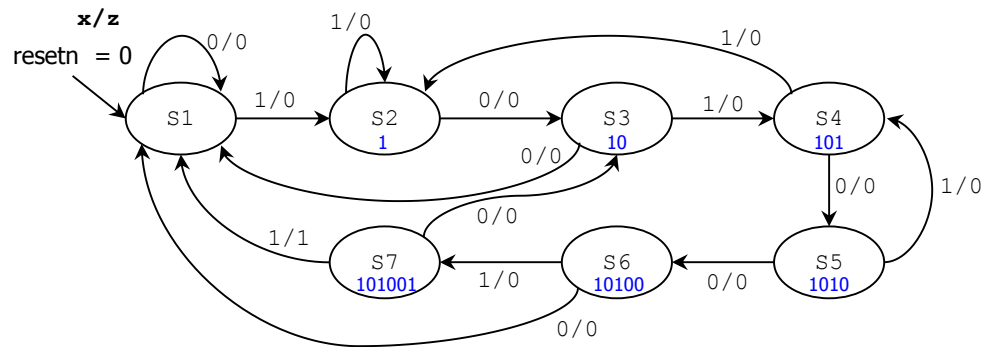S1: Q=000 S2: Q=001 S3: Q=010
S4: Q=011 S5: Q=100 S6: Q=101 S7: Q=110



PRESENT STATE				NEXT STATE			
x	STATE	STATE	z	x	Q ₂ Q ₁ Q ₀ (t)	Q ₂ Q ₁ Q ₀ (t+1)	z
0	S1	S1	0	0	0 0 0 0	0 0 0	0
0	S2	S3	0	0	0 0 0 1	0 1 0	0
0	S3	S1	0	0	0 0 1 0	0 0 0	0
0	S4	S5	0	0	0 0 1 1	1 0 0	0
0	S5	S6	0	0	0 1 0 0	1 0 1	0
0	S6	S1	0	0	0 1 0 1	0 0 0	0
0	S7	S3	0	0	0 1 1 0	0 1 0	0
1	S1	S2	0	0	0 1 1 1	X X X	X
1	S2	S2	0	1	1 0 0 0	0 0 1	0
1	S3	S4	0	1	1 0 0 1	0 0 1	0
1	S4	S2	0	1	1 0 1 0	0 1 1	0
1	S5	S4	0	1	1 0 1 1	0 0 1	0
1	S6	S7	0	1	1 1 0 0	0 1 1	0
1	S7	S1	1	1	1 1 0 1	1 1 0	0
				1	1 1 1 0	0 0 0	1
				1	1 1 1 1	X X X	X

This is a Mealy FSM. The output 'z' depends on the input as well as on the present state.

Excitation equations, minimization, and circuit implementation:

$$\begin{aligned}
 Q_2(t+1) &= \bar{x}Q_2\bar{Q}_1\bar{Q}_0 + xQ_2Q_0 + \bar{x}Q_1Q_0 \\
 Q_1(t+1) &= \bar{x}Q_2\bar{Q}_1Q_0 + xQ_2Q_1\bar{Q}_0 + xQ_2Q_1 + \bar{x}Q_2Q_1 = \bar{x}Q_2\bar{Q}_1Q_0 + xQ_2Q_1\bar{Q}_0 + Q_2(x \oplus Q_1) \\
 Q_0(t+1) &= Q_2Q_1\bar{Q}_0 + xQ_2 \\
 z &= xQ_2Q_1
 \end{aligned}$$

$Q_2(t+1)$

	x_{Q_2}	00	01	11	10
Q_1Q_0					
00		0	1	0	0
01		0	0	1	0
11		1	X	X	0
10		0	0	0	0

$Q_1(t+1)$


	x_{Q_2}	00	01	11	10
Q_1Q_0					
00		0	0	1	0
01		1	0	1	0
11		0	X	X	0
10		0	1	0	1

$Q_0(t+1)$

	x_{Q_2}	00	01	11	10
Q_1Q_0					
00		0	1	1	1
01		0	0	0	1
11		0	X	X	1
10		0	0	0	1



z

	x_{Q_2}	00	01	11	10
Q_1Q_0					
00		0	0	0	0
01		0	0	0	0
11		0	X	X	0
10		0	0	1	0

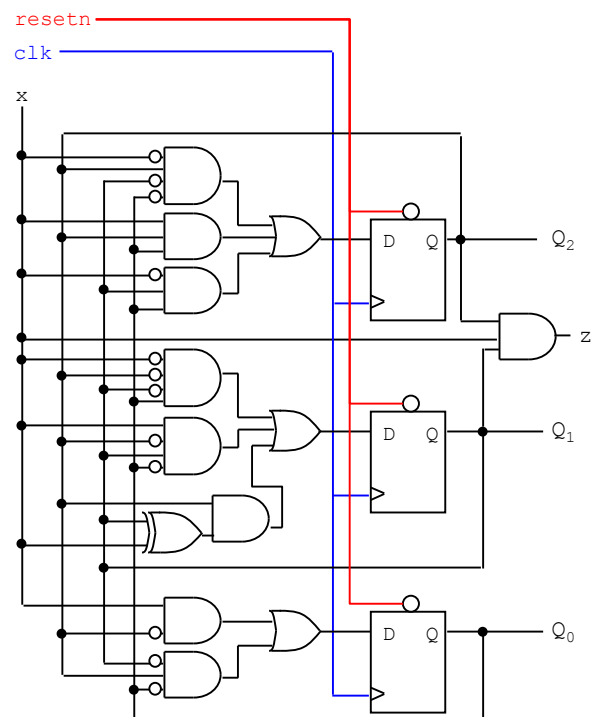

 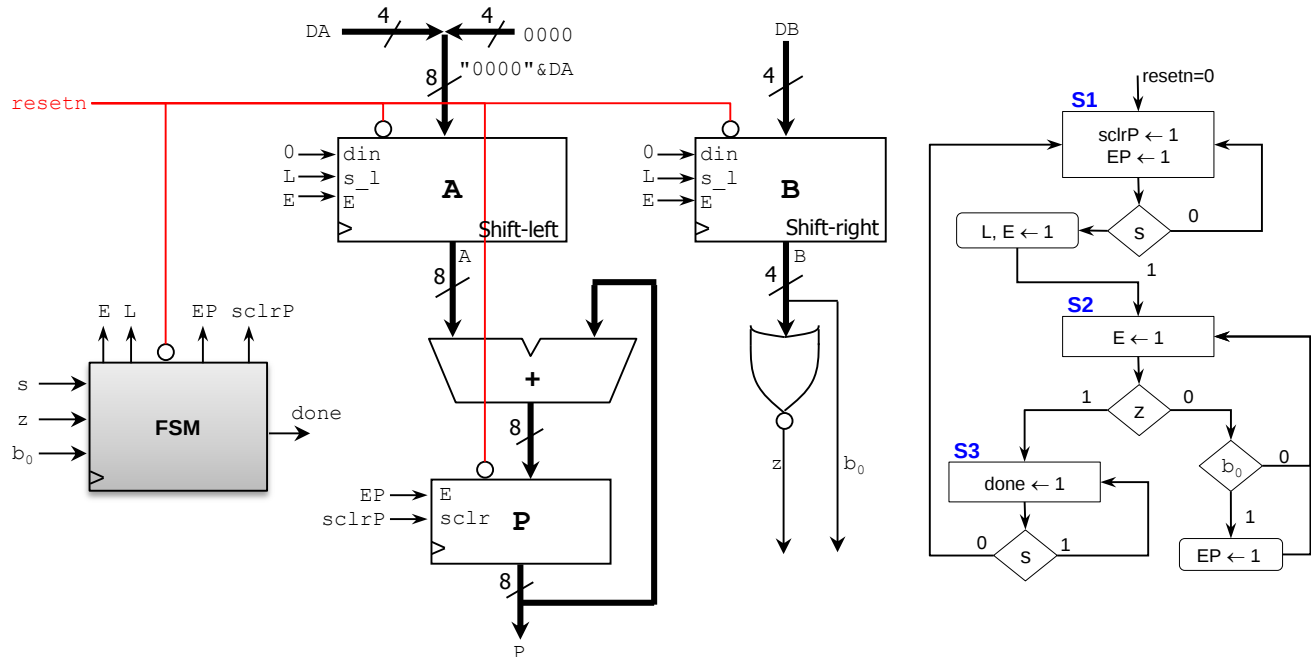PROBLEM 5 (20 PTS)

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
Register (for P): *sclr*: synchronous clear. Here, if *sclr* = *E* = 1, the register contents are initialized to 0.
Parallel access shift registers (for A and B): If *E* = 1: *s_l* = 1 → Load, *s_l* = 0 → Shift




PROBLEM 6 (16 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

 entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```



```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '0' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;

                when S2 =>
                    if q = '1' then y <= S1; else y <= S3; end if;

                when S3 =>
                    if p = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '1' then
                            w <= '1';
                            if p = '0' then
                                x <= '1';
                            end if;
                        end if;

            when S2 => if p = '1' then x <= '1'; end if;
                       if q = '0' then z <= '1'; end if;

            when S3 => if p = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

This is a Mealy FSM. The outputs 'x,w,z' depend on the input as well as on the present state.

