

Solutions - Homework 1

(Due date: September 21st @ 5:30 pm)
Presentation and clarity are very important!

PROBLEM 1 (25 PTS)

- a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (12 pts)


✓ $F(X, Y, Z) = \prod(M_0, M_1, M_4, M_6)$

✓ $F = (A + \bar{C} + D)(\bar{A}C + \bar{D})$


✓ $F = \overline{X(\bar{Y} \oplus \bar{Z})} + \bar{Y}$

✓ $F = \overline{(A + B)C + AB\bar{D}}$

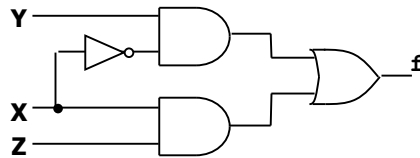
✓ $F(X, Y, Z) = \prod(M_0, M_1, M_4, M_6) = \sum(m_2, m_3, m_5, m_7) = \bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XYZ = \bar{X}Y(\bar{Z} + Z) + XZ(\bar{Y} + Y) = \bar{X}Y + XZ$



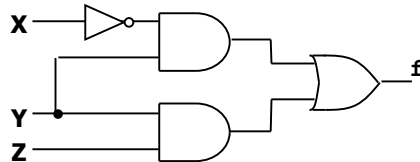
✓ $F = \overline{X(\bar{Y} \oplus \bar{Z})} + \bar{Y} = \overline{X(Y \oplus Z)} + \bar{Y} = (\bar{X} + \overline{Y \oplus Z})\bar{Y} = (\bar{X} + YZ + \bar{Y}\bar{Z})\bar{Y} = \bar{X}\bar{Y} + Y\bar{Z}$



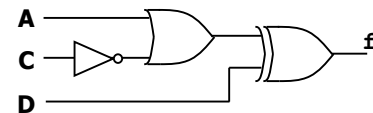✓ $F = (A + \bar{C} + D)(\bar{A}C + \bar{D}) = (X + D)(\bar{X} + \bar{D}) = X\bar{D} + \bar{X}D, X = A + \bar{C}$
 $= (A + \bar{C})\bar{D} + \bar{A}CD = A\bar{D} + \bar{C}\bar{D} + \bar{A}CD$



✓ $F = \overline{(A + B)C + AB\bar{D}} = \overline{(A + B)C} \cdot \overline{AB\bar{D}} = \overline{A}\bar{B}\bar{C} \cdot \overline{AB\bar{D}} = (A + B + \bar{C})(\bar{A} + \bar{B} + D)$
 $= A\bar{A} + A\bar{B} + AD + B\bar{A} + B\bar{B} + BD + \bar{C}\bar{A} + \bar{C}\bar{B} + \bar{C}D = A\bar{B} + \bar{A}\bar{C} + \bar{C}\bar{B} + AD + \bar{A}B + BD + \bar{C}D$
 $= A\bar{B} + \bar{A}\bar{C} + AD + \bar{A}B + \bar{C}D = A\bar{B} + \bar{A}B + AD + \bar{A}\bar{C} + \bar{C}D = A \oplus B + AD + \bar{A}\bar{C}$

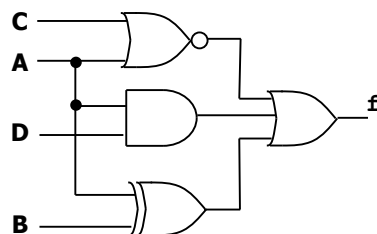

- b) Determine whether or not the following expression is valid, i.e., whether the left- and right-hand sides represent the same function. Suggestion: complete the truth tables for both sides: (5 pts)

$$\overline{x_1} \overline{x_3} + x_2 x_3 + x_1 \overline{x_2} = \overline{x_1} x_2 + x_1 x_3 + \overline{x_2} \overline{x_3}$$

Left-hand side:

$$\overline{x_1}(x_2 + \overline{x_2}) \overline{x_3} + (x_1 + \overline{x_1}) x_2 x_3 + x_1 \overline{x_2}(x_3 + \overline{x_3}) = \overline{x_1} x_2 \overline{x_3} + \overline{x_1} \overline{x_2} \overline{x_3} + x_1 x_2 x_3 + \overline{x_1} x_2 x_3 + x_1 \overline{x_2} x_3 + x_1 \overline{x_2} \overline{x_3} = \sum m(0,2,3,4,5,7)$$

Right-hand side:

$$\overline{x_1} x_2 (x_3 + \overline{x_3}) + x_1 (x_2 + \overline{x_2}) x_3 + (x_1 + \overline{x_1}) \overline{x_2} \overline{x_3} = \overline{x_1} x_2 x_3 + \overline{x_1} x_2 \overline{x_3} + x_1 x_2 x_3 + x_1 \overline{x_2} x_3 + x_1 \overline{x_2} \overline{x_3} + \overline{x_1} \overline{x_2} \overline{x_3} = \sum m(0,2,3,4,5,7)$$

Both left-hand and right-hand equations represent the same Boolean function.

- c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

x	y	z	f ₁	f ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

Sum of Products

$$f_1 = \overline{x} \overline{y} z + \overline{x} y \overline{z} + x \overline{y} \overline{z} + xyz$$

$$f_2 = \overline{x} \overline{y} z + x y \overline{z} + xyz$$

Product of Sums



$$f_1 = (x + y + z)(x + \overline{y} + \overline{z})(\overline{x} + y + \overline{z})(\overline{x} + \overline{y} + z)$$

$$f_2 = (x + y + z)(x + \overline{y} + z)(x + \overline{y} + \overline{z})(\overline{x} + y + z)(\overline{x} + y + \overline{z})$$

Minterms and maxterms:



$$f_1 = \sum(m_1, m_2, m_4, m_7) = \prod(M_0, M_3, M_5, M_6)$$
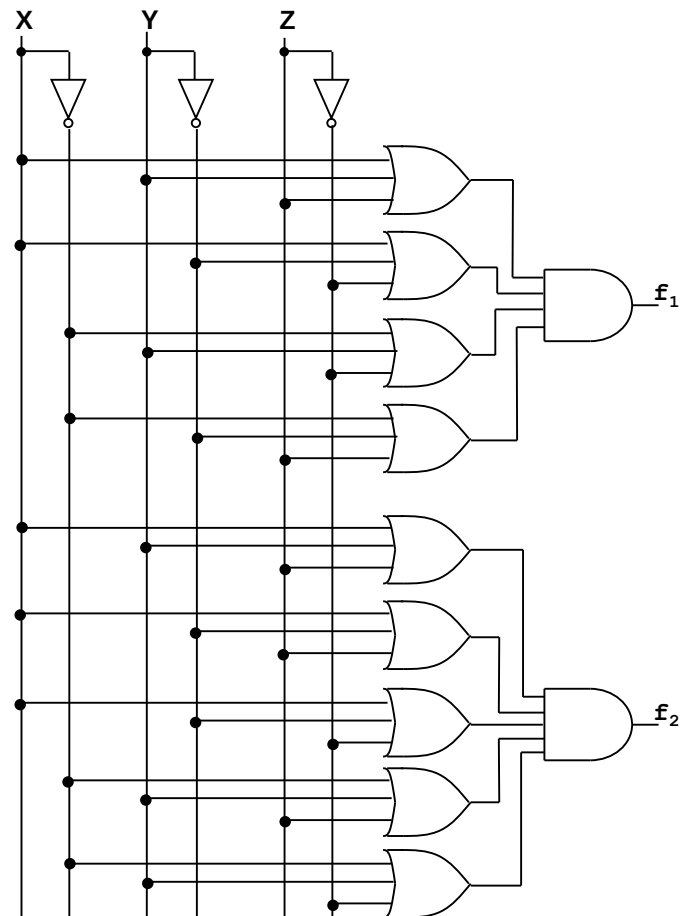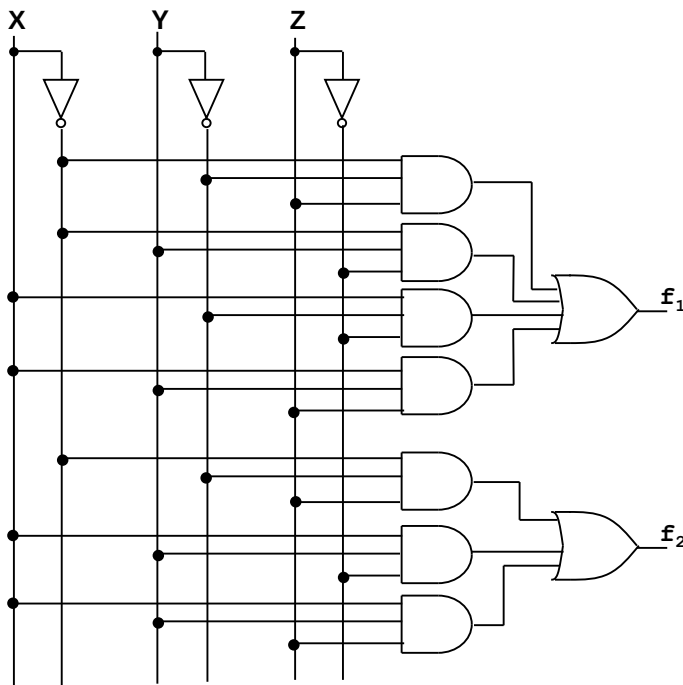
$$f_2 = \sum(m_1, m_6, m_7) = \prod(M_0, M_2, M_3, M_4, M_5)$$




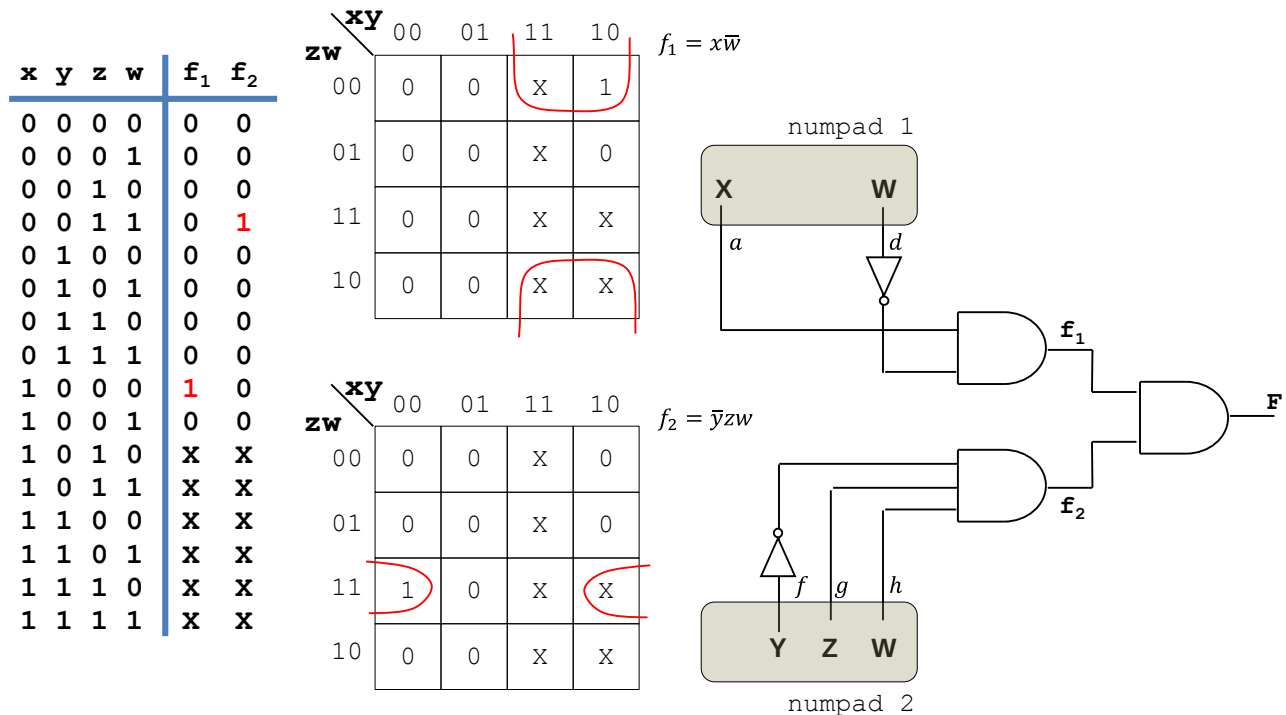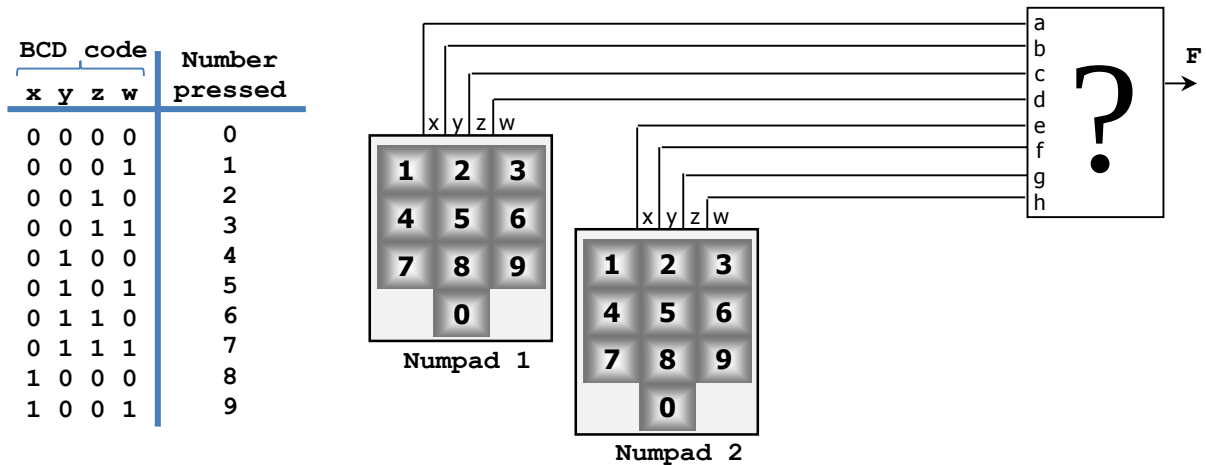PROBLEM 2 (15 PTS)

- Design a logic circuit (simplify your circuit) that opens a lock ($f = 1$) whenever the user presses the correct number on each numpad (numpad 1: **8**, numpad2: **3**). The numpad encodes each decimal number using BCD encoding (see figure). We expect that the 4-bit groups generated by each numpad be in the range from 0000 to 1001. Note that the values from 1010 to 1111 are assumed not to occur.
Suggestion: Create two circuits: one that verifies the first number (**8**), and another that verifies the second number (**3**). Then perform the AND operation on the two outputs. This avoids creating a truth table with 8 inputs.
- Sketch the resulting logic circuit using ONLY 2-input NAND gates. (5 pts)



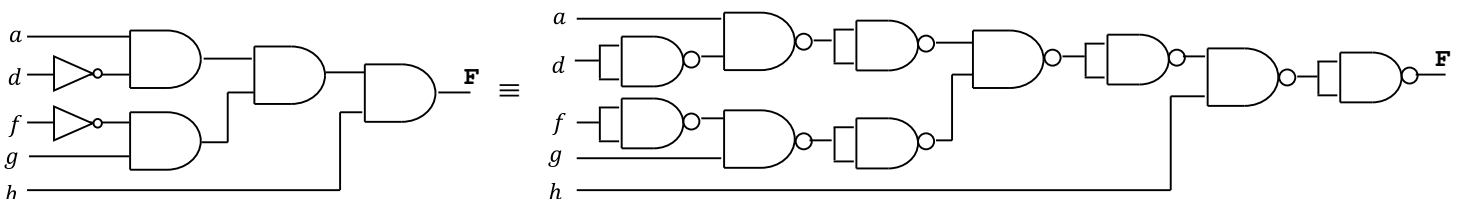
$$F = a\bar{d}\bar{f}gh = (\bar{a}\bar{d})(\bar{f}g)h$$




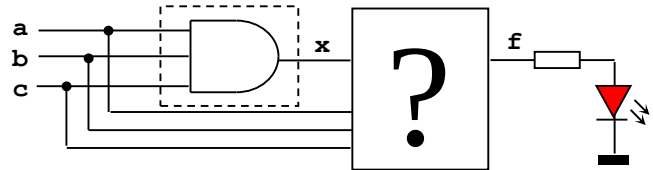PROBLEM 3 (11 PTS)

- Design a circuit (simplify your circuit) that verifies the logical operation of a 3-input AND gate. $f = '1'$ (LED ON) if the AND gate works properly. Assumption: when the AND gate is not working, it generates 1's instead of 0's and vice versa.



x	a	b	c	f	x _{good}
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	1	1

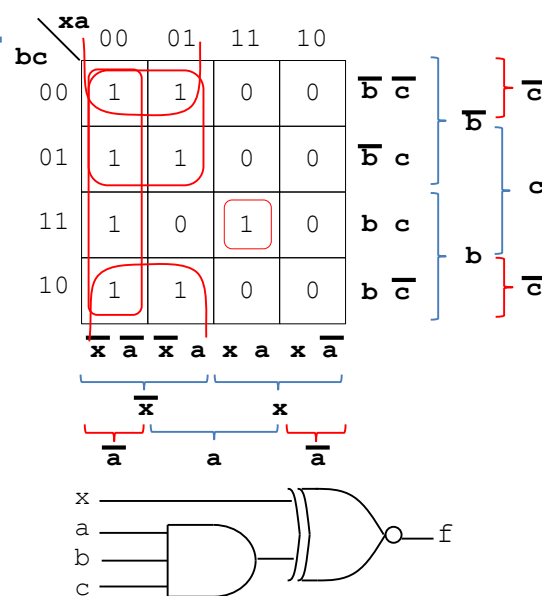


$$f = \bar{x}\bar{c} + \bar{x}\bar{b} + \bar{x}\bar{a} + xabc$$

$$f = \bar{x}(\bar{a} + \bar{b} + \bar{c}) + xabc$$


$$f = \bar{x}\bar{a}\bar{b}\bar{c} + xabc$$

$$f = x \oplus abc$$

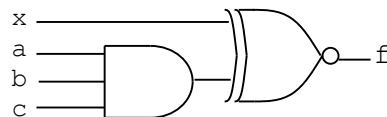

PROBLEM 4 (23 PTS)

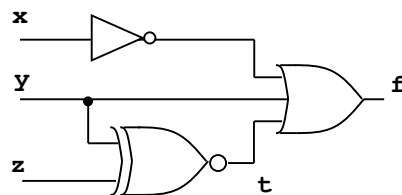- a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (5 pts).



x	y	z	t	f
0	0	0	1	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

$$f = \bar{x} + y + \bar{z}$$


- b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

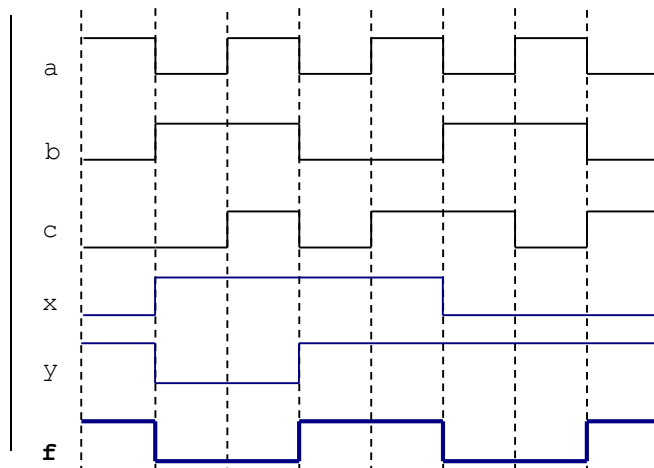architecture struct of circ is
    signal x, y: std_logic;
begin
    x <= a xnor c;
    y <= x nand b;
    f <= y and (not b);
end struct;
    
```




- c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;


architecture struct of wav is

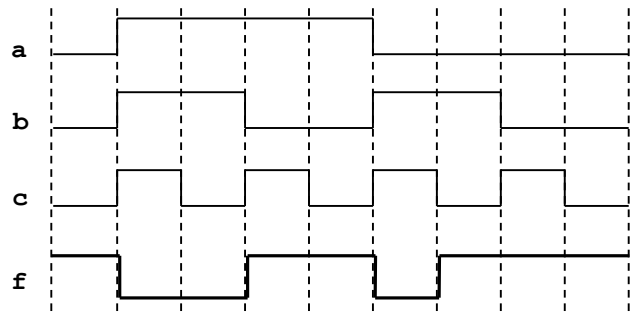begin
  f <= not(b) or (a nor c)
end struct;
```





a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

ab \ c	00	01	11	10
0	1	1	0	1
1	1	0	0	1

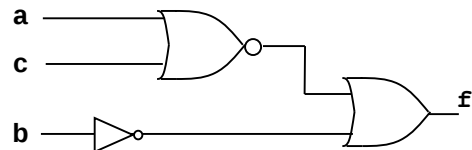
$$f = \bar{b} + \bar{a}\bar{c} = \bar{b} + \overline{a+c}$$

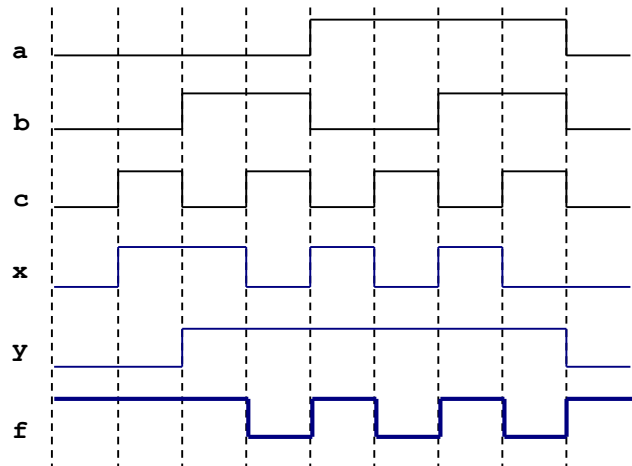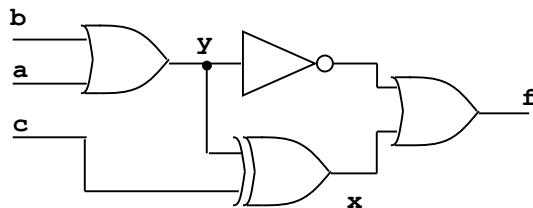
- d) Complete the timing diagram of the following circuit: (5 pts)



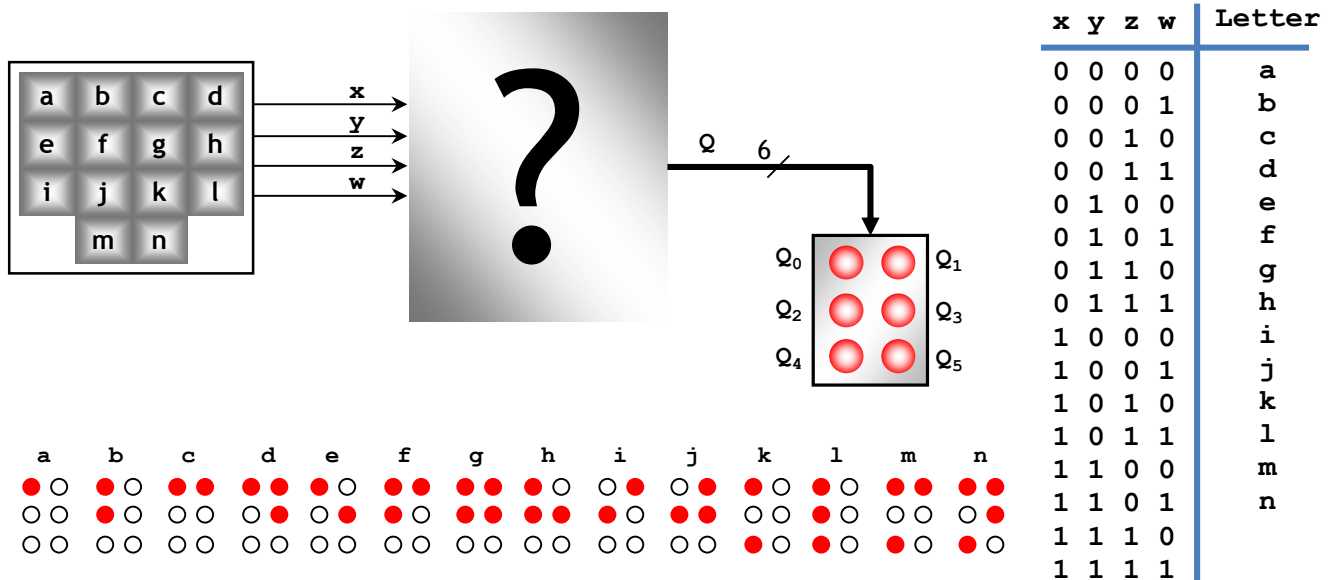PROBLEM 5 (26 PTS)

- A 14-letter keypad produces a 4-bit code as shown in the table. We want to design a logic circuit that converts those 4-bit codes to Braille code, where the 6 dots are represented by LEDs. A raised (or embossed) dot is represented by an LED ON (logic value of '1'). A missing dot is represented by a LED off (logic value of '0').
- Complete the truth table for each output (Q_0 - Q_5).
- Provide the simplified expression for each output (Q_0 - Q_5). Use Karnaugh maps for Q_5, Q_4, Q_1, Q_0 and the Quine-McCluskey algorithm for Q_3 - Q_2 . Note it is safe to assume that the codes 1110 and 1111 will not be produced by the keypad.



x	y	z	w	Q_5	Q_4	Q_3	Q_2	Q_1	Q_0	Letter
0	0	0	0	0	0	0	0	0	1	a
0	0	0	1	0	0	0	1	0	1	b
0	0	1	0	0	0	0	0	1	1	c
0	0	1	1	0	0	1	0	1	1	d
0	1	0	0	0	0	1	0	0	1	e
0	1	0	1	0	0	0	1	1	1	f
0	1	1	0	0	0	1	1	1	1	g
0	1	1	1	0	0	1	1	0	1	h
1	0	0	0	0	0	0	1	1	0	i
1	0	0	1	0	0	1	1	1	0	j
1	0	1	0	0	1	0	0	0	1	k
1	0	1	1	0	1	0	1	0	1	l
1	1	0	0	0	1	0	0	0	1	m
1	1	0	1	0	1	1	0	1	1	n
1	1	1	0	X	X	X	X	X	X	
1	1	1	1	X	X	X	X	X	X	

Q_4 Karnaugh Map:

zw \ xy	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	X	1
10	0	0	X	1

Q_1 Karnaugh Map:

zw \ xy	00	01	11	10
00	0	0	1	1
01	0	1	1	1
11	1	0	X	0
10	1	1	X	0

Q_0 Karnaugh Map:

zw \ xy	00	01	11	10
00	1	1	1	0
01	1	1	1	0
11	0	1	X	1
10	1	1	X	1

$$\begin{aligned}
 Q_5 &= 0 \\
 Q_4 &= xz + xy \\
 Q_3 &= \bar{x}y\bar{w} + \bar{x}zw + x\bar{z}w \\
 Q_2 &= yz + \bar{x}\bar{z}w + x\bar{y}\bar{z} + x\bar{y}w \\
 Q_1 &= \bar{x}\bar{y}z + y\bar{z}w + \bar{x}z\bar{w} + x\bar{z} \\
 Q_0 &= \bar{x} + y + z
 \end{aligned}$$

- $Q_3 = \sum m(3,4,6,7,9,13) + \sum d(14,15)$.

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_4 = 0100$ ✓	$m_{4,6} = 01-0$	$m_{6,14,7,15} = -11-$ $m_{6,7,14,15} = -11-$	We can't combine any further, so we stop here
2	$m_3 = 0011$ ✓ $m_6 = 0110$ ✓ $m_9 = 1001$ ✓	$m_{3,7} = 0-11$ $m_{6,7} = 011-$ ✓ $m_{6,14} = -110$ ✓ $m_{9,13} = 1-01$		
3	$m_7 = 0111$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{13,15} = 11-1$ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

Prime Implicants		Minterms					
		3	4	6	7	9	13
$m_{4,6}$	$\bar{x}y\bar{w}$		X	X			
$m_{3,7}$	$\bar{x}zw$	X			X		
$m_{9,13}$	$x\bar{z}w$					X	X
$m_{13,15}$	xyw						X
$m_{6,14,7,15}$	yz			X	X		

$$\rightarrow Q_3 = \bar{x}y\bar{w} + \bar{x}zw + x\bar{z}w$$

- $Q_2 = \sum m(1,5,6,7,8,9,11) + \sum d(14,15)$.

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_1 = 0001$ ✓ $m_8 = 1000$ ✓	$m_{1,5} = 0-01$ $m_{1,9} = -001$ $m_{8,9} = 100-$	$m_{6,7,14,15} = -11-$ $m_{6,14,7,15} = -11-$	We can't combine any further, so we stop here
2	$m_5 = 0101$ ✓ $m_6 = 0110$ ✓ $m_9 = 1001$ ✓	$m_{5,7} = 01-1$ $m_{6,7} = 011-$ ✓ $m_{6,14} = -110$ ✓ $m_{9,11} = 10-1$		
3	$m_7 = 0111$ ✓ $m_{11} = 1011$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{11,15} = 1-11$ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

Prime Implicants		Minterms						
		1	5	6	7	8	9	11
$m_{1,5}$	$\bar{x}\bar{z}w$	X	X					
$m_{1,9}$	$\bar{y}\bar{z}w$	X					X	
$m_{8,9}$	$x\bar{y}\bar{z}$					X	X	
$m_{5,7}$	$\bar{x}yw$		X		X			
$m_{9,11}$	$x\bar{y}w$						X	X
$m_{11,15}$	xzw							X
$m_{6,7,14,15}$	yz			X	X			

$$\rightarrow Q_2 = yz + \bar{x}\bar{z}w + x\bar{y}\bar{z} + \bar{x}yw$$