


Solutions - Homework 4

(Due date: November 21st @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (14 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1011$, $Q = Q_3Q_2Q_1Q_0$




PROBLEM 2 (18 PTS)

- Design a counter using a Finite State Machine (FSM):


Counter features:

 - ✓ Count: 000, 001, 011, 101, 111, 010, 100, 110, 000, 001, 011, 101, ...
- ✓ $resetn$: Asynchronous active-low input signal. It initializes the count to '000'.
- ✓ Input E : Synchronous input that increases the count when it is set to '1'.
- ✓ output z : It becomes '1' when the count is 110.



- Provide the State Diagram (any representation), State Table, and the Excitation Table. Is this a Mealy or a Moore machine? Why? (8 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (5 pts)

- State Diagram and State Table:

 

The output 'z' only depends on the present state $\Rightarrow$ Moore FSM.

PRESENT		NEXT	
E	STATE	STATE	z
0	S1	S1	0
0	S2	S2	0
0	S3	S3	0
0	S4	S4	0
0	S5	S5	0
0	S6	S6	0
0	S7	S7	0
0	S8	S8	1
1	S1	S2	0
1	S2	S3	0
1	S3	S4	0
1	S4	S5	0
1	S5	S6	0
1	S6	S7	0
1	S7	S8	0
1	S8	S1	1

State Assignment and Excitation Table:

- ✓ S1: Q = 000
- ✓ S2: Q = 001
- ✓ S3: Q = 011
- ✓ S4: Q = 101
- ✓ S5: Q = 111
- ✓ S6: Q = 010
- ✓ S7: Q = 100
- ✓ S8: Q = 110

PRESENT STATE				NEXTSTATE	
E	Q ₂ Q ₁ Q ₀ (t)			Q ₂ Q ₁ Q ₀ (t+1)	z
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	1	1	0
0	0	1	0	0	0
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	0	0	0
1	1	1	0	0	1

Excitation equations and minimization:

$$Q_2(t+1) = \bar{E}Q_2 + Q_2\bar{Q}_1 + E\bar{Q}_2Q_1 = \bar{E}Q_1Q_2 + E\bar{Q}_1Q_2 = Q_2 \oplus (EQ_1)$$

$$Q_1(t+1) = \bar{E}Q_1 + EQ_2\bar{Q}_1 + Q_2Q_1Q_0 + E\bar{Q}_1Q_0 = \bar{E}Q_1 + E\bar{Q}_1(Q_2 + Q_0) + Q_2Q_1Q_0$$


$$Q_0(t+1) = \bar{Q}_1Q_0 + \bar{E}Q_0 + \bar{Q}_2Q_0 + E\bar{Q}_2\bar{Q}_1 = \bar{E}Q_2\bar{Q}_1Q_0 + E\bar{Q}_2\bar{Q}_1$$

$$z = Q_2Q_1\bar{Q}_0$$

Q ₂ (t+1)		Q ₁ (t+1)	
EQ ₂		EQ ₂	
Q ₁ Q ₀	00 01 11 10	Q ₁ Q ₀	00 01 11 10
00	0 1 1 0	00	0 0 1 0
01	0 1 1 0	01	0 0 1 1
11	0 1 0 1	11	1 1 1 0
10	0 1 0 1	10	1 1 0 0

Q ₀ (t+1)		z	
EQ ₂		EQ ₂	
Q ₁ Q ₀	00 01 11 10	Q ₁ Q ₀	00 01 11 10
00	0 0 0 1	00	0 0 0 0
01	1 1 1 1	01	0 0 0 0
11	1 1 0 1	11	0 0 0 0
10	0 0 0 0	10	0 1 1 0



Circuit Implementation:

 

 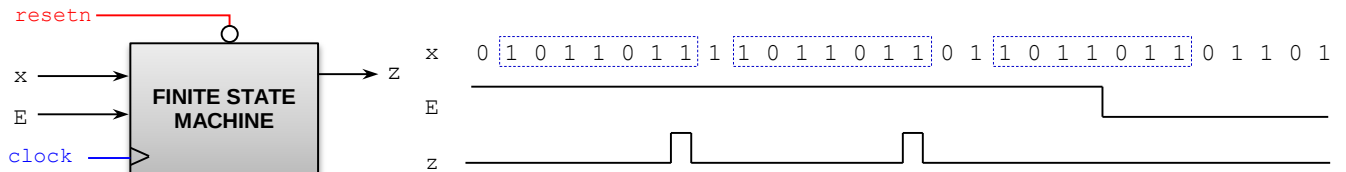PROBLEM 3 (34 PTS)

- Sequence detector: Provide the State Diagram (any representation) and the Excitation Table of a circuit with an input x and output z . The machine has to generate $z = 1$ when it detects the sequence 1011011. Right after the sequence is detected, the circuit looks for a new sequence. (10 pts).

The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid. The figure below illustrates the behavior for a certain input stream.



					PRESENT STATE					NEXTSTATE				
PRESENT			NEXT											
E	x	STATE	STATE	z	E	x	$Q_2Q_1Q_0(t)$			$Q_2Q_1Q_0(t+1)$			z	
0	X	S1	S1	0	0	X	0	0	0	0	0	0	0	
0	X	S2	S2	0	0	X	0	0	1	0	0	1	0	
0	X	S3	S3	0	0	X	0	1	0	0	1	0	0	
0	X	S4	S4	0	0	X	0	1	1	0	1	1	0	
0	X	S5	S5	0	0	X	1	0	0	1	0	0	0	
0	X	S6	S6	0	0	X	1	0	1	1	0	1	0	
0	X	S7	S7	0	0	X	1	1	0	1	1	0	0	
1	0	S1	S1	0	1	0	0	0	0	0	0	0	0	
1	0	S2	S3	0	1	0	0	0	1	0	1	0	0	
1	0	S3	S1	0	1	0	0	1	0	0	0	0	0	
1	0	S4	S3	0	1	0	0	1	1	0	1	0	0	
1	0	S5	S6	0	1	0	1	0	0	1	0	1	0	
1	0	S6	S1	0	1	0	1	0	1	0	0	0	0	
1	0	S7	S3	0	1	0	1	1	0	0	1	0	0	
1	1	S1	S2	0	0	1	0	0	0	0	0	1	0	
1	1	S2	S2	0	0	1	0	0	1	0	0	1	0	
1	1	S3	S4	0	0	1	0	1	0	0	1	1	0	
1	1	S4	S5	0	0	1	0	1	1	1	0	0	0	
1	1	S5	S2	0	0	1	1	0	0	0	0	1	0	
1	1	S6	S7	0	0	1	1	0	1	1	1	0	0	
1	1	S7	S1	1	0	1	1	1	0	0	0	0	1	
					X	X	1	1	1	X	X	X	X	

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following FSM.

w : input, z : output, Q_1Q_0 : state. (10 pts).

$$Q_1(t+1) = (Q_1 + Q_0)w$$


$$Q_0(t+1) = \overline{Q_1}Q_0w$$

$$z = Q_1\overline{Q_0}$$

State Assignment:

S1: $Q = 00$ S2: $Q = 01$


S3: $Q = 10$ S4: $Q = 11$

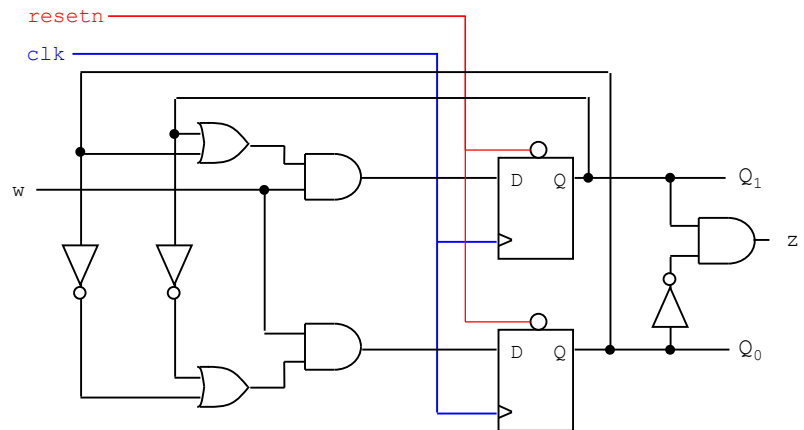

PRESENT STATE			NEXTSTATE	
w	$Q_1Q_0(t)$		$Q_1Q_0(t+1)$	z
0	0 0		0 0	0
0	0 1		0 0	0
0	1 0		0 0	1
0	1 1		0 0	0
1	0 0		0 1	0
1	0 1		1 1	0
1	1 0		1 1	1
1	1 1		1 0	0




w	PRESENT STATE	NEXT STATE	z
0	S1	S1	0
0	S2	S1	0
0	S3	S1	1
0	S4	S1	0
1	S1	S2	0
1	S2	S4	0
1	S3	S4	1
1	S4	S3	0

 

- Provide the state diagram (in ASM form) and complete the timing diagram of the FSM whose VHDL description is listed below. (14 pts)


```
library ieee;
use ieee.std_logic_1164.all;

 entity circ is
port ( clk, resetn: in std_logic;
      a, b: in std_logic;
      x,w,z: out std_logic);
end circ;
```




```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        if b = '1' then y <= S3; else y <= S1; end if;
                    else
                        y <= S2;
                    end if;
                when S2 =>
                    if a = '1' then y <= S3; else y <= S2; end if;
                when S3 =>
                    if b = '1' then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

     Outputs: process (y, a, b)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '1' then x <= '1'; end if;
            when S2 => if b = '1' then w <= '1'; end if;
            when S3 => z <= '1';
        end case;
    end process;
end behavioral;
```



 PROBLEM 4 (20 PTS)

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
Register (for P): *sclr*: synchronous clear. Here, if *sclr* = *E* = 1, the register contents are initialized to 0.
Parallel access shift registers (for A and B): If *E* = 1: *s_l* = 1 → Load, *s_l* = 0 → Shift



PROBLEM 5 (14 PTS)

- Attach a printout of your Project Status Report (no more than two pages, single-spaced, 2 columns). This report should contain the current status of the project. You **MUST** use the provided template (Final Project - Report Template.docx).