

(October 19th @ 5:30 pm)

PROBLEM 1 (20 PTS)

Decimal	BCD	Binary	Reflective Gray Code
37	00110111	100101	110111
50	01010000	110010	101011
128	000100101000	10000000	11000000


REPRESENTATION			
Decimal	Sign-and-magnitude	1's complement	2's complement
-17	110001	101110	101111
-64	11000000	10111111	1000000
-32	1100000	1011111	100000
-24	111000	100111	101000
41	0101001	0101001	0101001
-36	1100100	1011011	1011100

PROBLEM 2 (15 PTS)

- [illegible]

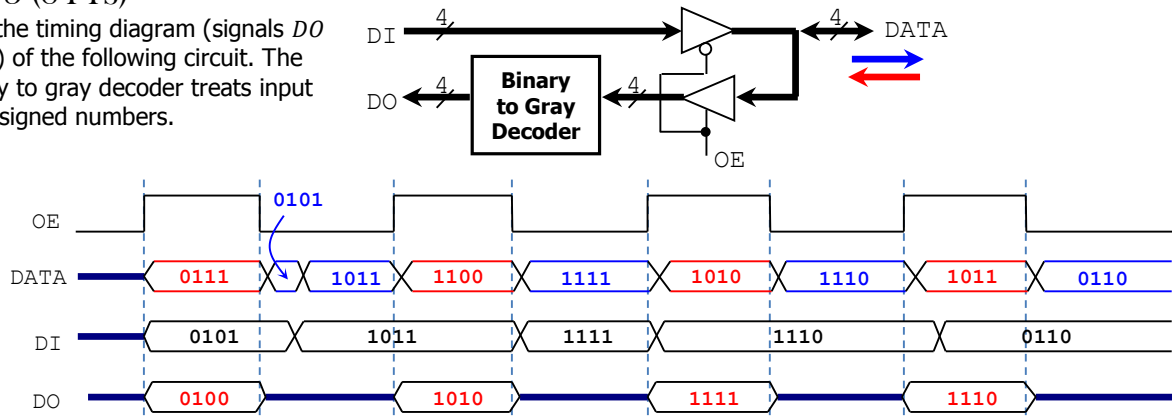PROBLEM 3 (8 PTS)

- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The 4-bit binary to gray decoder treats input data as unsigned numbers.



PROBLEM 4 (12 PTS)

- A microprocessor has a memory space of 1 MB. Each memory address occupies one byte. $1\text{KB} = 2^{10}$ bytes, $1\text{MB} = 2^{20}$ bytes, $1\text{GB} = 2^{30}$ bytes. We want to connect four 256 KB memory chips to this microprocessor.
 - What is the address bus size (number of bits of the address) of the microprocessor? (1 pt).

Size of memory space: $1\text{MB} = 2^{20}$ bytes. Thus, we require 20 bits to address the memory space.


- For a memory chip of 256 KB, how many bits do we require to address 256 KB of memory? (1 pt).

256 KB memory device: $256\text{KB} = 2^{18}$ bytes. Thus, we require 18 bits to address the memory device.

- Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips in the figure. (4 pts).

Address		8 bits
0000 0000 0000 0000 0000	0x00000	1
0000 0000 0000 0000 0001	0x00001	256KB
...	...	
0011 1111 1111 1111 1111	0x3FFFF	
0100 0000 0000 0000 0000	0x40000	2
0100 0000 0000 0000 0001	0x40001	256KB
...	...	
0111 1111 1111 1111 1111	0x7FFFF	
1000 0000 0000 0000 0000	0x80000	3
1000 0000 0000 0000 0001	0x80001	256KB
...	...	
1011 1111 1111 1111 1111	0xBFFFF	
1100 0000 0000 0000 0000	0xC0000	4
1100 0000 0000 0000 0001	0xC0001	256KB
...	...	
1111 1111 1111 1111 1111	0xFFFFF	

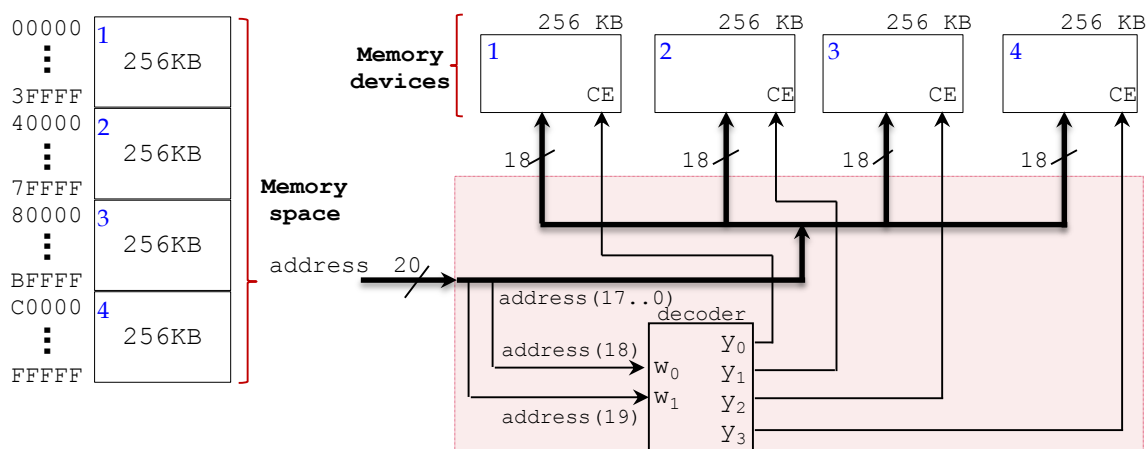- Sketch the circuit that: i) addresses the memory chips, and ii) enables only one memory chip (via CE: chip enable) when the address falls in the corresponding range. Example: if address=0x5FFFF, → only memory chip 2 is enabled (CE=1). If address=0xD0123, → only memory chip 4 is enabled.



PROBLEM 5 (17 PTS)

- a) Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every carry (or borrow) from c_0 to c_n (or b_0 to b_n). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher byte. (6 pts)

✓ $17 + 50$

$$\begin{array}{r} \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \\ 50 = 0 \times 32 = 1 \ 1 \ 0 \ 0 \ 1 \ 0 + \\ 17 = 0 \times 11 = 0 \ 1 \ 0 \ 0 \ 0 \ 1 \\ \hline \text{Overflow!} \rightarrow 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 1 \end{array}$$

✓ $37 - 41$

$$\begin{array}{r} \text{Borrow out!} \rightarrow \overset{1}{\text{Borrow}} \quad \overset{1}{\text{Borrow}} \quad \overset{1}{\text{Borrow}} \quad \overset{1}{\text{Borrow}} \quad \overset{1}{\text{Borrow}} \quad \overset{1}{\text{Borrow}} \\ 37 = 0 \times 25 = 1 \ 0 \ 0 \ 1 \ 0 \ 1 - \\ 41 = 0 \times 29 = 1 \ 0 \ 1 \ 0 \ 0 \ 1 \\ \hline 1 \ 1 \ 1 \ 1 \ 0 \ 0 \end{array}$$

- b) Perform the following operations, where numbers are represented in 2's complement. Indicate every carry from c_0 to c_n . For each case, use the fewest number of bits to represent the summands and the result so that overflow is avoided. (8 pts)

✓ $-36 + 50$

$$\begin{array}{r} n = 7 \text{ bits} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \\ c_7 \oplus c_6 = 0 \\ \text{No Overflow} \\ -36 = 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 + \\ 50 = 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \\ \hline 14 = 0 \ 0 \ 0 \ 1 \ 1 \ 1 \ 0 \\ -36 + 50 = 14 \in [-2^6, 2^6-1] \rightarrow \text{no overflow} \end{array}$$

✓ $-41 - 24$

$$\begin{array}{r} n = 7 \text{ bits} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \quad \overset{1}{\text{Carry}} \\ c_7 \oplus c_6 = 1 \\ \text{Overflow!} \\ -41 = 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 1 + \\ -24 = 1 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \\ \hline 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 1 \\ -41 - 24 = -65 \notin [-2^6, 2^6-1] \rightarrow \text{overflow!} \end{array}$$

To avoid overflow: $n = 8$ bits (sign-extension)

$$\begin{array}{r} c_8 \oplus c_7 = 0 \\ \text{No Overflow} \\ -41 = 1 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 1 + \\ -24 = 1 \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \\ \hline 1 \ 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 1 \\ -41 - 24 = -65 \in [-2^7, 2^7-1] \rightarrow \text{no overflow} \end{array}$$

- c) Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (3 pts)


✓ -7×9

$$\begin{array}{r} 1 \ 0 \ 0 \ 1 \times \\ 0 \ 1 \ 0 \ 0 \ 1 \\ \hline 1 \ 0 \ 0 \ 1 \\ 1 \ 0 \ 0 \ 1 \\ 1 \ 0 \ 0 \ 1 \\ 0 \ 0 \ 0 \ 0 \\ \hline 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 1 \\ \hline 1 \ 0 \ 0 \ 0 \ 0 \ 0 \ 1 \end{array}$$

PROBLEM 6 (10 PTS)

- Given two 4-bit unsigned numbers A , B , sketch the circuit that computes $|A - 2B|$. For example: $A = 1010, B = 1110 \rightarrow |A - 2B| = |10 - 2 \times 14| = 18$. You can only use full adders and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.

 $A = a_3a_2a_1a_0, B = b_3b_2b_1b_0$: unsigned numbers $A = 0a_3a_2a_1a_0, B = 0b_3b_2b_1b_0$: signed numbers (2C) $A, B \in [0, 15] \rightarrow 2B \in [0, 30]$ requires 6 bits in 2C.✓ $X = A - 2B \in [-30, 15]$ requires 6 bits in 2C. Thus, the operation $A - 2B$ requires 6 bits (we sign-extend A).✓ $|X| = |A - 2B| \in [0, 30]$ requires 6 bits in 2C. Thus, the second operation $0 \pm X$ only requires 6 bits.□ If $x_5 = 1 \rightarrow X < 0 \rightarrow$ we do $0 - X$.□ If $x_5 = 0 \rightarrow X \geq 0 \rightarrow$ we do $0 + X$.

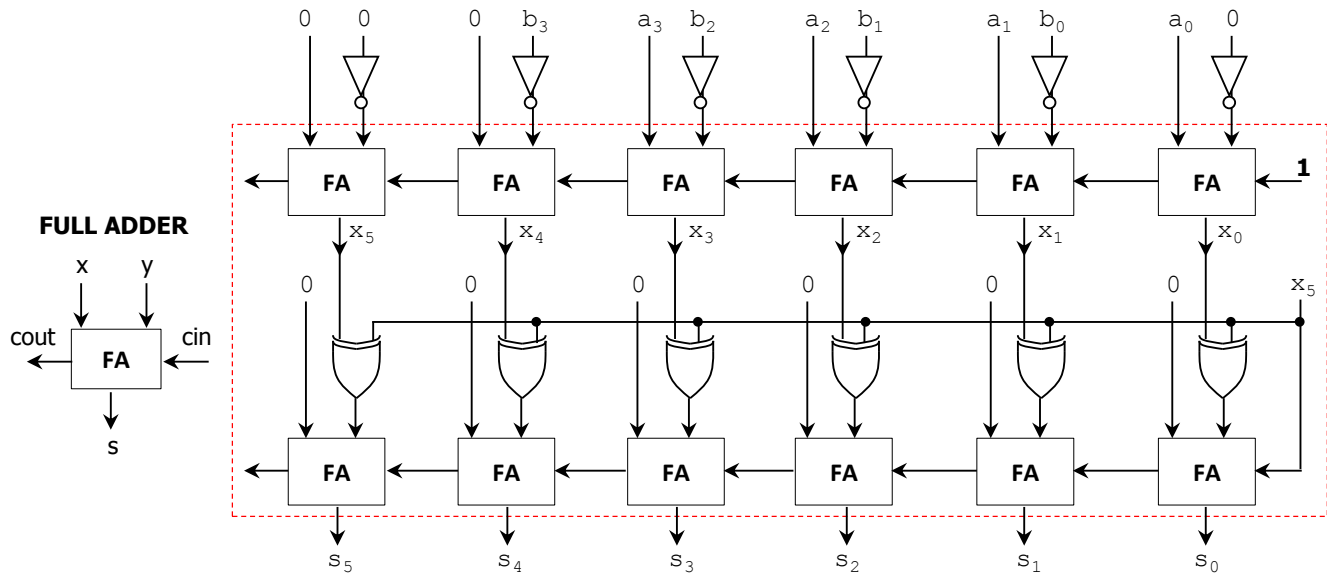

PROBLEM 7 (18 PTS)

- Sketch the circuit that implements the following Boolean function: $f(a, b, c, d) = (a \oplus \bar{b})(c \oplus d)$
 ✓ Using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)


$$f(a, b, c, d) = \bar{a}f(0, b, c, d) + af(1, b, c, d) = \bar{a}(\bar{b}(c \oplus d)) + a(b(c \oplus d)) = \bar{a}g(b, c, d) + ah(b, c, d)$$

$$g(b, c, d) = \bar{b}g(0, c, d) + bg(1, c, d) = \bar{b}(c \oplus d) + b(0)$$


$$h(b, c, d) = \bar{b}h(0, c, d) + bh(1, c, d) = \bar{b}(0) + b(c \oplus d)$$

$$t(c, d) = c \oplus d = \bar{c}t(0, d) + ct(1, d) = \bar{c}(d) + c(\bar{d})$$
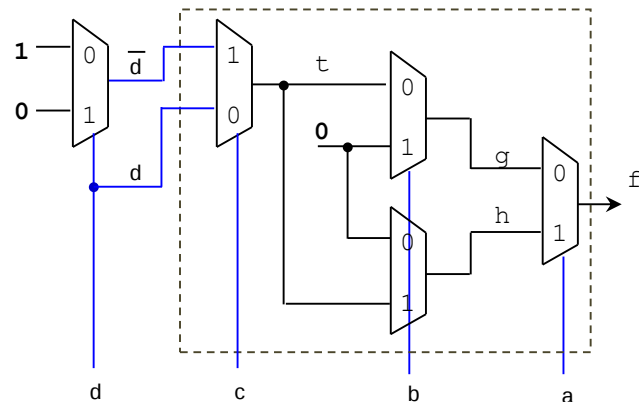
$$\text{Also: } \bar{d} = \bar{d}(1) + d(0)$$



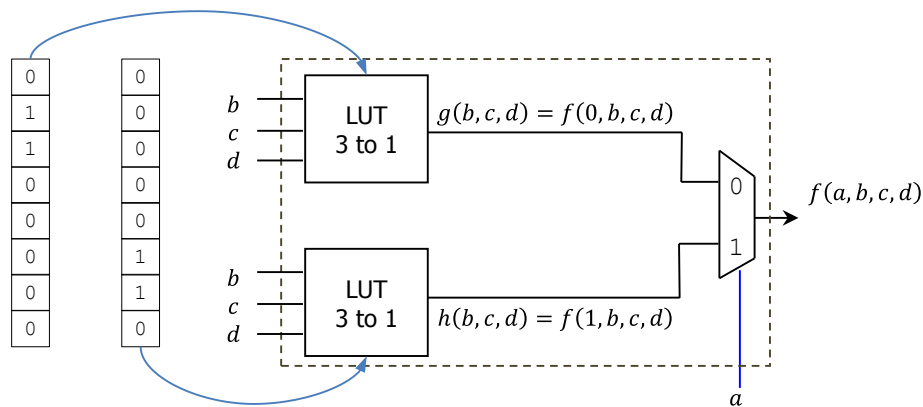- ✓ Using two 3-to-1 LUTs and a 2-to-1 MUX. Specify the contents of each of the 3-to-1 LUTs. (6 pts)



a	b	c	d	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0