

Homework 1

(Due date: September 20th @ 5:30 pm)
Presentation and clarity are very important!

PROBLEM 1 (27 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (14 pts)

✓ $F = \overline{(A \oplus B)}C + ABC$
 ✓ $F = \overline{XY} + Y(\overline{Z} + \overline{X})$

✓ $F(A, B, C) = \prod(M_0, M_3, M_5, M_7)$
 ✓ $F = (A + \overline{C} + \overline{D})(\overline{B} + \overline{C} + D)(A + \overline{B} + \overline{C})$

b) Using ONLY Boolean Algebra Theorems, demonstrate: (5 pts)
 $X(Y \oplus Z) = (XY) \oplus (XZ)$


c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

x	y	z	f ₁	f ₂
0	0	0	1	0
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

PROBLEM 2 (26 PTS)

 a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (7 pts).



x	y	z	f
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


f =

b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)



```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

 architecture st of circ is
-- ???
begin
-- ???
end st;
```



  c) Complete the timing diagram of the following circuit: (5 pts)




d) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;


 
architecture st of circ is
  signal x, y: std_logic;
begin
  y <= x nand c;
  x <= a and b;
  f <= (not y) xor b;
end st;
```



  PROBLEM 3 (9 PTS)

Security combinations: A lock only opens ($z = 1$) when the 6 switches (a, b, c, d, e, f) are set in any of the 3 configurations shown in the figure, otherwise the lock is closed ($z = 0$).


✓ Provide the Boolean equation for the output z and sketch the logic circuit.



PROBLEM 4 (13 PTS)

 a) The following circuit has the following logic function: $f = \bar{s}a + sb$.

✓ Complete the truth table of the circuit, and sketch the logic circuit (3 pts)




b) We can use several instances of the previous circuit to implement different functions. (10 pts)

For example, the following selection of inputs produce the function: $g = x_2 + x_1\bar{x}_3$. Demonstrate that this is the case.

in1	in2	in3	in4	in5	in6	in7
x_1	0	x_3	x_2	1	x_3	x_2

Given the following inputs, provide the resulting function g (minimize the function).

in1	in2	in3	in4	in5	in6	in7
x_3	1	x_1	x_1	0	x_2	x_3

 

PROBLEM 5 (25 PTS)

- An array of seven LEDs is used to display the results of a roll of a die. Numeric data (1-6) is produced as a 3-bit value. We want to design a logic circuit that converts that 3-bit value to the corresponding 7-bit LED pattern in a die. For example, the code 101 is displayed such that it represents the number '5' in a die side.
 - In addition, we have an input R . When $R=0$, values are displayed as in a normal die. When $R=1$, values are displayed a little bit different. See figure for details.
 - Note: The LEDs are lit with a logical '1' (positive logic). The inputs are active high (or in positive logic).
- ✓ Complete the truth table for each output (a, b, c, d, e, f, g). Note that it is safe to assume that the inputs x, y, z will not produce the values 000 and 111.
- ✓ Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for a, b, c, d, e and the Quine-McCluskey algorithm for f, g .

Value	R	x	y	z	a	b	c	d	e	f	g
	0	0	0	0							
1	0	0	0	1							
2	0	0	1	0	1	0	0	0	0	0	1
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
	1	0	0	0							
1	1	0	0	1							
2	1	0	1	0							
3	1	0	1	1							
4	1	1	0	0							
5	1	1	0	1	0	0	1	1	1	1	1
6	1	1	1	0							
	1	1	1	1							