


Homework 3

(Due date: November 1st @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (12 PTS)

- Complete the timing diagram for the flip flop and the latch shown below: (7 pts)




 - Complete the timing diagram of the circuit shown below. (5 pts)




 PROBLEM 2 (40 PTS)


- Complete the timing diagram of the circuit shown below: (7 pts)



 
- Complete the timing diagram of the circuit shown below: (8 pts)



 - Complete the timing diagram of the circuit shown below: (10 pts)



 - Complete the timing diagram of the circuit shown below. $Q = Q_3Q_2Q_1Q_0$ (9 pts)



- Complete the timing diagram of the circuit whose VHDL description is shown below: (6 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( prn, a,x,clk: in std_logic;
          q: out std_logic);
end circ;


architecture t of circ is
    signal qt: std_logic;

begin
    process (prn, clk, a, x)
    begin
        if prn = '0' then
            qt <= '1';
        
```

```


        elsif (clk'event and clk = '0') then
            if x = '0' then
                qt <= qt xor not(a);
            end if;
        end if;
    end process;
    q <= qt;
end t;

```

 

 PROBLEM 3 (18 PTS)

- Given the following circuit, complete the timing diagram (signals *DO* and *DATA*).
 The LUT 6-to-6 implements the following function: $OLUT = [ILUT^{0.79}]$, where *ILUT* is a 6-bit unsigned number.
 For example $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.79}] = 17 (010001_2)$



PROBLEM 4 (30 PTS)

- The following circuit is a 4-bit parallel/serial load shift register with enable input.
 Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$
- Write a structural VHDL code. You MUST create a file for: i) flip flop, ii) MUX 2-to-1, and iii) top file (where you will interconnect the flip flops and MUXes). Provide a printout. (10 pts)
- Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 50 MHz with 50% duty cycle. Provide a printout. (20 pts)

