

# Laboratory 2

(Due date: **002/003**: October 8<sup>th</sup>, **004**: October 9<sup>th</sup>, **005**: October 10<sup>th</sup>)

## OBJECTIVES


- ✓ Use the Structural Description on VHDL.
- ✓ Test arithmetic circuits on an FPGA.

## VHDL CODING


- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

## FIRST ACTIVITY (100/100)

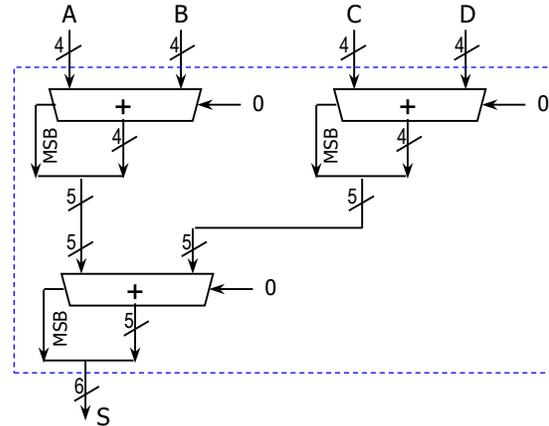- **PROBLEM:** Addition of four 4-bit unsigned numbers. The addition result requires 6 bits. This circuit can be built out of two 4-bit adders and one 5-bit adder as depicted in the figure ⇒



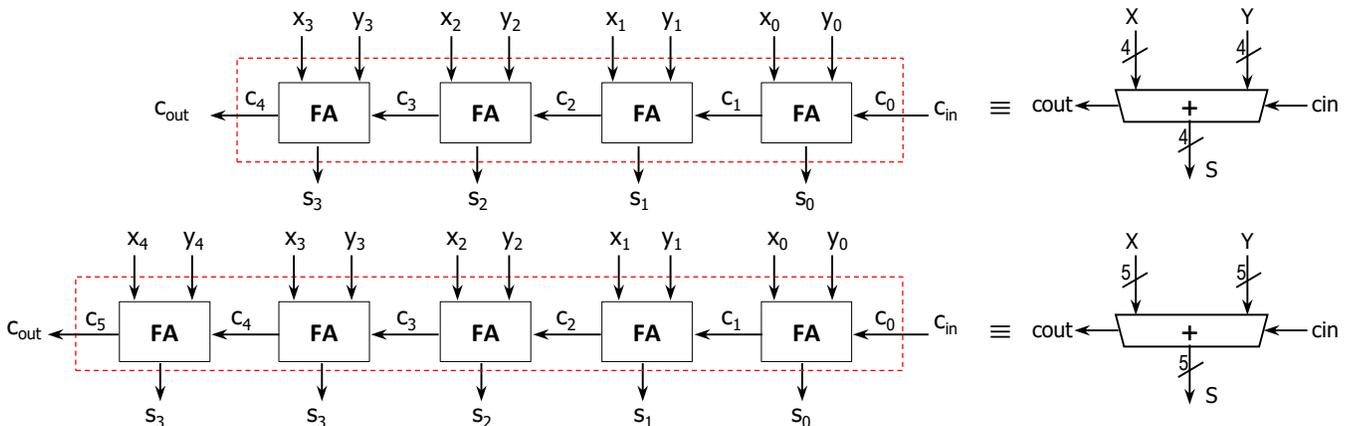- The figure below depicts the internal architecture of the 4-bit adder and the 5-bit adder. The full adder circuit is also shown.





- ✓ Create a new Vivado Project. Select the **XC7A100T-1CSG324 Artix-7 FPGA** device.
- ✓ Write the VHDL code for the Adder of four 4-bit unsigned numbers. Use the **Structural Description**: Create a separate file for the Full Adder, the 4-bit adder, the 5-bit adder, and the top file (Adder of 4 4-bit numbers).
- ✓ Write the VHDL testbench to test the circuit to test the following cases:

- ♦ **A=0x8, B=0xE, C=0xF, D=0x9** → S=101110
- ♦ **A=0xF, B=0xE, C=0x7, D=0x3** → S=100111
- ♦ **A=0xA, B=0x6, C=0x4, D=0x8** → S=011100

- ✓ Perform **Functional Simulation** and **Timing Simulation** of your design. **Demonstrate this to your TA.**
- ✓ I/O Assignment: Create the XDC file. Nexys-4 DDR: Use SW15-SW0 for the inputs, and LED5-LED0 for the outputs.
- ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**

### FULL ADDER

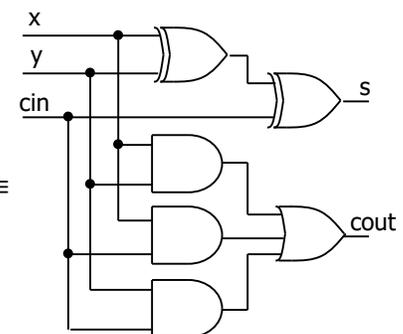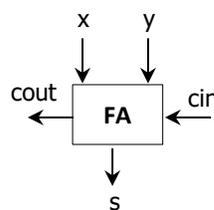

- Submit (as a .zip file) the five generated files: VHDL code (4 files), VHDL testbench, and XDC file to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

TA signature: \_\_\_\_\_

Date: \_\_\_\_\_