

- b) Using ONLY Boolean Algebra Theorems, demonstrate: (5 pts)
 $X(Y \oplus Z) = (XY) \oplus (XZ)$

$$(XY) \oplus (XZ) = \overline{XY}(XZ) + XY(\overline{XZ}) = (\bar{X} + \bar{Y})XZ + XY(\bar{X} + \bar{Z}) = \bar{Y}XZ + XY\bar{Z} = X(\bar{Y}Z + Y\bar{Z}) = X(Y \oplus Z)$$

- c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

x	y	z	f ₁	f ₂
0	0	0	1	0
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Sum of Products

$$f_1 = \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

$$f_2 = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

Product of Sums



$$f_1 = (x + y + \bar{z})(x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z})(\bar{x} + \bar{y} + z)$$

$$f_2 = (x + y + z)(x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z})(\bar{x} + \bar{y} + z)$$

Minterms and maxterms:


$$f_1 = \sum(m_0, m_2, m_4, m_7) = \prod(M_1, M_3, M_5, M_6).$$
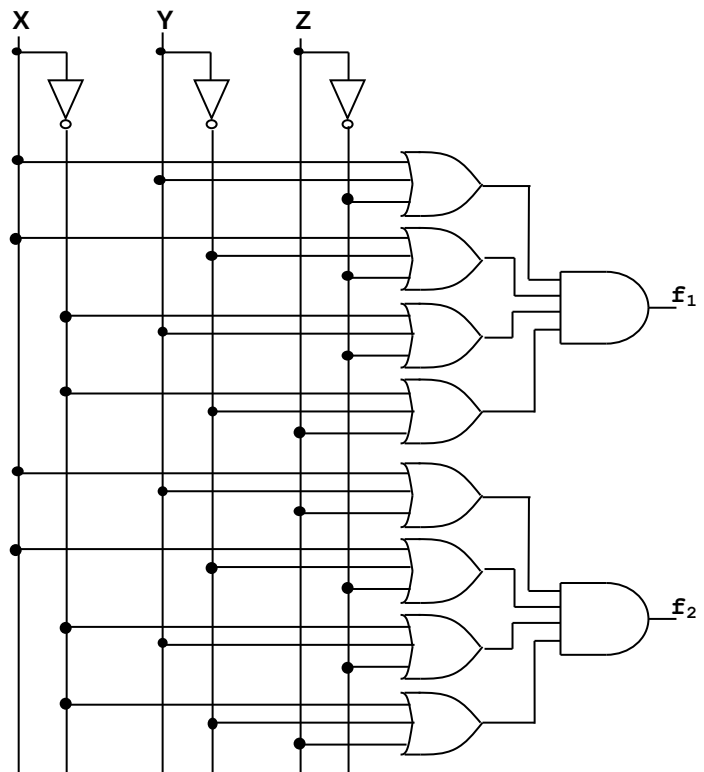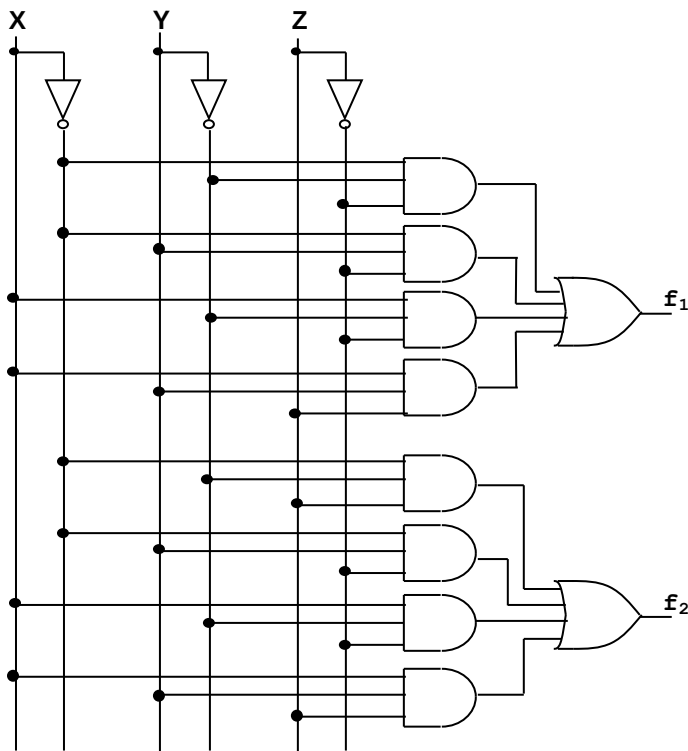
$$f_2 = \sum(m_1, m_2, m_4, m_7) = \prod(M_0, M_3, M_5, M_6).$$



PROBLEM 2 (26 PTS)

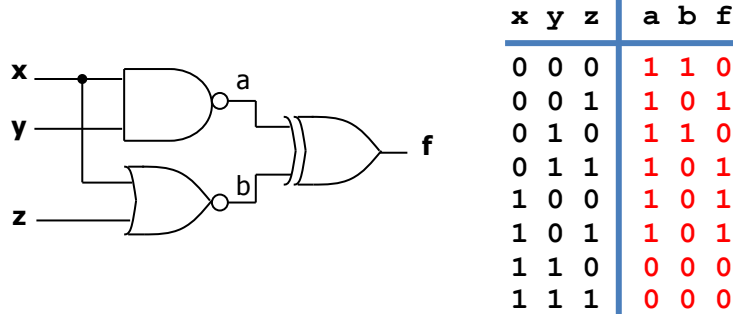- a) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (7 pts).




$$f = \bar{a}\bar{b} = a \oplus b = (xy) \oplus (x+z) = (\bar{x}\bar{y})(x+z) + xy(\bar{x}+\bar{z}) = (\bar{x}+\bar{y})(x+z) + xy(\bar{x}\bar{z}) = (x+z)(\bar{x}+\bar{y}) = \bar{x}z + x\bar{y}$$

- b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;


entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

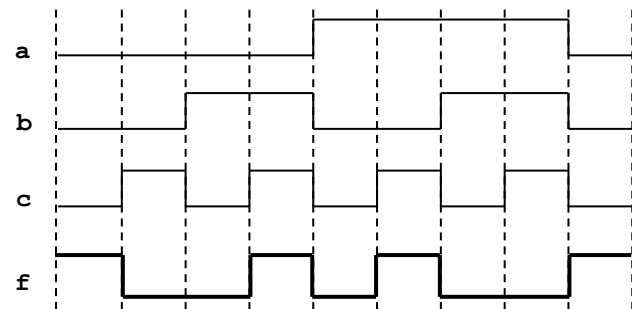architecture st of circ is
  signal x, y: std_logic;
begin
  x <= a and not(b) and c;
  y <= a nor (b xor c);
  f <= x or y;
end st;
```




a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

	ab			
c	00	01	11	10
0	1	0	1	0
1	0	1	0	0

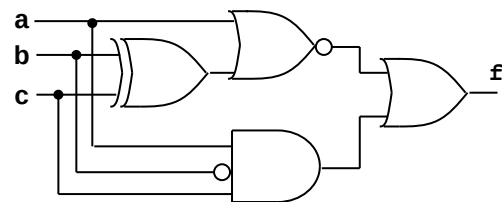


$$f = \bar{a}\bar{b}\bar{c} + \bar{a}bc + a\bar{b}c = \bar{a}(\bar{b}\bar{c} + b\bar{c}) + a\bar{b}c = \bar{a} + (b\bar{c}) + a\bar{b}c$$

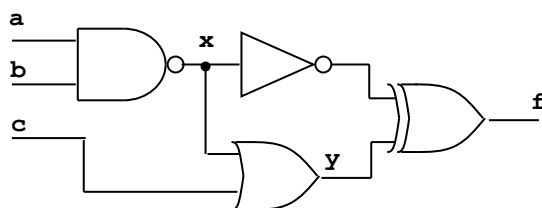- c) Complete the timing diagram of the following circuit: (5 pts)


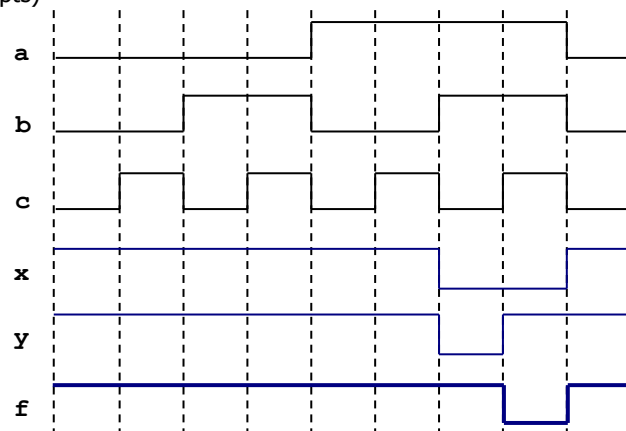
$$f = \bar{x} \oplus y = \overline{x \oplus y}$$




d) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (6 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

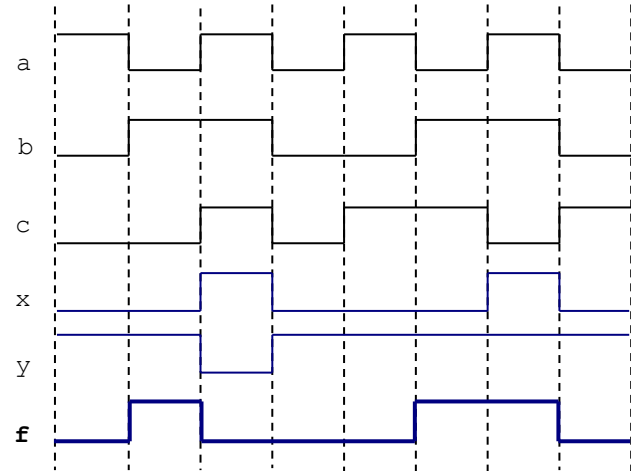architecture st of circ is
  signal x, y: std_logic;
begin
  y <= x nand c;
  x <= a and b;
  f <= (not y) xor b;
end st;
```




PROBLEM 3 (9 PTS)

- Security combinations: A lock only opens ($z = 1$) when the 6 switches (a, b, c, d, e, f) are set in any of the 3 configurations shown in the figure, otherwise the lock is closed ($z = 0$).

- ✓ Provide the Boolean equation for the output z and sketch the logic circuit.


ON (1)

OFF (0)

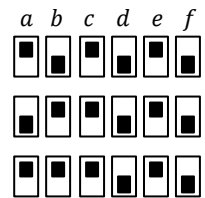

a	b	c	d	e	f	z
1	0	1	0	1	0	1
0	1	1	0	1	0	1
1	1	1	0	1	0	1
All remaining cases						0

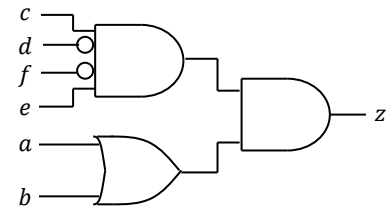
$$z = \bar{a}\bar{b}c\bar{d}e\bar{f} + \bar{a}bc\bar{d}e\bar{f} + abc\bar{d}e\bar{f} = c\bar{d}e\bar{f}(\bar{a}\bar{b} + \bar{a}b + ab) = c\bar{d}e\bar{f}(a + b)$$



PROBLEM 4 (13 PTS)

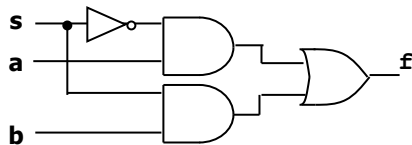a) The following circuit has the following logic function: $f = \bar{s}a + sb$.

- ✓ Complete the truth table of the circuit, and sketch the logic circuit (3 pts)




s	a	b	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

b) We can use several instances of the previous circuit to implement different functions. (10 pts)

- For example, the following selection of inputs produce the function: $g = x_2 + x_1\bar{x}_3$. Demonstrate that this is the case.

in1	in2	in3	in4	in5	in6	in7
x_1	0	x_3	x_2	1	x_3	x_2

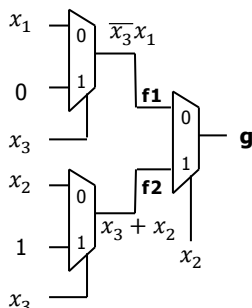


$$f_1 = \bar{x}_3(x_1) + x_3(0) = \bar{x}_3x_1$$

$$f_2 = \bar{x}_3(x_2) + x_3(1) = x_3 + x_2$$


$$g = \bar{x}_2(\bar{x}_3x_1) + x_2(x_3 + x_2) = \bar{x}_3x_1\bar{x}_2 + x_2x_3 + x_2$$
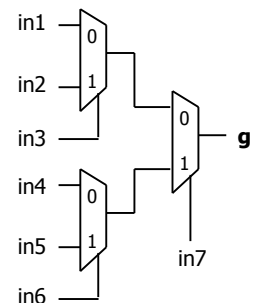
$$g = \bar{x}_3x_1\bar{x}_2 + x_2 = (x_2 + \bar{x}_2)(x_2 + \bar{x}_3x_1) = x_2 + x_1\bar{x}_3$$



- Given the following inputs, provide the resulting function g (minimize the function).

in1	in2	in3	in4	in5	in6	in7
x_3	1	x_1	x_1	0	x_2	x_3

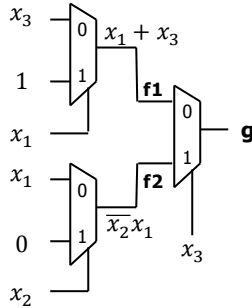

$$f_1 = \overline{x_1}(x_3) + x_1(1) = x_1 + x_3$$


$$f_2 = \overline{x_2}(x_1) + x_2(0) = \overline{x_2}x_1$$

$$g = \overline{x_3}(x_1 + x_3) + x_3(\overline{x_2}x_1) = \overline{x_3}x_1 + x_3\overline{x_2}x_1$$

$$g = x_1(\overline{x_3} + x_3\overline{x_2}) = x_1(\overline{x_3} + \overline{x_3}) = x_1\overline{x_3} + x_1\overline{x_2}$$

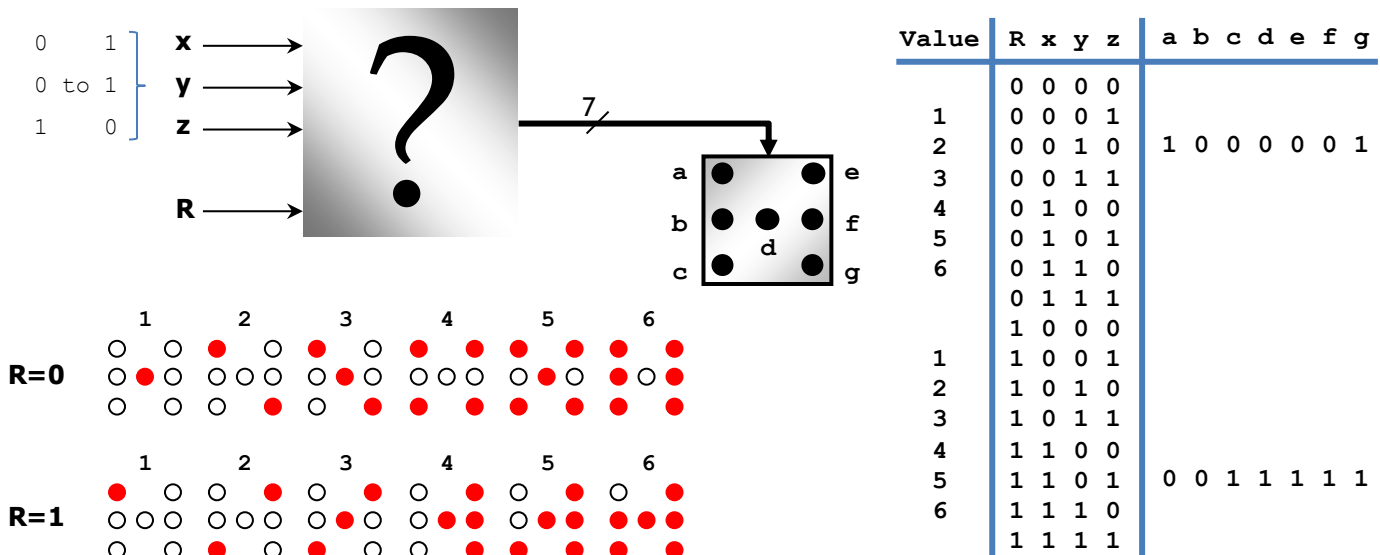PROBLEM 5 (25 PTS)

- An array of seven LEDs is used to display the results of a roll of a die. Numeric data (1-6) is produced as a 3-bit value. We want to design a logic circuit that converts that 3-bit value to the corresponding 7-bit LED pattern in a die. For example, the code 101 is displayed such that it represents the number '5' in a die side.
- In addition, we have an input R . When $R=0$, values are displayed as in a normal die. When $R=1$, values are displayed a little bit different. See figure for details.
- Note: The LEDs are lit with a logical '1' (positive logic). The inputs are active high (or in positive logic).
- Complete the truth table for each output (a, b, c, d, e, f, g). Note that it is safe to assume that the inputs x, y, z will not produce the values 000 and 111.
- Provide the simplified expression for each output (a, b, c, d, e, f, g). Use Karnaugh maps for a, b, c, d, e and the Quine-McCluskey algorithm for f, g .



- To fill out the truth table, note that xyz will not produce the values 000 and 111. Thus, we can use don't care outputs on those instances.

Value	R	x	y	z	a	b	c	d	e	f	g
	0	0	0	0	x	x	x	x	x	x	x
1	0	0	0	1	0	0	0	1	0	0	0
2	0	0	1	0	1	0	0	0	0	0	1
3	0	0	1	1	1	0	0	1	0	0	1
4	0	1	0	0	1	0	1	0	1	0	1
5	0	1	0	1	1	0	1	1	1	0	1
6	0	1	1	0	1	1	1	0	1	1	1
	0	1	1	1	x	x	x	x	x	x	x
	1	0	0	0	x	x	x	x	x	x	x
1	1	0	0	1	1	0	0	0	0	0	0
2	1	0	1	0	0	0	1	0	1	0	0
3	1	0	1	1	0	0	1	1	1	0	0
4	1	1	0	0	0	0	0	1	1	1	1
5	1	1	0	1	0	0	1	1	1	1	1
6	1	1	1	0	0	1	1	1	1	1	1
	1	1	1	1	x	x	x	x	x	x	x

$$a = R\bar{x}\bar{y} + \bar{R}x + \bar{R}y$$

$$b = xy$$

$$c = \bar{R}x + xy + Ry$$

$$d = Rx + yz + \bar{R}z$$

$$e = x + Ry$$

a	Rx	00	01	11	10
yz	00	x	1	0	x
	01	0	1	0	1
	11	1	x	x	0
	10	1	1	0	0
b	Rx	00	01	11	10
yz	00	x	0	0	x
	01	0	0	0	0
	11	0	x	x	0
	10	0	1	1	0
c	Rx	00	01	11	10
yz	00	x	1	0	x
	01	0	1	1	0
	11	0	x	x	1
	10	0	1	1	1
d	Rx	00	01	11	10
yz	00	x	0	1	x
	01	1	1	1	0
	11	1	x	x	1
	10	0	0	1	0
e	Rx	00	01	11	10
yz	00	x	1	1	x
	01	0	1	1	0
	11	0	x	x	1
	10	0	1	1	1

$$f = \sum m(6,12,13,14) + \sum d(0,7,8,15).$$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
0	$m_0 = 0000$ ✓	$m_{0,8} = -000$		We can't combine any further, so we stop here
1	$m_8 = 1000$ ✓	$m_{8,12} = 1-00$		
2	$m_6 = 0110$ ✓ $m_{12} = 1100$ ✓	$m_{6,7} = 011-$ ✓ $m_{6,14} = -110$ ✓ $m_{12,13} = 110-$ ✓ $m_{12,14} = 11-0$ ✓	$m_{6,7,14,15} = -11-$ $m_{7,15,6,14} = -11-$ $m_{12,13,14,15} = 11--$ $m_{12,14,13,15} = 11--$	
3	$m_7 = 0011$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{13,15} = 11-1$ ✓ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

$$f = \bar{x}\bar{y}\bar{z} + R\bar{y}\bar{z} + xy + Rx$$

Prime Implicants		Minterms			
		6	12	13	14
$m_{0,8}$	$\bar{x}\bar{y}\bar{z}$				
$m_{8,12}$	$R\bar{y}\bar{z}$		x		
$m_{6,7,14,15}$	xy	x			x
$m_{12,13,14,15}$	Rx		x	x	x

$$f = xy + Rx$$

- $g = \sum m(2,3,4,5,6,12,13,14) + \sum d(0,7,8,15)$.

Too many minterms. We better optimize: $\bar{g} = \sum m(1,9,10,11) + \sum d(0,7,8,15)$

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
0	$m_0 = 0000$ ✓	$m_{0,1} = 000-$ ✓ $m_{0,8} = -000$ ✓	$m_{0,1,8,9} = -00-$ $m_{0,8,1,9} = -00-$	We can't combine any further, so we stop here
1	$m_1 = 0001$ ✓ $m_8 = 1000$ ✓	$m_{1,9} = -001$ ✓ $m_{8,9} = 100-$ ✓ $m_{8,10} = 10-0$ ✓	$m_{8,9,10,11} = 10--$ $m_{8,10,9,11} = 10--$	
2	$m_9 = 1001$ ✓ $m_{10} = 1010$ ✓	$m_{9,11} = 10-1$ ✓ $m_{10,11} = 101-$ ✓		
3	$m_{11} = 1011$ ✓	$m_{11,15} = 1-11$		
4	$m_{15} = 1111$ ✓			

$$\bar{g} = Ryz + \bar{x}\bar{y} + R\bar{x}$$

Prime Implicants		Minterms			
		1	9	10	11
$m_{11,15}$	Ryz				X
$m_{0,1,8,9}$	$\bar{x}\bar{y}$	X	X		
$m_{8,9,10,11}$	$R\bar{x}$		X	X	X

$$\bar{g} = \bar{x}\bar{y} + R\bar{x} = \bar{x}(R + \bar{y}) \Rightarrow g = \overline{\bar{x}(R + \bar{y})} = x + \bar{R}y$$