

Solutions - Quiz 3

(November 6th @ 5:30 pm)


PROBLEM 1 (30 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;



entity circ is
    port ( rstn, a,b, x, clk: in std_logic;
          q: out std_logic);
end circ;
```
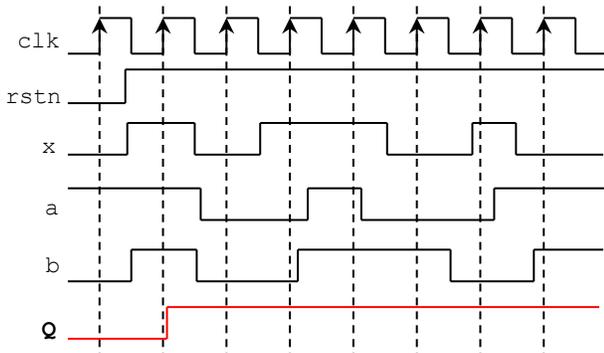
```
architecture xst of circ is
    signal qt: std_logic;
begin
    process (rstn, clk, a, b, x)
    begin
        if rstn = '0' then
            qt <= '0';
        elsif (clk'event and clk = '1') then
            if x = '1' then
                qt <= a xnor b;
            end if;
        end if;
    end process;
    q <= qt;
end xst;
```



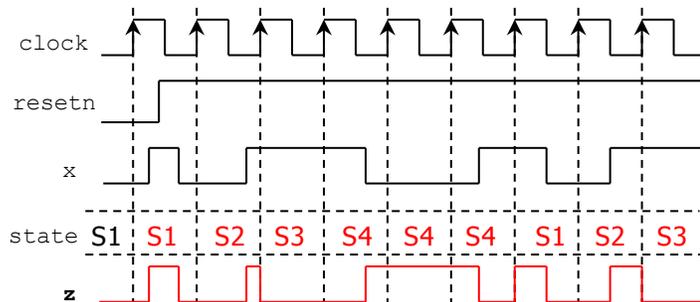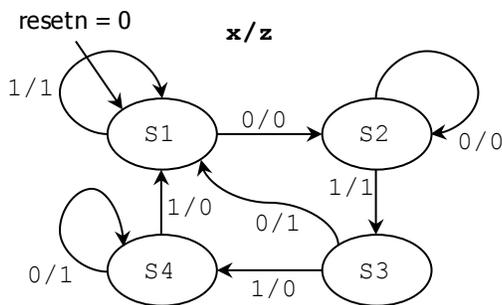PROBLEM 2 (30 PTS)

- Complete the timing diagram of the following state machine:



PROBLEM 3 (40 PTS)

- Complete the timing diagram of the following circuit:

