

# Solutions - Quiz 4

(November 27<sup>th</sup> @ 5:30 pm)

## PROBLEM 1 (35 PTS)


- Provide the Excitation equations (including the Boolean equation for  $z$ ) and the Excitation Table of the following FSM:

$$Q_1(t+1) \leftarrow (Q_1(t) + Q_0(t))w$$

$$Q_0(t+1) \leftarrow \overline{Q_1(t)}Q_0(t)w$$



$$z = Q_1(t)Q_0(t)$$

PRESENT STATE			NEXTSTATE	
w	Q <sub>1</sub> Q <sub>0</sub> (t)	Q <sub>1</sub> Q <sub>0</sub> (t+1)	z	
0	0 0	0 0	0	
0	0 1	0 0	0	
0	1 0	0 0	1	
0	1 1	0 0	0	
1	0 0	0 1	0	
1	0 1	1 1	0	
1	1 0	1 1	1	
1	1 1	1 0	0	

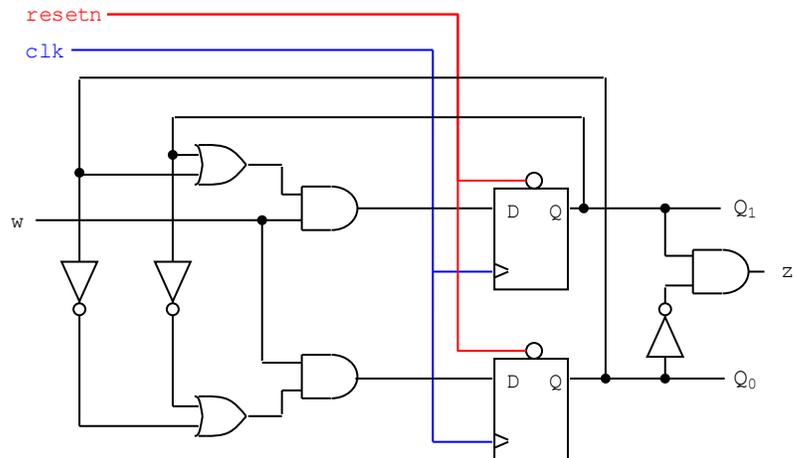
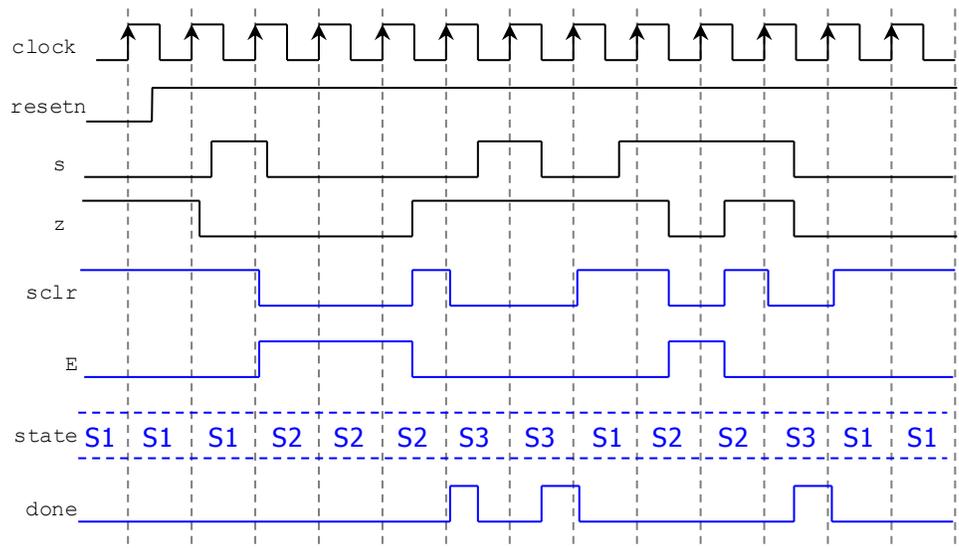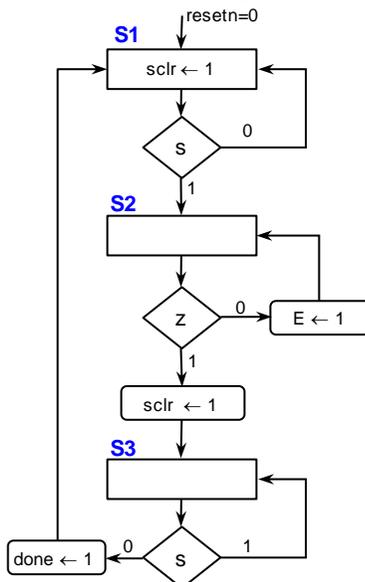
## PROBLEM 2 (35 PTS)

- Complete the timing diagram of the following FSM (represented in ASM form):



PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input  $x$  and output  $z$ . The detector asserts  $z = 1$  when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.

