

Traffic Light Controller

By: Kyle Alspach and Ryan Kelly



Introduction

- Traffic controller for 4-way intersection
- Day and night mode
 - Day mode: 13 second green/red. 2 second yellow/red. 1 second red/red.
 - Night mode: Flashing red and yellow.


Components

- Nexys A7 using Vivado 2019.3
- 5 Counters (Pulse Generators)
- 2 Finite State Machines
- 1 Multiplexer
- Breadboards
- 12 LEDs
- 12 Resistors


How it works

- The counters determine how many seconds have elapsed for active green, yellow and red lights.
- The FSM's control the switching of the lights (states) based on the counters.
- A multiplexer is used to switch between day and night mode. This function is implemented with a switch on Nexys A7.
- Reset connected to CPU RESET on Nexys A7.


Block Diagram

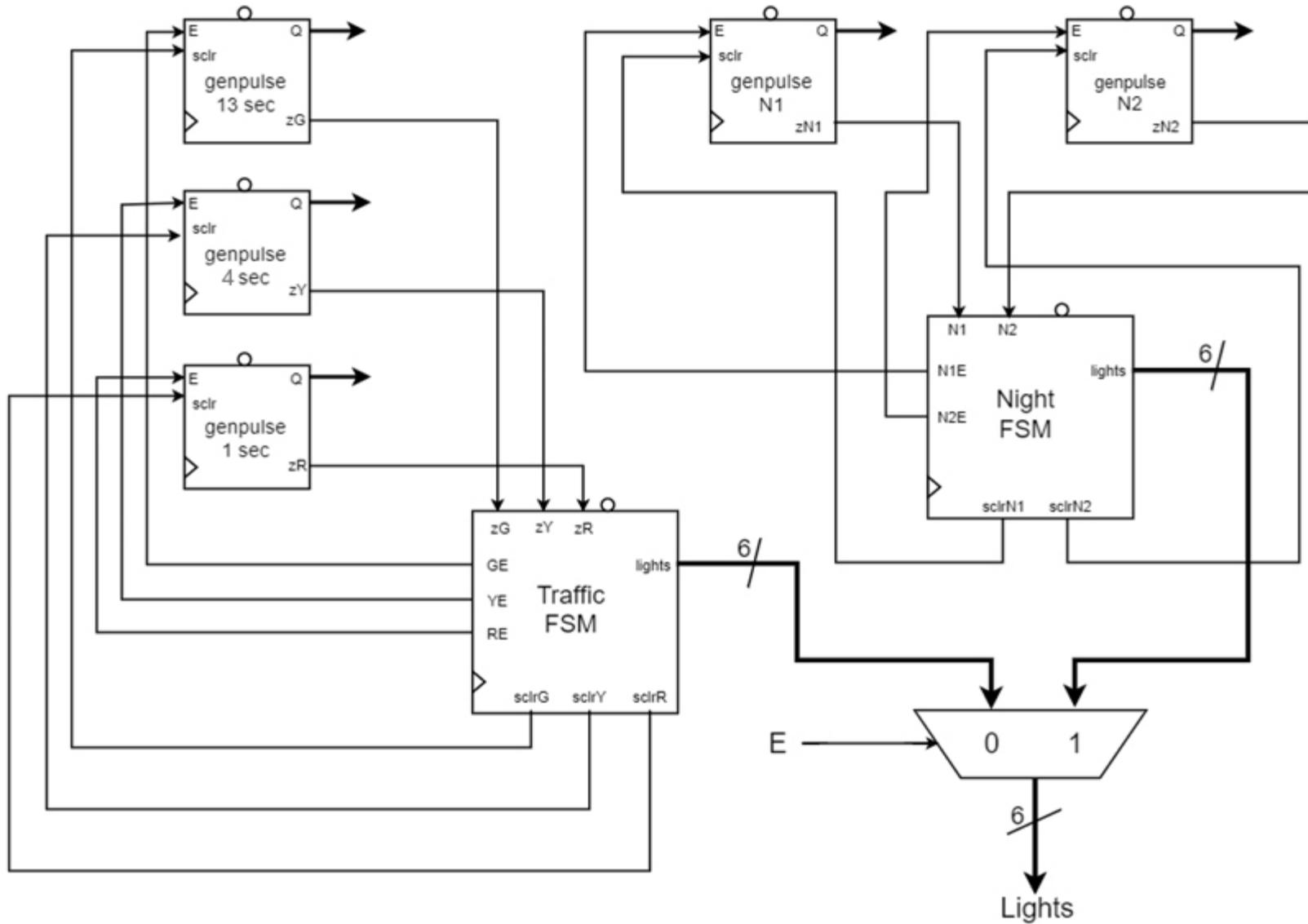

Day Mode ASM State Diagram

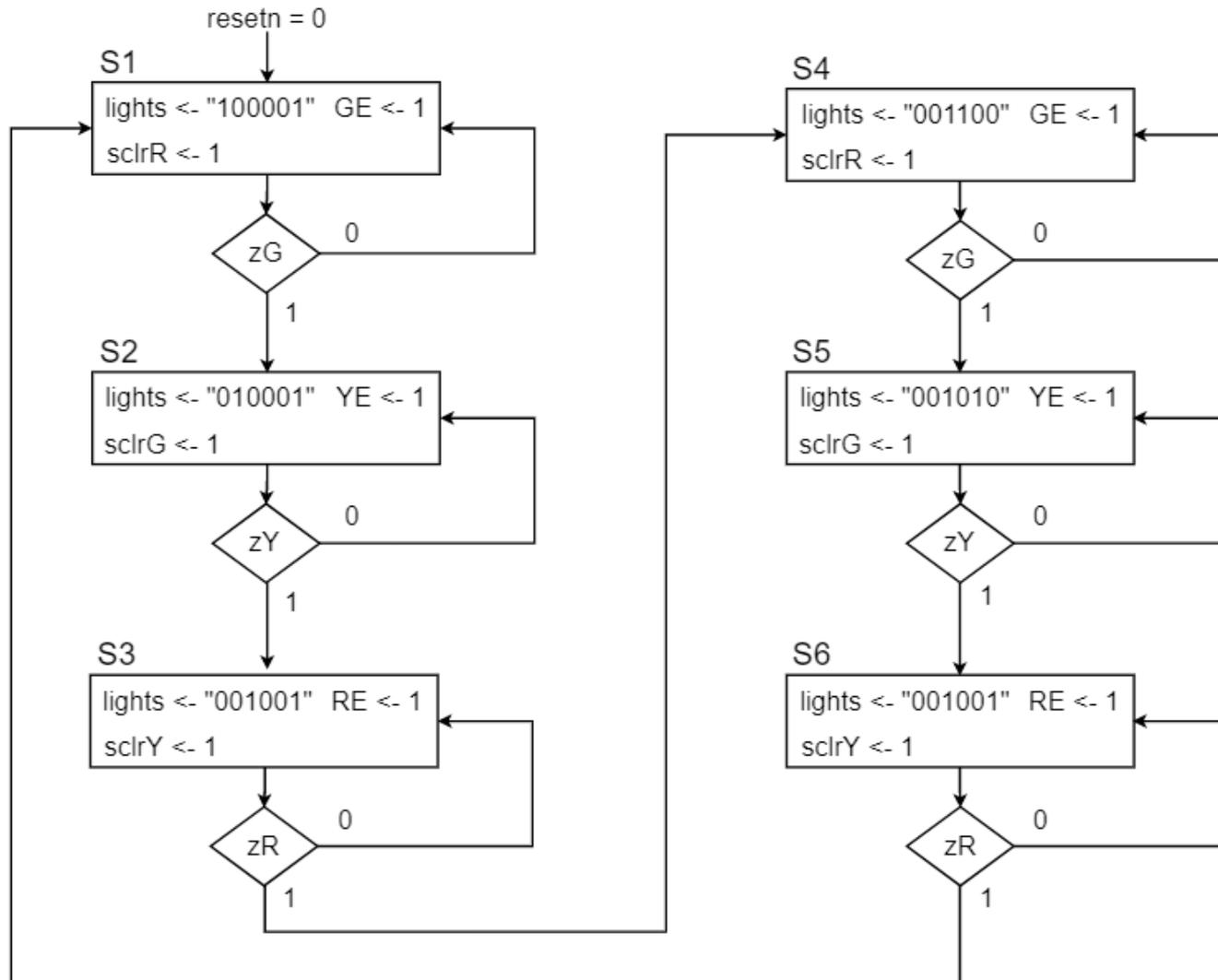

Night Mode ASM State Diagram

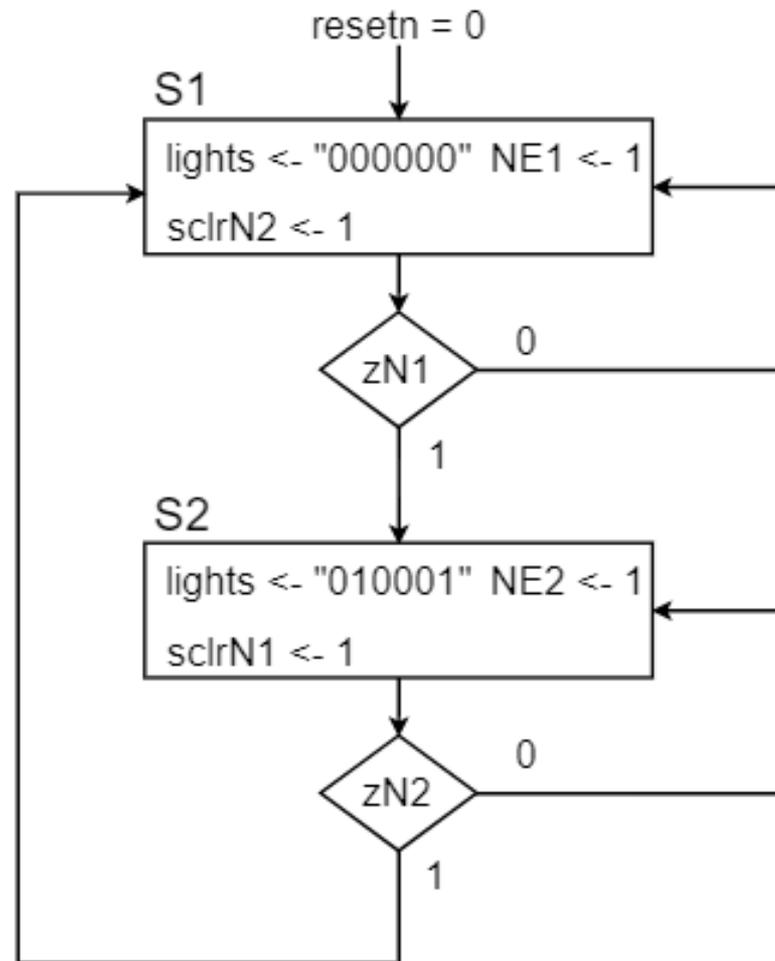

Issues and Improvements

- Issues
 - Went through a couple of designs
 - Behavioral Simulations
 - Timing
- Improvements
 - Sensors
 - More FSM's for different traffic scenarios