

Banner on a 7-segment Display

By Steven DeCoste, Kurtis Rhein, Ghaith Kachi, Brandon Holtz

Project Description


- Circuit outputs to a series of 8, 7-segment displays on a Nexys A7-50t board
- The circuit has two messages loaded onto it that the user can select from. The first message being “HELLO” and the second message being “ECE2700”
- The user has access to two switches on the board: one that controls the holding and scrolling of the message on the display, and another that allows the user to pick between the two messages.




Design & Components

Output: Eight 7-Segment Displays, 8 Anode Enable Signals.


Internal Components:

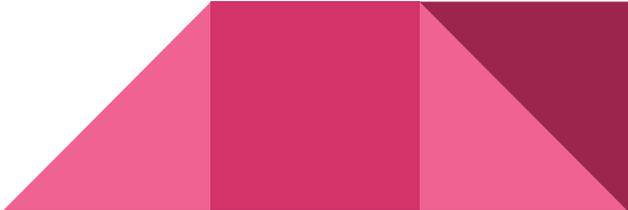- Eight Registers, Chained together to make a shift RAM module
 - One 8-to-1 7-Bit Bus MUX for controlling the display
 - One 2 to 1 8-bit MUX for selecting the message the user wants
 - One FSM to control Anode enable
 - Two counters, one for registers and another for FSM control
- 



Circuit Diagram (TOP LEVEL)

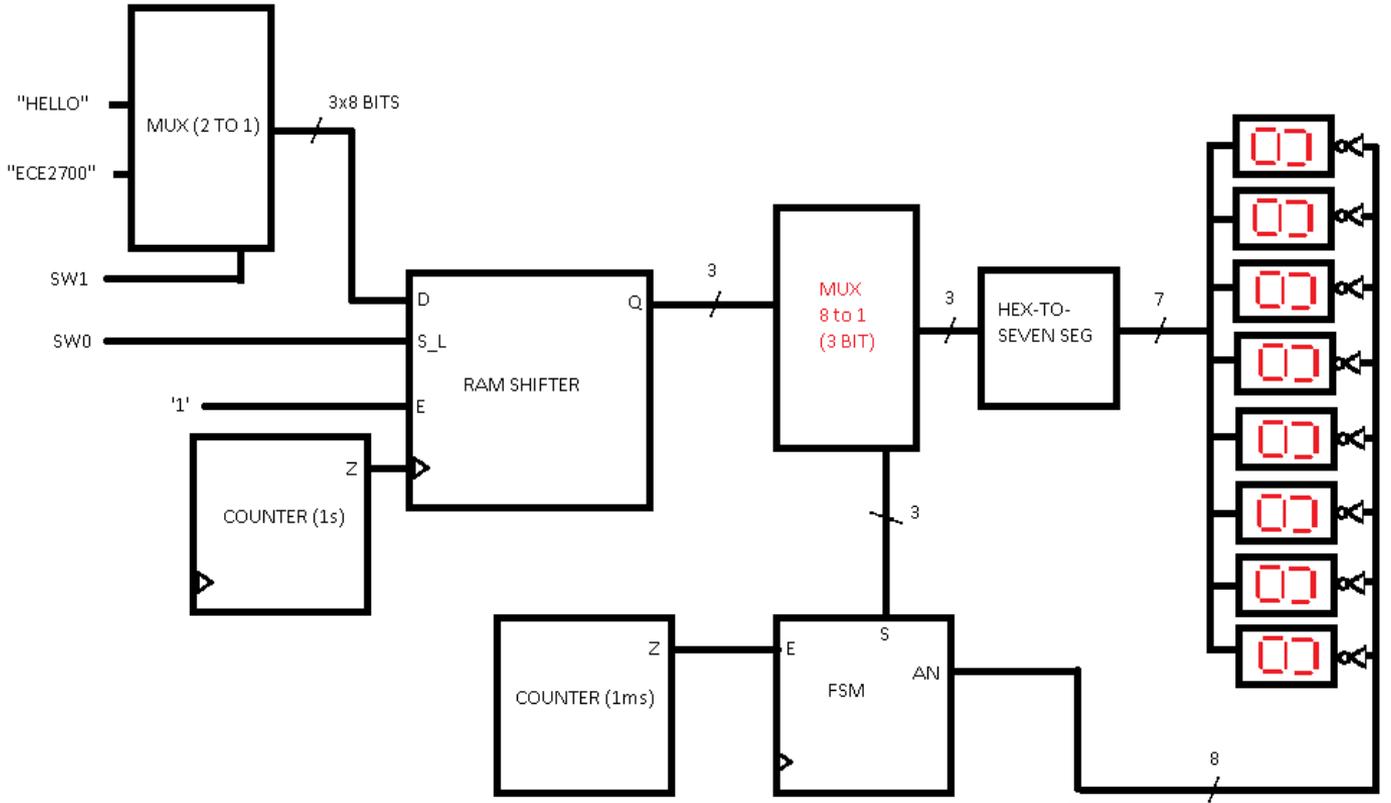

Circuit Diagram (FSM FLOWCHART)

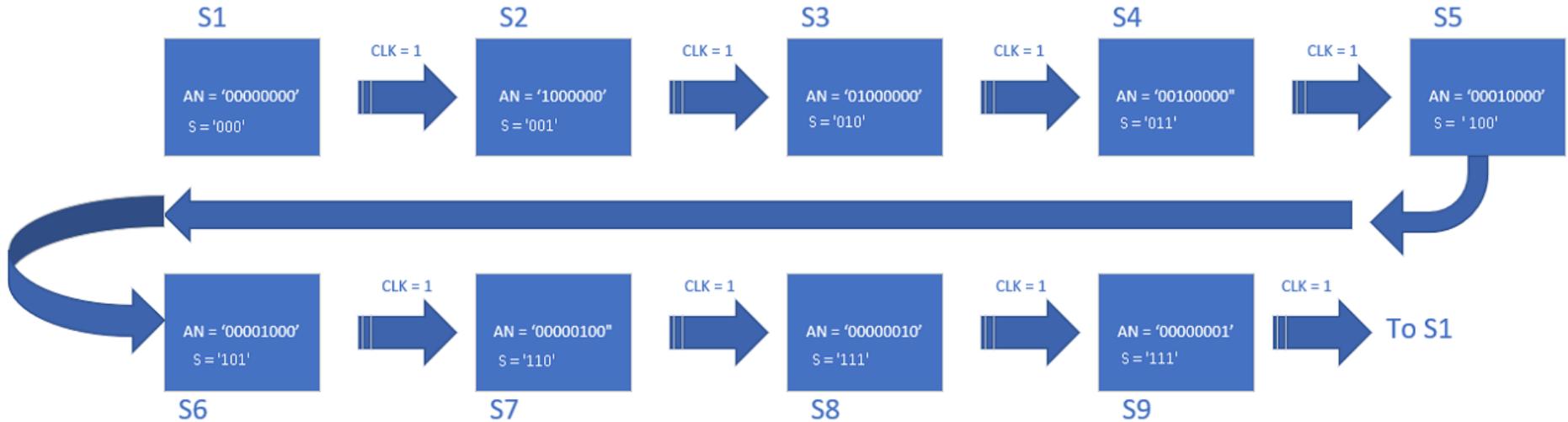


Circuit Diagram (RAMshifter)

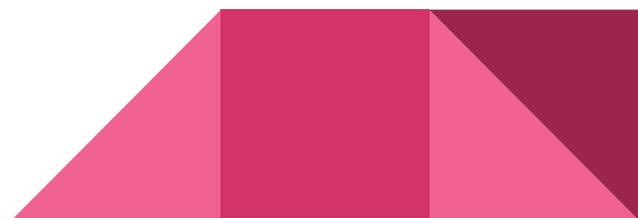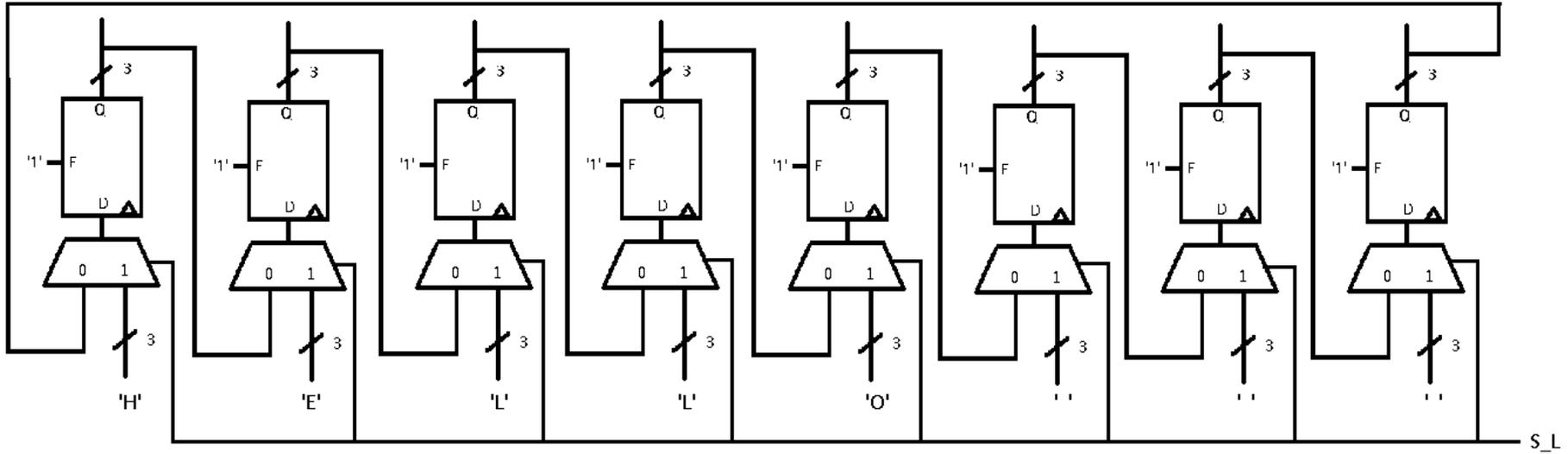

Challenges

- Designing a custom data type for an array of `STD_LOGIC_VECTORs`
- Deciding on a method for shifting the letters across the displays
 - FSM or no FSM?
- Issue implementing the counters into the top file
 - Dealing with generics
 - Math involved to get the timing to work properly (1 second and 1 millisecond)
- General Debugging
 - Waiting for a long time for the program to generate a bitstream while debugging issues.

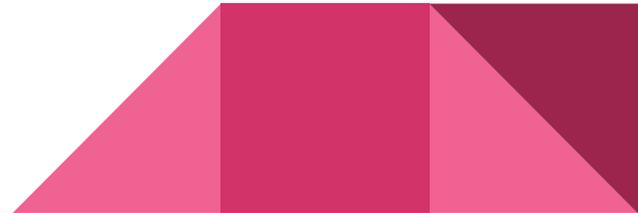



DEMONSTRATION