




BCD TO BINARY/HEX CONVERTER


BY: RAMI SULAIMAN
ANDROW ATTYA
RACHELLE GALAN
JOSH BIRIAC

OVERVIEW

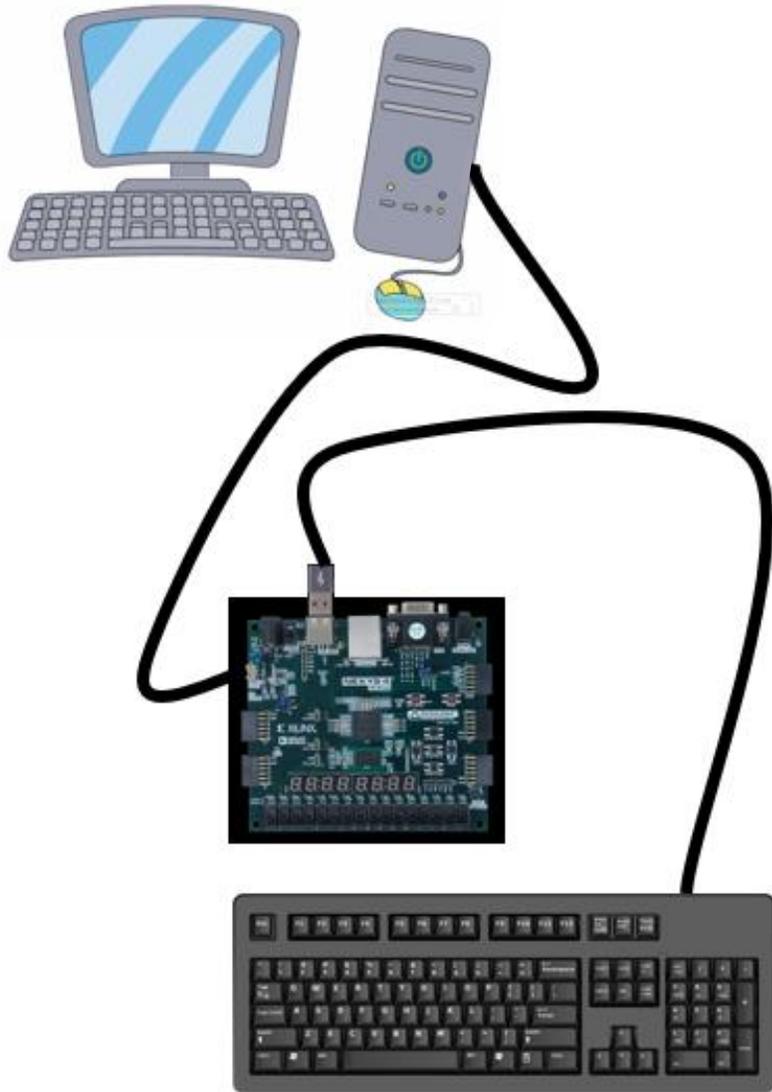- ▶ Keyboard is connected to a FPGA board via USB port, and entering a BCD number using the keyboard.
- ▶ Using VHDL code to convert the input BCD code to Binary and Hex
- ▶ A Seven Segment Display is used to display the BCD number inputted, result of Binary, and Hex
- ▶ Switch 0 is used to display Binary, Switch 1 is used to display Hex, and Switch 2 to rest.




TOP LEVEL BLOCK DIAGRAM

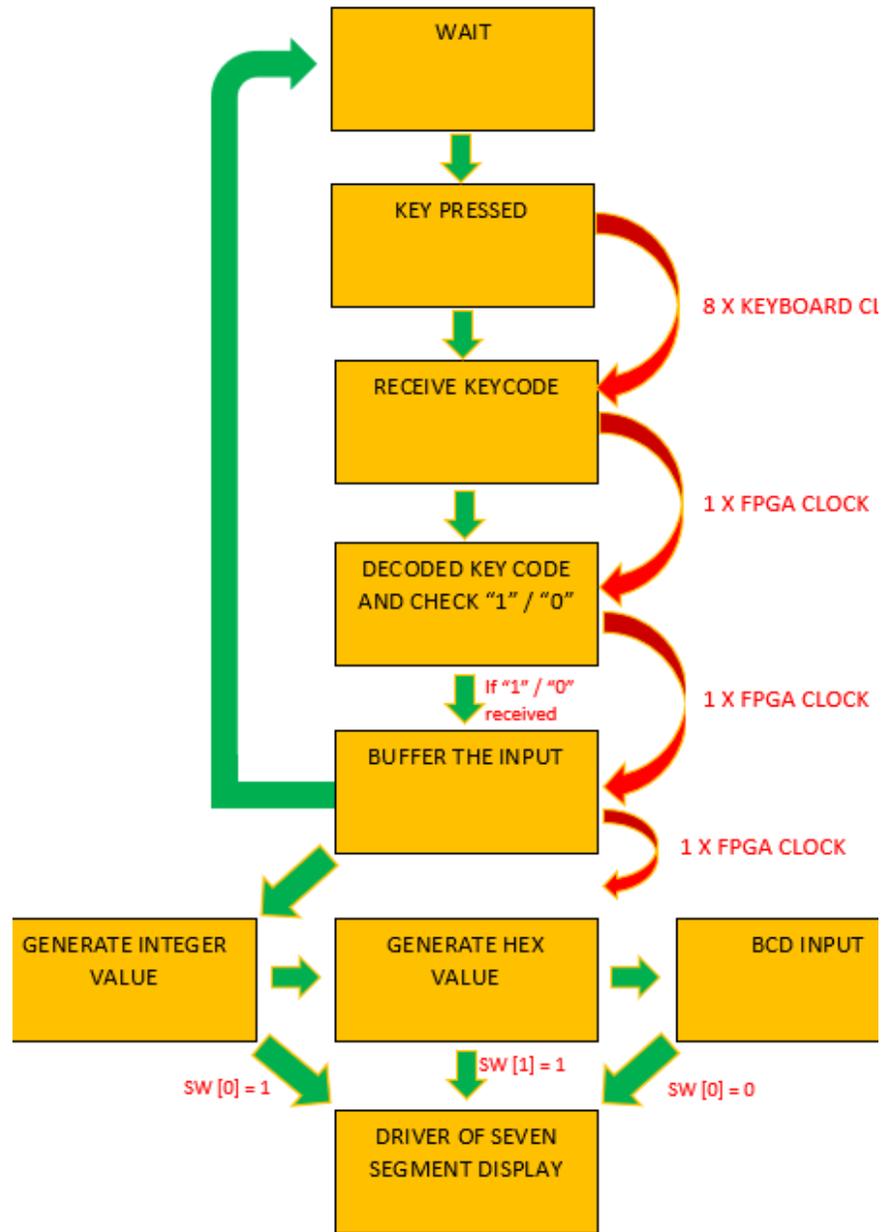


PROCESS BLOCK DIAGRAM

DATA PATH SCHEMATICS

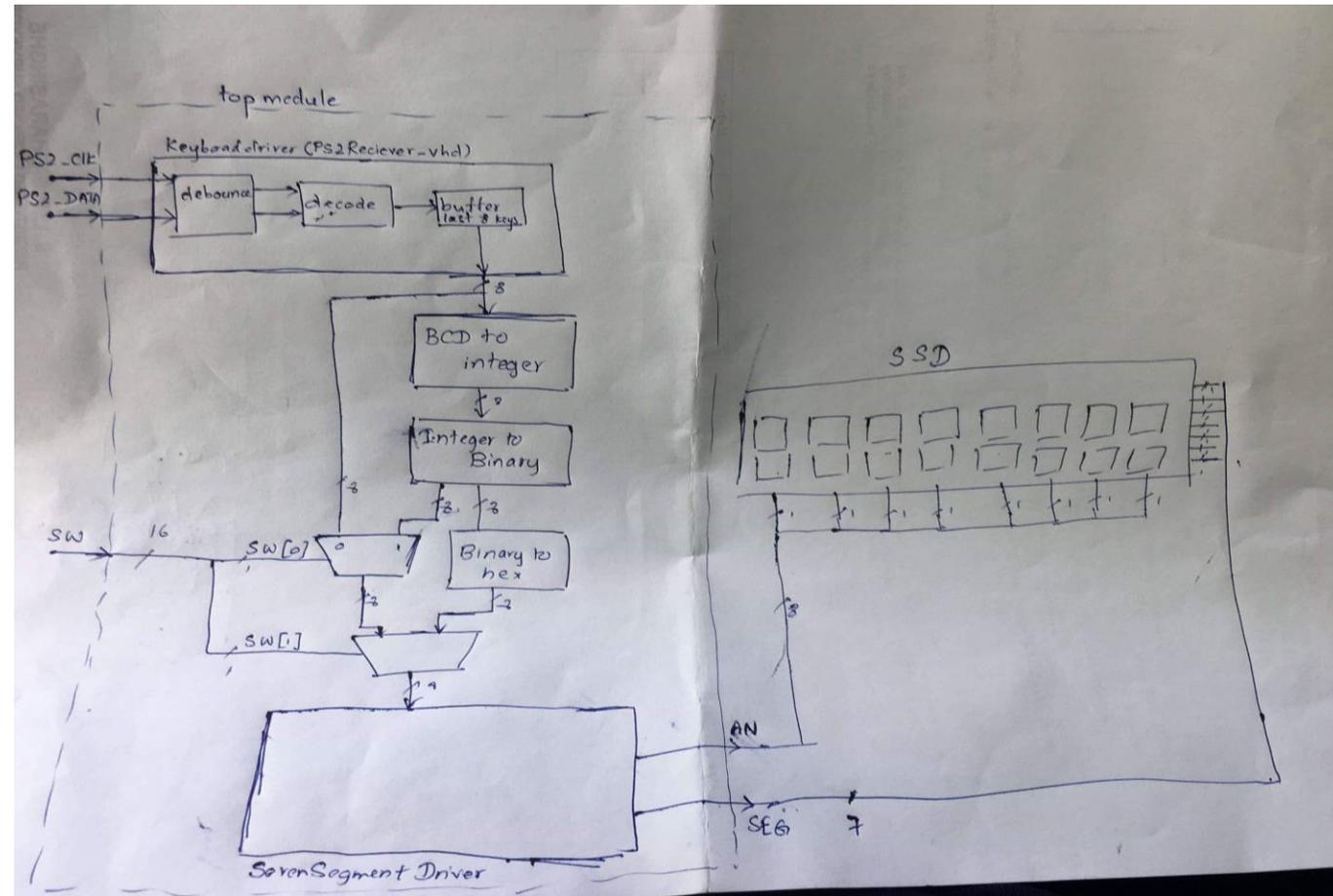

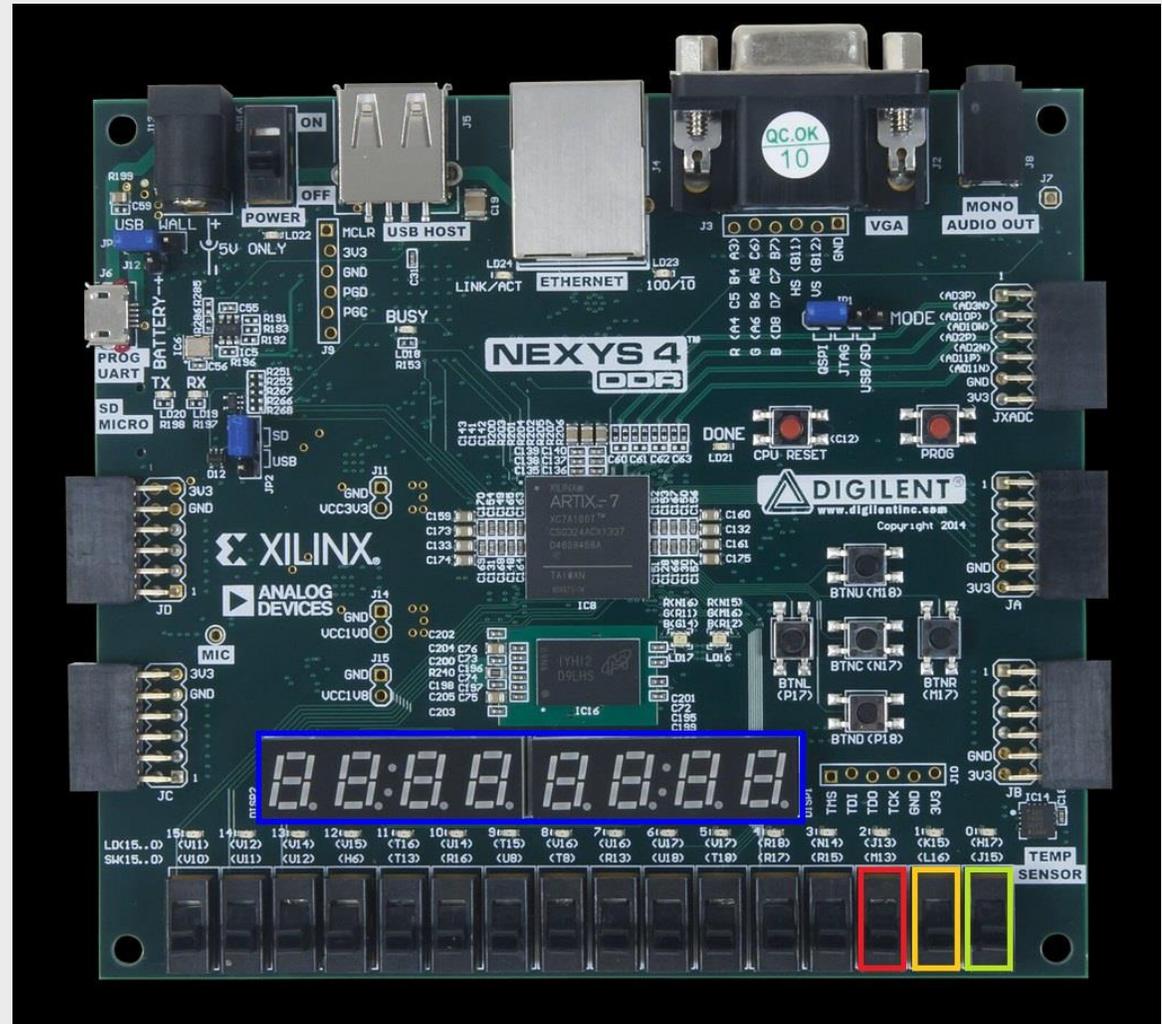
- BINARY
- HEX
- RESET
- SEVEN SEGMENT DISPLAY



EXPERIMENTAL SETUP

TRIAL #	DECIMAL #	INPUT (BCD)	OUTPUT (BINARY)	OUTPUT (HEX)
1	19	0001-1001	00010011	13
2	7	0000-0111	00000111	7
3	93	1001-0011	01011101	5D
4	9	0000-1001	00001001	9
5	48	0100-1000	00110000	30

SIMULATION

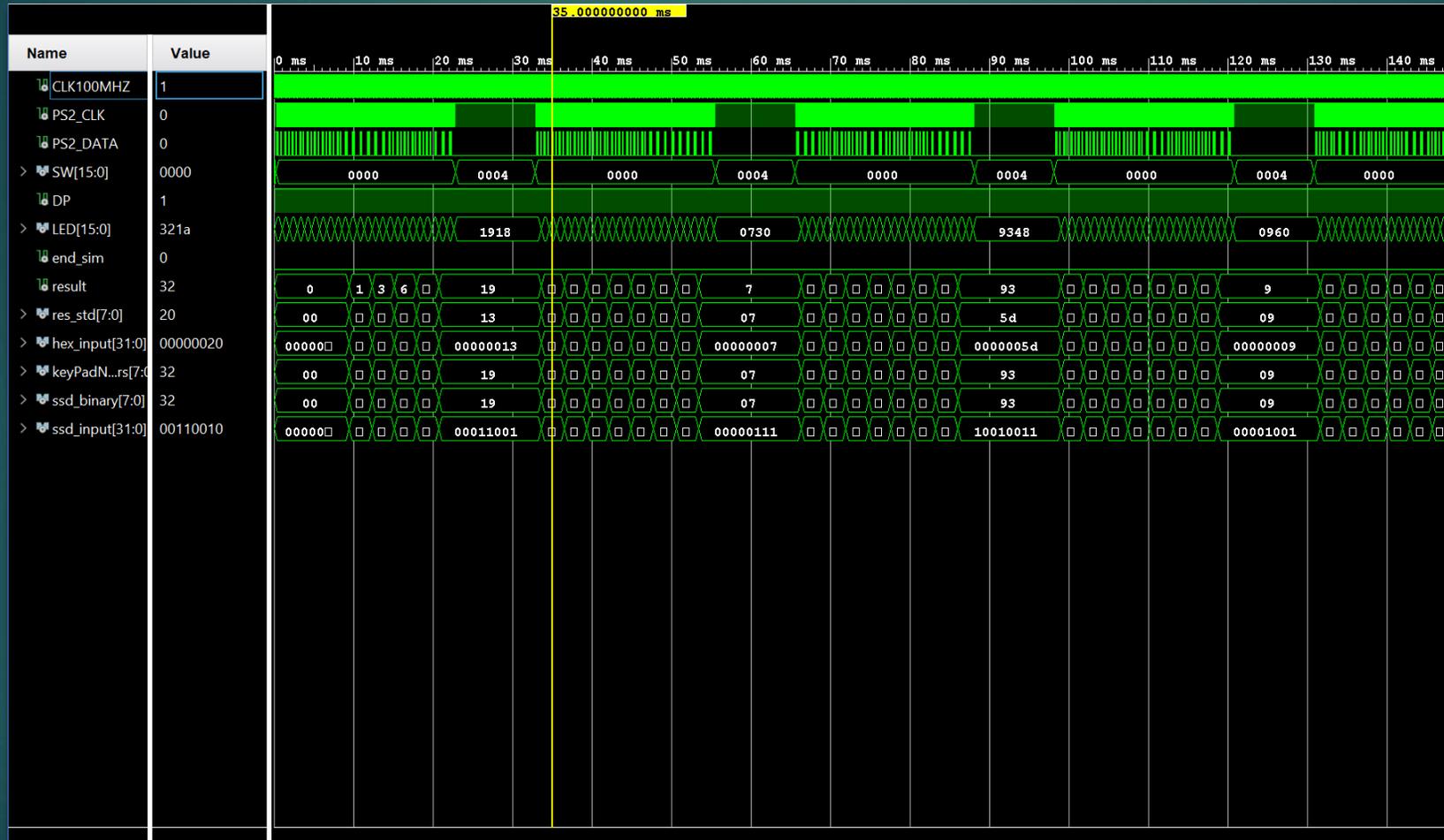

CONCLUSION

- ▶ The process of converting BCD to binary and hex was successfully implemented on an FPGA along with connecting a Keyboard via USB
- ▶ Connecting a keyboard to a Nexys Board was more difficult than expected especially as the user enters the BCD number, the numbers must shift to the left every time the user enters a new number "0 or 1".



ANY
QUESTIONS