

# Laboratory 4

(Due date : **002/003**: October 28<sup>th</sup>, **004**: October 29<sup>th</sup>, **005**: October 30<sup>th</sup>)

## OBJECTIVES


- ✓ Use the Concurrent Description and the Structural Description in VHDL.
- ✓ Implement Combinational circuits on an FPGA.

## VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

### FIRST ACTIVITY: (100/100)

- **SIMPLE 4-BIT ARITHMETIC LOGIC UNIT (ALU):** This circuit selects between arithmetic (absolute value, addition) and logical (AND, XNOR) operations. Only one result (hexadecimal value) can be shown on the 7-segment display. This is selected by the input  $sel(1..0)$ .
- Input  $EN$ : If  $EN=1 \rightarrow$  result appears on the 7-segment display. If  $EN=0 \rightarrow$  all LEDs in the 7-segment display are off.
- Arithmetic operations: The 4-bit inputs  $A$  and  $B$  are treated as unsigned numbers.
  - ✓  $A+B$ : If there is a carry out, ignore it.
  - ✓  $|A-B|$ : 4-bit result, since  $|A-B| \in [0,15]$ .  
Tip: zero-extend the inputs to 5 bits and implement  $A-B$  (5-bit signed result). Then, implement  $|A-B|$ , where the 5-bit signed result is always positive. Finally, use the magnitude (4 LSBs) as the unsigned output.
- Logic Operations ( $A \text{ xnor } B$ ,  $A \text{ and } B$ ): These are bit-wise operations.
- **Nexys-4 A7:** Each 7-segment display has active-low inputs ( $CA-CG$ ) and an active-low enable  $AN$ . Make sure that only one 7-segment display is activated (e.g.: to use only the right-most 7-segment display, set  $AN0=0$ ,  $AN1-AN7=1$ ).

 

- ✓ **NEXYS A7-50T:** Create a new Vivado Project. Select the **XC7A50T-1CSG324 Artix-7 FPGA** device.
  - ✓ Write the VHDL code for the given circuit.
    - **IMPORTANT:** For  $A+B$  and  $|A-B|$  circuits, you must use full adders and logic gates (as in Lab 2).
    - To implement the Bus MUX and decoder, it is strongly advised that you use the VHDL concurrent statements. To implement the top file, use the Structural Description: Create a separate file for the Arithmetic and Logic circuits, the 4-to-1 Bus MUX, and the Hex to 7-segment decoder.
  - ✓ Write the VHDL testbench to simulate the circuit. Use 16 sets of  $A$  and  $B$  values. For each set, make  $sel$  vary from 0 to 3. Also, include at least one case where  $EN=0$  to verify that that the 7-segment display is OFF.
  - ✓ Perform Functional Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
  - ✓ I/O Assignment: Create the XDC file. Nexys A7-50T: Use  $SW0$  to  $SW7$  for the inputs  $A$  and  $B$ ,  $SW8$  to  $SW10$  for the inputs  $sel$  and  $EN$ ,  $CA-CG$  (7-segment display signals), and  $AN7-AN0$  (anode enable for each 7-segment display).
  - ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**
- Submit (as a .zip file) all the generated files: VHDL code files, VHDL testbench, and XDC file to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

TA signature: \_\_\_\_\_

Date: \_\_\_\_\_