


Solutions - Final Exam

(December 9th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

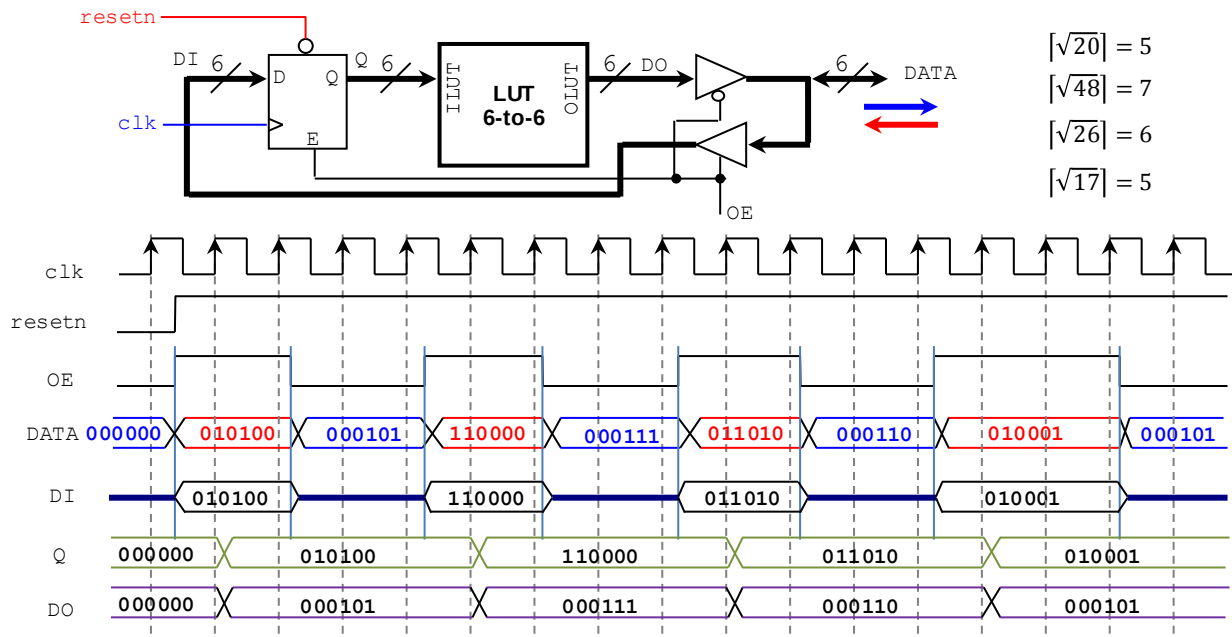
PROBLEM 1 (12 PTS)

- Given the following circuit, complete the timing diagram.
The LUT 6-to-6 implements the following function: $OLUT = \lceil \sqrt{ILUT} \rceil$, where $ILUT$ is a 6-bit unsigned number.
For example $ILUT = 35 (10011_2) \rightarrow OLUT = \lceil \sqrt{35} \rceil = 6 (000110_2)$



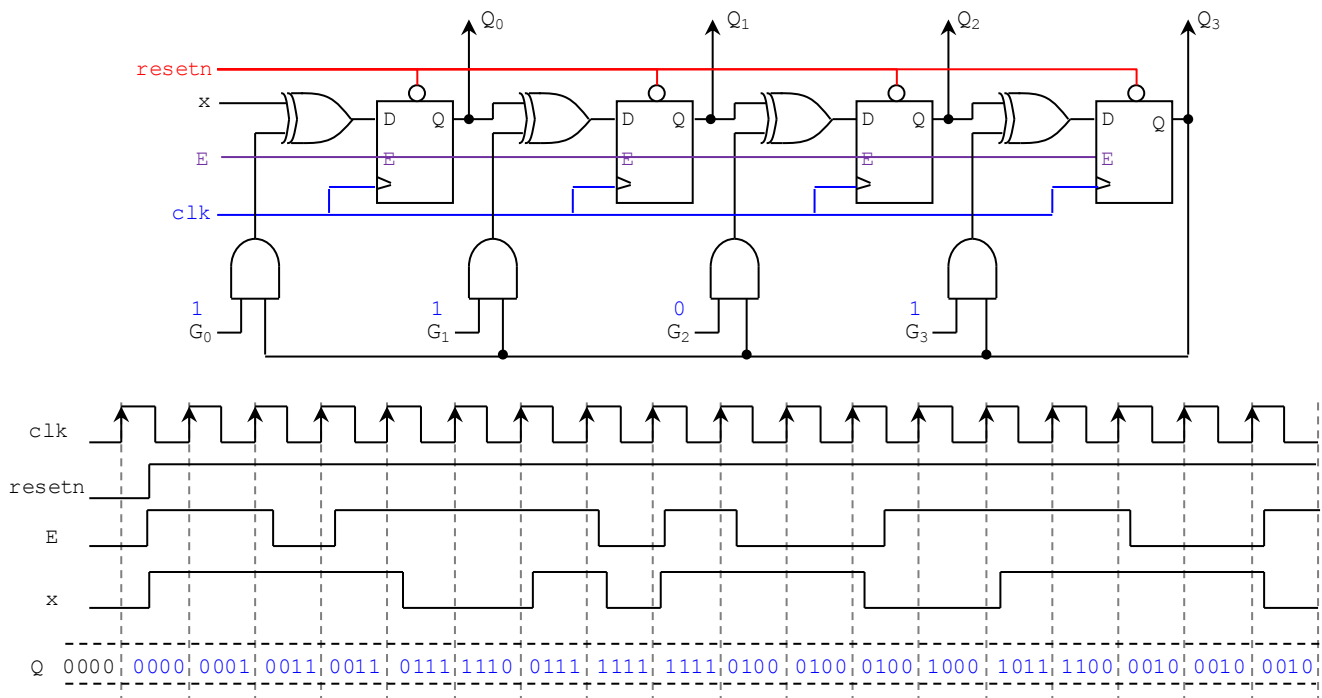
PROBLEM 2 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1011$, $Q = Q_3Q_2Q_1Q_0$



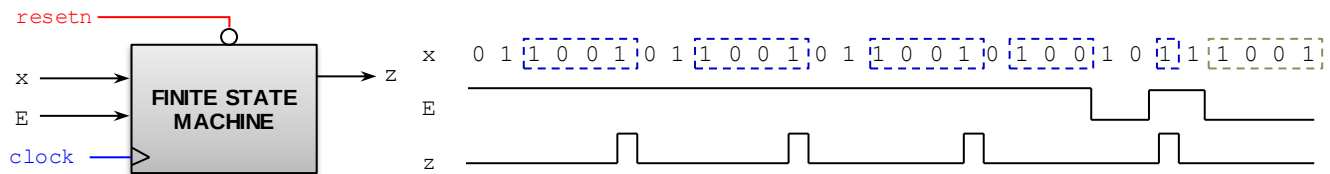
PROBLEM 3 (22 PTS)

- Sequence detector: The machine has to generate $z = 1$ when it detects the sequence 1001. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with inputs E and x and output z . Is this a Mealy or a Moore machine? Why? (15 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (4 pts)
- Sketch the circuit. (3 pts)

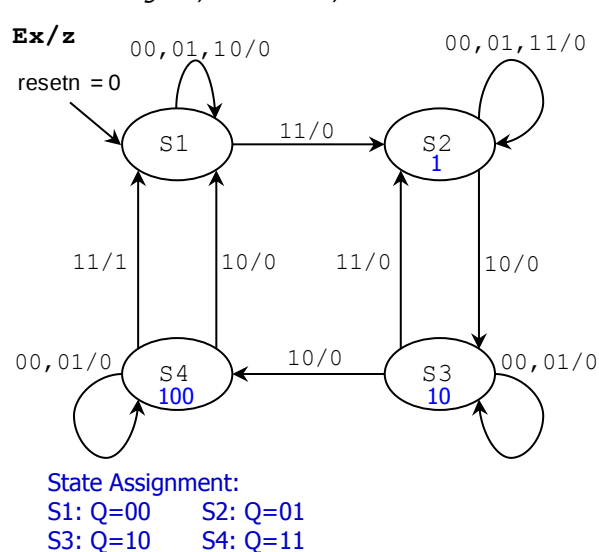State Diagram, State Table, and Excitation Table:



		PRESENT STATE		NEXT STATE				PRESENT STATE		NEXT STATE	
		E	x	STATE	STATE	z		E	x	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1) z
0	0	0	0	S1	S1	0		0	0	0 0	0
0	0	0	0	S2	S2	0		0	0	0 1	0
0	0	0	0	S3	S3	0		0	0	1 0	0
0	0	0	0	S4	S4	0		0	0	1 1	0
0	1	0	1	S1	S1	0		0	1	0 0	0
0	1	0	1	S2	S2	0		0	1	0 1	0
0	1	0	1	S3	S3	0		0	1	1 0	0
0	1	0	1	S4	S4	0		0	1	1 1	0
1	0	1	0	S1	S1	0		1	0	0 0	0
1	0	1	0	S2	S3	0		1	0	0 1	0
1	0	1	0	S3	S4	0		1	0	1 1	0
1	0	1	0	S4	S1	0		1	0	1 1	0
1	1	1	1	S1	S2	0		1	1	0 0	0
1	1	1	1	S2	S2	0		1	1	0 1	0
1	1	1	1	S3	S2	0		1	1	1 0	0
1	1	1	1	S4	S1	1		1	1	1 1	1

This is a Mealy Machine. The output z depends on the input as well as on the present state.


- Excitation equations, minimization, and circuit implementation:

$$Q_1(t+1) \leftarrow \bar{E}Q_1 + E\bar{x}Q_1Q_0 + \bar{x}Q_1\bar{Q}_0$$

$$Q_0(t+1) \leftarrow \bar{E}Q_0 + E\bar{x}Q_1 + E\bar{x}Q_0$$

$$z = E\bar{x}Q_1Q_0$$

		Q ₁ (t+1)						Q ₀ (t+1)			
		Ex						Ex			
		00	01	11	10			00	01	11	10
Q ₁ Q ₀		0	0	0	0	Q ₁ Q ₀		0	0	1	0
00						01		1	1	1	0
01		0	0	0	1	11		1	1	0	0
11		1	1	0	0	10		0	0	1	1
10		1	1	0	1						

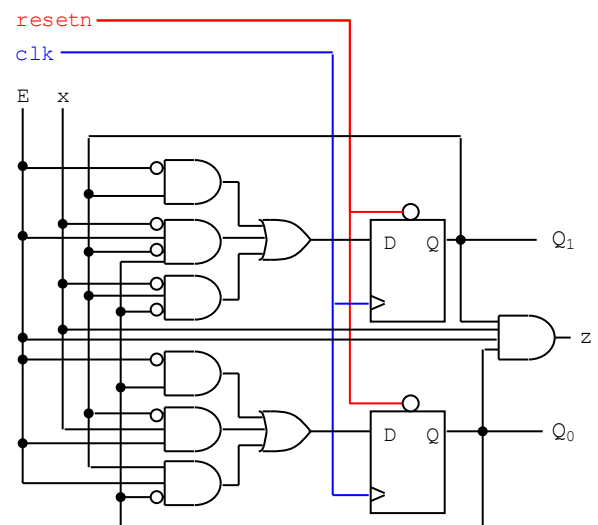


PROBLEM 4 (21 PTS)

- Given the following State Machine Diagram: (10 pts)
 - ✓ Provide the State Table and the Excitation Table.
 - ✓ Get the excitation equations and the Boolean equation for z .
Use S1 (Q=00), S2 (Q=01), S3 (Q=10), S4 (Q=11) to encode the states.
 - ✓ Sketch the Finite State Machine circuit.

PRESENT STATE			NEXTSTATE	
w	$Q_1Q_0(t)$		$Q_1Q_0(t+1)$	z
0	0 0		1 0	0
0	0 1		0 0	0
0	1 0		0 0	0
0	1 1		0 0	1
1	0 0		0 1	0
1	0 1		1 1	0
1	1 0		1 1	0
1	1 1		1 0	0



PRESENT STATE		NEXT STATE		z
w	STATE	STATE	z	
0	S1	S3	0	
0	S2	S1	0	
0	S3	S1	0	
0	S4	S1	1	
1	S1	S2	0	
1	S2	S4	0	
1	S3	S4	0	
1	S4	S3	0	

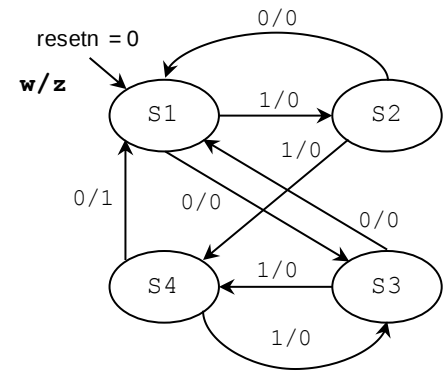


$$Q_1(t+1) \leftarrow \overline{(Q_1 + Q_0)} \oplus w$$

$$Q_0(t+1) \leftarrow Q_1 Q_0 w$$

$$z = \overline{w} Q_1 Q_0$$

State Assignment:

S1: Q=00 S2: Q=01
S3: Q=10 S4: Q=11

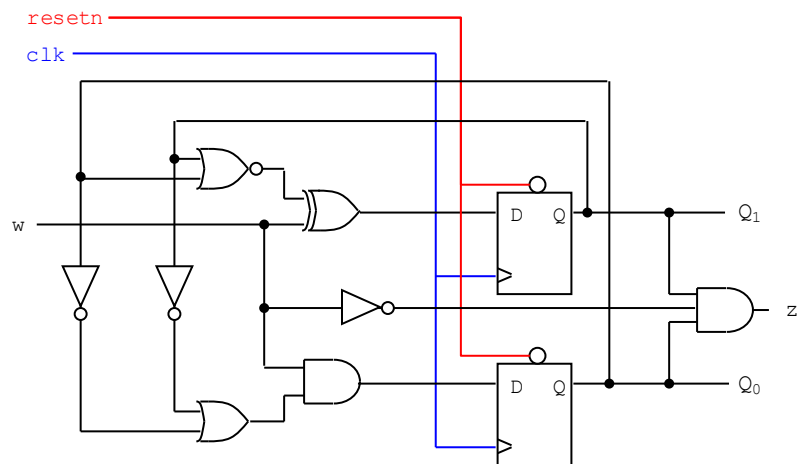

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (11 pts)


$$Q_1(t+1) \leftarrow (Q_1 + Q_0)w$$

$$Q_0(t+1) \leftarrow (\overline{Q_1} Q_0) \oplus w$$

$$z = Q_1 + Q_0$$

State Assignment:

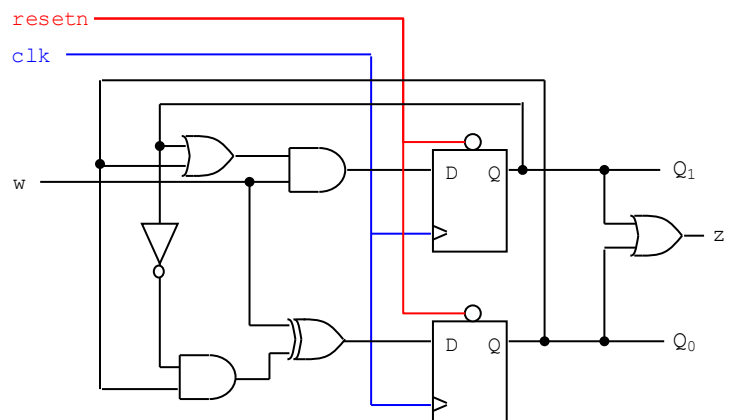
S1: Q = 00
S2: Q = 01
S3: Q = 10
S4: Q = 11



PRESENT STATE			NEXTSTATE	
w	$Q_1Q_0(t)$		$Q_1Q_0(t+1)$	z
0	0 0		0 0	0
0	0 1		0 1	1
0	1 0		0 0	1
0	1 1		0 0	1
1	0 0		0 1	0
1	0 1		1 0	1
1	1 0		1 1	1
1	1 1		1 1	1



PRESENT STATE		NEXT STATE		z
w	STATE	STATE	z	
0	S1	S1	0	
0	S2	S2	1	
0	S3	S1	1	
0	S4	S1	1	
1	S1	S2	0	
1	S2	S3	1	
1	S3	S4	1	
1	S4	S4	1	

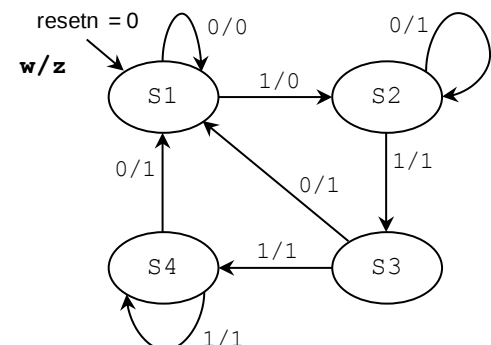


PROBLEM 5 (15 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

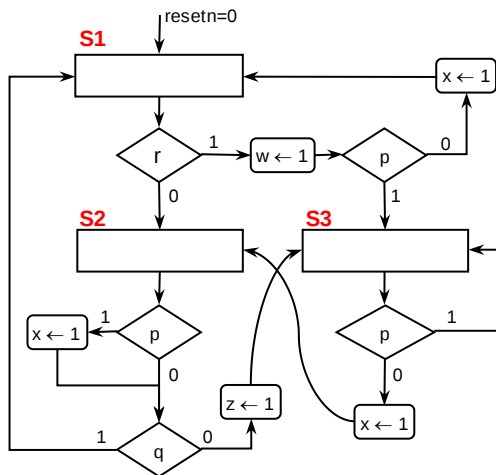
entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```



```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '0' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;
                when S2 =>
                    if q = '1' then y <= S1; else y <= S3; end if;
                when S3 =>
                    if p = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 =>
                if r = '1' then
                    w <= '1';
                    if p = '0' then
                        x <= '1';
                    end if;
                end if;
            when S2 =>
                if p = '1' then x <= '1'; end if;
                if q = '0' then z <= '1'; end if;
            when S3 =>
                if p = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

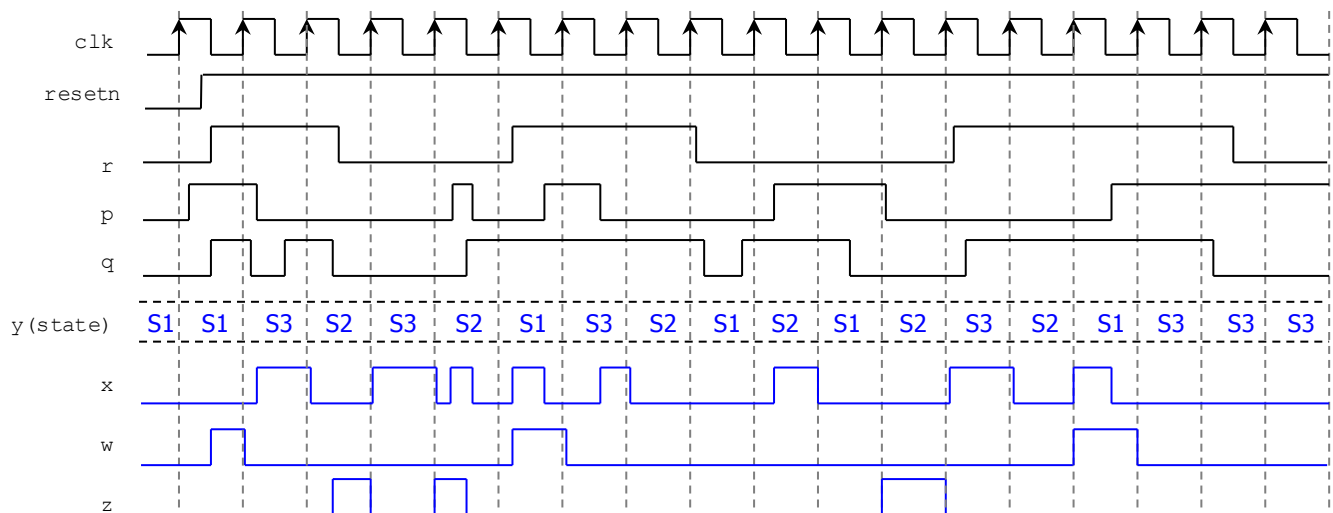This is a Mealy FSM. The outputs x, w, z depend on the inputs as well as on the present state.



PROBLEM 6 (18 PTS)

- “Counting 1’s” Circuit: It counts the number of bits in register A that has the value of ‘1’.
The digital system is depicted below: FSM + Datapath. Example: For $n = 8$: if $A = 00110110$, then $C = 0100$.
✓ m-bit counter: If $E = sclr = 1$, the count is initialized to zero. If $E = 1, sclr = 0$, the count is increased by 1.
✓ Parallel access shift register: If $E = 1: s_l = 1 \rightarrow \text{Load}, s_l = 0 \rightarrow \text{Shift}$.
- Complete the timing diagram where $n = 8, m = 4$.

