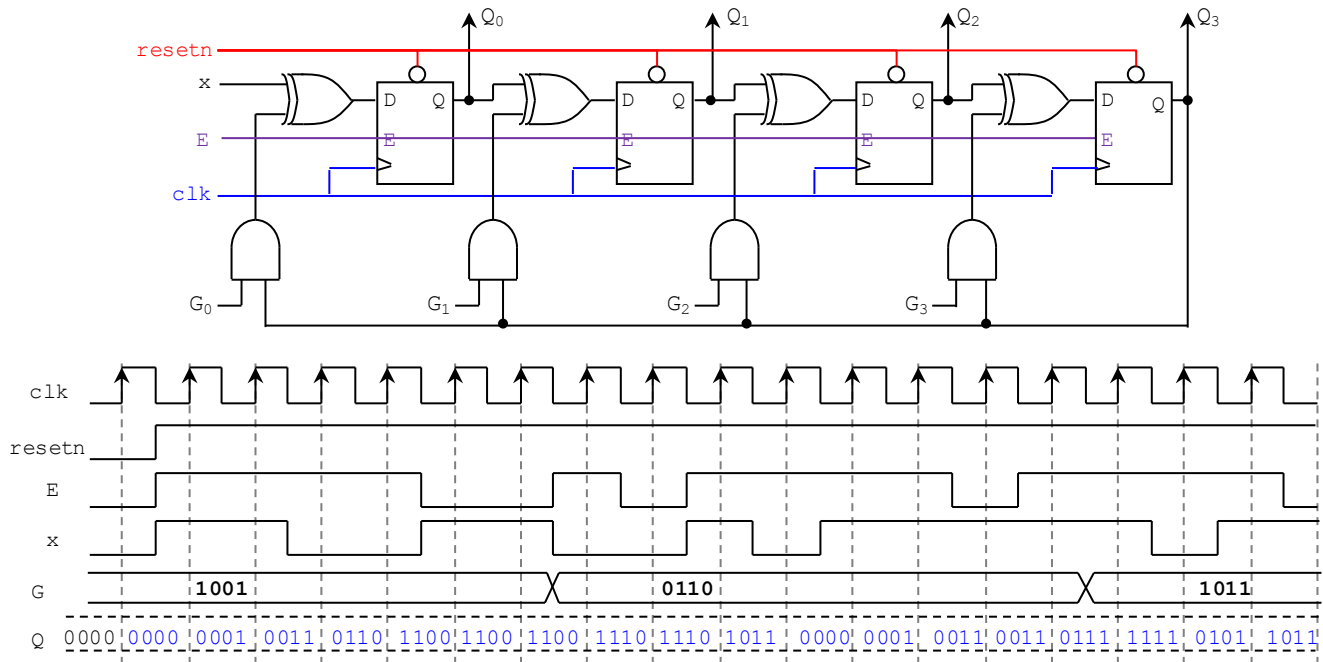


Solutions - Homework 4

(Due date: November 21st (001), November 20th (006) @ 5:30 pm)
Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (14 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0$, $Q = Q_3Q_2Q_1Q_0$.




PROBLEM 2 (18 PTS)

Design a counter using a Finite State Machine (FSM):

Counter features:

 - ✓ Count: **000**, 010, 111, 011, 110, 100, 001, 101, **000**, 010, 111, ...
- ✓ *resetn*: Asynchronous active-low input signal. It initializes the count to "000"
- ✓ Input *E*: Synchronous input that increases the count when it is set to '1'.
- ✓ output *z*: It becomes '1' when the count is 101.




- Provide the State Diagram (any representation), State Table, and the Excitation Table. Is this a Mealy or a Moore machine? Why? (10 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)

- State Diagram, State Table, State Assignment, and Excitation Table:

S1: Q = 000
S2: Q = 001
S3: Q = 010
S4: Q = 011
S5: Q = 100
S6: Q = 101
S7: Q = 110
S8: Q = 111

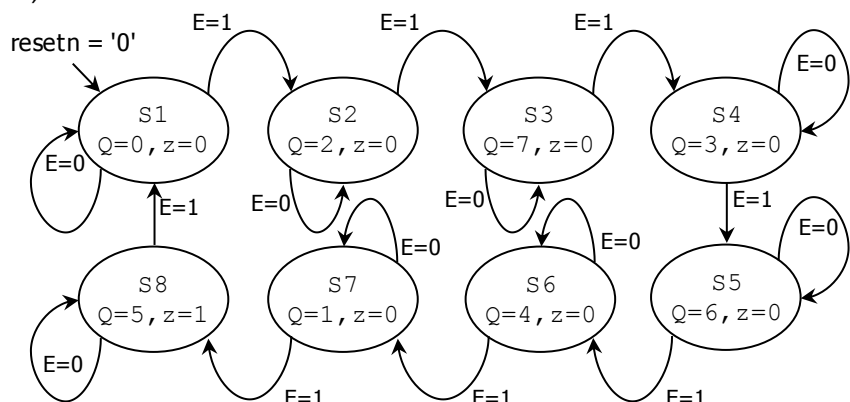The output *z* only depends on the present State. Thus, it is a Moore FSM.



PRESENT STATE		NEXT STATE		z	PRESENT STATE				NEXTSTATE				z
E	STATE	STATE			E	$Q_2Q_1Q_0(t)$			$Q_2Q_1Q_0(t+1)$				
0	S1	S1	0		0	0	0	0	0	0	0	0	0
0	S2	S2	0		0	0	1	0	0	1	0	0	0
0	S3	S3	0		0	1	1	1	1	1	1	1	0
0	S4	S4	0		0	0	1	1	0	1	1	1	0
0	S5	S5	0		0	1	1	0	1	1	1	0	0
0	S6	S6	0		0	1	0	0	1	0	0	0	0
0	S7	S7	0		0	0	0	0	1	0	0	1	0
0	S8	S8	1		0	1	0	1	1	1	0	1	1
1	S1	S2	0	1	0	0	0	0	0	1	0	0	
1	S2	S3	0	1	0	1	0	0	1	1	1	0	
1	S3	S4	0	1	1	1	1	1	0	1	1	0	
1	S4	S5	0	1	0	1	1	1	1	1	0	0	
1	S5	S6	0	1	1	1	1	0	1	0	0	0	
1	S6	S7	0	1	1	1	0	0	0	0	1	0	
1	S7	S8	0	1	0	0	0	1	1	0	1	0	
1	S8	S1	1	1	1	0	1	1	0	0	0	1	

- Excitation equations, minimization, and circuit implementation:

$$Q_2(t+1) \leftarrow \bar{E}Q_2 + E\bar{Q}_2Q_0 + EQ_1\bar{Q}_0$$

$$Q_1(t+1) \leftarrow Q_1Q_0 + \bar{E}Q_1 + E\bar{Q}_2\bar{Q}_0$$

$$Q_0(t+1) \leftarrow \bar{E}Q_0 + Q_0(Q_1 \oplus Q_2) + E\bar{Q}_0(Q_1 \oplus Q_2)$$

$$z = Q_2\bar{Q}_1Q_0$$


$Q_2(t+1)$

EQ_2	00	01	11	10
Q_1Q_0				
00	0	1	0	0
01	0	1	0	1
11	0	1	0	1
10	0	1	1	1

$Q_1(t+1)$

EQ_2	00	01	11	10
Q_1Q_0				
00	0	0	0	1
01	0	0	0	0
11	1	1	1	1
10	1	1	0	1

- Circuit Implementation:

 

$Q_0(t+1)$

EQ_2	00	01	11	10
Q_1Q_0				
00	0	0	1	0
01	1	1	0	1
11	1	1	1	0
10	0	0	0	1

z


EQ_2	00	01	11	10
Q_1Q_0				
00	0	0	0	0
01	0	1	1	0
11	0	0	0	0
10	0	0	0	0

PROBLEM 4 (15 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

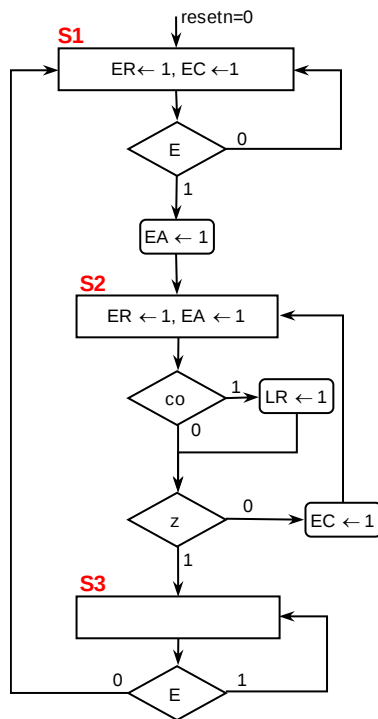entity myfsm is
    port ( clk, resetn: in std_logic;
          z, E, co: in std_logic;
          ER,LR,EC,EA: out std_logic);
end myfsm;
```



```
architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, z, E, co)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if E = '1' then y <= S2; else y <= S1; end if;

                when S2 =>
                    if z = '1' then y <= S3; else y <= S2; end if;


                when S3 =>
                    if E = '1' then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, z, E, co)
    begin
        ER <= '0'; LR <= '0'; EC <= '0'; EA <= '0';
        case y is
            when S1 => ER <= '1'; EC <= '1';
                if E = '1' then EA <= '1'; end if;

            when S2 => ER <= '1'; EA <= '1';
                if co = '1' then LR <= '1'; end if;
                if z = '0' then EC <= '1'; end if;



            when S3 =>
            end case;
        end process;
    end behavioral;
```

 This is a Mealy FSM. The outputs LR, EC, EA depend on the input as well as on the present state.



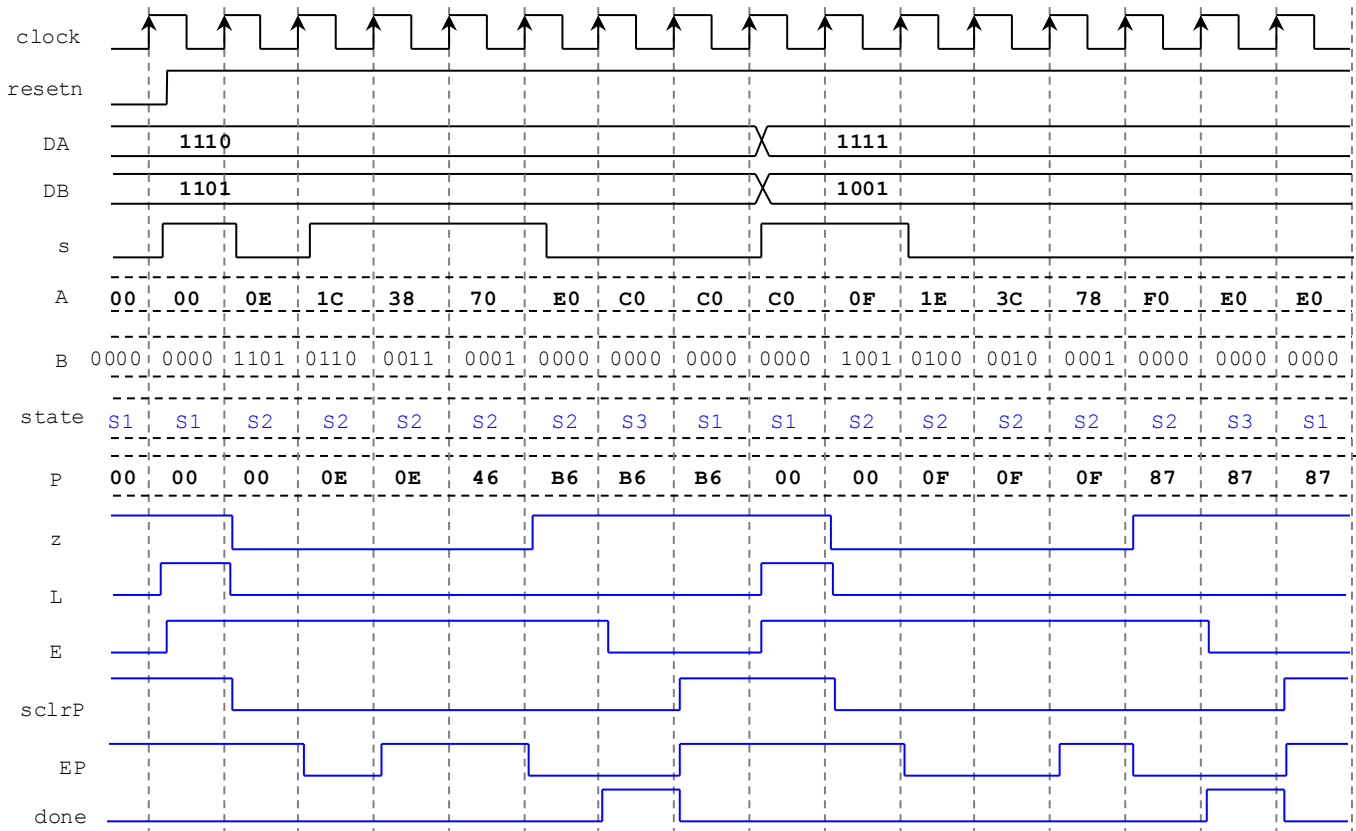 PROBLEM 5 (18 PTS)

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit. Register (for P): *sclr*: synchronous clear. Here, if *sclr* = *E* = 1, the register contents are initialized to 0. Parallel access shift registers (for A and B): If *E* = 1: *s_l* = 1 → Load, *s_l* = 0 → Shift



PROBLEM 6 (15 PTS)

- Attach a printout of your Project Status Report (no more than two pages, single-spaced, 2 columns). This report should contain the current status of the project. You **MUST** use the provided template (Final Project - Report Template.docx).