

Solutions - Quiz 3


(November 5th @ 5:30 pm)

PROBLEM 1 (30 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;

 entity circ is
port ( rstn, a, b, x, clk: in std_logic;
      q: out std_logic);
end circ;
```





```
architecture xst of circ is
    signal qt, f: std_logic;
begin
    f <= a xor b;

    process (rstn, clk, f, x)
    begin
        if rstn = '0' then
            qt <= '0';
        elsif (clk'event and clk = '1') then
            if x = '1' then
                qt <= qt xor f;
            end if;
        end if;
    end process;
    q <= qt;
end xst;
```

  PROBLEM 2 (30 PTS)

- Complete the timing diagram of the following state machine:



PROBLEM 3 (40 PTS)

- Complete the timing diagram of the following circuit. $Q = Q_3Q_2Q_1Q_0$
- Get the excitation equation for Q_3 . (5 pts)

$$Q_3(t+1) \leftarrow x \oplus Q_0(t)$$

