

Solutions - Quiz 4


(November 25th @ 5:30 pm)

PROBLEM 1 (30 PTS)

- Draw the state diagram (in ASM form) of the FSM whose VHDL description is listed below:

```
library ieee;
use ieee.std_logic_1164.all;

 entity circ is
port ( clk, rstn: in std_logic;
      r, p, q: in std_logic;
      x, w, z: out std_logic);
end circ;
```



```
architecture behavioral of circ is
type state is (S1, S2, S3);
signal y: state;
begin
Transitions: process (rstn, clk, r, p, q)
begin
if rstn = '0' then y <= S1;
elsif (clk'event and clk = '1') then
case y is
when S1 =>
if r = '1' then y <= S2;
else if p = '1' then y <= S3; else y <= S1; end if;
end if;
when S2 =>
if p = '1' then y <= S1; else y <= S3; end if;
when S3 =>
if q = '1' then y <= S3; else y <= S2; end if;
end case;
end if;
end process;

Outputs: process (y, r, p, q)
begin
x <= '0'; w <= '0'; z <= '0';
case y is
when S1 => if r = '0' then x <= '1'; end if;
when S2 => if q = '0' then w <= '1'; end if;
if p = '0' then z <= '1'; end if;
when S3 => if q = '0' then w <= '1'; end if;
end case;
end process;
end behavioral;
```

PROBLEM 2 (40 PTS)


- Provide the excitation equations (including the Boolean equation for z) and the Excitation Table for the following FSM:

$$Q_1(t+1) \leftarrow Q_0(t)$$

$$Q_0(t+1) \leftarrow Q_1(t) \oplus w$$

$$z = Q_1(t) \oplus Q_0(t) \oplus w$$

PRESENT STATE			NEXTSTATE		
w	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)	z	
0	0 0		0 1	0	
0	0 1		1 1	1	
0	1 0		0 0	1	
0	1 1		1 0	0	
1	0 0		0 0	1	
1	0 1		1 0	0	
1	1 0		0 1	0	
1	1 1		1 1	1	

 

- Is this a Mealy or a Moore FSM? Why? (5 pts)
The output z depends on input w as well as on the present state. Thus, it is a Mealy FSM.

PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input x and output z . The detector asserts $z = 1$ when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.

