

Student Honor Pledge:

All work submitted is completed by me directly without the use of any unauthorized resources or assistance

Final Exam


Initials: _____

(December 14th @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

 
PROBLEM 1 (18 PTS)

- Complete the timing diagram of the circuit shown below. (8 pts)




- Complete the timing diagram of the following bit-serial adder. $DX=1001$, $DY=1110$. (10 pts)

 ✓ This circuit includes three 4-bit parallel access shift registers, a flip flop, and a full adder.



 
PROBLEM 2 (13 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



 
PROBLEM 3 (13 PTS)

- Given the following circuit that represents a Finite State Machine, provide: (12 pts)
 - Excitation equations and output Boolean equation.
 - Excitation Table, State Table.
 - State Diagram (any representation).
- Is this a Mealy or a Moore Machine? (1 pt.)



 PROBLEM 4 (16 PTS)

- Sequence detector: The machine generates $z = 1$ when it detects the sequence 1101. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E=1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation) of this circuit with inputs E and x and output z . (7 pts.)
- Complete the State Table and the Excitation Table. (8 pts.)
- Is this a Mealy or a Moore machine? Why?

PROBLEM 5 (18 PTS)

- “Counting 0’s” Circuit: It counts the number of bits in register *A* that has the value of ‘0’.
- ✓ Example: for $n = 8$: if $A = 00110010$, then $C = 0101$.
- ✓ The behavior (on the clock tick) of the generic components is as follows:



```

m-bit counter (modulo-n+1): If E=0, the count stays.
if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← Q+1
  end if;
end if;
    
```

```

n-bit Parallel access shift register: If E=0, the output is kept.
if E = 1 then
  if s_l = '1' then
    Q ← D
  else
    Q ← shift in 'din' (to the right)
  end if;
end if;
    
```

  - Complete the timing diagram where $n = 8, m = 4$. *A* is represented in hexadecimal format, while *C* is in binary format.



PROBLEM 6 (22 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. (6 pts)
- Provide the State Table and the Excitation Table. Is it a Mealy or a Moore FSM? (6 pts).
- Provide the excitation equations and the Boolean output equations (simplify your circuit: K-maps or Quine-McCluskey).
- Sketch the circuit. (3 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( clk, rstn: in std_logic;
        a, b: in std_logic;
        x, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (rstn, clk, a, b)
  begin
    if rstn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if a = '1' then
            y <= S2;
          else
            if b = '1' then y <= S3; else y <= S1; end if;
          end if;
        when S2 =>
          if b = '1' then y <= S2; else y <= S1; end if;
        when S3 =>
          if b = '1' then y <= S3; else y <= S1; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, a, b)
  begin
    x <= '0'; z <= '0';
    case y is
      when S1 => if a = '0' then z <= '1'; end if;
      when S2 => x <= '1';
      when S3 => if a = '0' then x <= '1'; end if;
    end case;
  end process;
end behavioral;
```