

UNSIGNED 2X2 MATRIX MULTIPLIER

ECE 2700 Final Project Presentation

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} e & f \\ g & h \end{bmatrix} = \begin{bmatrix} ae+bg & af+bh \\ ce+dg & cf+dh \end{bmatrix}$$

James Sherwood


Tim Kozen

Oakland University, College of Engineering

12/7/2020

Input Circuit Schematic

Input from Switches

 


Output to Adders

Input Components


Switches

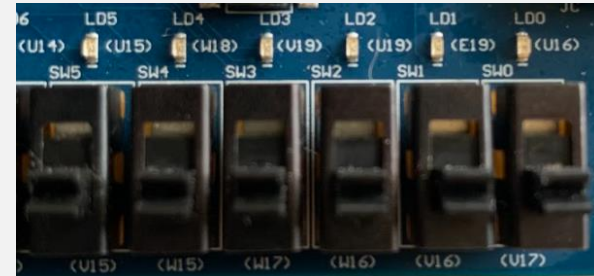- (5) Switches for a 5-bit binary number
- (3) Switches for binary numbers representing each of the eight elements in the input matrices.




Decoder

 - 2 to 1 Decoder that has a 3-bit input from the matrix selectors along with a logic signal representing the register write function. The inputs are paired with a 9-bit output that associates a memory slot in the registry with the matrix element selection.




Registry

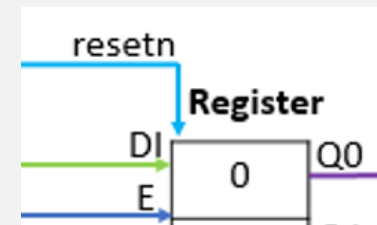- (8) memory slots for each matrix element.
- Receives and stores the 5-bit binary input.




Multiplier

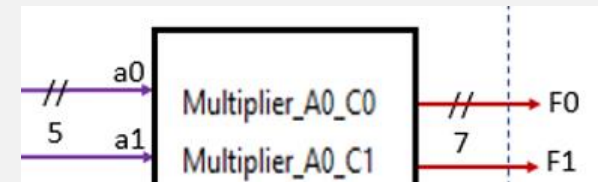- Performs multiplication of registry data in accordance with a 2x2 matrix multiplication algorithm.




Multiplier Timing Diagram

 

$$\begin{bmatrix} 9 & 8 \\ 7 & 6 \end{bmatrix} \times \begin{bmatrix} 5 & 4 \\ 3 & 2 \end{bmatrix} = (9*5)+(8*3), (9*4)+(8*2), (7*5)+(6*3), (7*4)+(6*2) =$$

$$45 + 24, 36 + 16, 35 + 18, 28 + 12$$


Output Circuit Schematic

 

Output Components


7-bit Adders

 - (4) Adders, one for each resultant matrix element
- Inputs two 7-bit unsigned signals each
- Output one 8-bit unsigned signal each




Multiplexers

 - 4 to 1 MUX selects resultant matrix element displayed
- 3 to 1 MUX to control character displayed




Finite State Machine

 - (3) states, one for each 7-seg display used
- Input enable signal from counter (every 100us)
- Output “sel2” signal controlling serial 7-seg display




BIN to BCD Converter

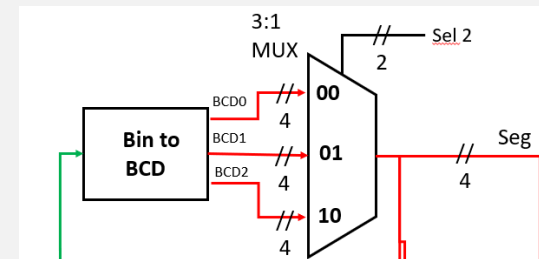- Input 8-bit 4 to 1 MUX output “mout”
- Output three 4-bit BCD signals
- One BCD signal for each digit to be displayed



Display Control Timing Diagram

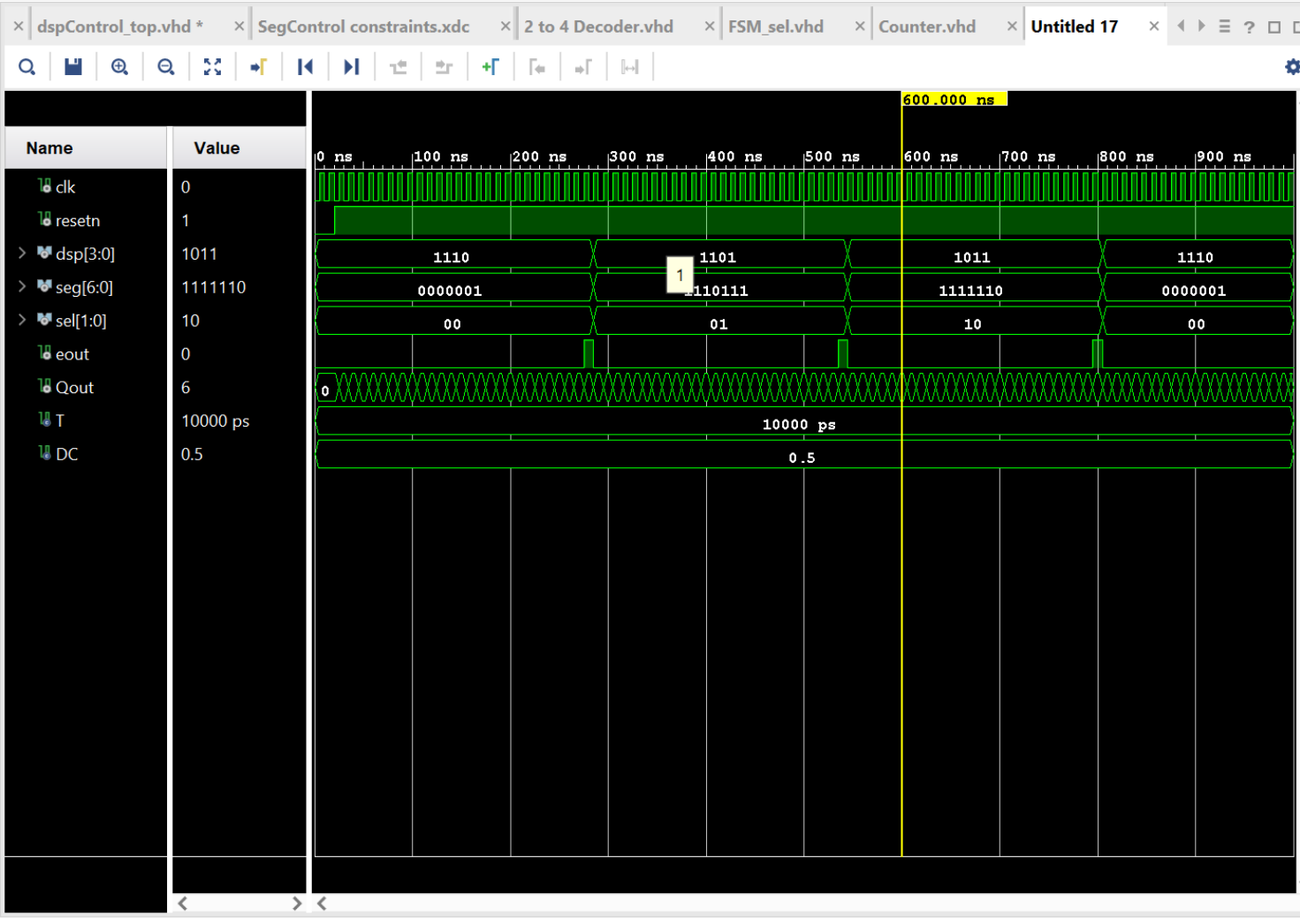

Functionality Demonstration

Input Matrices

$$\begin{bmatrix} 9 & 8 \\ 6 & 5 \end{bmatrix} \times \begin{bmatrix} 9 & 4 \\ 7 & 3 \end{bmatrix}$$

Output Matrix

$$R = \begin{bmatrix} 137 & 60 \\ 89 & 39 \end{bmatrix}$$

