

RGB Controller with an ADXL362 Accelerometer

David Sheridan, Jermaine Juarez,
Tajwar Eram






Approach to RGB Control

SPI Communications

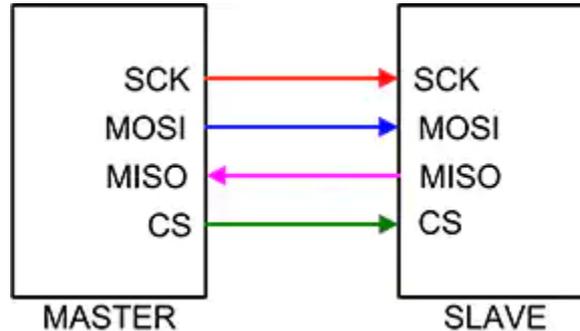
- Able to communicate between an Artix 7 (Master) and ADXL362 (Slave) through SPI
 - SCLK, nCS, MOSI, MISO





Approach to RGB Control

Accelerometer Data and PWM

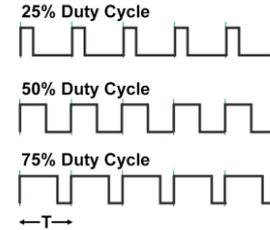

- Variation based on change in orientation read from the Accelerometer
- Pulse width modulation to change intensities of RLED and BLED
- The Green LED is not changed by the data from the Accelerometer
- Selector used for reading different registers for axes (X, Y, and Z)




Approach to RGB Control

FSMs and Reference code

- Through FSMs and referencing the ADXL362 “wr_reg_adxl362” data acquisition code and also allows the right SPI communications to send the measurements from accelerometer to Artix 7



Overall Block Diagram

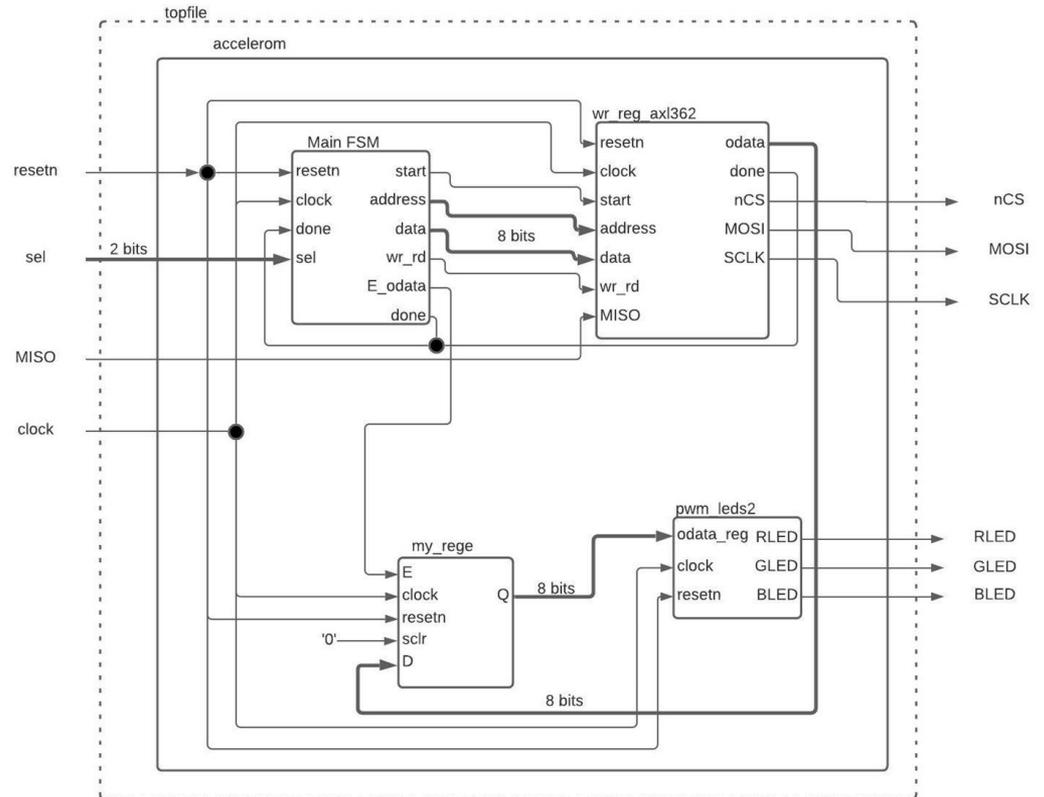- Input sel selects the axis to be displayed
- Inputs resetn and clock are universal






PWM Block

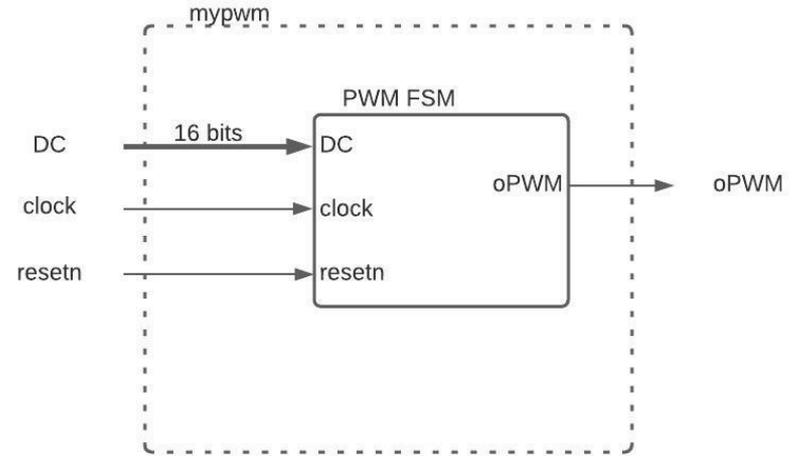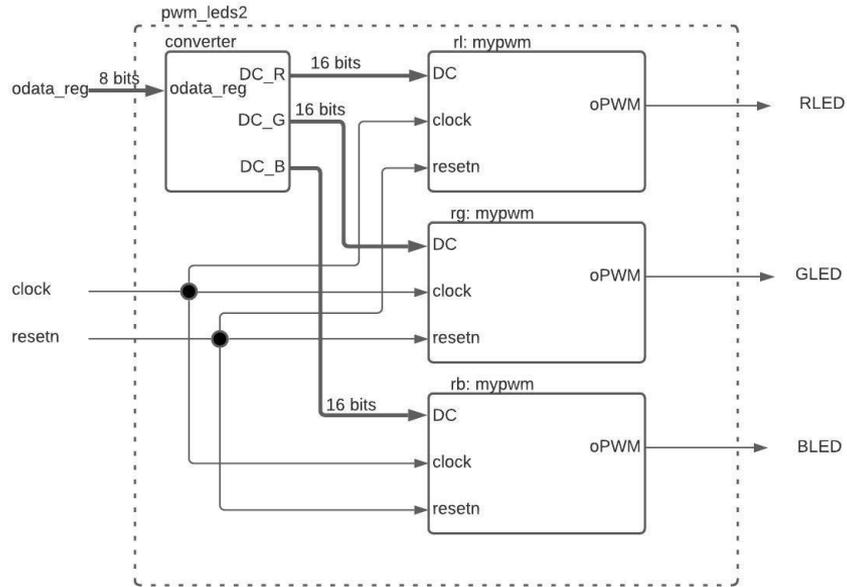

PWM FSM

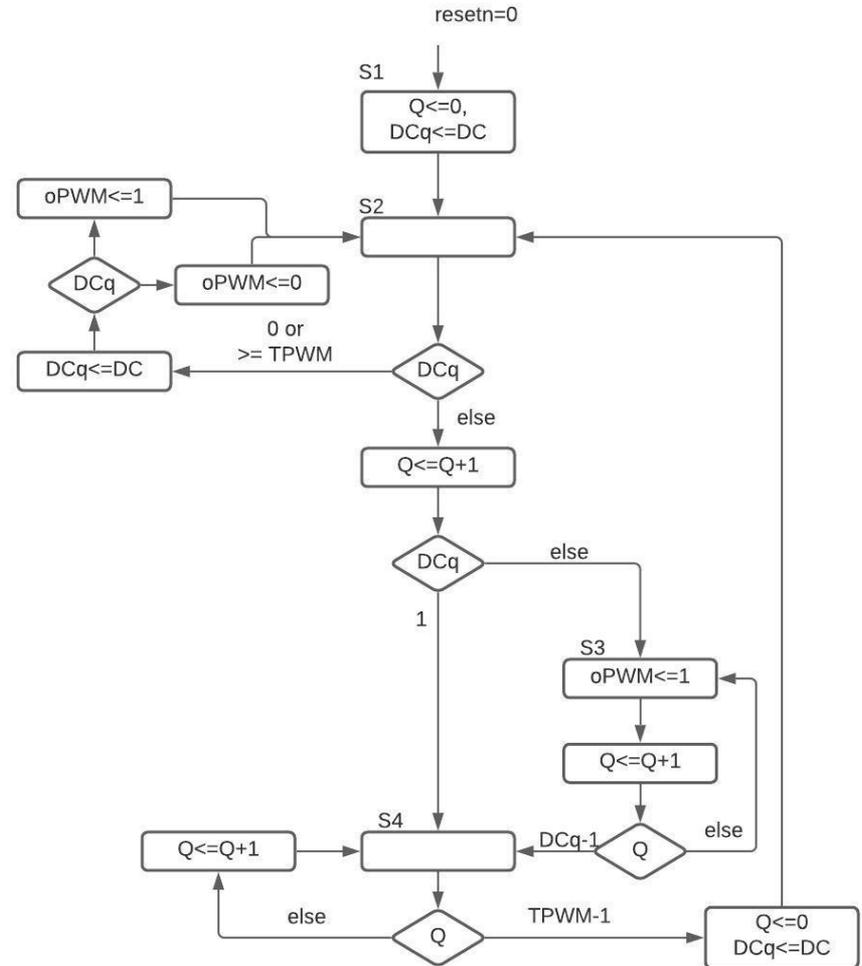
- Duty Cycle is value between 0 and TPWM
- Can be thought of as a percentage
- Duty Cycle determines amount of time that LEDs are on, resulting in a certain “Brightness”
- State 1
 - Reset
- State 2
 - Ensures DC is within bounds
- State 3
 - Counts until DC value is reached
- State 4
 - Counts until TPWM is reached






Pins for ADXL362

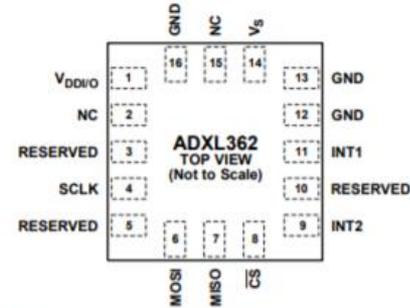- SPI Communication
- Interrupts are not used
- MOSI signal comes from board
- MISO signal comes from sensor
- Slave Select is required for communication to be initiated
- Serial Clock comes from the board



NOTES
1. NC = NO CONNECT. THIS PIN IS NOT INTERNALLY CONNECTED.


ADXL362 Pins

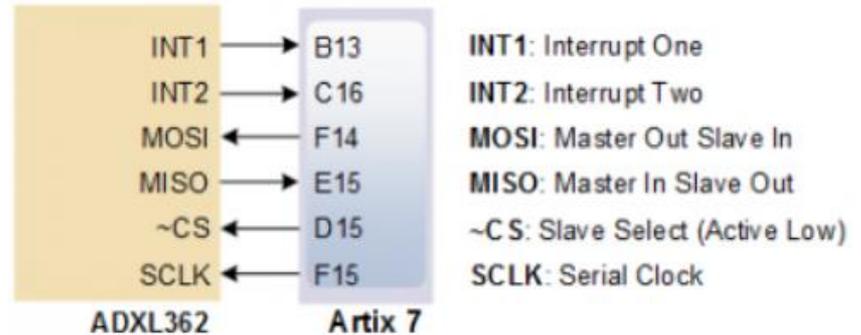

Pins Between Board and Sensor



Accelerometer

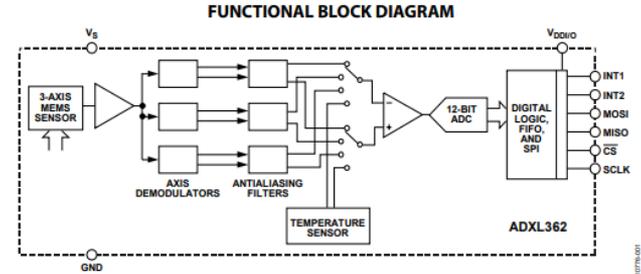


- 4 main components: PWM Block, Accelerometer FSM, wr_reg, and register.
- Measures 3 axis: x-axis, y-axis, and z-axis data.
- Option for the 12 bit register or 8 bit register. 12 bit accuracy is not really needed, so we chose an 8-bit register for effectiveness.




Accelerometer Registers

wr_reg

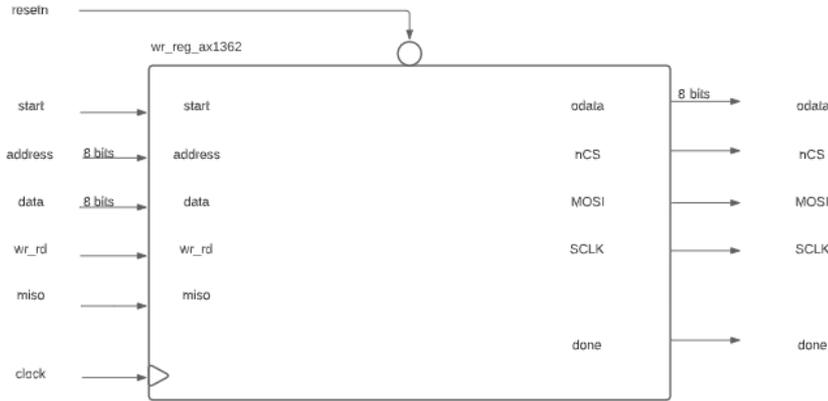

- Wr_reg is made of shift register, primarily, and other components all utilizing a finite state machine to process the data given

register

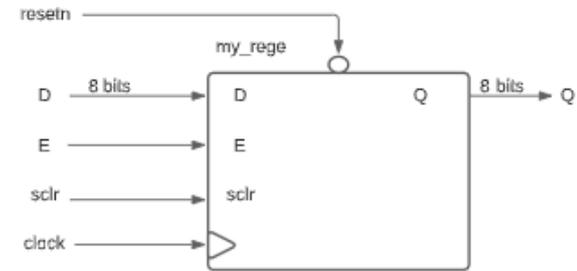

- 8-bit register with enable



wr_reg_ADXL362

- Modulo-8 Counter
- Shift Registers (To Read the address and data for the correct mode)
 - Address (0x2D) allows writing on the register and reading from X, Y, Z data
 - Data allows the FSM to eventually reach measurement mode (0x02)
- FSM is used mainly to read data and make sure SPI communication is correctly done




Things to Improve

- Smoother Color change
- Limitation with the Green LED not really affected by orientation (Less variety)
- Dedicating more bits to each LED instead of 4 bits (More variety)
- Limitation with low precision X, Y, and Z values



Backup Demo-Video

 

https://drive.google.com/file/d/18-S0khEEsZucu41_RXv80wXxLXT6weCo/view?u