


# Digital Stopwatch

---

Elena Huizar, Emilee Otten, Patty Hasa
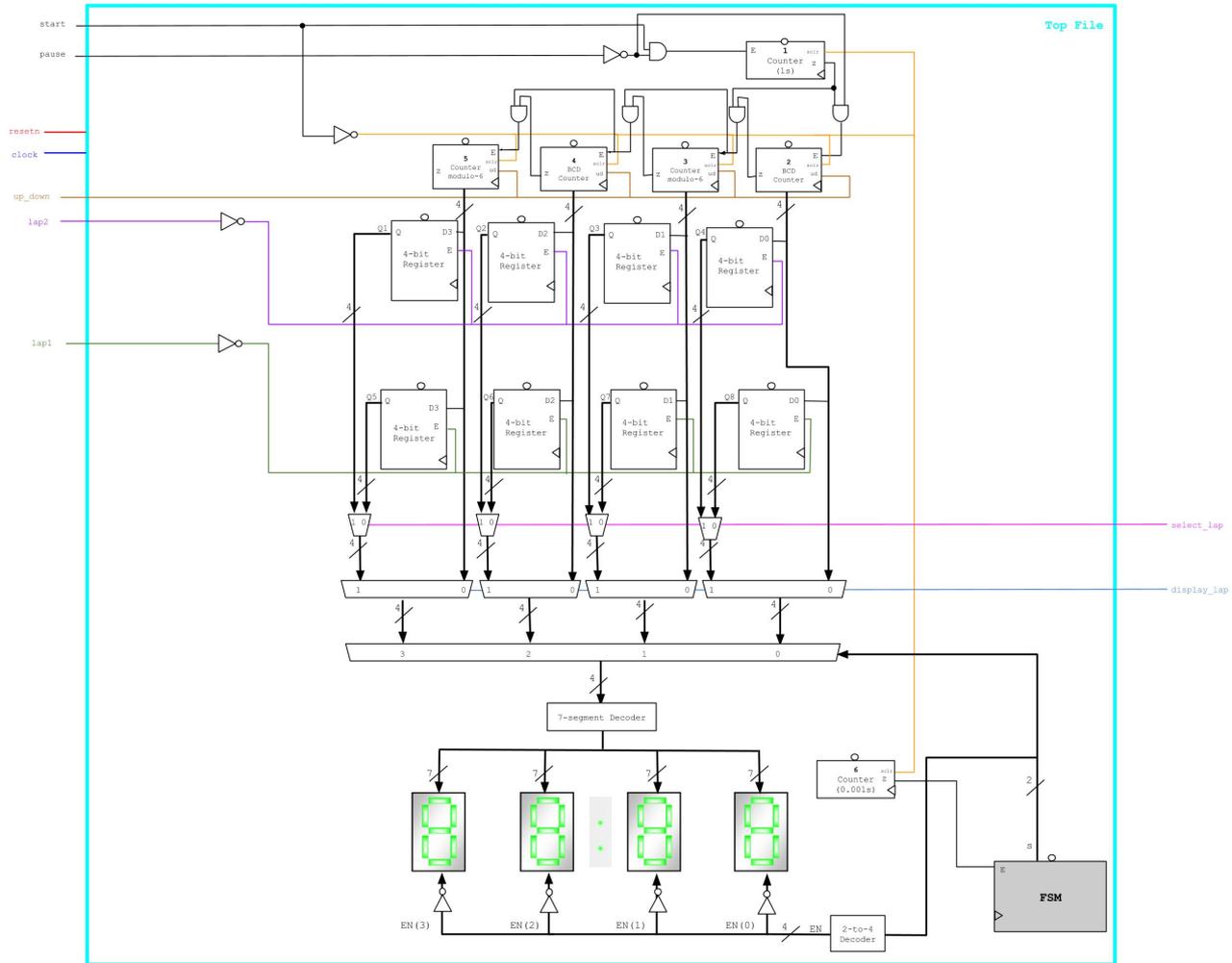
# Functionality of Stopwatch

- Counts minutes and seconds
- Can count up or down in time
- Lap capabilities
  - Records up to two lapped values
- Displays current or lapped time on seven-segment displays
  - Possible through implementation on Basys-3 board



# Main Components of Digital System


---



# Laps and Lap Displays

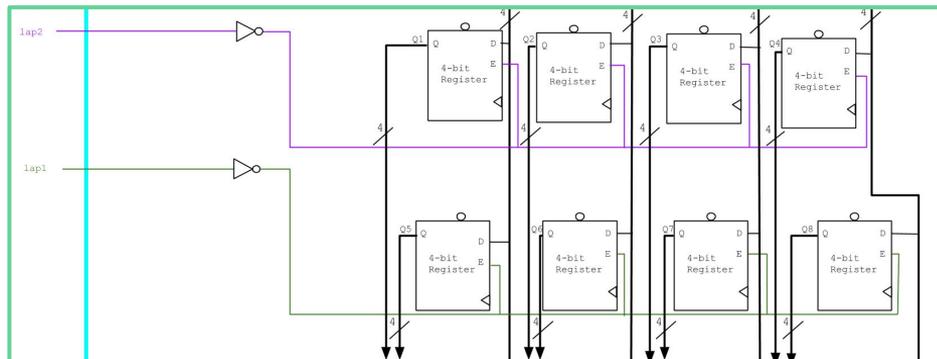
## Lapping of Time

- Two sets of four four-bit registers
- Register enables controlled by a NOT gate and a switch
  - $lap2 = '1'$  → activates memory state of first set of registers
  - $lap1 = '1'$  → activates memory state of second set of registers


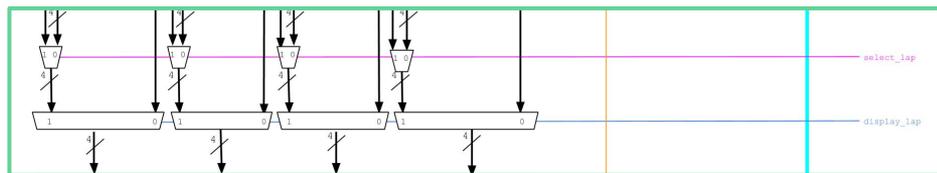
## Displaying of Lap

- $select\_lap$ 
  - Selects the first or second lap
- $display\_lap$ 
  - Displays current time or lapped time





# FSM

- **ASM Chart**


- Functionality of FSM
- State  $S$  is used as:
  - Selector in 4-to-1 Mux
  - Input to 2-to-4 decoder

- **Displays current count or lapped time**

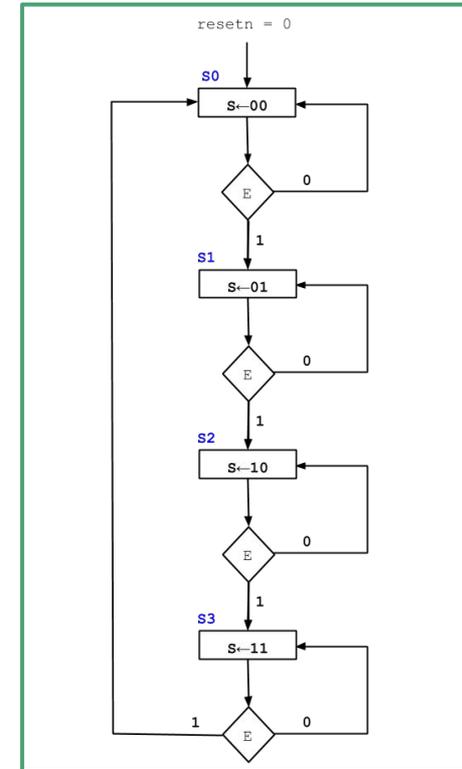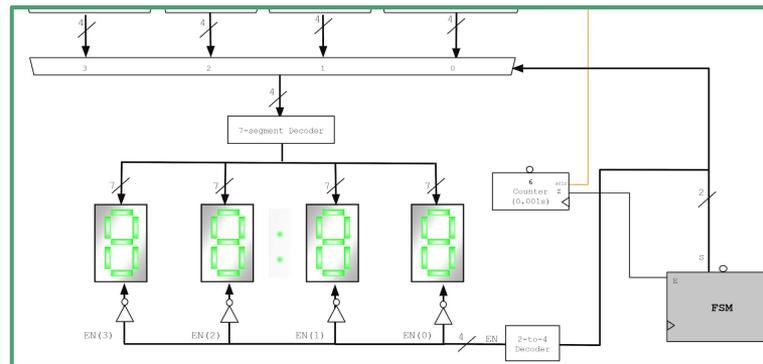- $E\_fsm$  wired to  $z$  of counter to display every 0.001s



# Our Stopwatch at Work

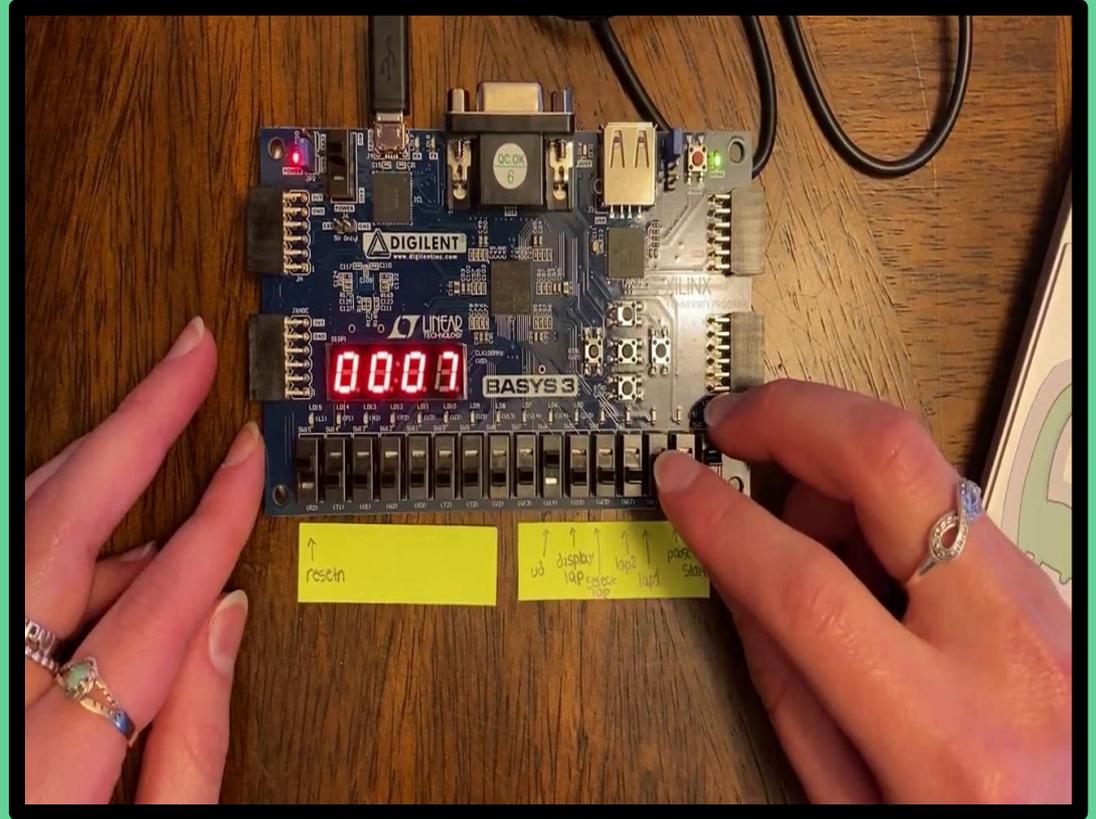

[https://drive.google.com/file/d/1qtMjPt\\_YUe1DLOftuVjQ\\_FgYC6ToEedz/view?usp=sharing](https://drive.google.com/file/d/1qtMjPt_YUe1DLOftuVjQ_FgYC6ToEedz/view?usp=sharing)