

Solutions - Quiz 1

(September 28th @ 5:30 pm)


PROBLEM 1 (35 PTS)

- Complete the timing diagram of the logic circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;


entity test is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end test;

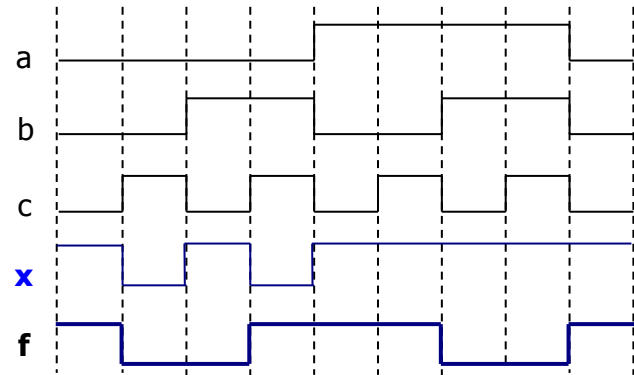architecture struct of test is
    signal x: std_logic;
begin
    f <= x xnor (not (b));
    x <= a or (not (c));
end struct;
```



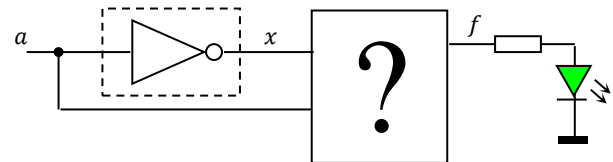
PROBLEM 2 (30 PTS)

- Design a circuit that verifies the logical operation of a NOT gate. f='1' (LED ON) if the NOT gate does not work properly. Assumption: when the NOT gate is not working, it generates 1's instead of 0's and vice versa.



a	x	f
0	0	1
0	1	0
1	0	0
1	1	1

$$f = \bar{a}\bar{x} + ax$$

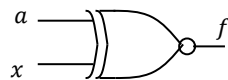

PROBLEM 3 (35 PTS)

- The following is the timing diagram of a logic circuit with three inputs. Simplify the Boolean expression of the circuit and sketch the minimized circuit.

ab	00	01	11	10
c				
0	0	0	1	0
1	1	0	1	1

$$f = ab + \bar{b}c$$

