

VHDL Digital Stopwatch

ECE2700 Final Project




By Colin Steed, Eduardo Garcia, David Dzierzawski, Muhammad Imtiaz

ECE2700 - Digital Logic Design

Presented on 12/6/21

Our Objective

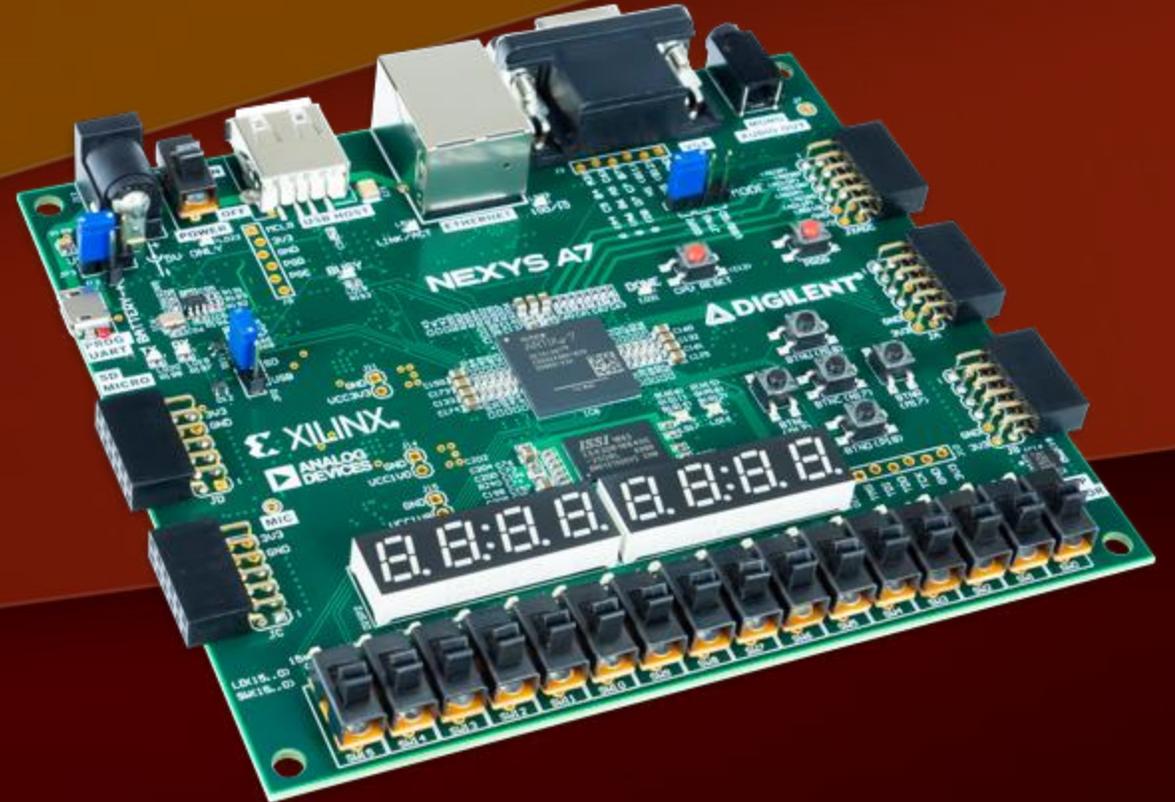- We wanted to create a fully functional Digital Stopwatch
- We will be using the Nexys A7 Programmable Board
- Our Stopwatch can Display:
 - Hours
 - Minutes
 - Seconds
 - Hundredths of Second
 - Tenths of Second
- Watch Features Include:
 - Start
 - Pause
 - Reset
 - Lap
- Our Stopwatch is able to Store up to Four Lap Times




Board Layout & Controls

- Our Stopwatch will utilize the Pushbuttons and Switches for the Watch Controls
- Switch #0 - Switch #3 (SW0-SW3) are utilized to display its designated Lap Time
- Switch #15 (SW15) is utilized for the Start/Stop Feature
- The Up Button (BNTU) is utilized to toggle and record the lap times
- The Reset Button (CPU RESET) is utilized to Reset the Stopwatch




System Power On

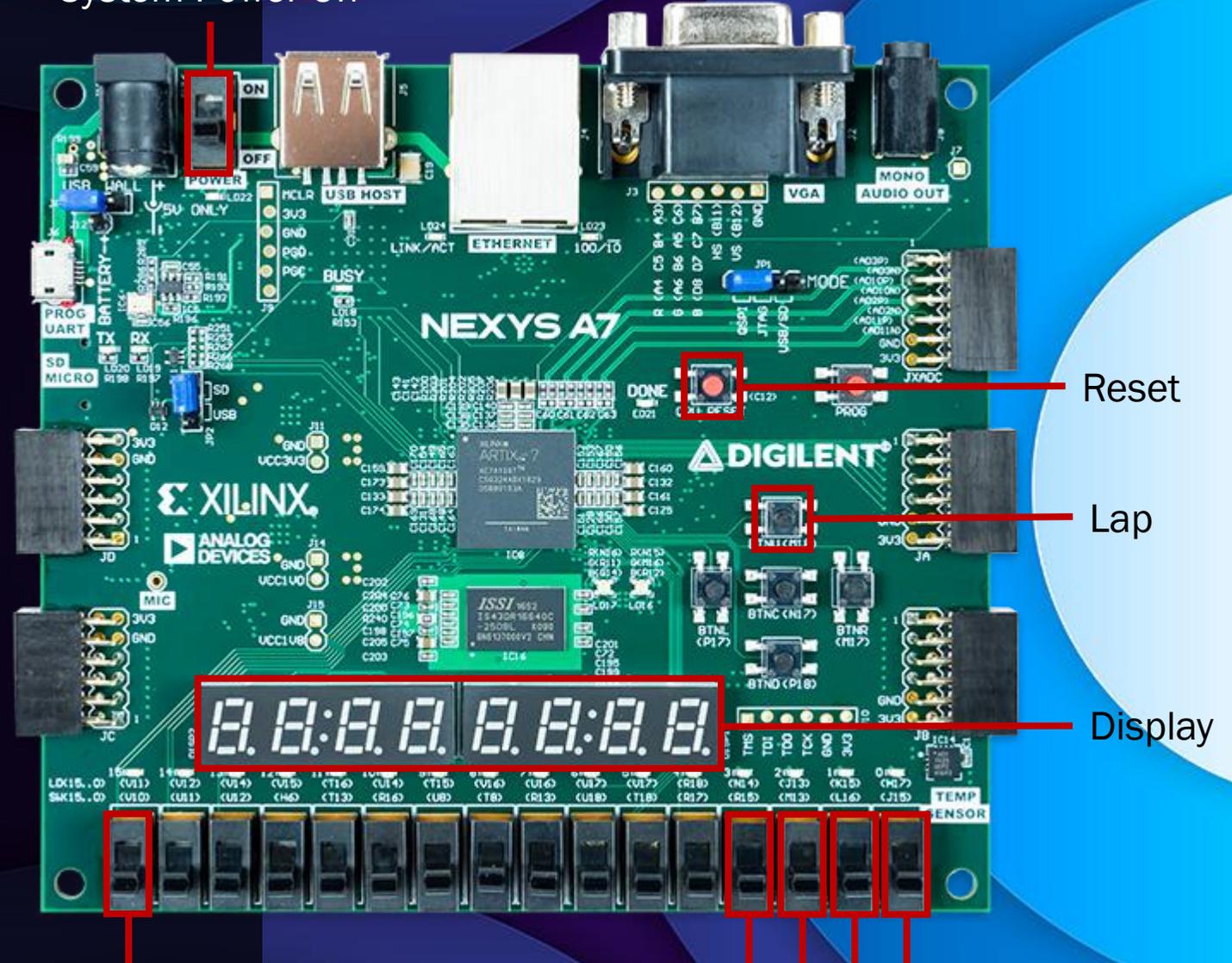


Start/Stop

Display Lap Times: 4 3 2 1


The Display

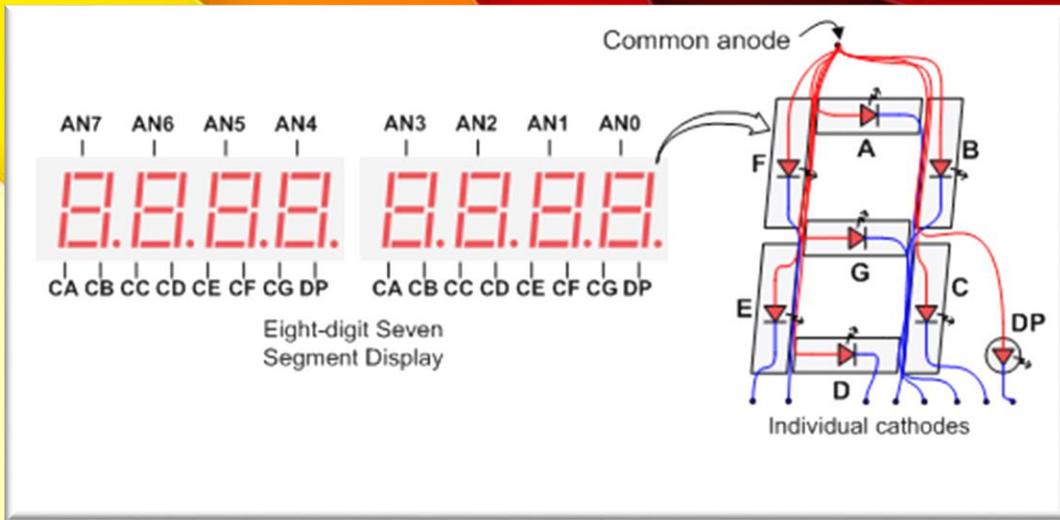

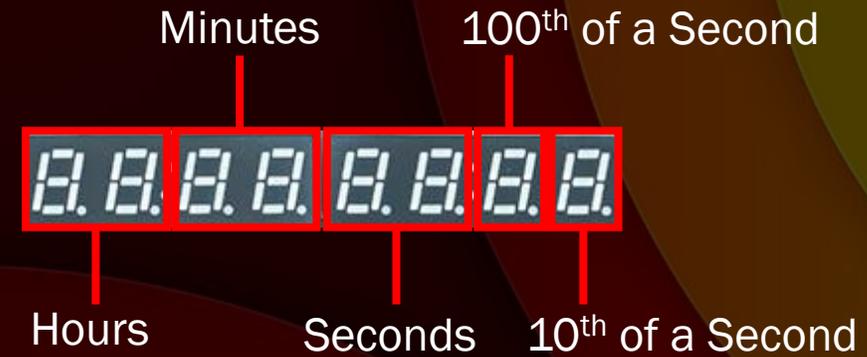- The Nexys A7 board contains two four-digit common anode seven-segment LED displays
- They are configured to behave like a single eight-digit display
- On the left is an example of illuminated numbers 1-9 being displayed on a seven-segment LED display
- The diagram below shows the configuration of the display inputs



Stopwatch System Layout

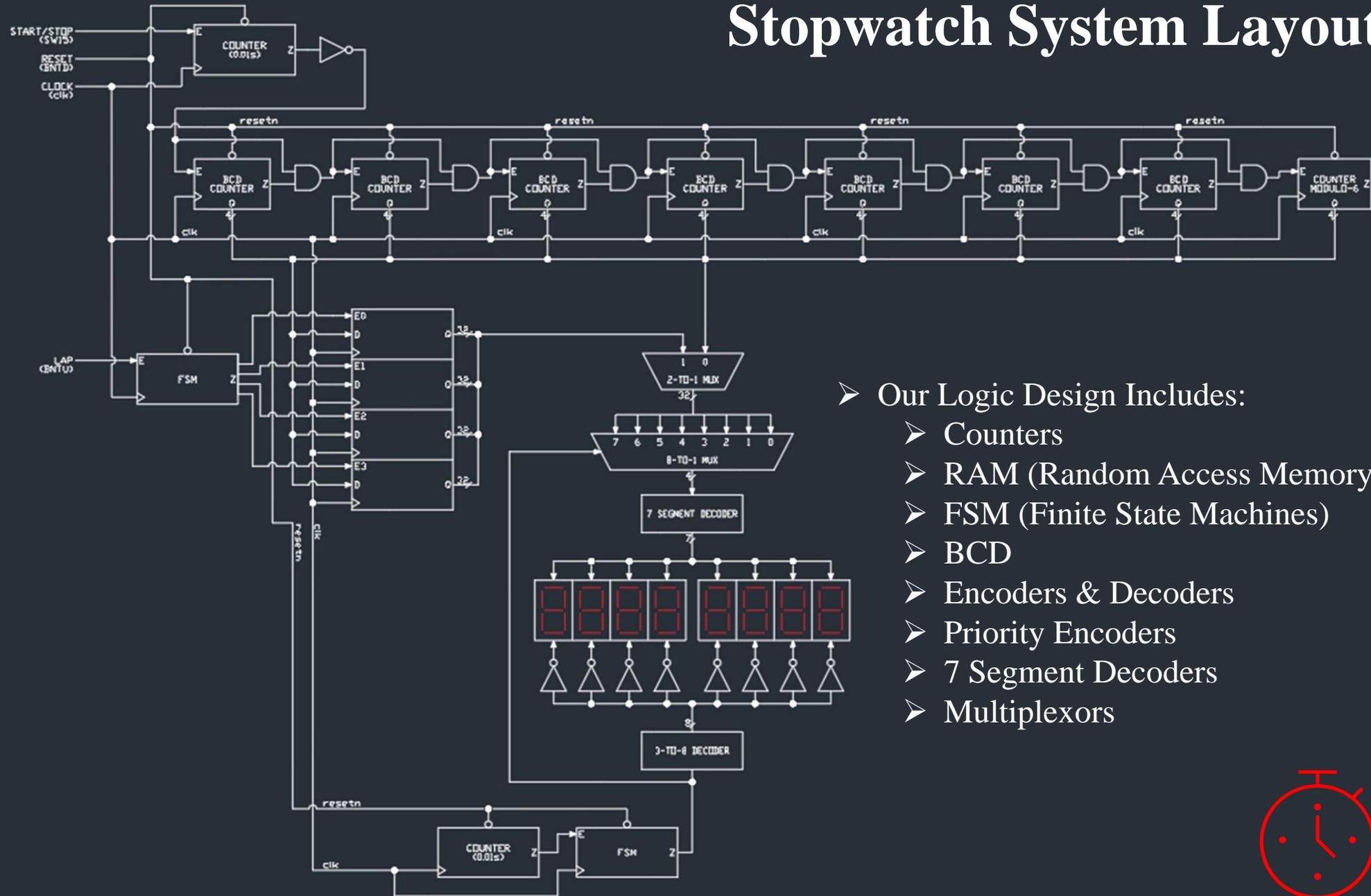


➤ Our Logic Design Includes:

- Counters
- RAM (Random Access Memory)
- FSM (Finite State Machines)
- BCD
- Encoders & Decoders
- Priority Encoders
- 7 Segment Decoders
- Multiplexors




Finite State Machine

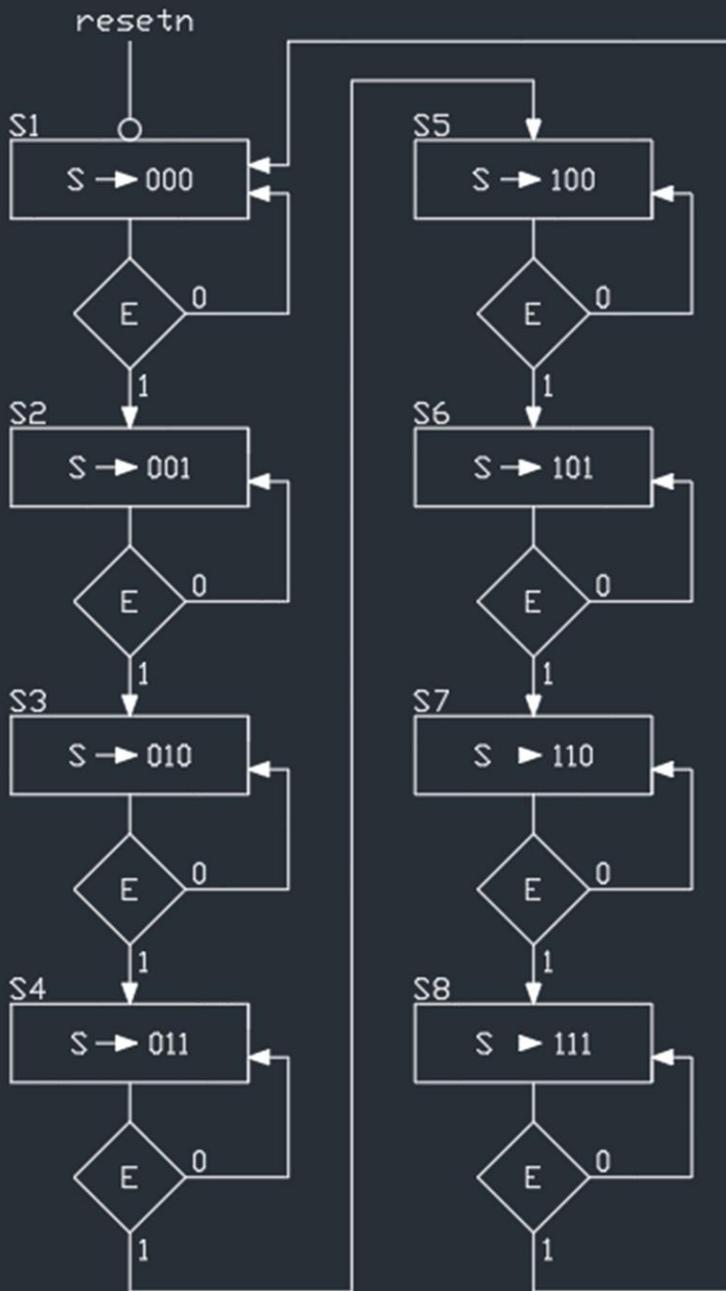- Our FSM has eight states
- Each state is associated to a specific Seven Segment Display
- The FSM is controlled by a 1ms counter
- The FSM shifts between states in coordination with the counter and sends its values to the output 'S'




BCD Counter

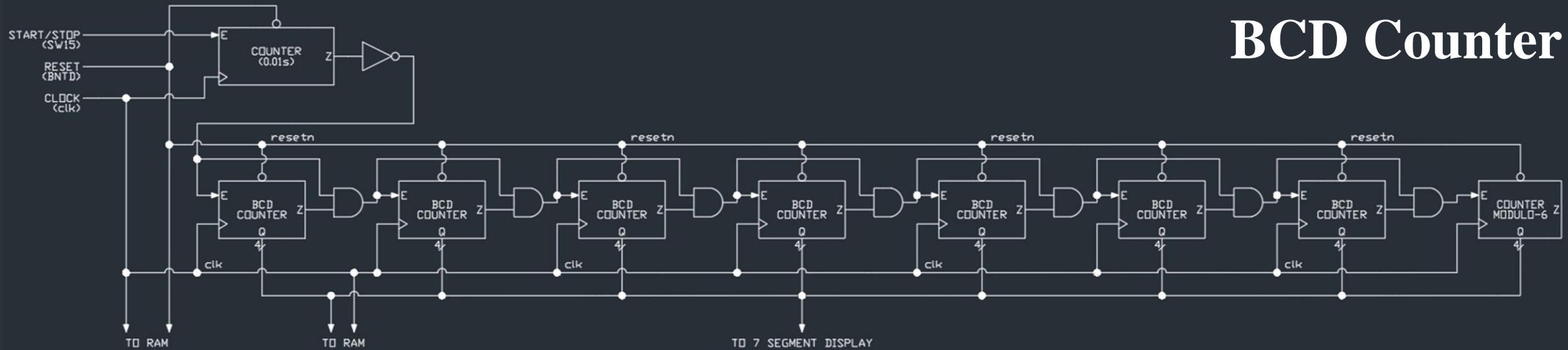

- Our Logic utilizes Nine counters
- The lead counter increments by a hundredth of a second (0.01s) and feeds into the rest of the counters
- Switch #15 (SW15) is utilized for the Start/Stop Feature
- The Counters then feed into the RAM system and the Seven Segment Display System



Random Access Memory

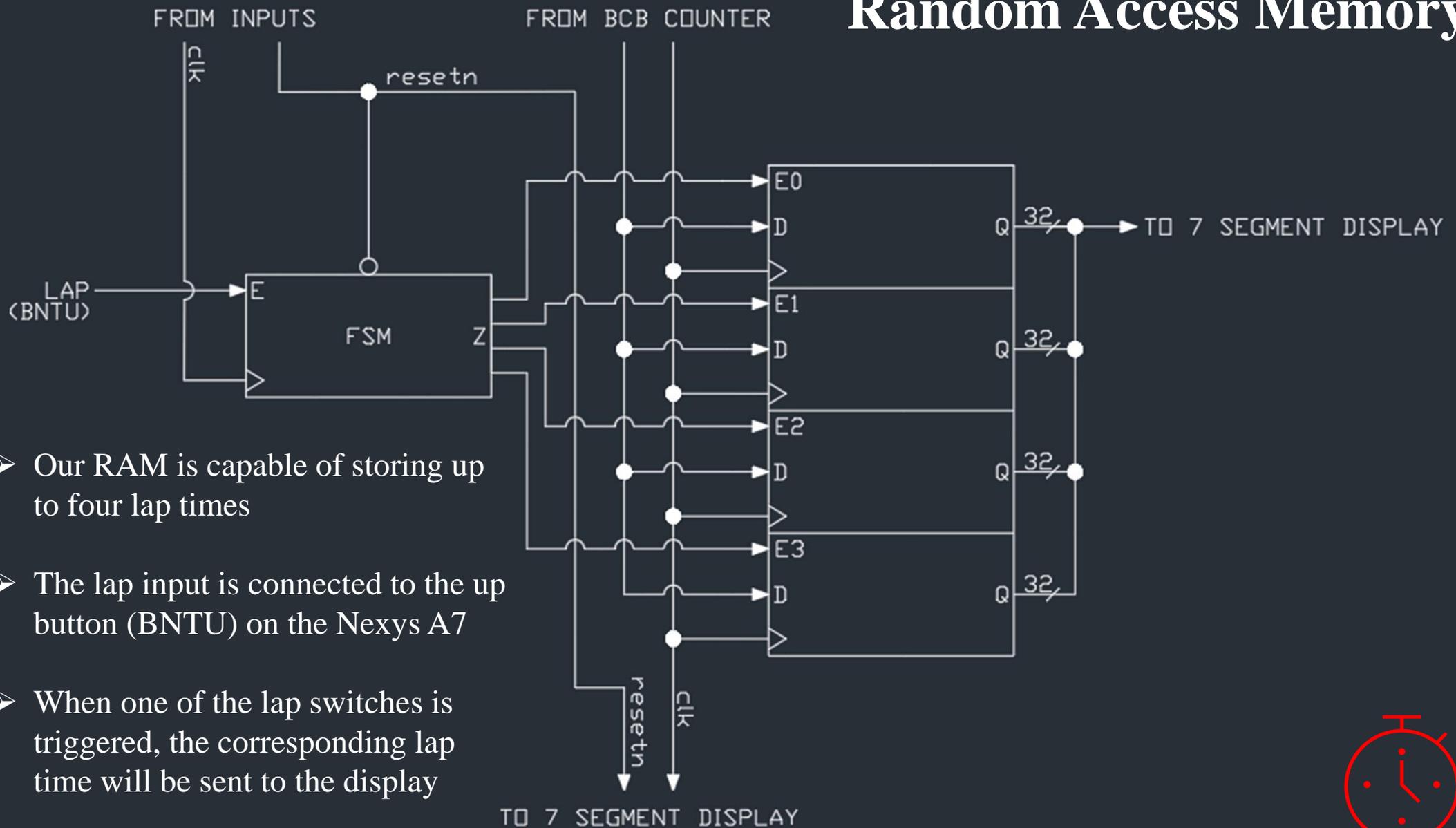


- Our RAM is capable of storing up to four lap times
- The lap input is connected to the up button (BNTU) on the Nexys A7
- When one of the lap switches is triggered, the corresponding lap time will be sent to the display



Seven Segment Display

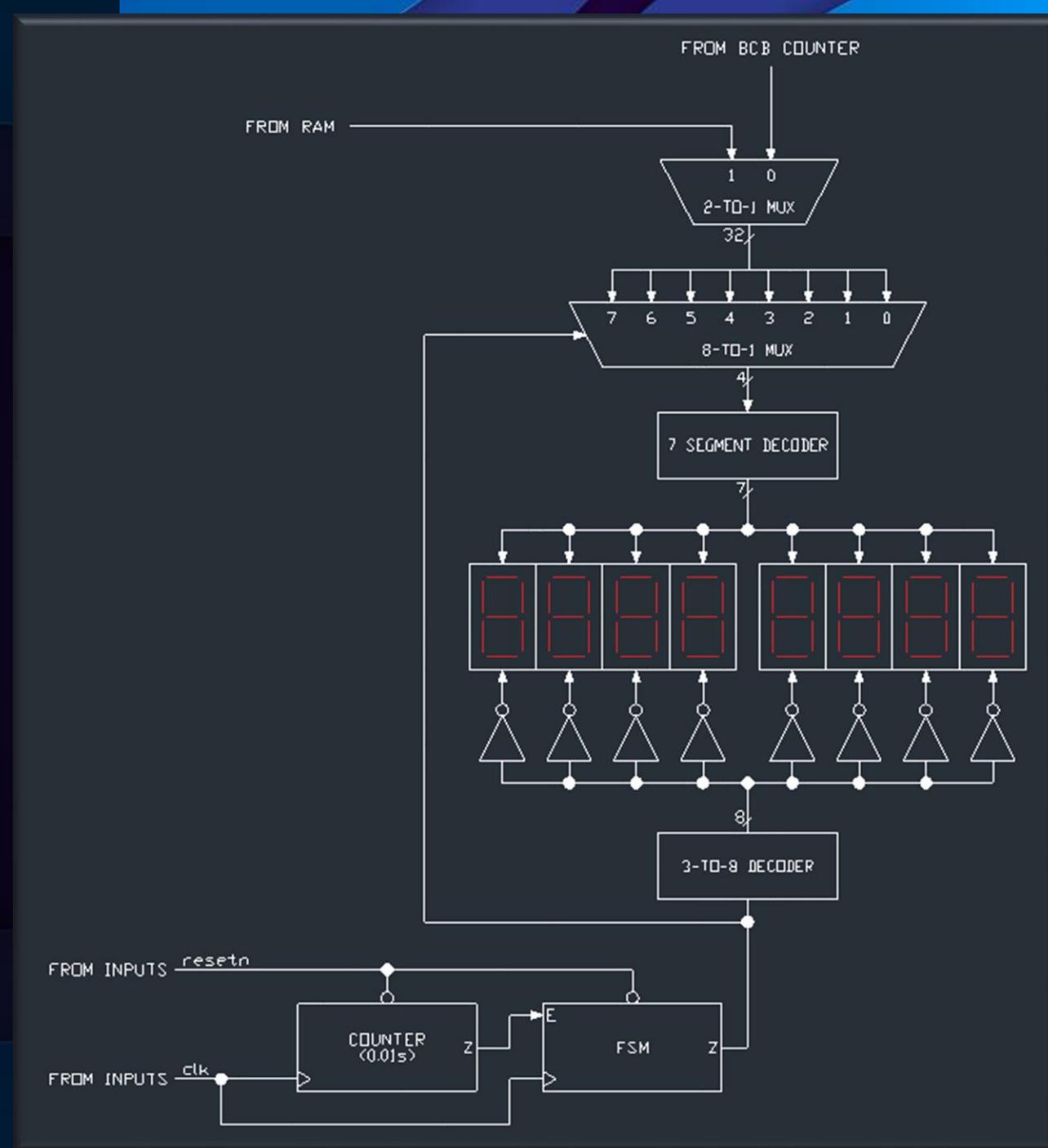- The display is controlled by a 2-to-1 Mux to determine whether a lap time will be displayed, or the current watch time is displayed
- Following the 2-to-1 Mux is an 8-to-1 Mux and a 7 Segment Decoder
- The Up Button (BNTU) is utilized to toggle and record the lap times
- The First Four Switches: (SW0-SW3) are utilized to display its designated Lap Time



Thank You For Listening

VHDL Digital Stopwatch

ECE2700 Final Project

By Colin Steed, Eduardo Garcia, David Dzierzawski, Muhammad Imtiaz

ECE2700 - Digital Logic Design

Presented on 12/6/21



References

<https://digilent.com/reference/programmable-logic/nexys-a7/reference-manual>

<http://www.secs.oakland.edu/~llamocca/index.html>