


# 4 Way Traffic Light Controller

Cali Malone, Bianca Muller, Azra Jakupovic,  
Marielly Perez



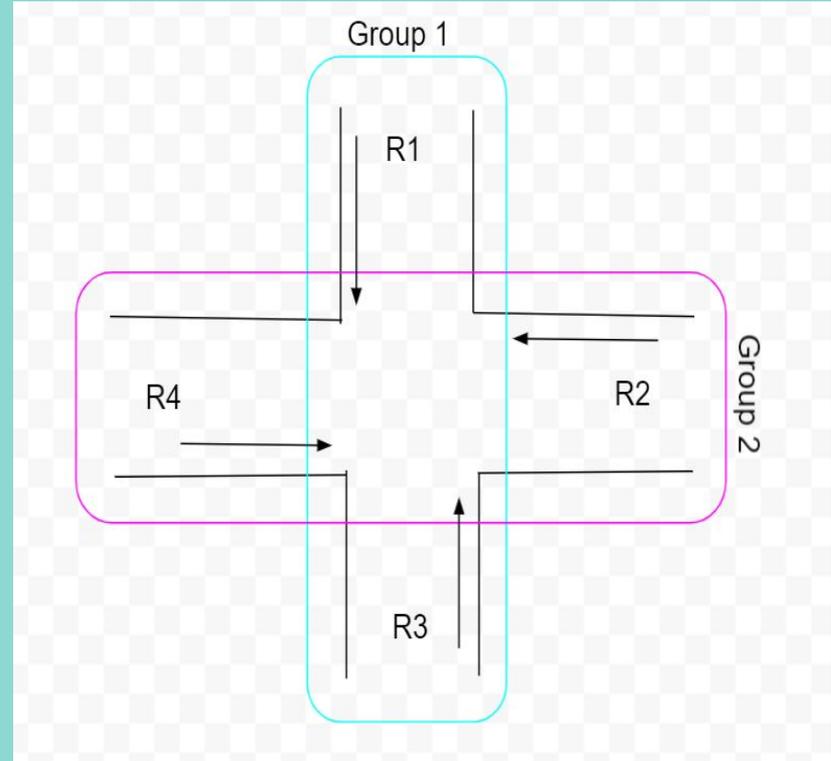
# Methodology


- A 4 way traffic light controller was created in order to simulate a real life scenario of how traffic light timing works in an intersection.
  - The traffic lights are divided into two perpendicular groups. One group goes north and south and the other goes from east and west.
  - When group 1 is green, group 2 will be red, and vice versa.
  - Each group will have different timing for the yellow and then green lights so that the cars may slow down before they transition to red.
  - There will be a period where both groups will be red, acting as the reset of the cycle.
- 
- **Hardware:** Artix-7 Nexys A7 DDR Board
  - **Software:** Xilinx Vivado using VHDL



# Circuit for Traffic Light

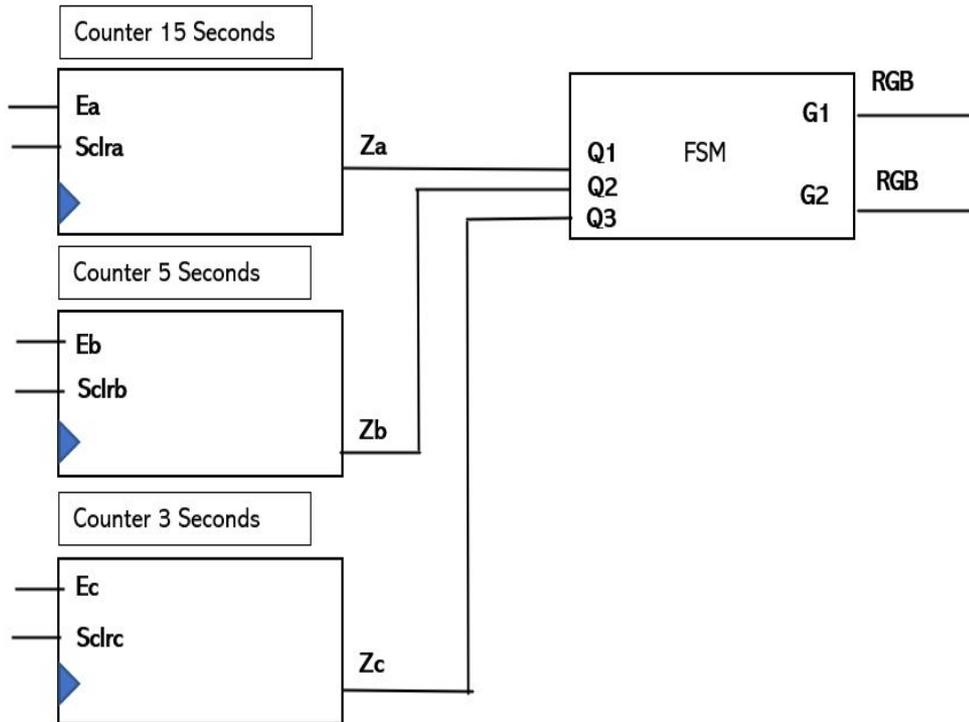

- We will be utilizing 3 counters and an FSM machine.
- Each counter will be responsible for a specific period of time.
- We have 6 inputs in total from the counters
  - **Ea, and Sclra** - inputs for the first counter.
  - **Eb, and Sclrb** - inputs for the second counter.
  - **Ec and Sclrc** - inputs for the third counter.
  - **Q1** - Input from **Za**
  - **Q2**- Input from **Zb**
  - **Q3**- Input from **Zc**
- The output from the FSM will be
  - **G1**- Group 1 for **RGB**
  - **G2**- Group 2 for **RGB**

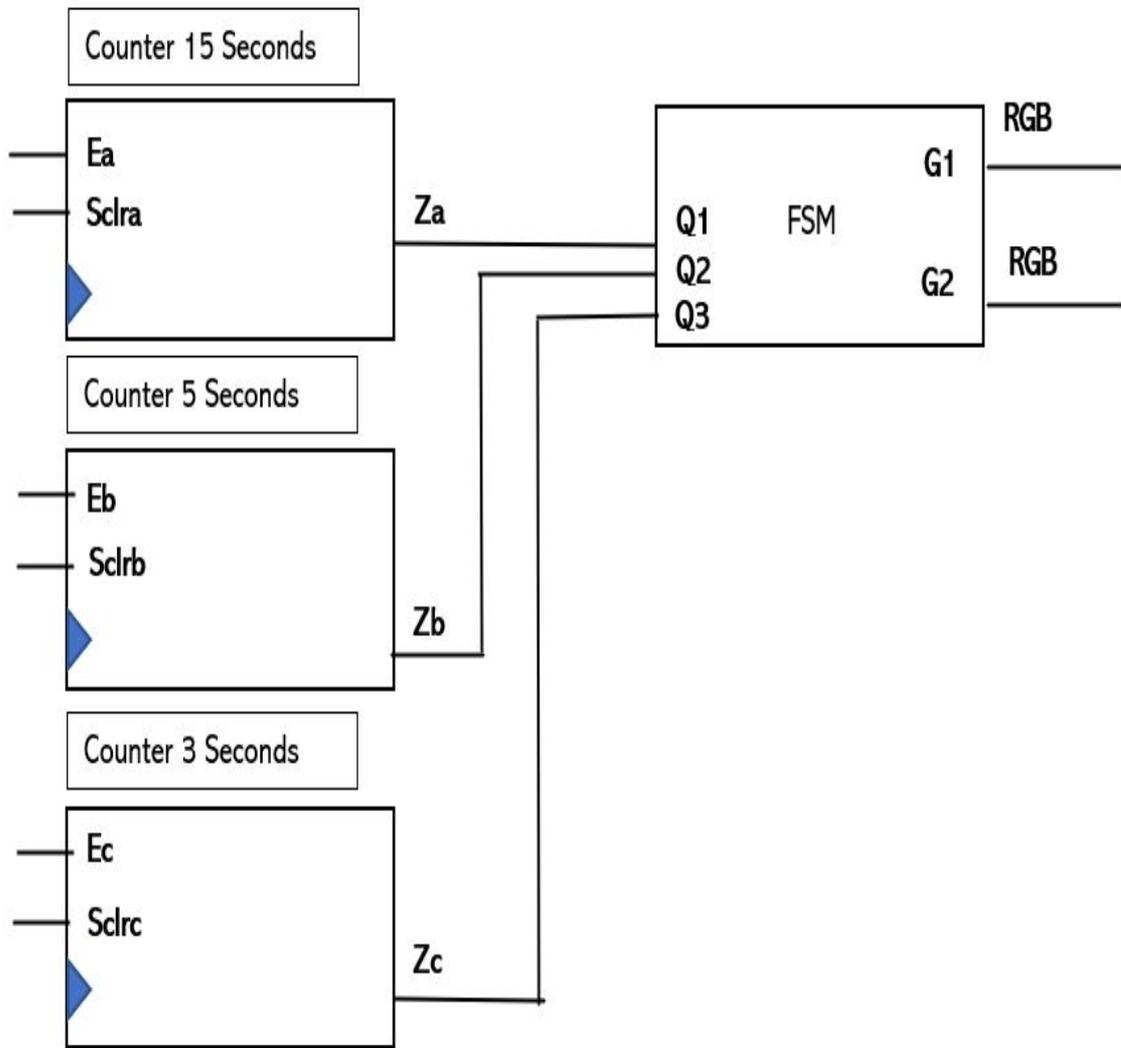

## Counter :

This counter will be used to sequence pulses. This digital device is a form of a flip-flop.

- Counter A will pulse the clock for 15 seconds.
- Counter B will pulse the clock for 5 seconds.
- Counter C will pulse the clock for 3 seconds.

## FSM :

FSMs are used to represent system with a finite number of states. In our case it will have states S1-S5, which will control the RBG lights.

- States S1-S5 will be controlled by
- Inputs **Q1, Q2, Q3**
  - Outputs **G1, G2**

# Inputs/ Outputs

Name	Inputs	Outputs
Counter 1	Ea	Za
	Sc1ra	
Counter 2	Eb	Zb
	Sc1rb	
Counter 3	Ec	Zc
	Sc1rc	
FSM	Q1, Q2, Q3	G1, G2, RGBs

<b>Group 1</b>	Green	Yellow
<b>Group 2</b>	Red	
<b>Time (seconds)</b>	15	5

<b>Group 2</b>	Green	Yellow
<b>Group 1</b>	Red	
<b>Time (seconds)</b>	15	5

<b>Group 1</b>	Red	
<b>Group 2</b>	Red	
<b>Time (seconds)</b>	3	

Outputs	Group	Signal	Description
Road 1 Road 3	1	G1G	Group 1 Green Light
		G1Y	Group 1 Yellow Light
		G1R	Group 1 Red Light
Road 2 Road 4	2	G2G	Group 2 Green Light
		G2Y	Group 2 Yellow Light
		G2R	Group 2 Red Light


- Road 1 and 3, which are relatively N and S are in Group 1, represented with **(G1G)** for green, **(G1Y)** for yellow, **(G1R)** for red.
- Road 2 and 4, which are relatively E and W will be Group 2, represented with **(G2G)** for green, **(G2Y)** for yellow, **(G2R)** for red.
- Group 1 will be green for 15 seconds, and yellow sequentially following for 5 seconds. Simultaneously, group 2 will be red for the entirety of the 20 seconds.
- Afterwards, both groups will be red for 3 seconds serving as a reset. This will allow all the cars to come to a halt before the process cycles again.
- The process is the same vice versa for Group 2.

# State Table/Excitation Table

Input (za   zb   zc)			Present State	Next State	Output	
1	X	X	S1	S2	G1G	G2R
X	1	X	S2	S3	G1Y	G2R
X	X	1	S3	S4	G1R	G2R
1	X	X	S4	S5	G1R	G2G
X	1	X	S5	S3	G1R	G2Y
0	X	X	S1	S1	G1G	G2R
X	0	X	S2	S2	G1Y	G2R
X	X	0	S3	S3	G1R	G2R
0	X	X	S4	S4	G1R	G2G
X	0	X	S5	S5	G1R	G2Y

Input (za   zb   zc)			Present State	Next State	Output (G1   G2)	
1	X	X	000	001	010	100
X	1	X	001	010	110	100
X	X	1	010	011	100	100
1	X	X	011	100	100	010
X	1	X	100	010	100	110
0	X	X	000	000	010	100
X	0	X	001	001	110	100
X	X	0	010	010	100	100
0	X	X	011	011	100	010
X	0	X	100	100	100	110

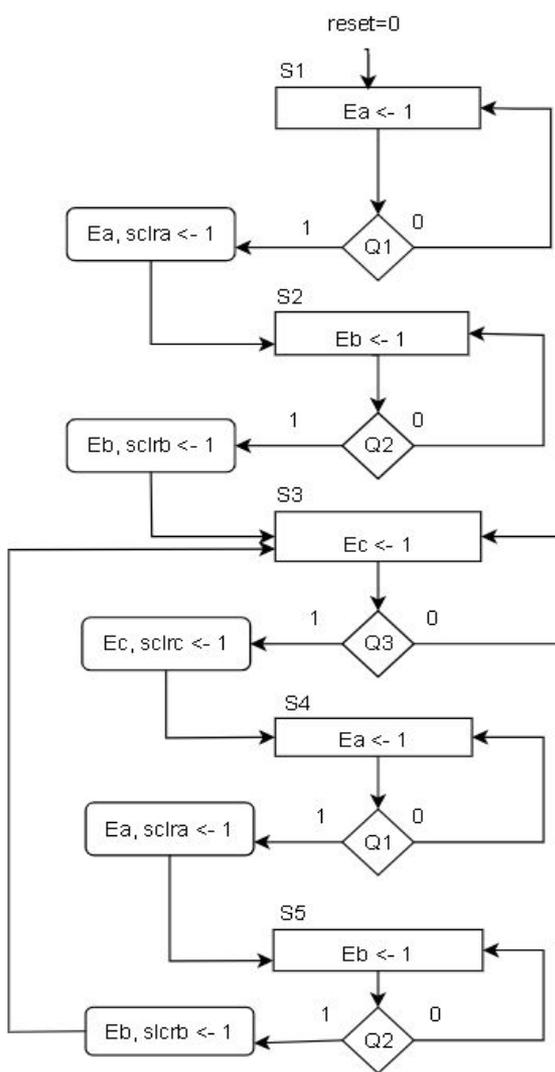- Inputs za, zb, and zc control the states.
- Only one input is need at a time.
- When za, zb, or zc is 1 it will prompt the circuit to move to the next state.
- If za, zb, or zc is 0, the circuit remains in the same state.
- When the input in S3 is 1, it changes to S4.



### S1:

- In S1 Group 1 would be green and Group 2 would be red.
- When **Q1 = 0** stays in S1.
- When **Q1 = 1** the state changes **S2** the counter runs for 15 seconds. sclra will also be **1**. While **Ea** will always be **1**.

### S2:

- In S2 Group 1 would be yellow and Group 2 would stay red.
- **Q2 = 0** stays in S2.
- **Q2 = 1** the state changes to **S3** and the counter runs for 5 seconds. sclrb will also be 1. While **Eb** will always be 1.

### S3:

- In S3 Group 1 would be red and Group 2 would be red.
- **Q3 = 0** stays in S3.
- **Q3 = 1** the state changes to **S4** and the counter runs for 3 seconds. Scrc will also be 1. While **Ec** will always be 1.
- **S3** is the rest state where both lights will be red.

### S4:



- In S4 Group 1 would stay red and Group 2 would be green.
- **Q1 = 0** stays in S4.
- **Q1 = 1** the state changes to **S5**, and the counter runs for 15 seconds. sclra will also be 1. While **Ea** will always be 1.

### S5:

- In S5 Group 1 would stay red and Group 2 would be yellow..
- **Q2 = 0** goes to S5.
- **Q2 = 1** changes the state to **S3** and the counter runs for 5 seconds.. sclrb will also be 1. While **Eb** will always be 1.



# Simulation

 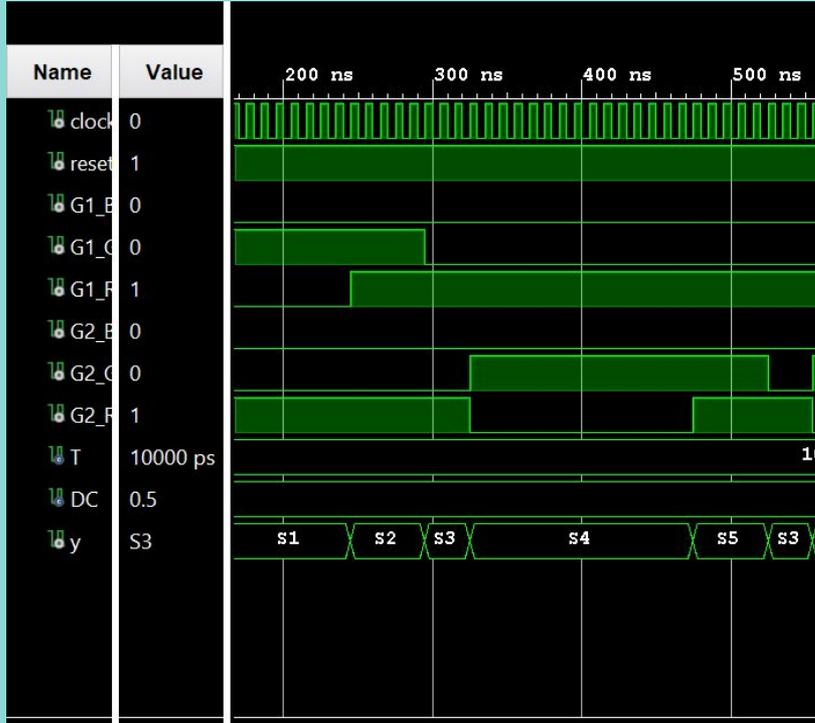



# References

[1] Llamocca. “RECRLab.” *VHDL Coding for Fpgas*,  
<http://www.secs.oakland.edu/~llamocca/VHDLforFPGAs.html>.

[2] “Finite State Machines: Sequential Circuits: Electronics Textbook.” *All About Circuits*,  
<https://www.allaboutcircuits.com/textbook/digital/chpt-11/finite-state-machines/>.

[3] “Digital Circuits - Finite State Machines.” *Digital Circuits - Finite State Machines*,  
[https://www.tutorialspoint.com/digital\\_circuits/digital\\_circuits\\_finite\\_state\\_machines.htm](https://www.tutorialspoint.com/digital_circuits/digital_circuits_finite_state_machines.htm).

[4] *Vivado Tutorial - Xilinx*.  
[https://www.xilinx.com/support/documentation/university/Vivado-Teaching/HDL-Design/2013x/Nexys4/Verilog/docs-pdf/Vivado\\_tutorial.pdf](https://www.xilinx.com/support/documentation/university/Vivado-Teaching/HDL-Design/2013x/Nexys4/Verilog/docs-pdf/Vivado_tutorial.pdf).