

Laboratory 1

(Due date: **004/011**: Sep. 21st, **005**: Sep. 22nd, **007**: Sep. 23rd)

OBJECTIVES

- ✓ Introduce VHDL Coding for FPGAs.
- ✓ Learn to write testbenches in VHDL.
- ✓ Learn the Xilinx FPGA Design Flow with the Vivado HL: Synthesis, Simulation, and Bitstream Generation.
- ✓ Learn how to assign FPGA I/O pins and download the bitstream on the Nexys™ A7-50T Board.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

NEXYS™ A7-50T FPGA TRAINER BOARD SETUP

- The Nexys A7-50T Board can receive power from the Digilent USB-JTAG Port (J6). Connect your Board to a computer via the USB cable. If it does not turn on, connect the power supply of the Board.
- Nexys A7-50T documentation: Available in [class website](#).

FIRST ACTIVITY (100/100)

DESIGN PROBLEM

- A lock is opened ($f=1$) only for three combinations of four switches: 0111, 1001, 0101, where '1' represents the ON state of the lock and '0' the OFF state. The state of the switches is represented by the Boolean variables a, b, c, d.

- ✓ Complete the truth table for this circuit: (5 pts)

- ✓ Derive (simplify if possible) the Boolean expression: (10 pts)

$f =$

a	b	c	d	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

PROCEDURE

- **Vivado Design Flow for FPGAs: complete the following steps (follow the order strictly): (85 pts)**

- ✓ Create a new Vivado Project. Select the corresponding Artix-7 FPGA device as per the table:

Kit	Artix-7 FPGA Device	Master XDC File	Comments
Nexys A7-50T	XC7A50T-1CSG324I	Nexys-A7-50T-Master.xdc	Recommended board.
Nexys A7-100T	XC7A100T-1CSG324C	Nexys-A7-100T-Master.xdc	
Basys 3	XC7A35T-1CPG236C	Basys-3-Master.xdc	Suggested if you only take ECE2700
Nexys 4 Nexys 4 DDR	XC7A100T-1CSG324C	Nexys4_Master.xdc Nexys4DDR_Master.xdc	Discontinued

- ✓ Write the VHDL code that implements the simplified Boolean expression. Synthesize your circuit (Run Synthesis).

