



Solutions - Homework 4

(Due date: November 17th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

  
PROBLEM 1 (14 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1011$, $Q = Q_3Q_2Q_1Q_0$



 
PROBLEM 2 (18 PTS)

- Sequence detector: The machine generates $z = 1$ when it detects the sequence 0110. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E=1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation) of this circuits with inputs E and x and output z. (5 pts)
- Complete the State Table and the Excitation Table. (4 pts)
- Provide the excitation equations and the Boolean output equation (simplify your circuit: K-maps or Quine-McCluskey) (5 pts)
- Sketch the circuit. (3 pts)
- Which type is this FSM? (Mealy) (Moore) Why? _____

 State Diagram, State Table, and Excitation Table:



State Assignment:
S1: Q=00 S2: Q=01
S3: Q=10 S4: Q=11

E	x	PRESENT STATE	NEXT STATE	z	PRESENT STATE				NEXT STATE				
		STATE	STATE		E	x	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1)	z				
0	0	S1	S1	0	0	0	0	0	0	0	0	0	0
0	0	S2	S2	0	0	0	0	1	0	0	1	0	0
0	0	S3	S3	0	0	0	1	0	1	0	0	0	0
0	0	S4	S4	0	0	0	1	1	1	1	0	0	0
0	1	S1	S1	0	0	1	0	0	0	0	0	0	0
0	1	S2	S2	0	0	1	0	1	0	1	0	0	0
0	1	S3	S3	0	0	1	1	0	0	1	0	0	0
0	1	S4	S4	0	0	1	1	1	1	1	0	0	0
1	0	S1	S2	0	1	0	0	0	0	1	0	0	0
1	0	S2	S2	0	1	0	0	1	0	0	1	0	0
1	0	S3	S2	0	1	0	1	0	0	1	0	0	0
1	0	S4	S1	1	1	0	1	1	0	0	0	0	1
1	1	S1	S1	0	1	1	0	0	0	0	0	0	0
1	1	S2	S3	0	1	1	0	1	1	0	1	0	0
1	1	S3	S4	0	1	1	1	0	1	1	0	0	0
1	1	S4	S1	0	1	1	1	1	1	1	0	0	0

This is a Mealy Machine. The output z depends on the input as well as on the present state.

Excitation equations, minimization, and circuit implementation:


$$Q_1(t+1) \leftarrow \bar{E}Q_1(t) + ExQ_1(t)Q_0(t) + xQ_1(t)Q_0(t)$$

$$Q_0(t+1) \leftarrow \bar{E}Q_0(t) + E\bar{x}Q_1(t) + EQ_1(t)Q_0(t)$$

$$z = E\bar{x}Q_1(t)Q_0(t)$$


Q ₁ Q ₀	Ex			
	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	0	0
10	1	1	1	0

Q ₁ Q ₀	Ex			
	00	01	11	10
00	0	0	0	1
01	1	1	0	1
11	1	1	0	0
10	0	0	1	1

 


 
PROBLEM 3 (35 PTS)

- The following FSM has 4 states, one input w and one output z. (10 pts)
 - The excitation equations are given by:
 - $Q_1(t+1) \leftarrow Q_0(t)$
 - $Q_0(t+1) \leftarrow Q_1(t) \oplus w$
 - The output equation is given by: $z = Q_1(t) \oplus Q_0(t) \oplus w$
- Provide the State Diagram (any representation) and the Excitation Table.
- Sketch the Finite State Machine circuit.




PRESENT STATE		NEXT STATE		z
w	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1)	z	
0	00	01	0	0
0	01	11	1	1
0	10	00	1	1
0	11	10	0	0
1	00	00	1	1
1	01	10	0	0
1	10	01	0	0
1	11	11	1	1

 

 

 - Given the following State Machine Diagram. (10 pts)
 - Is this a Mealy or a Moore machine? Why?
 - Provide the State Table and the Excitation Table. (3 pts)
 - Get the excitation equations and the Boolean equation for z. (6 pts)
- Use S0 (Q=00), S1 (Q=01), S2 (Q=10), S3 (Q=11) to encode the states.



PRESENT STATE		NEXT STATE		z
x	STATE	STATE	z	
0	S0	S2	0	0
0	S1	S1	0	0
0	S2	S1	0	0
0	S3	S0	1	0
1	S0	S1	0	0
1	S1	S3	0	0
1	S2	S3	0	0
1	S3	S2	0	0

x	PRESENT STATE		NEXT STATE		z
	Q ₁ Q ₀ (t)	Q ₁ Q ₀ (t+1)	z		
0	0 0	1 0	0		
0	0 1	0 1	0		
0	1 0	0 1	0		
0	1 1	0 0	1		
1	0 0	0 1	0		
1	0 1	1 1	0		
1	1 0	1 1	0		
1	1 1	1 0	0		

$$Q_1(t+1) \leftarrow x \oplus (Q_1(t) + Q_0(t))$$

$$Q_0(t+1) \leftarrow (Q_1(t) \oplus Q_0(t)) + xQ_0(t)$$


$$z = \bar{x}Q_1(t)Q_0(t)$$

This is a Mealy Machine. The output z depends on the input as well as on the present state.

- Provide the state diagram (in ASM form) and complete the timing diagram of the FSM whose VHDL description is listed below. (15 pts)


```
library ieee;
use ieee.std_logic_1164.all;

 entity myfsm is
    port ( clk, resetn: in std_logic;
          a, b: in std_logic;
          x,w,z: out std_logic);
end myfsm;
```





```
architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if b = '1' then
                        if a = '1' then y <= S3; else y <= S1; end if;
                    else
                        y <= S2;
                    end if;
                when S2 =>
                    if a = '1' then y <= S3; else y <= S2; end if;
                when S3 =>
                    if a = b then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

     Outputs: process (y, a, b)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if b = '1' then x <= '1'; end if;
            when S2 => w <= '1';
            when S3 => if a = b then z <= '1'; end if;
        end case;
    end process;
end behavioral;
```



  PROBLEM 4 (18 PTS)

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
- Refer to the Lecture Notes for more details of the behavior of the generic components.
 - Register (for P): *sclr*: synchronous clear. Here, if $E = sclr = 1$, the register contents are initialized to 0.
 - Parallel access shift registers (for A and B): If $E = 1$: $s_l = 1 \rightarrow$ Load, $s_l = 0 \rightarrow$ Shift



PROBLEM 5 (15 PTS)

- Attach a printout of your Project Status Report (no more than 3 pages, single-spaced, 2 columns). This report should contain the current status of the project, including more details about the design and its components. You **MUST** use the provided template (Final Project - Report Template.docx).