



# Final Exam

(December 12<sup>th</sup> @ 3:30 pm)

Presentation and clarity are very important! Show your procedure!

 
 
## PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 1001$ ,  $Q = Q_3Q_2Q_1Q_0$



  
## PROBLEM 2 (12 PTS)

- Given the following circuit, complete the timing diagram. The LUT 6-to-6 implements the following function:  $OLUT = \lceil \sqrt{ILUT} \rceil$ , where  $ILUT$  is a 6-bit unsigned number. For example  $ILUT = 41 (101001_2) \rightarrow OLUT = \lceil \sqrt{41} \rceil = 7 (000111_2)$




 **PROBLEM 3 (20 PTS)**

- Complete the timing diagram of the circuit shown below: (8 pts)




 - Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (12 pts)



 **PROBLEM 4 (24 PTS)**

- Sequence detector: The machine generates  $z = 1$  when it detects the sequence 1001. Once the sequence is detected, the circuit looks for a new sequence.
- The signal  $E$  is an input enable: It validates the input  $x$ , i.e., if  $E = 1$ ,  $x$  is valid, otherwise  $x$  is not valid.



- Draw the State Diagram (any representation) of this circuit with inputs  $E$  and  $x$  and output  $z$ . (7 pts.)
- Complete the State Table and the Excitation Table (8 pts.)
- Provide the excitation equations and the Boolean output equation (simplify your circuit: K-maps or the Quine-McCluskey)
- Sketch the circuit. (3 pts)
- Which type is this FSM? (Mealy) (Moore) Why? \_\_\_\_\_

**PROBLEM 5 (14 PTS)**

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. (6 pts.)
- Complete the Timing Diagram (7 pts.)
- Is it a Mealy or a Moore FSM?

```
library ieee;
use ieee.std_logic_1164.all;

entity myfsm is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end myfsm;
```

```
architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;


                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;

                when S3 =>
                    if q = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                if p = '0' then
                    z <= '1'; x <= '1';
                end if;
            end if;

            when S2 => if q = '0' then x <= '1'; end if;
                if p = '0' then w <= '1'; end if;

             when S3 => if q = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```



PROBLEM 6 (18 PTS)

- "Counting 1's" Circuit: It counts the number of bits in register *A* that has the value of '1'.
  - ✓ Example: for  $n = 8$ : if  $A = 10110110$ , then  $C = 0101$ .
  - ✓ The digital system (FSM + Datapath) is depicted below. The behavior (on the clock tick) of the generic components is as follows:

*m*-bit counter (modulo- $n+1$ ): If  $E=0$ , the count stays.

```

if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← Q+1
  end if;
end if;
    
```

*n*-bit Parallel access shift register: If  $E=0$ , the output is kept.

```

if E = 1 then
  if s_1 = '1' then
    Q ← D
  else
    Q ← shift in 'din' (to the right)
  end if;
end if;
    
```

- Complete the timing diagram where  $n = 8, m = 4$ . *A* is represented in hexadecimal format, while *C* is in binary format.

