 





The architecture 3x3 Matrix Multiplication for unsigned numbers.

Team Members: Nour Alnounou, Genbela Lifo, Maryam Yaqo, Maryam Zadoyan
e-mails: nalnounou@oakland.edu, lifo@oakland.edu,
maryamyaqo@oakland.edu, maryamzadoyan@oakland.edu.

Introduction



The project shows step-by-step the planning of the architectural design, the implementation, and the final results.

The architecture of the matrix multiplexer project was implemented through VHDL in the Xilinx Vivado Design Suite. For this project, an external keyboard was utilized as the system's input, which is connected through a USB port to the Nexys A7-100T board. The board will be programmed to turn the 8-bit input from the keyboard into a 4-bit input and to complete the 3x3 matrix. After the signal goes through the matrix process it will be converted from Hex to a 7-segment decoder which after will display the results on the board.

 

System State Diagram

- Starting from the Reset to the first state.
- After getting the data from the keyboard the done is received.
- The enable for the decoder will be one and the address 00000 is sent.
- The second enable remains 1 and Dd done for the flip flop will be 0.
- This process repeats until state 18. After the last data from the keyboard will receive the done. Then both enables and the dd will be 1 which concludes all the data and the process goes back to state 1.

  


Register

Multiplier

Mux

Serialize

FSM

 

Components used
for the circuit

Register
Mux
FSM
Decoder


$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix} \begin{bmatrix} j & k & l \\ m & n & o \\ p & q & r \end{bmatrix}$$

$$= \begin{bmatrix} (aj + bm + cp) & (ak + bn + cq) & (al + bo + cr) \\ (dj + em + fp) & (dk + en + fq) & (dl + eo + fr) \\ (gj + hm + ip) & (gk + hn + iq) & (gl + ho + ir) \end{bmatrix}$$


Methodology


The process of building the circuit consists of one somewhat challenging circuit. The circuit not only requires knowledge on how to wire and code the components together but also understand how metrics work. The picture on the side shows the math behind the multiplication of two 3 by 3 matrices

Simulation

 

Simulation

 

 

Demo Video

Thank you!!

