

BCD to Binary Converter

Shrutee Rakshit
Mahdee Rahman
Preethi Venkatesan
Sahijnoor Mahal

Function of Circuit

- Conversion from 16 bit BCD to 14 bit binary
- Output
 - 14 bit binary outputted through LEDs
- Input
 - 16 bit BCD inputted through keyboard

9999

(Decimal)



1111 1111 1111 1111

(BCD)



10011100001111

(Binary)

Block Diagram


Keyboard Code: provide the output done ≤ 1 when a key has been released. DOUT outputs the scan code of a key.

FSM: to determine the order of the keys pressed.

Registers: store the data for the values of DOUT.

Decoders: will take the scan code of each key and output the corresponding number in BCD.

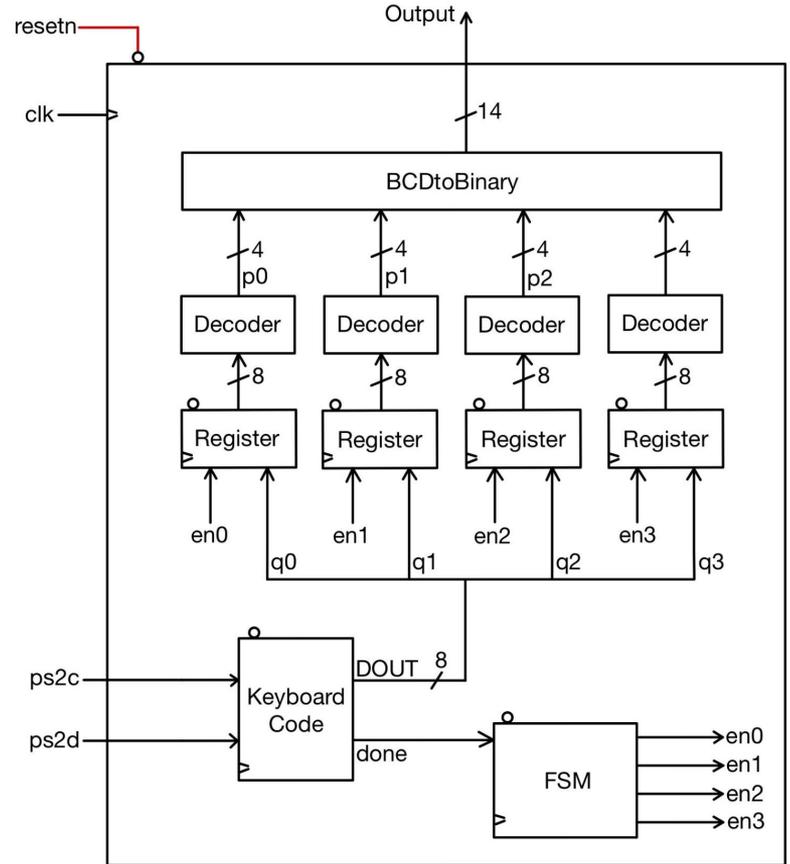BCDtoBinary: converts BCD values from decoders into a binary output.



FSM

S1

Begins with first BCD and is the MSB. In S1 when the user lets go of a key the done will be issued. Enable 0 is now 1 which allows register 1 to be open.

S2


At S2, the second done is issued; at which enable 1 = 1 and this allows register 2 to be open.

S3

At S3, the third done is issued; at which enable 2 = 1 and this allows register 3 to be open.

S4

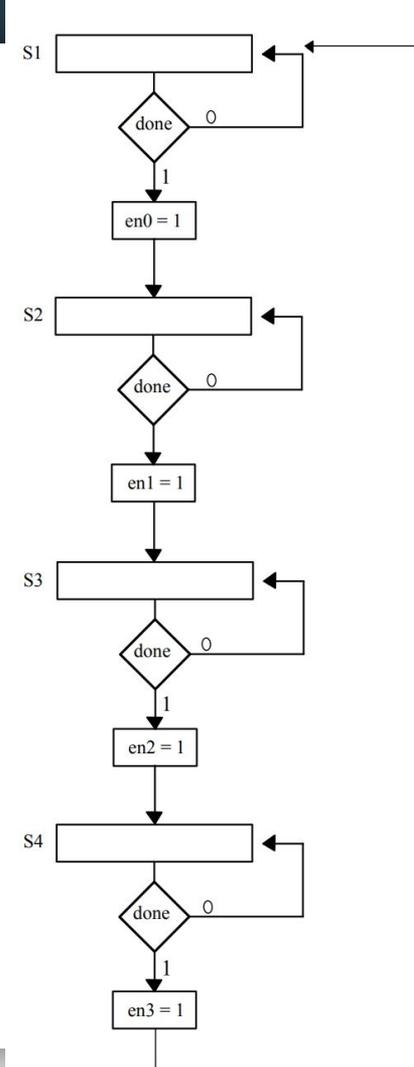At S4, the fourth done is issued; at which enable 3 = 1 and this allows register 4 to be open.




Components - BCD to Binary Converter

4 bit BCD inputs are concatenated to make them 10 bits.

The 10 bit BCD numbers are multiplied by a factor of 10 to get the outputs m_3 , m_2 , m_1 , m_0 .

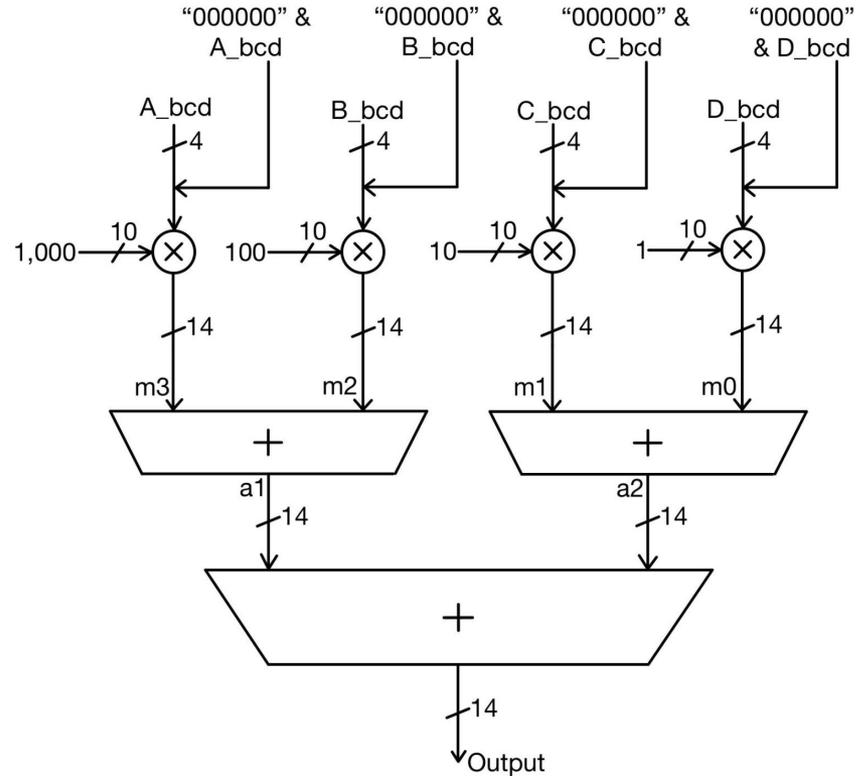The outputs from the multipliers are grouped together and added using full adders. This will output the binary of the input.




BCD to Binary Converter - Sub-Components

The output of the keyboard will be transferred to the four 4-bit registers as the BCD input. Those 4 registers will be further multiplied using 14-bit multipliers.


The most significant bit will be multiplied by 1000(10^3) and the second most significant bit will be multiplied by 100(10^2). The 3rd most significant bit will be multiplied by 10(10^1) and the least significant bit will be multiplied by 1(10^0).

Multiplied outputs of the most significant and the second most significant bit will be added together using a 14-bit adder and the multiplied output of the 3rd most significant bit will be added with the least significant bit using a 14-bit adder.

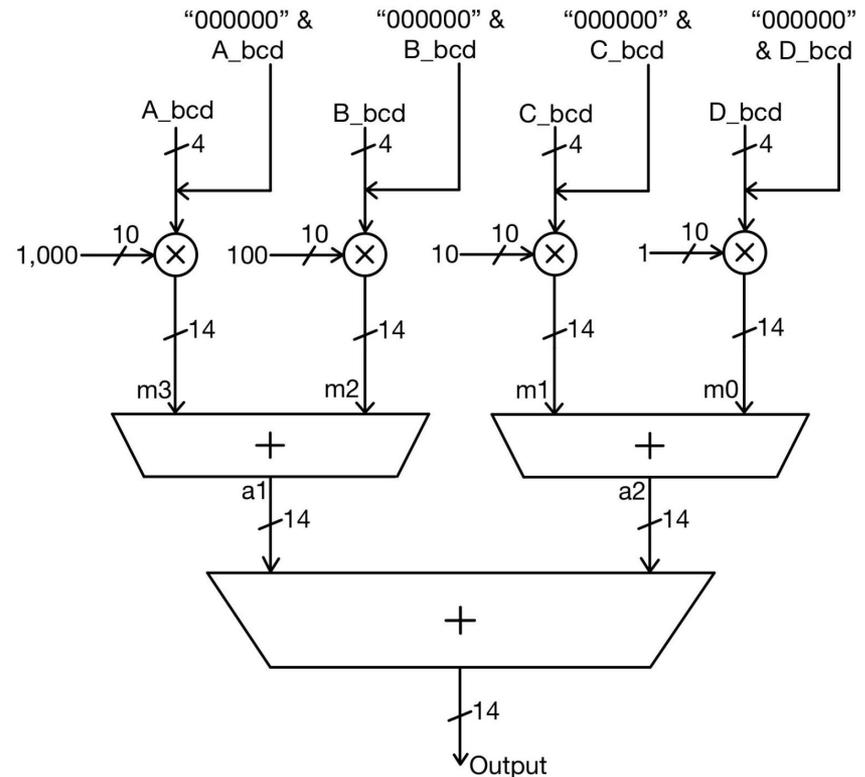Output of both the 14-bit adders will then be added together using another 14-bit adder. The output of this adder would give us our binary output which will be the result of the BCD input.




BCD to Binary Converter - Simulation

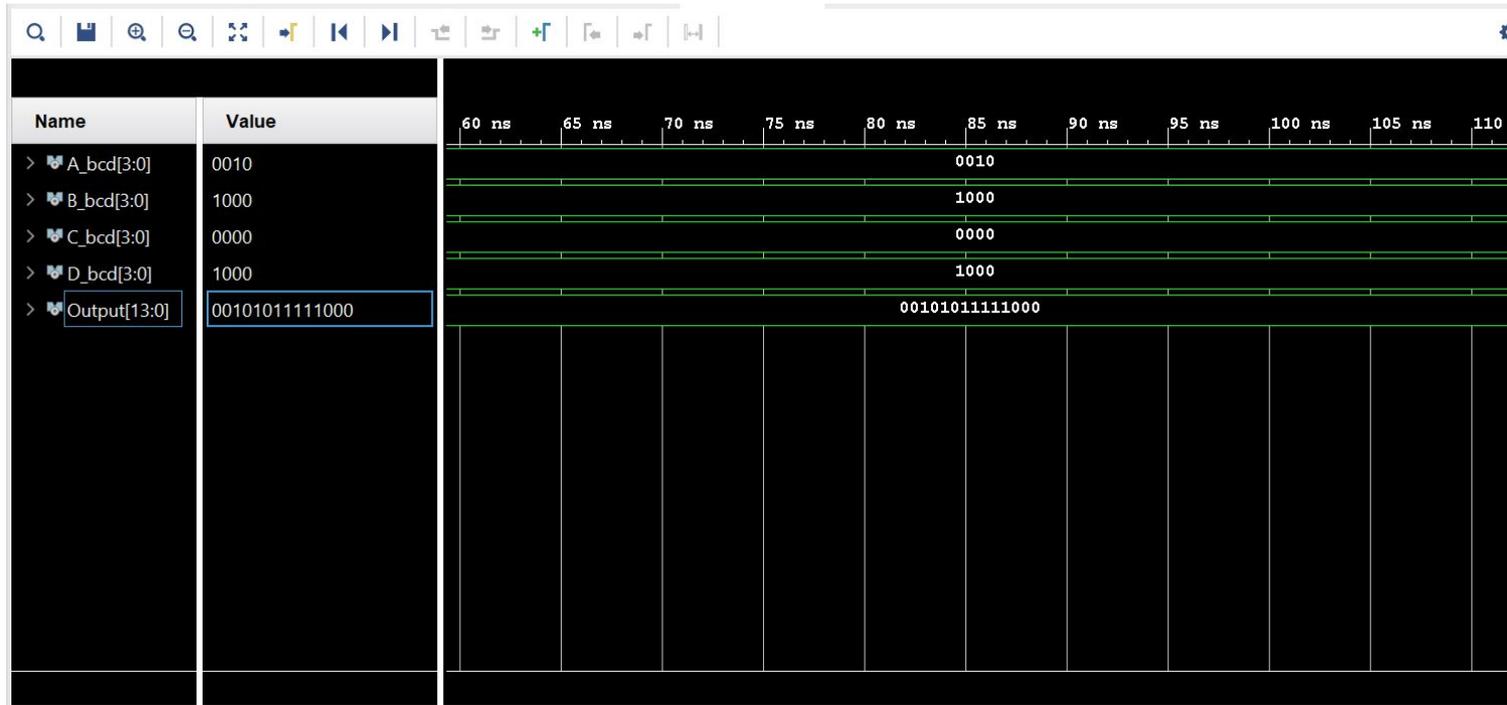

0010 1000 0000 1000 (BCD) => 2808 (Decimal) => 101011111000 (Binary)


Simulation

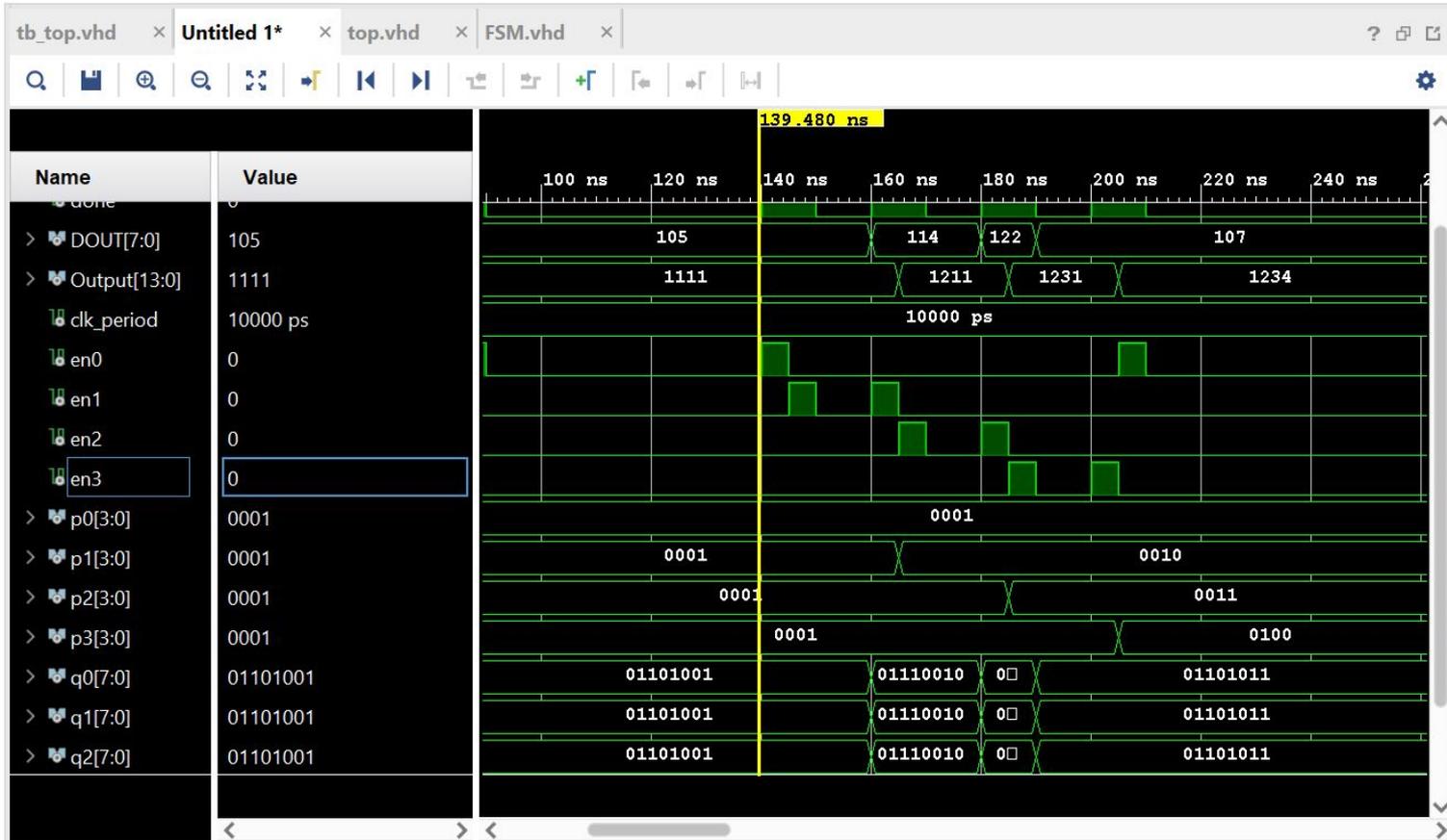



Thank you!


Demo

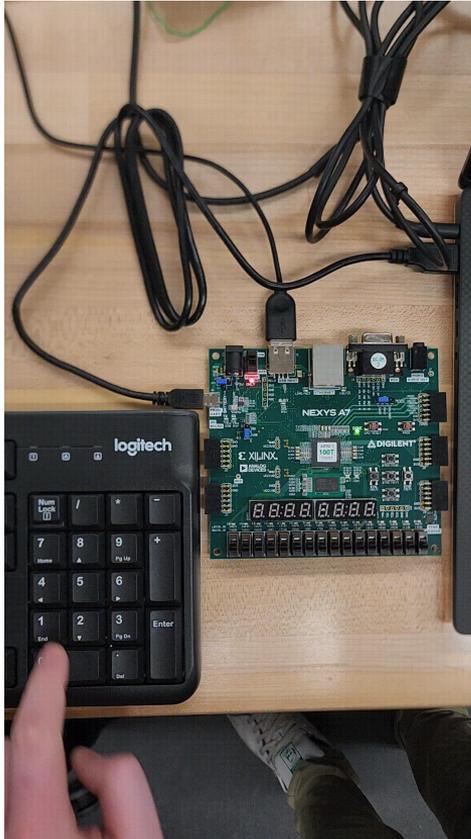

0001 0001 0001 1000 (BCD)



1010110110011 (Binary)

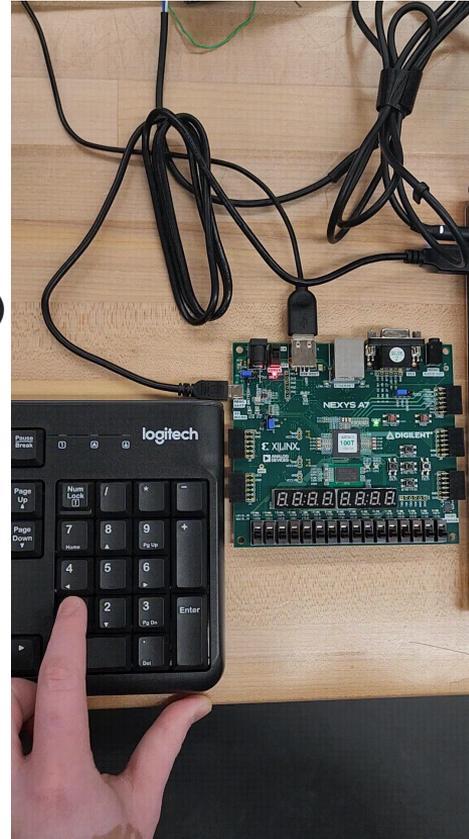

0001 0010 0100 0101 (BCD)



10011011101 (Binary)