


Homework 3

(Due date: October 31st @ 11:59 pm)


Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (11 PTS)

- Complete the timing diagram of the circuit shown below. (5 pts)




 - Complete the timing diagram of the circuits shown below: (6 pts)



 
PROBLEM 2 (30 PTS)

- Complete the timing diagram of the circuit shown below. Get the excitation equation for Q. (10 pts)



$Q_{t+1} \leftarrow$

 - Complete the timing diagram of the circuit shown below. Get the excitation equation for Q. (7 pts)



$Q_{t+1} \leftarrow$

- Complete the timing diagram of the circuit whose VHDL description is shown below: (6 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( prn, a , clk: in std_logic;
        q: out std_logic);
end circ;


architecture t of circ is
  signal qt: std_logic;

begin
  process (prn, clk, x, a)
  begin
    if prn = '0' then
      qt <= '1';
    
```


```

    elsif (clk'event and clk = '1') then
      if x = '1' then
        qt <= a xnor qt;
      end if;
    end if;
  end process;
  q <= qt;
end t;

```

 


 - Complete the timing diagram of the following circuit: $Q = Q_3Q_2Q_1Q_0$. Get the excitation equation for Q_3 . (7 pts)



 
PROBLEM 3 (11 PTS)

- Given the following circuit, complete the timing diagram (signals *DO* and *DATA*). The LUT 6-to-6 implements the following function: $OLUT = [ILUT^{0.75}]$, where *ILUT* is an unsigned number. For example $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.75}] = 15 (001111_2)$



 
PROBLEM 4 (10 PTS)

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$




 
PROBLEM 5 (20 PTS)

- The following circuit is a multiple-input compressor circuit (MIC), a component in Built-in Self-Test systems. $Q = Q_3Q_2Q_1Q_0$. $P = P_3P_2P_1P_0$
 - Write structural VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). (10 pts)
 - Write a VHDL testbench according to the timing diagram shown below (50 MHz clock with 50% duty cycle). Run the simulation (Behav. Simulation). Verify the results: compare them with the manually completed timing diagram (10 pts)
- Upload (as a .zip file) the following files to Moodle (an assignment will be created):
 - VHDL code files and testbench.
 - A screenshot of your Vivado simulation results for (it should all the values for Q).



  PROBLEM 6 (8 PTS)

- Complete the timing diagram (output DO) of the following Random Memory Access (RAM) Emulator.
- RAM Emulator: It has 8 addresses, where each address holds a 4-bit data. The memory positions are implemented by 4-bit registers. The *resetn* and *clock* signals are shared by all the registers. Data is written or read onto/from one of the registers (selected by the signal address).
- Operations:
 - ✓ Writing onto memory (*wr_rd*=‘1’): The 4-bit input data (DI) is written into one of the 8 registers. The address signal selects which register is to be written.
 - For example: if address = “101”, then the value of DI is written into register 5.
 - Note that because the BusMUX 8-to-1 includes an enable input, if *wr_rd*=1, then the BusMUX outputs are 0’s.
 - ✓ Reading from memory (*wr_rd*=‘0’): The address signal selects the register from which data is read. This data appears on the BusMUX output.
 - For example: If address = “010”, then data from register 2 appears on BusMUX output.



PROBLEM 7 (10 PTS)

- Attach your Project Status Report (no more than 1 page, single-spaced, 2 columns, only one submission per group). This report should contain the initial status of your project. For formatting, use the provided template (Final Project - Report Template.docx). The sections included in the template are the ones required in your Final Report. At this stage, you are only required to:
 - ✓ Include a (draft) project description and title.
 - ✓ Include a draft Block Diagram of your hardware architecture.
- As a guideline, the figure shows a simple Block Diagram. There are input and output signals, as well as internal components along with their interconnection.
 - ✓ At this stage, only a rough draft is required. There is no need to go into details: it is enough to show the tentative top-level components that would constitute your system as well as the tentative inputs and outputs.
- Only student is needed to attach the report (make sure to indicate all the team members).

