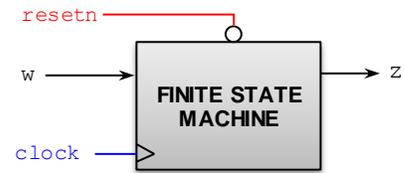


Quiz 4

(November 17th @ 5:30 pm)



PROBLEM 1 (35 PTS)

- The following FSM has 4 states, one input w and one output z . (12 pts)
 - ✓ The excitation equations are given by:
 - $Q_1(t+1) \leftarrow Q_0(t)$
 - $Q_0(t+1) \leftarrow \overline{Q_1(t)} \oplus w$
 - ✓ The output equation is given by: $z = Q_1(t) \oplus Q_0(t) \oplus w$
 - ✓ Provide the Excitation Table and the State Diagram (any representation).



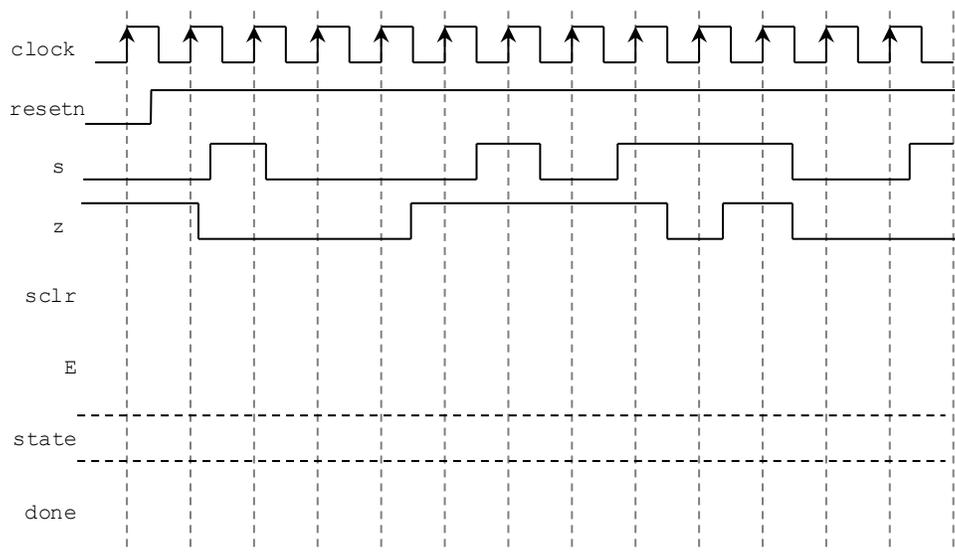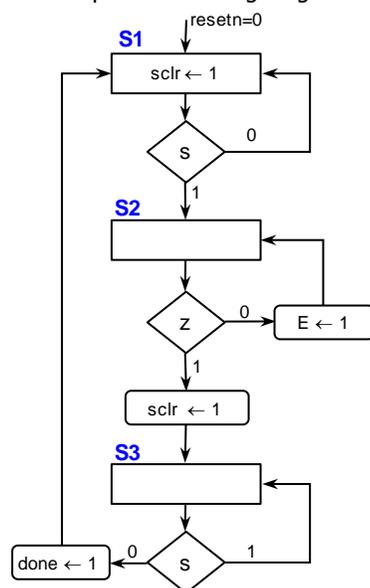PROBLEM 2 (35 PTS)

- Complete the timing diagram of the following FSM (represented in ASM form):



PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input x and output z . The detector asserts $z = 1$ when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.