


# Solutions - Homework 4

(Due date: Nov. 14<sup>th</sup> (008), Nov. 15<sup>th</sup> (010) @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!
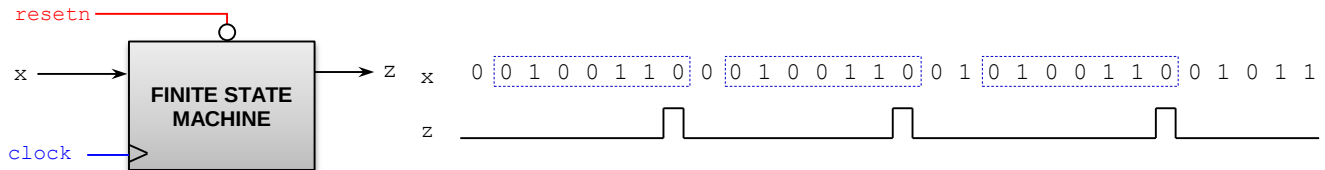
## PROBLEM 1 (23 PTS)

- Sequence Detector: The machine generates  $z = 1$  when it detects the sequence 0100110. Once the sequence is detected, the circuit looks for a new sequence.




- Draw the State Diagram (any representation), State Table, and Excitation Table. Is this a Mealy or a Moore machine? Why?
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)

- State Diagram, State Table, and Excitation Table:

State Assignment:

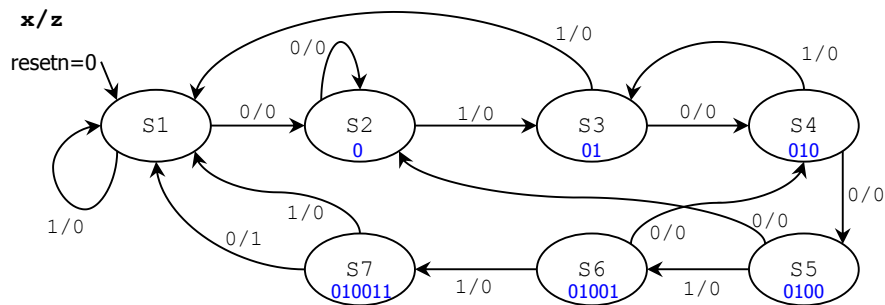S1: Q=000  
S2: Q=001  
S3: Q=010  
S4: Q=011  
S5: Q=100  
S6: Q=101  
S7: Q=110




| PRESENT STATE |       |            |   | NEXT STATE |                                                  |                                                    |   |
|---------------|-------|------------|---|------------|--------------------------------------------------|----------------------------------------------------|---|
| x             | STATE | NEXT STATE | z | x          | Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub> (t) | Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub> (t+1) | z |
| 0             | S1    | S2         | 0 | 0          | 0 0 0 0                                          | 0 0 1                                              | 0 |
| 0             | S2    | S2         | 0 | 0          | 0 0 0 1                                          | 0 0 1                                              | 0 |
| 0             | S3    | S4         | 0 | 0          | 0 0 1 0                                          | 0 1 1                                              | 0 |
| 0             | S4    | S5         | 0 | 0          | 0 0 1 1                                          | 1 0 0                                              | 0 |
| 0             | S5    | S2         | 0 | 0          | 0 1 0 0                                          | 0 0 1                                              | 0 |
| 0             | S6    | S4         | 0 | 0          | 0 1 0 1                                          | 0 1 1                                              | 0 |
| 0             | S7    | S1         | 1 | 0          | 0 1 1 0                                          | 0 0 0                                              | 1 |
| 1             | S1    | S1         | 0 | 0          | 0 1 1 1                                          | X X X                                              | X |
| 1             | S2    | S3         | 0 | 1          | 1 0 0 0                                          | 0 0 0                                              | 0 |
| 1             | S3    | S1         | 0 | 1          | 1 0 0 1                                          | 0 1 0                                              | 0 |
| 1             | S4    | S3         | 0 | 1          | 1 0 1 0                                          | 0 0 0                                              | 0 |
| 1             | S5    | S6         | 0 | 1          | 1 0 1 1                                          | 0 1 0                                              | 0 |
| 1             | S6    | S7         | 0 | 1          | 1 1 0 0                                          | 1 0 1                                              | 0 |
| 1             | S7    | S1         | 0 | 1          | 1 1 0 1                                          | 1 1 0                                              | 0 |
|               |       |            |   | 1          | 1 1 1 0                                          | 0 0 0                                              | 0 |
|               |       |            |   | 1          | 1 1 1 1                                          | X X X                                              | X |

This is a Mealy FSM. The output 'z' depends on the input as well as on the present state.

- Excitation equations, minimization, and circuit implementation:

$$\begin{aligned}
 Q_2(t+1) &\leftarrow xQ_2\bar{Q}_1 + \bar{x}Q_1Q_0 \\
 Q_1(t+1) &\leftarrow Q_2Q_0 + xQ_0 + \bar{x}\bar{Q}_2Q_1\bar{Q}_0 \\
 Q_0(t+1) &\leftarrow \bar{x}\bar{Q}_1 + Q_2\bar{Q}_1\bar{Q}_0 + \bar{x}\bar{Q}_2\bar{Q}_0 \\
 z &= \bar{x}Q_2Q_1
 \end{aligned}$$

| $z$<br>$Q_1 Q_0$ | $x Q_2$<br>00 | 01 | 11 | 10 |
|------------------|---------------|----|----|----|
| 00               | 0             | 0  | 0  | 0  |
| 01               | 0             | 0  | 0  | 0  |
| 11               | 0             | X  | X  | 0  |
| 10               | 0             | 1  | 0  | 0  |

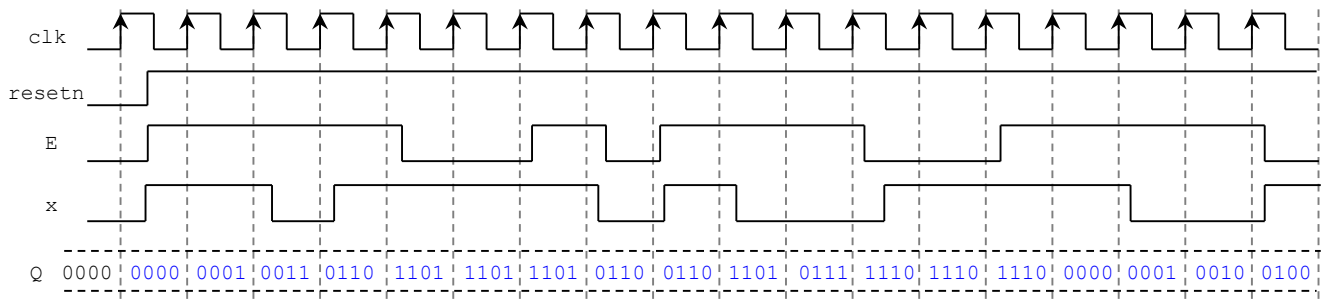

### PROBLEM 3 (12 PTS)

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following FSM.

w: input, z: output,  $Q_1Q_0$ : state.

$$Q_1(t+1) \leftarrow (Q_1 + Q_0)w$$


$$Q_0(t+1) \leftarrow Q_1 \oplus w$$

$$z = wQ_1Q_0$$

State Assignment:

S1:  $Q=00$     S2:  $Q=01$


S3:  $Q=10$     S4:  $Q=11$

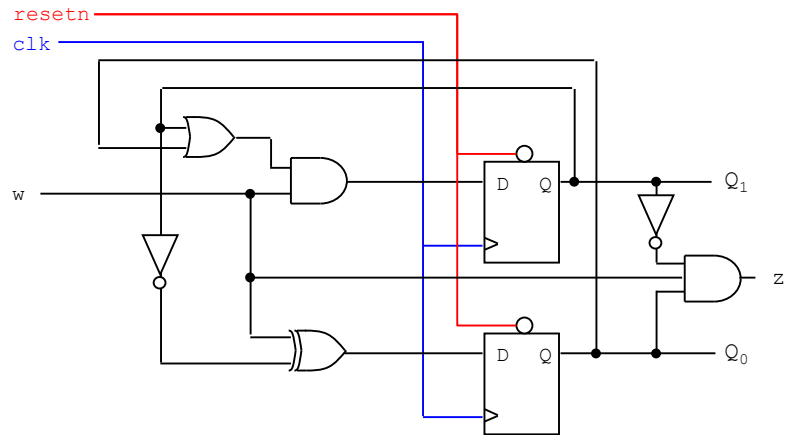

| PRESENT STATE |             |   | NEXTSTATE     |   |  |
|---------------|-------------|---|---------------|---|--|
| w             | $Q_1Q_0(t)$ |   | $Q_1Q_0(t+1)$ | z |  |
| 0             | 0 0         | 0 | 0 1           | 0 |  |
| 0             | 0 1         | 0 | 0 1           | 0 |  |
| 0             | 1 0         | 0 | 0 0           | 0 |  |
| 0             | 1 1         | 0 | 0 0           | 0 |  |
| 1             | 0 0         | 0 | 0 0           | 0 |  |
| 1             | 0 1         | 1 | 1 0           | 1 |  |
| 1             | 1 0         | 1 | 1 1           | 0 |  |
| 1             | 1 1         | 1 | 1 1           | 0 |  |



| w | PRESENT STATE | NEXT STATE | z |
|---|---------------|------------|---|
| 0 | S1            | S2         | 0 |
| 0 | S2            | S2         | 0 |
| 0 | S3            | S1         | 0 |
| 0 | S4            | S1         | 0 |
| 1 | S1            | S1         | 0 |
| 1 | S2            | S3         | 1 |
| 1 | S3            | S4         | 0 |
| 1 | S4            | S4         | 0 |

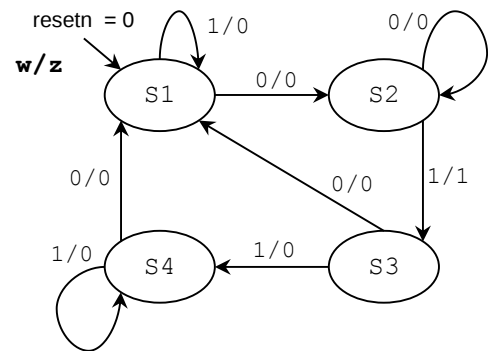

## PROBLEM 4 (17 PTS)


- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram. (9 pts.)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( clk, resetn: in std_logic;
        r, p, q: in std_logic;
        x, w, z: out std_logic);
end circ;

```

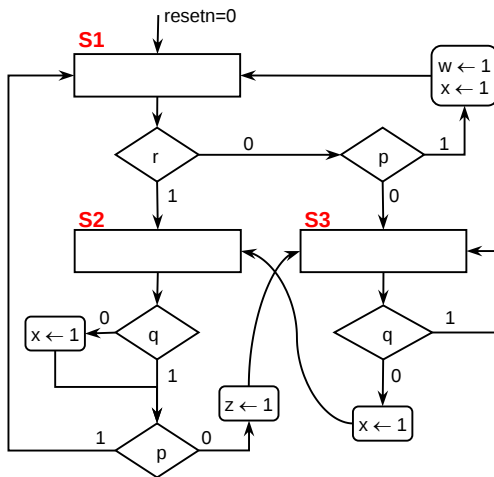


```

architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, r, p, q)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if r = '1' then
            y <= S2;
          else
            if p = '1' then y <= S1; else y <= S3; end if;
          end if;
        when S2 =>
          if p = '1' then y <= S1; else y <= S3; end if;
        when S3 =>
          if q = '1' then y <= S3; else y <= S2; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, r, p, q)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => if r = '0' then
                    if p = '1' then
                      w <= '1'; x <= '1';
                    end if;
                  end if;
      when S2 => if q = '0' then x <= '1'; end if;
                  if p = '0' then z <= '1'; end if;
      when S3 => if q = '0' then x <= '1'; end if;
    end case;
  end process;
end behavioral;



```

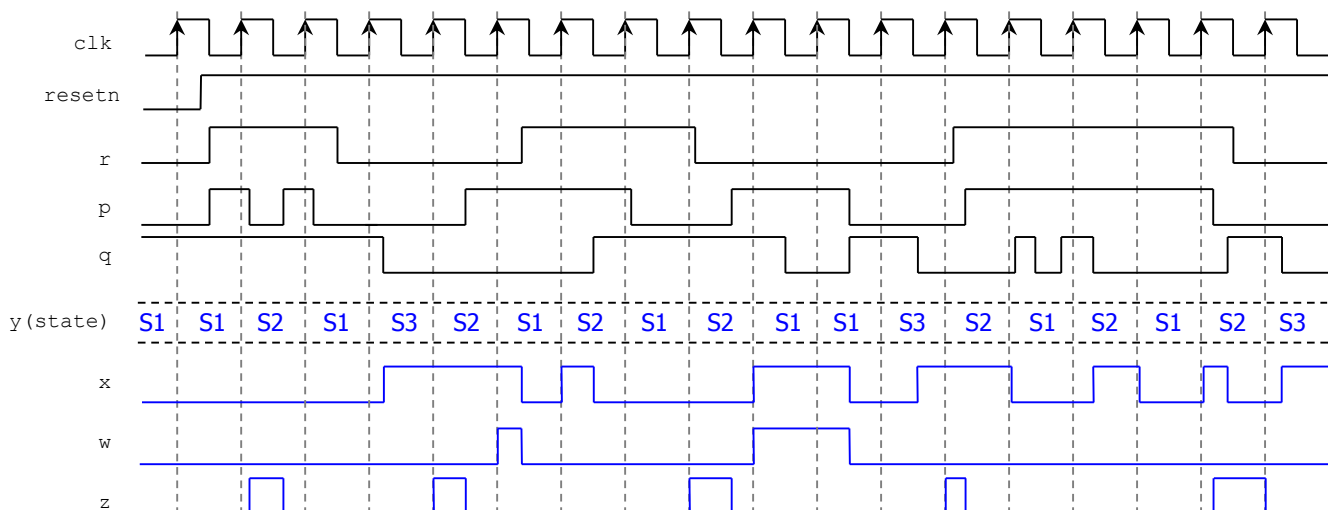This is a Mealy FSM. The outputs 'x,w,z' depend on the input as well as on the present state.


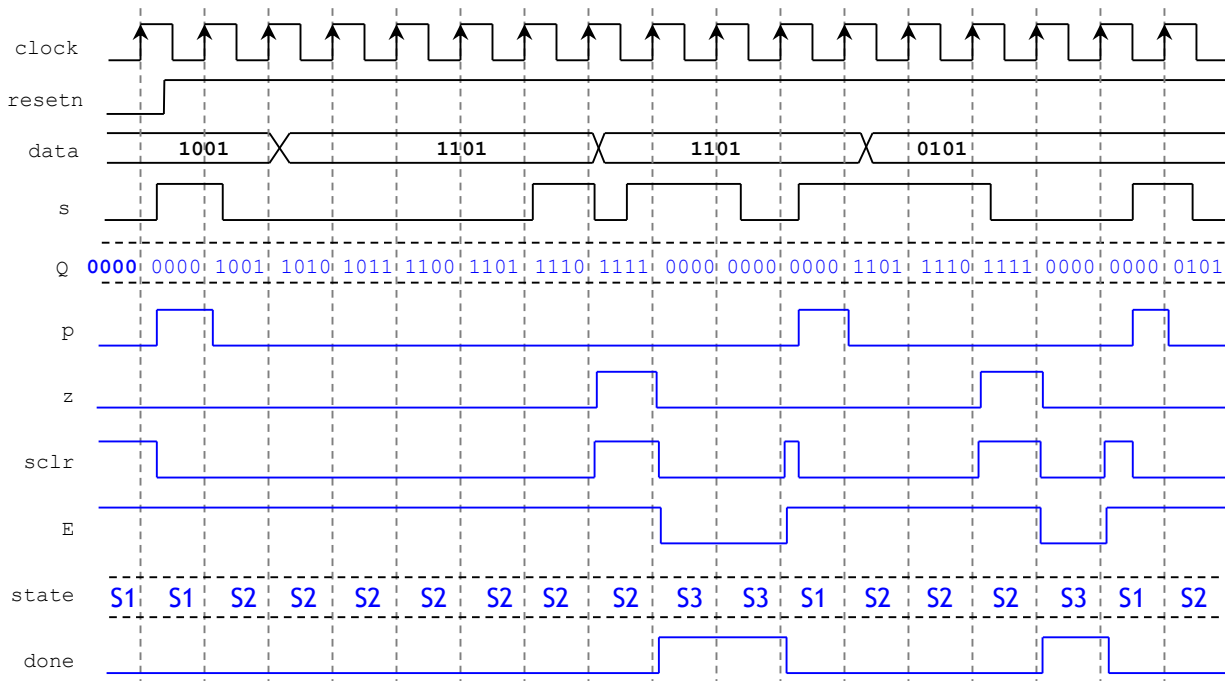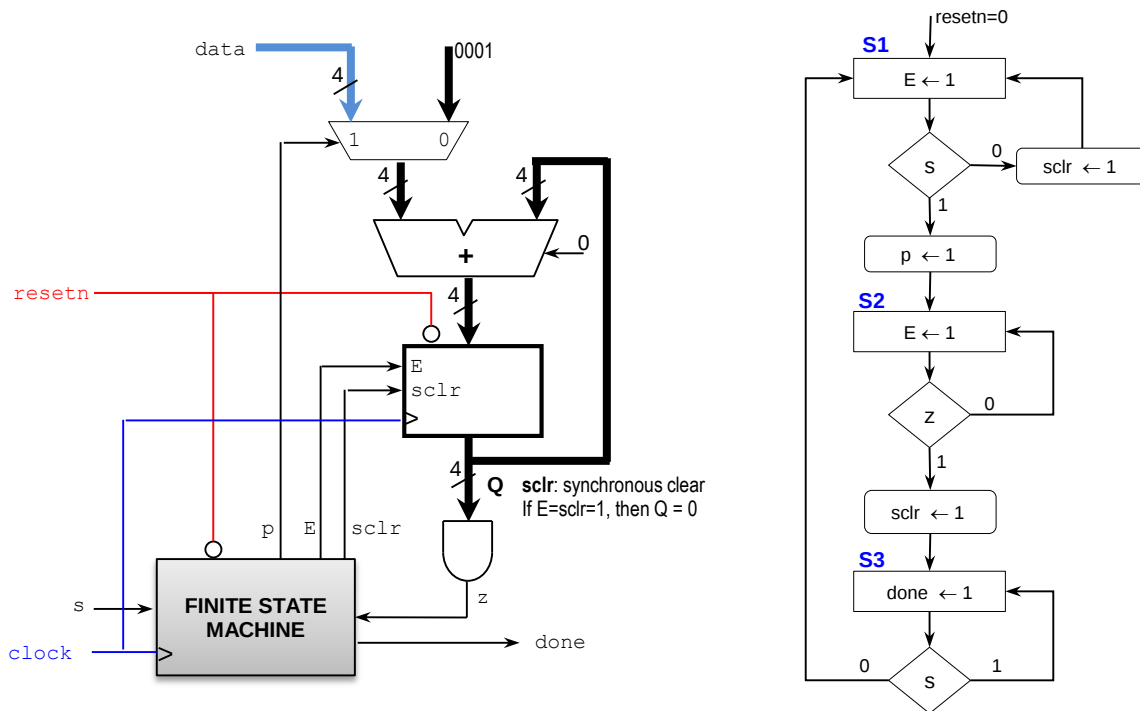
### PROBLEM 5 (18 PTS)

- Complete the timing diagram of the following digital circuit that includes an FSM (in ASM form) and a datapath circuit.



### PROBLEM 6 (15 PTS)

- Attach a printout of your Project Status Report (no more than three pages, single-spaced, 2 columns). This report should contain the current status of the project. You **MUST** use the provided template (Final Project - Report Template.docx).