


PROBLEM 3 (11 PTS)

- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The circuit in the blue box computes the signed operation *T-4*, with the result having 5 bits. *T* is a 4-bit signed (2C) number.

✓ Example: if $T=1010$:

$DO = 1010 - 0100 = 11010 + 11100$

$DO = 10110$

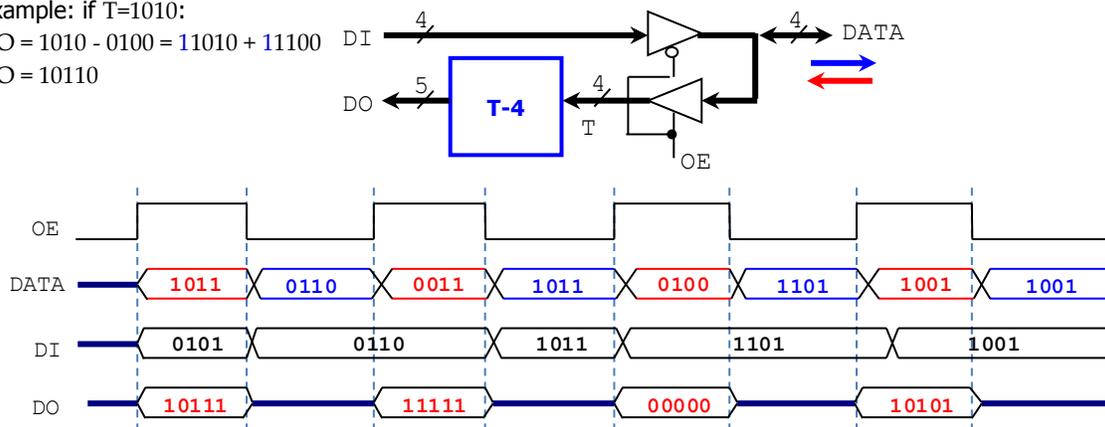

PROBLEM 4 (10 PTS)

- A microprocessor has a memory space of 2 MB. Each memory address occupies one byte. 1 KB = 2^{10} bytes, 1 MB = 2^{20} bytes, 1 GB = 2^{30} bytes.

✓ What is the address bus size (number of bits of the address) of this microprocessor?



Size of memory space: 2 MB = 2^{21} bytes. Thus, we require 21 bits to address the memory space.

✓ What is the range (lowest to highest, in hexadecimal) of the memory space for this microprocessor? (1 pt.)

With 21 bits, the address range is $0x000000$ to $0x1FFFFFF$.

✓ The figure (right) shows four memory chips that are placed in the given positions:

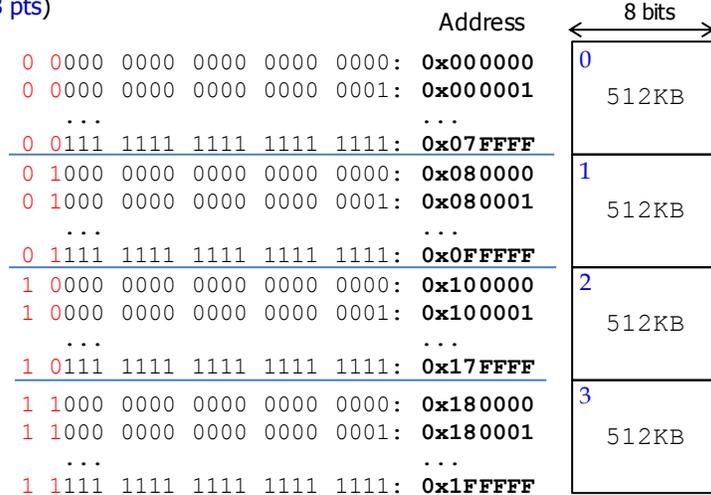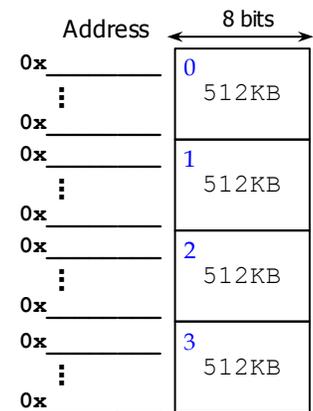- Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips. (8 pts)





PROBLEM 5 (15 PTS)

- Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every carry (or borrow) from c_0 to c_n (or b_0 to b_n). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher bit. (6 pts)


✓ $39 + 41$

✓ $39 - 41$

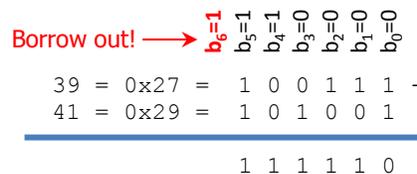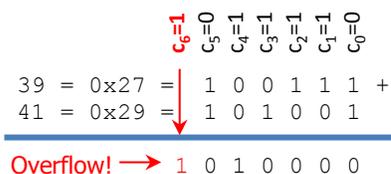


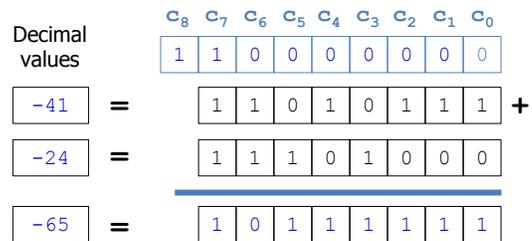b) The figure shows two 8-bit operands represented in 2's complement. Perform the 8-bit addition operation, i.e., complete all the carries and the summation bits. Also, indicate the corresponding decimal numbers for the 8-bit operands and the 8-bit result.

Does this 8-bit operation incur in overflow? Yes ~~No~~
 Value of the overflow bit: $c_8 \oplus c_7 = 0$
 Value of carry out bit: $c_8 = 1$



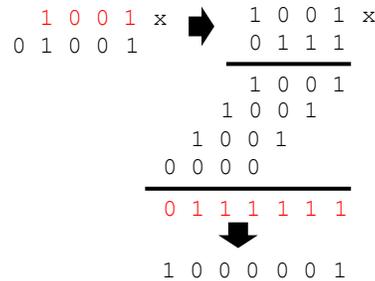
c) Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (4 pts)
 $\checkmark -7 \times 9$



PROBLEM 6 (10 PTS)

Sketch the circuit that computes $|A - B|$, where A, B are 4-bit unsigned numbers. For example, $A = 0101, B = 1101 \rightarrow |A - B| = |5 - 13| = 8$. You can only use full adders (or multi-bit adders) and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.

- $A = a_3a_2a_1a_0, B = b_3b_2b_1b_0$
- $A, B \in [0,15] \rightarrow A, B$ require 4 bits in unsigned representation. However, to get the proper result of $A - B$, we need to use the 2C representation, where A, B require 5 bits in 2C.
- $\checkmark X = A - B \in [-15,15]$ requires 5 bits in 2C. Thus, we need to zero-extend A and B to convert them to 2C representation.
- $\checkmark |X| = |A - B| \in [0,15]$ requires 5 bits in 2C. Thus, the second operation $0 \pm X$ only requires 5 bits.
 - \square If $x_4 = 1 \rightarrow X < 0 \rightarrow$ we do $0 - X$.
 - \square If $x_4 = 0 \rightarrow X \geq 0 \rightarrow$ we do $0 + X$.
- $\checkmark R = |A - B| \in [0,15]$ requires 5 bits in 2C. Note that the MSB is always 0. The unsigned result only requires 4 bits.

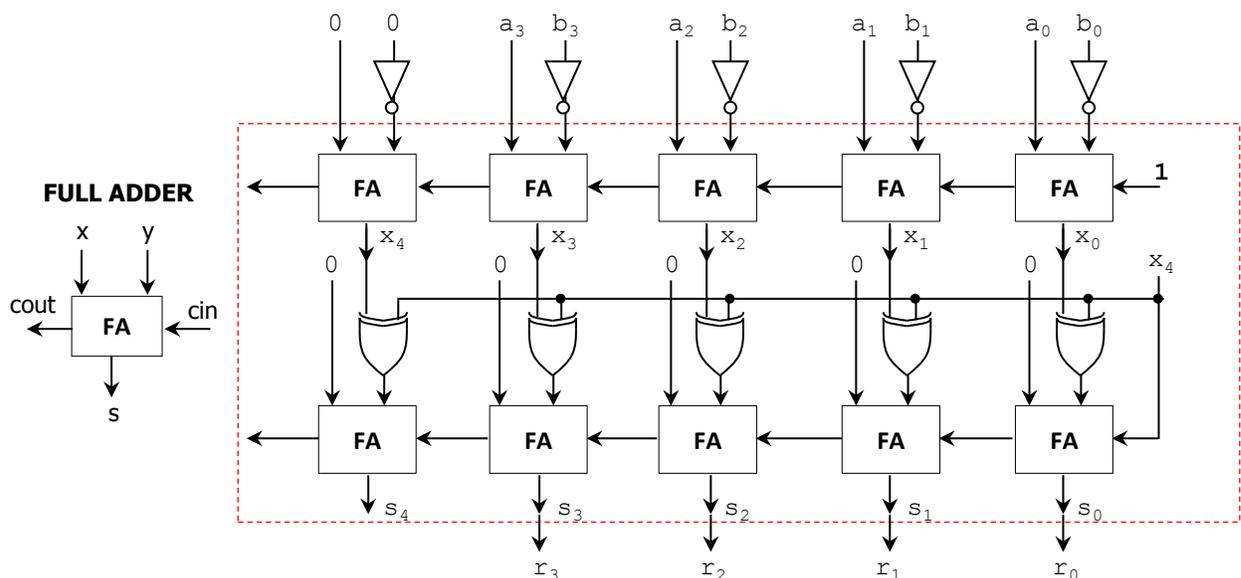

PROBLEM 6 (18 PTS)

- Sketch the circuit that implements the following Boolean function: $f(a, b, c, d) = (c \oplus d)(\overline{a \oplus b})$
- Using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)


$$f(a, b, c, d) = \overline{a}f(0, b, c, d) + af(1, b, c, d) = \overline{a}(\overline{b(c \oplus d)}) + a(b(c \oplus d)) = \overline{a}g(b, c, d) + ah(b, c, d)$$

$$g(b, c, d) = \overline{b}g(0, c, d) + bg(1, c, d) = \overline{b}(c \oplus d) + b(0)$$

$$h(b, c, d) = \overline{b}h(0, c, d) + bh(1, c, d) = \overline{b}(0) + b(c \oplus d)$$

$$t(c, d) = c \oplus d = \overline{c}t(0, d) + ct(1, d) = \overline{c}(d) + c(\overline{d})$$

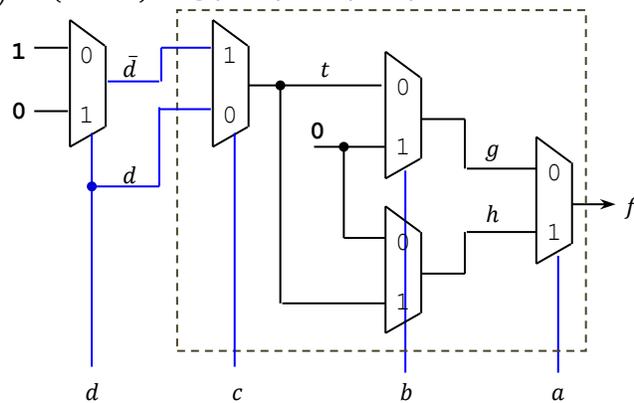Also: $\overline{d} = \overline{d}(1) + d(0)$



- Using two 3-to-1 LUTs and a 2-to-1 MUX. Specify the contents of each of the 3-to-1 LUTs. (6 pts)

